

Electronics for Scientists

*Principles and Experiments
for Those Who Use Instruments*

H. V. Malmstadt
University of Illinois

and

C. G. Enke
Princeton University

with the assistance of

E. C. Toren, Jr.
Duke University

W. A. Benjamin, Inc.

New York

1963

ELECTRONICS FOR SCIENTISTS

Principles and Experiments for Those Who Use Instruments

Copyright © 1962 by W. A. Benjamin, Inc.
All rights reserved

Library of Congress Catalog Card Number: 62-15645
Manufactured in the United States of America

*First printing, September 1962;
Second printing, with corrections,
March 1963.*

*The publisher is pleased to acknowledge the assistance
of Russell F. Peterson, who produced the illustrations,
and William Prokos, who designed the cover,
dust jacket, and end papers*

W. A. BENJAMIN, INC.
2465 Broadway, New York 25, New York

Contents

Preface	v
Introduction	3
Chapter 1 ELECTRICAL MEASUREMENTS	7
1-1 Measurement of Voltage and Current	8
1-2 The Moving-Coil Meter	10
1-3 The Ammeter	13
1-4 The Voltmeter	16
1-5 The Ohmmeter	18
1-6 The Multimeter	21
1-7 The Vacuum-Tube Voltmeter (VTVM)	23
1-8 The Oscilloscope	26
References	36
Problems	37
Experiments	39
Chapter 2 POWER SUPPLIES	47
2-1 General Considerations	47
2-2 Scheme for Converting A-C Line Voltage to D-C Voltage	48

2-3	Power Transformers	50
2-4	Rectifiers	51
2-5	Rectifier Circuits	60
2-6	Filtering the Rectified Voltage	65
2-7	Regulation of the Output D-C Voltage	74
2-8	Batteries as Sources of D-C Voltage	76
2-9	Conversion of Direct Current to Alternating Current	86
	References	87
	Problems	87
	Experiments	89

Chapter 3 AMPLIFICATION BY VACUUM TUBES AND TRANSISTORS

		97
3-1	Amplification	97
3-2	The Vacuum Triode	98
3-3	The Triode Common-Cathode Amplifier	101
3-4	The Vacuum Pentode	111
3-5	The Pentode Common-Cathode Amplifier	114
3-6	The Transistor	117
3-7	The Transistor Common-Emitter Amplifier	124
3-8	The Cathode-Follower (Common-Collector) Amplifier	134
3-9	The Common-Base (Grounded-Grid) Amplifier	145
3-10	The Unipolar Field-Effect Transistor (FET)	148
	References	153
	Problems	153
	Experiments	156

Chapter 4 AMPLIFIER CIRCUITS

		161
4-1	Audio Preamplifiers	161
4-2	Audio Power Amplifier	171
4-3	The Direct-Coupled Amplifier	177
4-4	The Difference Amplifier	184
4-5	Noise and Distortion in Amplifiers	190
4-6	The Radio-Frequency Amplifier	198
4-7	Amplifiers with Feedback	202
	References	212
	Problems	213
	Experiments	214

Contents	ix
Chapter 5 OSCILLATORS	223
5-1 General Considerations	223
5-2 Feedback Oscillators	225
5-3 Sinusoidal Negative-Resistance Oscillators	231
5-4 Relaxation Oscillators	234
5-5 Oscillator Stabilization	239
5-6 Modulation and Demodulation	242
References	246
Problems	246
Experiments	247
Chapter 6 COMPARISON MEASUREMENTS	251
6-1 The Principles of Comparison Methods	251
6-2 Accurate D-C Voltage Measurement by the Comparison Method	254
6-3 D-C Current Measurement by Comparison Method	273
6-4 Resistance Measurement by a Comparison Procedure	273
6-5 Impedance Measurement by Comparison Procedures	276
6-6 Frequency Measurements by the Comparison Procedure	283
References	284
Problems	284
Experiments	286
Chapter 7 SERVO SYSTEMS	291
7-1 General Description of Servomechanisms	291
7-2 The Automatic Recording Potentiometer—A Simple Servomechanism	293
7-3 The Instrument Servomotor	295
7-4 The Signal Controller for Servo Potentiometers	298
7-5 Information-Feedback Devices for the Servo Potentiometer	304
7-6 The Command Signal—Input Transducers	306
7-7 Servo Stability—The Dynamics Problem	307
7-8 Antihunt Methods	316
7-9 Synchro-Generator-Control-Transformer System	318
7-10 High-Power Prime Movers and Signal Controllers	321
7-11 Standard Block Diagram and Terminology	327
7-12 Open-Loop Control	329
References	329
Problems	329
Experiments	330

Chapter 8 OPERATIONAL AMPLIFIERS FOR MEASUREMENT AND CONTROL	341
8-1 An Amplifier Designed for Feedback Control	342
8-2 Operational Amplifiers for Electrical Measurements	353
8-3 The Chopper-Stabilized Operational Amplifier	359
8-4 The Generation of Precise Voltages and Waveforms	364
8-5 The Precise Control of Current and Voltage	368
8-6 Computation and Simulation	372
8-7 The Regulated Power Supply	376
8-8 Control for A-C-Operated Loads	383
References	388
Problems	388
Experiments	390
Chapter 9 ELECTRONIC SWITCHING AND TIMING AND DIGITAL COUNTING SYSTEMS	397
9-1 Counting, Switching, and Timing	397
9-2 Characteristics of Pulses and Pulse Amplifiers	403
9-3 Wave Shaping by the RC Circuit	406
9-4 Diode Switching Circuits	411
9-5 Amplification Elements as Switches	420
9-6 The Bistable Multivibrator	424
9-7 Schmitt Trigger (Cathode-Coupled Bistable Multivibrator)	431
9-8 Astable Multivibrator	434
9-9 Monostable Multivibrator	440
9-10 Blocking Oscillators	444
9-11 The Triggered-Sweep Oscilloscope	445
9-12 Scalers and Electronic Counters	447
9-13 Frequency and Time-Interval Meters	452
9-14 Electronic Digital-to-Analog Converters	456
9-15 Analog-to-Digital Converters	457
References	461
Problems	461
Experiments	463
Supplements	469
1 An Integrated System of Instruments, Test Equipment, and Rapid-Connect Parts	471
SI-1 Wired Test Equipment. EUW-12	473
SI-2 Universal Chassis and Parts. EUW-13	474

Contents**xi**

S1-3	Special Experimental Parts. EUW-14	489
S1-4	Universal Power Supply. EUW-15	493
S1-5	Voltage Reference Source. EUW-16	503
S1-6	Transistorized Power Supply. EUW-17	510
S1-7	Laboratory Meter. EUW-18	514
S1-8	Operational-Amplifier System. EUW-19	516
S1-9	Servo Recorder. EUW-20	525

2	D-C Circuits	528
----------	---------------------	------------

S2-1	Resistance	529
S2-2	Current	532
S2-3	Potential	533
S2-4	Series Circuits	534
S2-5	Parallel Circuits	536
S2-6	Networks	537

3	Electrical Signals and Reactive Circuits	545
----------	---	------------

S3-1	Introduction to Signals and Reactive Components	546
S3-2	Capacitors	554
S3-3	Inductors	555
S3-4	Sine-Wave Signals and Reactive Circuits	556
S3-5	Nonsinusoidal Signals and Reactive Circuits	573
S3-6	Mutual Inductance	579

Appendixes	583
-------------------	------------

A	Transistor Parameter Equivalents and Interconversion Tables	585
B	Vacuum-Tube Characteristic Curves	589
C	Resistors (EIA-JAN Values)	595
D	Power-Transformer Color Code	597

Index	599
--------------	------------

Preface

This book is a practical book for scientists and science students. It is written expressly for *chemists, physicists, engineers, medical researchers, biologists*, and other science students and research workers who have little or no background in electronics but who need to gain a working knowledge of electronic devices and circuits. The text begins with *electronic principles, basic circuits, and components*. It leads systematically into *serve systems, operational amplifiers, feedback control, digital circuits*, and other devices used in current laboratory research and engineering control problems. The liberal use of diagrams attests to the authors' belief that a picture can speak louder than a thousand words.

The order of presentation is laboratory-centered. There is a natural progression from the basic measurement techniques necessary to start experimentation toward the complete instruments and systems. Specific components are usually introduced in the chapter where the most common or important applications are first described. Circuits with *new and special devices* are presented as well as the widespread *transistor and vacuum-tube circuits*. Most circuit diagrams contain actual component values so that they can be used as working drawings. A selected list of references with specific comments concerning the nature of the contents is included at the end of each chapter.

The three supplements at the end of the book serve several functions. Supplement 1 introduces and gives specifications on the universal experimental system used to perform the experiments in the book, and the pictures acquaint the reader with the individual components. Supplements 2 and 3 serve primarily as review of and reference to the *basic laws and component characteristics* which are usually introduced in basic courses of college

Preface

physics. For scientists who do not remember or have had little exposure to these basic relationships, Supplements 2 and 3 are a good starting point.

This book should be especially useful as a text for a one-semester course at the junior-senior level in various physics, chemistry, or engineering college curricula, or as a self-teaching text for scientists on the job. For those who already have a good basic training in electronics, the chapters on comparison measurements, operational amplifiers, feedback control, servo systems, and digital circuits should provide both new information and reference material, because all these topics are presented in a way that the authors believe to be unique. As explained in the introduction, the authors have also found the material in this book to provide a practical working background in electronics for both graduate and postdoctoral students, especially if combined with thorough discussions of specific systems related to individual disciplines.

There have been many people influential in the start, preparation, and completion of this book. Professor H. A. Laitinen encouraged us from the beginning, both in support of the course from which this book developed and by his enthusiasm for the experimental system that we originated. The staff of the Heath Company (Benton Harbor, Michigan), especially W. Kooy, E. B. Mullings, and A. Robertson, was responsible for taking our original system and ideas and developing them into the completely integrated system of components and laboratory instruments now available for performing the experiments. Several valuable discussions took place with Professors Harry Pardue and Robert Kerr concerning portions of the manuscript. Great appreciation goes to Professor D. Lazarus of the University of Illinois Physics Department. He read all the chapters and made many important suggestions that greatly influenced our presentation of several topics. Mr. Verle Walters contributed in many ways to the construction of the original experimental system. Julia Zvilius, Frances Watson, and Linda Leahy were all very helpful in typing and assembling various parts of the manuscript. We are especially grateful for the help and encouragement of our wives, Gay Malmstadt and Mary Enke.

H. V. MALMSTADT
C. G. ENKE

Urbana, Illinois
Princeton, New Jersey
July 1962

Introduction

Go into a clinical laboratory, a chemistry, biological, or soil-science laboratory—in fact, go into laboratories in all areas of science and technology—and you will find them loaded with instruments that depend upon electronic circuits for operation. Talk to the experimental personnel, the people who do the research and accumulate the data, and you learn that these scientists are using a powerful array of tools with considerable success to probe the mysteries of their specialties. But you also learn of problems! Problems of how to put a new instrument into operation, how to modify a commercial instrument for a new research problem, how to increase sensitivity, how to eliminate electrical noise, how to prevent inaccuracies because of interaction between the measurement device and the system under test, how to automate a process or analytical method.

Unless answers to these questions can be readily provided by the available scientific personnel, a research project might be stalled, a breakthrough in science or production delayed. At the University we have observed research students waste weeks and months of valuable time because of the improper use of perfectly good instruments or the use of inadequate ones. Seldom do they understand what instrument changes should be made to keep pace with the developments in their research. Reports from several industrial-research directors indicate that the same situation prevails among many scientists on the job. This is to be expected, of course, because electronics has come of age since many of them completed their formal training.

Fortunately, however, there is an increasing awareness among experimental scientists that instruments can be used more effectively and that

more reliable measurements can be obtained if some basic understanding and working ability in electronics can be "picked up along the way." It is the purpose of this book to help the already trained scientist or advanced college science student to acquire this understanding and working ability.

Obviously, if unlimited time were available, a thorough program of study in an electronics department over a period of years would be desirable. However, the number of courses in most scientific curricula are already overwhelming, and the scientist at work is generally overloaded with his regular responsibilities. It was therefore a major concern to develop a course of study and experimentation that would permit a breakthrough of the "electronics barrier" in a minimum amount of time.

In the Chemistry Department at the University of Illinois many different ideas were tested with chemistry graduate students. The senior author of this book presented lectures, special seminars, and various laboratory courses over several years. It became increasingly apparent that a laboratory-oriented course was essential to provide the desired results. Finally a set of experiments evolved, together with descriptive material and a new, unique, and rapid method of connecting electronic circuits; the three proved to be an efficient and effective combination in taking scientifically trained students across the "electronics barrier"—to the point where they were working not with "magic boxes" but with scientific instruments. As would be hoped and expected, it also paved their way for further study and furnished a new awareness of how electronics might be useful in their work. It was found that this could be accomplished in 15 half days of laboratory work with at least an equivalent amount of time for study. This amounts to about one very full day per week during the regular 15-week college semester.

Many scientists throughout the country heard of our semester course and asked whether it would be possible to have a special concentrated course. Therefore a 3-week course was arranged for the summer of 1960, covering the same material as that in the semester course. All in attendance had scientific B.S., M.S., or Ph.D. degrees. Some were research group leaders with their companies; others were relatively new college graduates or Ph.D.'s. Upon completion of the course this group left no doubt that the venture was successful, and the scientists in attendance encouraged us to repeat the course. The second year there were more applicants than the course could accommodate. There are now requests by applicants to be put on waiting lists for future summer classes. Inquiries concerning both the regular and concentrated courses come from industries, colleges, and medical laboratories throughout the United States and many other countries as well. Several schools would like to set up similar courses. Some individuals in laboratories would like descriptive material, experiments, equipment, and parts to work with in their spare time on the job

or at home. The many indications of interest demonstrate a need and desire for a special type of training in experimental electronics and have prompted the writing of this book.

Concentrating so much in a 3-week period does not mean that one is "getting something for nothing." Rather, an all-out effort is required. The important point is that the material can be absorbed, and absorbed effectively, in this short period of time. The schedules and responsibilities of many thousands of scientists and engineers are such that a longer period away from their regular jobs is impossible.

The authors' experience has indicated that the experiments can be performed most efficiently and the basic concepts grasped most easily by working in small laboratory sections of five or six students per instructor. As in the regular semester course, each student works at a desk complete with test equipment, parts, and tools which are for his individual use throughout a 4- to 5-hr laboratory period. With an instructor available throughout this period, the give-and-take certainly stimulates the thinking and performance of each person.

There are many who find it necessary to get such training either at home or on the job or not at all. Therefore the problems and experiments have been presented with the hope that the book could serve as a self-teaching text. The circuits could be successfully built, tested, understood, and used by a scientist or engineer working in his home or laboratory. The disadvantage of missing the discussions with instructors and other students could be compensated for by additional reading from the references supplied and by allowing somewhat longer times for the experiments.

As sketched in the following paragraphs, an electronics-instrumentation laboratory made up of relatively inexpensive units is a unique feature of the courses and is described in the book. This carefully planned and tested laboratory setup, which is described in detail, provides the possibility for efficient experimentation either for self-training at home or on the job or in an organized course.

The construction of the circuits described in this book would take much longer than the scheduled 15 half days if only conventional soldering techniques were used. Therefore, many available "breadboarding" schemes were tested to speed up the construction of the circuits. Unfortunately, all had shortcomings, primarily because they were not typical of good wiring practice and the connected circuits had characteristics considerably inferior to those with soldered joints. Therefore a scheme was devised which has subsequently proved completely satisfactory. It increases the speed of construction, testing, and component interchange in circuits at least threefold.

Parts and wires are connected point to point as in conventional practice, but spring clips permit the same parts and wires to be used over

and over again, hundreds of times. The clips bind tightly so that circuit characteristics are, in general, quite similar to those with soldered joints. Component placement and the finished circuit are very similar to that of standard chassis wiring. The complete laboratory system is described in Supplement 1.

The preparation of the original experimental setup was a long and tedious job. The hand making of the parts was very time-consuming and a deterrent to others who wished to use the system. Fortunately, however, all parts and chassis are now commercially produced. All the basic experiments described in this book, including servomechanisms and operational amplifiers for computation and control, can be performed by using the commercially available kits and inexpensive instrumentation laboratory. Hundreds of other useful circuits can also be constructed with the same parts.

Many of those who have taken the course have expressed a keen desire to have a similar complete system at their work or at home and always available for rapidly testing new ideas before permanent construction is attempted. Needless to say, such a system is an excellent aid in building or modifying instruments.

The order in which topics were introduced was changed many times so that the most systematic presentation might be achieved. Discontinuities in the order were revealed by the troubles and questions of the students working in the laboratory. For 3 years now the order has remained essentially unchanged because the response of the students indicated that each experiment and its descriptive material followed logically from previous experiments and descriptive material. On the basis of this experience, it is recommended that anyone unfamiliar with electronics start at the beginning and proceed consecutively through the chapters. To do otherwise would be to risk wasting time in studying and working with the more complex circuits in the later chapters. Those who have some background in electronics may want to delve immediately into the later chapters on servomechanisms, operational amplifiers, and digital systems. For convenient reference and review on basic d-c and a-c circuits, Supplements 2 and 3 have been provided. In these sections the basic laws of electricity, such as Ohm's and Kirchhoff's laws, are presented. Resistors, capacitors, and inductors and their simple networks are discussed. Important tables are included in the Appendix.

Each chapter opens with a discussion of the important basic principles. This is followed by a section of experiments that emphasize the most important aspects of each subject. Although valuable information can be obtained by reading only the discussion sections, there is no doubt that it is by working the experiments that great strides can be made in exploring the new possibilities of electronics in one's own research.

chapter one

Electrical Measurements

The operation of electronic circuits and systems which make up most modern scientific instruments depends on correct values for the components, such as resistors and capacitors, and on the use of suitable voltages and currents of proper phase and frequency within the circuits. To test and study operational characteristics or to trouble-shoot (i.e., determine the cause of instrument failure), it is especially important to make accurate measurements of current, voltage, resistance, phase angle, and frequency. It is the purpose of the discussion and experiments in this chapter to introduce the various test instruments and show how they can be used to obtain reliable information.

Some of the test equipment is relatively simple, and the methods of operation follow directly from a few well-known basic laws of electricity. In such cases, a thorough understanding of the equipment is possible at this point. However, some test equipment, for example, the oscilloscope, is an assemblage of several more or less complex electronic circuits, many of which are the subject of study and experimentation in subsequent chapters. Therefore a detailed understanding of the oscilloscope is not possible at this time; yet it is important to learn now the general functions of its basic circuits and components and how to use it to obtain reliable measurements. With this indispensable test instrument, as well as the other meters available, it is possible to measure the most important variables in all the circuits that are to follow. Since many of the circuits to be studied are the

general building blocks for the oscilloscope as well as most scientific instruments, a greater appreciation and understanding of this test instrument will develop with the completion of subsequent chapters.

1-1 Measurement of Voltage and Current

The purpose of a *voltage* measurement is to determine the *potential difference*¹ between two points in a circuit. The potential difference between any two points in a circuit is measured by connecting the two voltmeter leads to these points (see Fig. 1-1). Thus the voltmeter is connected "across" or in *parallel*² with the circuit whose potential is to be measured.

Because the voltmeter *resistance*³ is not infinite and is connected between two points of unequal potential, a *current*⁴ will occur in the voltage-measuring circuit. The application of the voltmeter to the test points may change the current magnitudes in the circuit enough to cause a considerable change in the potential being measured. If a voltmeter has a resistance of 60 kilohms when switched on the 3-volt scale and its leads are connected across a 10-kilohm resistor in the circuit, the potential across the combination of 10 kilohms and 60 kilohms will no longer be 2.5 volts. The parallel resistance = $(10K \times 60K)/(10K + 60K) = 8.6K$. The potential that the voltmeter will indicate is $10 \text{ volts} \times [8.6K/(30K + 8.6K)] = 2.23 \text{ volts}$. To avoid this kind of error, a voltmeter of sufficiently high internal resistance must be used to make the measurement. The method of determining a voltmeter's resistance is discussed in Sec. 1-2. The slide-wire potentiometer, which makes a potential measurement under conditions approaching zero current through the instrument, is discussed in Chap. 6.

¹ *Voltage* is the difference in electric pressure between two points. The *potential difference* between two points is the work required to transfer a unit quantity of electricity from one point to the other. Between any two points the voltage and the potential difference are the same and are measured in volts. Both terms are commonly used interchangeably and are abbreviated *V*, *E*, or *emf*, although voltage (*V*) usually implies that if the two points were connected in a closed circuit a flow of current would result. A potential difference (*E* or *emf*) may exist between two electrically isolated points simply because of a difference in electrostatic charge. For this reason the terms potential or potential difference are sometimes used to indicate the zero-current or open-circuit potential between two points.

² Circuit components are said to be arranged in *parallel* when each component has both terminals in common with the two terminals of the other components. The voltage is the same across all components connected in parallel.

³ *Resistance* is the opposition to the flow of current offered by a device or circuit element. Resistance (*R*) has for units ohms, abbreviated Ω .

⁴ *Current* is the rate of electric charge transfer from one point to another. Current (*I* or *i*) is measured in amperes, abbreviated *A*. The current in a circuit is related to the voltage and resistance by Ohm's law ($E = IR$), as explained in Supplement 1.

* When kilohms are used in calculations, the symbol *K* is often employed.

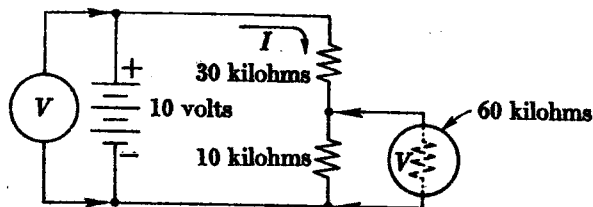


Figure 1-1 Voltage measurement.

The purpose of a current measurement is to determine the rate of electron flow in any given branch of a circuit. The usual current meter must be put in *series*⁵ with the components in that branch so that the electrons flow through the meter coil (see Fig. 1-2). The circuit must be broken to connect the ammeter; therefore the ammeter becomes an essential part of the circuit being measured. Since the ammeter has some internal resistance, its insertion into the circuit may considerably decrease the current in the measured branch. Consider the effect of introducing a milliammeter which has a resistance of 100 ohms in the circuit of Fig. 1-2. The resistance in the R_3 branch will increase to 1.1 kilohms. This will cause only a small change in the potential across R_2 and R_3 . The resistance of R_2 in parallel with R_3 and meter = 525 ohms. The potential across R_2 and R_3 is 1.5 volts ($525/1525$) = 0.517 volt. The current through the meter is then $0.517 \text{ volt}/1.1 \text{ kilohms} = 0.468 \text{ ma}$,⁶ instead of the 0.5 ma that would be read if the meter had zero resistance. The determination of the resistance of a meter is discussed in the next section. This information is important

⁵ Components are said to be in *series* when there is only one point of connection between them. The current through all components arranged in a simple series circuit is the same.

⁶ *Milliampere*, thousandth of an ampere, is abbreviated ma.

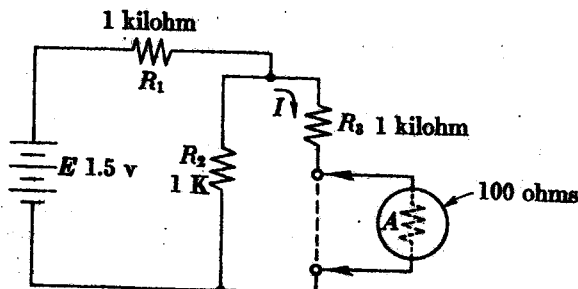


Figure 1-2 Current measurement.

because the meter resistance must be allowed for in connecting current meters into circuits.

1-2 The Moving-Coil Meter

Of all the devices (meters) that convert an electrical quantity to the physical displacement of a pointer or light beam, the moving-coil meter is by far the most common. The moving-coil meter owes its popularity to its great versatility, combined with reasonable ruggedness, accuracy, and simplicity. Discussion of other types of meters, which are used mostly in heavy-duty and special applications, will be found in the References.

The usual D'Arsonval moving-coil meter used in test instruments is shown in Fig. 1-3a. A coil of fine wire, wound on a rectangular aluminum frame, is mounted in the air space between the poles of a permanent horseshoe magnet. Hardened-steel pivots attached to the coil frame fit into jeweled bearings so that the coil rotates with a minimum of friction. An indicating pointer is attached to the coil assembly, and springs attached to the frame return the needle (and coil) to a fixed reference point. When electrons flow through the coil a magnetic field is developed that interacts with the magnetic field of the permanent magnet to force the coil to rotate as in an electric motor. The direction of rotation depends on the direction of electron flow in the coil. The magnitude of the pointer deflection is proportional to the rate of flow of electrons (the current). The laboratory galvanometer is a very sensitive moving-coil meter; it is discussed in Sec. 6-2. A recording galvanometer is shown in Fig. 1-3b. A writing stylus is used instead of a pointer. The stylus can have an ink tip, or it can have a tip that is the contact for an electro-sensitive, heat-sensitive, or pressure-sensitive paper. The roll of chart paper is usually driven by a constant-speed motor. If a writing arm of fixed length is used, the ordinate will be curved. In order to convert the curvilinear motion of the writing tip into rectilinear motion, various writing mechanisms have been devised to change the effective length of the writing arm as it moves across the chart.

The meter movement has three characteristics which are used to determine its effectiveness for a given measurement. These characteristics are sensitivity (milliamperes full scale, microamperes per centimeter, microamperes per degree, etc.), internal resistance (the d-c resistance of the coil in ohms), and accuracy (normally $\frac{1}{2}$ to 3 per cent of full scale deflection for general-purpose meters, and 0.1 to 1 per cent for laboratory types).

When the current through the meter changes value suddenly, it is desirable that the indicator move quickly to its new position with no overshoot or oscillations. This desired behavior is accomplished by *damping* or braking the meter movement. Some meters have a damper built in; others, particularly galvanometers, need to be damped by adjusting the re-