PRENTICE-HALL SERIES IN ELECTRICAL ENGINEERING



Anner



**Elementary Nonlinear** Electronic Circuits

SERIES IN NETWORKS

# ELEMENTARY NONLINEAR ELECTRONIC CIRCUITS

George E. Anner

Professor of Electrical Engineering University of Illinois PRENTICE-HALL INTERNATIONAL, INC., London
PRENTICE-HALL OF AUSTRALIA, PTY, LTD., Sydney
PRENTICE-HALL OF CANADA, LTD., Toronto
PRENTICE-HALL OF INDIA (PRIVATE) LTD., New Delhi
PRENTICE-HALL OF JAPAN, INC., Tokyo

©1967 by PRENTICE-HALL, INC. Englewood Cliffs, N.J.

All rights reserved. No part of this book may be reproduced in any form, by mimeograph or any other means, without permission in writing from the publisher.

Library of Congress Catalog Card Number 66–27953 Printed in the United States of America 25941C

Current printing (last digit): 10 9 8 7 6 5 4 3 2 1

## ELEMENTARY NONLINEAR ELECTRONIC CIRCUITS

#### PRENTICE-HALL ELECTRICAL ENGINEERING SERIES\*

William L. Everitt, Editor

Anner Elementary Nonlinear Electronic Circuits
Anner Elements of Television Systems
Armington & Volz An Introduction to Electric Circuit Analysis
Balabanian Network Synthesis
Barton Radar Systems Analysis
Benedict Introduction to Industrial Electronics
Blackwell & Kotzebue Semiconductor-Diode Parametric Amplifiers\*
Boisvert, Robert, & Robichaud Signal Flow Graphs and Applications
Carlin & Giordano Network Theory: An Introduction to Reciprocal and
Nonreciprocal Circuits

CHANG, K. N. Parametric and Tunnel Diodes CHANG, S. Energy Conversion\*

CHIRLIAN Integrated and Active Network Analysis and Synthesis

DAVIS & WEED Industrial Electronic Engineering

DEKKER Electrical Engineering Materials

DEL TORO Principles of Electrical Engineering

DE PIAN Linear Active Network Theory

DOWNING Modulation Systems and Noise\*

DUNN & BARKER Electrical Measurements Manual

Evans Experiments in Electronics

EVANS Introduction to Electronics

FETT Feedback Control Systems

FICH Transient Analysis in Electrical Engineering
FICH & POTTER Theory of A-C Circuits

LORES Computer Logic: The Functional Design of Digital Computers

FLORES The Logic of Computer Arithmetic\*

FOECKE Introduction to Electrical Engineering Science

GENTRY, ET AL. Semiconductor Controlled Rectifiers: Principles and

Applications of p-n-p-n Devices

GOLDMAN Information Theory

GOLDMAN Transformation Calculus and Electrical Transients

GOLOMB, ET AL. Digital Communications\*

GRAY Digital Computer Engineering\*

HERRERO & WILLONER Synthesis of Filters

HERSHBERGER Principles of Communication Systems

JORDAN Electromagnetic Waves and Radiating Systems

Kuo Analysis and Synthesis of Sampled-Data Control Systems\*

Kuo Automatic Control Systems

LECROISSETTE Transistors

LEGROS & MARTIN Transform Calculus for Electrical Engineers

\*This title is also in the Prentice-Hall International Series in Electrical Engineering. Prentice-Hall, Inc.; Prentice-Hall International, Inc., United Kingdom and Eire; Prentice-Hall of Canada, Ltd., Canada.

LO, ET AL. Transistor Electronics

MALEY & EARLE The Logic Design of Transistor Digital Computers\*

MALEY & SKIKO Modern Digital Computers

MARCUS Switching Circuits for Engineers

MARTIN Electronic Circuits

MARTIN Physical Basis for Electrical Engineering MARTIN Ultrahigh Frequency Engineering

MATSCH Capacitors, Magnetic Circuits, and Transformers
MOSKOWITZ & RACKER Pulse Techniques

NIXON Principles of Automatic Controls

NUSSBAUM Electromagnetic and Quantum Properties of Materials
NUSSBAUM Electromagnetic Theory for Engineers and Scientists
NUSSBAUM Semiconductor Device Physics\*

OGATA State Space Analysis of Control Systems
PARTRIDGE Principles of Electronic Instruments
PASKUSZ & BUSSELL Linear Circuit Analysis

PIERUSCHKA Principles of Reliability\*

POTTER & FICH Theory of Networks and Lines

PUMPHREY Electrical Engineering, 2nd ed.

Pumphrey Fundamentals of Electrical Engineering, 2nd ed. Reed Electric Networks Synthesis

REED Foundation for Electric Network Theory
RIDEOUT Active Networks

ROBERTS & VANDERSLICE Ultrahigh Vacuum and Its Applications
ROBICHAUD, ET AL. Signal Flow Graphs and Applications\*
RUSSELL Modulation and Coding in Information Systems
RYDER, F. L. Creative Engineering Analysis
RYDER, J. D. Electronic Engineering Principles, 3rd ed.

RYDER, J. D. Electronic Fundamentals and Applications, 3rd ed.
RYDER, J. D. Networks, Lines and Fields, 2nd ed.
SANFORD Physical Networks

SHEDD Fundamentals of Electromagnetic Waves
SKRODER & HELM Circuit Analysis by Laboratory Methods, 2nd ed.
SOOHOO Theory and Application of Ferrites
STOUT Basic Electrical Measurements, 2nd ed.
THOMSON Laplace Transformation, 2nd ed.

VAN DER ZIEL Noise

VAN DER ZIEL Solid State Physical Electronics VAN VALKENBURG Network Analysis, 2nd ed.

VON TERSCH & SWAGO Recurrent Electrical Transients
WALLMARK & JOHNSON Field-Effect Transistors: Physics, Technology
and Applications

WARD Introduction to Electrical Engineering, 2nd ed.
WARFIELD Introduction to Electronic Analog Computers
WEED & DAVIS Fundamentals of Electron Devices and Circuits

### NETWORKS SERIES Robert Newcomb, Editor

Anner Elementary Nonlinear Electronic Circuits
CARLIN & GIORDANO Network Theory: An Introduction to Reciprocal
and Non Reciprocal Circuits
HERRERO & WILLONER Synthesis of Filters
VAN VALKENBURG Network Analysis, 2nd ed.

#### **PREFACE**

A large number of excellent text books have been written on the subject of electronic circuits. Why, then, write another?

The answer is that in recent years books tend to emphasize the small signal, linear aspects of the circuits. In so doing they certainly have contributed to a clearer understanding of this phase of electronics, but we must face up to a fundamental truth about electronic devices: their behavior is nonlinear. If this fact is neglected, the consequences of nonlinearity, good or bad, cannot be considered, and worse—may, in fact, be forgotten. Yet many of these factors such as distortion, frequency translation and multiplication, and periodic signal amplitudes in oscillatory circuits are of primary importance in many applications. Some texts touch on these subjects by considering only the most gross features of nonlinearity through use of the piecewise linear technique.

It seems, then, that there is need for a companion text to this literature—a text which emphasizes the nonlinear character of electronic devices and its effect in some sample circuit configurations. This book has been written as such a supplementary text. As the title indicates, the methods used are elementary and teachable at the undergraduate level.

It is inevitable that a text so conceived will include much review material. Its inclusion, however, permits the establishment of a consistent method of approach and notation. With the latter, I have used current standards, despite the recent trend to depart from them.

### ELECTRONIC CIRCUITS

#### **CONTENTS**

#### 1. ONE-PORT DEVECES 1

Nonlinearity 3 Vacuum Diodes 4 power law 4 incremental response 6 Point Contact Diodes 9 modified exponential law 10 small signal response 13 Junction Diodes 14 Negative Resistance Diodes 15 Ideal Diode 18 Taylor Series Expansion 19 evaluation of the Taylor coefficients 20 accuracy of the expansion 22 Fourier Expansion 23 Polynomial Expansion 24 Conductance Expansion 26 Piecewise Linear (PWL) Approximation 28 Multiple Segment PWL Approximations 31 multiple segment PWL models 32 Negative-R PWL Models 39 Summary 42

x Contents

#### 2. TWO-PORT DEVICES 43

Vacuum Triodes 44 Series and Polynomial Expansions 48 Incremental Linear (IL) Models 51 Vacuum Triodes with Positive Grid 53 grid saturation 55 Vacuum Pentodes, Beam Power Tubes 56 conversion factors 59 transitron connection 61 Vacuum Tetrodes 64 Junction Transistors 65 common-base configuration 67 common-emitter configuration 68 Other Devices 73 unijunction transistor 73 field effect transistor 75 semiconductor photoresistors 78 PWL Models 79 triode PWL model 79 pentode PWL models 81 dynatron PWL models 83 transistor PWL models 84

#### 3. ZERO-ORDER SYSTEMS 87

One-Port Device System 88 quiescent point 88 transfer curve, shearing 89 Taylor expansion 92 Two-Port Device Systems 94 transfer curve 95 Taylor expansion 97 Feedback Circuits 98 current feedback 99 voltage feedback 102 Nonlinear Distortion 105 measured distortion 106 transformer-coupled power amplifier 108 calculating distortion 110 harmonic analysis 113 shift of operating point 114 nonsymmetrical waveforms 115 Transistor TPA 117 quiescent point 118 signal conditions 121

Contents xi

Conversion Factors 124 Multiplication 125

#### 4. ZERO-ORDER NEGATIVE RESISTANCE SYSTEMS 128

Negative Resistance Curves 128 Feedback Negative Resistance Circuits 131 voltage feedback circuit 132 current feedback circuit 134 transitron feedback circuit 135 Eccles Jordan Circuit 139 equivalent circuits 141 modes of operation 143 PWL analysis 145 mode sequences 147 graphical analysis 147 Transistorized Eccles Jordan Circuit 155 Transistorized OCS Circuit 158 Stable and Unstable Operating Points 165 Trigger Action 167 Other Applications 168 Compound Curves 170

#### 5. FIRST-ORDER SYSTEMS 177

Power Law Forms 177
Series and Polynomial Forms 179
PWL Solutions 184
Graphical Solutions 185
Isocline Method 186
Incremental Operator Method 188
series R-L circuit 188
TPA-high band 191
shunt R-L circuit; TPA low band 198
capacitive circuits 201
Relaxation Oscillations 205
astable operation 205
waveform calculation 207

#### 6. SECOND-ORDER SYSTEMS 212

Forced Oscillations with Driven Two Port 213

xii Contents

Polynomial Expansion 215 Graphical Analysis; the A-C Load Line 217 Graphical Analysis; Path of Operation 218 Frequency Multiplication 223 Linear Path of Operation 225 Incremental Operator Solution 229 Self Oscillations 235 Linear Oscillator 236 Second-Order Isocline Method 237 Direction of Increasing Time in the Phase Plane 241 Nonlinear Oscillator; van der Pol's Equation 242 van der Pol's Equation: Isocline Solution 245 Amplitude of Oscillation 247 harmonic balance 247 energy considerations 249 van der Pol's Equation, Graphical Solution 251 Nonlinear Oscillator; Rayleigh's Equation 253 The Lienard Construction 256 unnormalized form 259 incremental operation about a Q point 260 The Conventional Tank Circuit 261 The Toned-Plate Oscillator 262 Series Tank Circuit 264

INDEX 267

#### Chapter ONE

#### ONE-PORT DEVICES

Electronic devices inherently exhibit rather complicated behavior: first, their behavior is nonlinear; second, it is frequency dependent because of capacitive and transit-time effects; third, it is corrupted by internally generated noise signals, and fourth, it may be influenced by environmental conditions such as temperature. It is therefore rather difficult to find some means for expressing all aspects of this behavior in a simplified form.

It is fortunate, however, that this is usually unnecessary since in any given application of an electronic device not *all* these aspects are equally important or relevant. For example, it is usually true that when the signals applied to the device are so large that nonlinearity must be considered, they are also so much larger than the internally generated noise signals that the latter may be neglected.

Thus in any given application we seek a simplified representation of only the cogent aspects of the device behavior, omitting those aspects which have little or no effect in the particular application. This process of neglecting irrelevant behavior and representing the important aspects in simplified form is known as *modeling*.

In this book we shall be concerned primarily with the nonlinearity of electronic devices and we shall use the measured terminal characteristic curves of a device as the basic means of describing this at low frequencies. Our attempts at modeling will then follow two paths: the first will be mathe-

matical. Here we derive an equation giving an approximate fit to the device curves, either in a gross manner, or over only a limited range. The second path will lead to the arrangement of a set of linear circuit elements into a configuration whose response approximates the device curves. Notice, then, that we shall use three methods of approximating the performance of electronic devices—curves, equations, and circuit models. As might be expected all three methods of specification are equivalent for a particular electronic device only within the limits under which they are measured or derived.

From the point of view of modeling, we often face the problem of obtaining suitable device curves. This is because, at the present state of the art, it is impossible to manufacture a number of electronic devices which have identical characteristics even though they may have similar characteristics and hence may be grouped together under a certain identifying type number or designation.

A good example of this is afforded by Fig. 1-1 which displays the measured curves of the two sections of a 6AL5 twin-diode vacuum tube which was chosen at random. From the curves we may note, for example, that at e=1.6 volts, the currents of the two sections, which presumably should be identical, differ by roughly 8 per cent. It is not feasible for device manufacturers to furnish curves with each diode; instead the behavior of such a device type is usually described by average curves (or average parameter values) which are made available by the manufacturer. It must be remem-

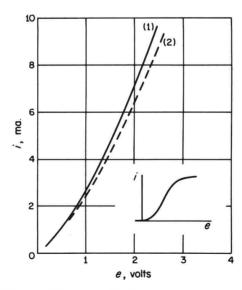


Fig. 1-1. Characteristic curves for the two sections of a 6AL5 vacuum twin diode. The inset shows a typical curve for e large enough for saturation and cutoff.

bered, however, that any particular sample of the type may differ considerably from these average specifications. In vacuum devices this deviation may run as high as  $\pm 20$  per cent and in semiconductor devices as much as  $\pm 50$  per cent. The latter are quite temperature sensitive and even greater deviations may occur when the operating temperature differs markedly from the published values. For these reasons we find that manufacturers are often reluctant to furnish even average curves for the semiconductor devices.

The analysis and design of electronic circuits, then, is not an exact business when we work from published average data. If a basic error of up to 50 per cent is present in specifying the device behavior, calculating circuit performance to 3 or 4 significant figures is pointless. In fact in many instances a chief concern of design is to minimize the effect of device parameter variation.

#### A. NONLINEARITY, NONLINEAR RESISTANCE

Since we shall be directing our primary attention to the subject of non-linearity, some clarification of notation should be made. At low frequencies, electronic devices are basically resistive in nature, i.e., a curve (or family of curves) in the current-voltage plane defines the device operation. Now if a passive resistance element is linear, it may be described for all values of e and i by the equation i = e/R, where R is the linear resistance. The corresponding curve in the i vs e plane would be a straight line through the origin with a slope of m = 1/R. Notice that m has the dimension of conductance and can also be symbolized by G, the conductance of the passive element.

A nonlinear passive resistance, which we may represent by the symbol  $\mathcal{R}$ , will, then, depart from this ideal. Two examples are shown in Fig. 1-2. At (a) we see a curve which is nonlinear in the usual sense that it is a curved rather than a straight line. This sort of curve is said to display a *soft* nonlinearity.

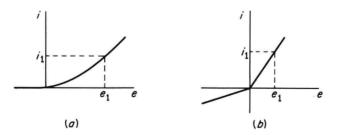


Fig. 1-2. Nonlinear resistance curves. (a) Soft nonlinearity. (b) Hard nonlinearity of piecewise linear form.

At (b) we observe a nonlinearity of a different type in that no curved region is present. The curve comprises two linear segments with a "breakpoint" or change of slope which, in this instance, lies at the origin. This type of curve is often called *piecewise linear*, abbreviated PWL, and is said to display a *hard* nonlinearity.

It is apparent that no single value of resistance, R, can be associated with the nonlinear resistance in Fig. 1-2. By convention we define two resistances as follows:

 $R_b$  = static or total resistance

$$=\frac{e}{i} \tag{1-1}$$

 $r_p$  = dynamic, differential, or incremental resistance

$$=\frac{de}{di} \tag{1-2}$$

It is apparent in Fig. 1-2(b) that  $R_b = r_p$  at any point, and further that  $R_b$  is constant for positive e and constant at a different value for negative e. In Fig. 1-2(a),  $R_b$  and  $r_p$  vary from point to point and are never equal for positive e. For negative e, however, and at the origin,  $R_b = r_p = \infty$ . As we encounter other nonlinear characteristics that differ in some manner from those of Fig. 1-2, we shall observe other properties of the total and incremental resistances.

In the remainder of this chapter we shall consider the characteristics of some common one-port or two-terminal, electronic devices. Their basic behavior is described by a single  $\mathcal{R}$  curve. We shall also investigate means for modeling these characteristics.

#### **B.** VACUUM DIODES

The characteristic curves of typical vacuum diodes have the form shown in Fig. 1-1 which is plotted for the 6AL5 twin diode. Shown at the inset is the curve for a larger range of positive e values. For large e where current is less dependent upon voltage the operation is said to be *saturated*. In this saturation region, which lies above the normal range of current and voltage, current is limited by emission from the cathode. For negative e, i = 0, i. e., the current is cut off. The reverse voltage region is often called the *cutoff* region.

#### B-1 POWER LAW

In trying to derive a mathematical model or equation to describe the device curve, we find it is helpful to replot the positive e data, say of curve (1) in