DIGITAL LOGIC CIRCUITS:

TESTS AND ANALYSIS ROBERT G. MIDDLETON



DIGITAL LOGIC CIRCUITS: TESTS AND ANALYSIS

Bob Middleton has been a professional free-lance technical writer in the electronic field for many years. His many books and magazine articles have proved invaluable to students, technicians, and engineers, because they have all been based on his own practical experience. His home workshop is filled with test equipment, receivers, and other equipment that he uses to check out every detail in preparing his many books.

Other Sams books by Mr. Middleton include 101 Ways to Use Your VOM, TVM & DVM, Know Your Oscilloscope, Troubleshooting With the Oscilloscope, Effectively Using the Oscilloscope, and many others.



DIGITAL LOGIC CIRCUITS: TESTS AND ANALYSIS BY ROBERT G. MIDDLETON

Bob Middleton has been a professional free-lance technical writer in the electronic field for many years. His many books and magazine articles have proved invaluable to students, technicians, and engineers, because they have all been based on his own practical experience. His home workshop is filled with test equipment, receivers, and other equipment that he uses to check out every detail in preparing his many books.

Other Sams books by Mr. Middleton include 101 Ways to Use Your VOM, TVM & DVM, Know Your Oscilloscope, Troubleshooting With the Oscilloscope, Effectively Using the Oscilloscope, and many others.



PREFACE

Troubleshooting digital logic circuits is now an activity of major concern to electronic technicians. A digital revolution has occurred and has irreversibly changed the structure of consumer electronics. For example, television receiver tuning is often accomplished by digital arrangements, and specialized models provide for extensive digital pre-programming of receiver operation. Digital controlled readout of the operating channel and the time may also be provided. Digital filtering techniques are utilized for optimum separation of chroma and Y signals. Scanner-monitor radio receivers employ automatic digital tuning techniques. A frequency readout is provided on am, fm, and communications receivers. Digital control techniques and programming routines have made significant entry in the high-fidelity scene. Personal computers have found widespread acceptance in homes and offices. Automobiles are becoming computerized to an everincreasing extent.

This book emphasizes practice—not theory. Its purpose is to show you how to make basic digital tests and measurements as efficiently as possible. The techniques are presented without frills or double talk. Most digital servicing is done with logic probes and logic pulsers. These instruments are in the category of go/no-go testers, although they also provide general test data concerning frequency, transient occurrences, and logic levels. Logic probes and pulsers are voltage-operated devices. They are supplemented advantageously by the current tracer which senses current flow in the circuit. Logic clips, comparators, and oscilloscopes are also used in practical test procedures. Sometimes malfunction in a digital system results merely from a marginal power-supply voltage—here, the dvm does yeoman service. Even the ohmmeter finds occasional application.

Copyright © 1982 by Howard W. Sams & Co., Inc. Indianapolis, IN 46268

FIRST EDITION FIRST PRINTING—1982

All rights reserved. No part of this book shall be reproduced, stored in a retrieval system, or transmitted by any means, electronic, mechanical, photocopying, recording, or otherwise, without written permission from the publisher. No patent liability is assumed with respect to the use of the information contained herein. While every precaution has been taken in the preparation of this book, the publisher assumes no responsibility for errors or omissions. Neither is any liability assumed for damages resulting from the use of the information contained herein.

International Standard Book Number: 0-672-21799-6 Library of Congress Catalog Card Number: 81-86555

Edited by: Welborn Associates Illustrated by: Christine Lixon

Printed in the United States of America.

CONTENTS

PART 1 INTRODUCTION

Section 1

| Basic Test Equipment Logic Pulser—Basic Gates—Common Troubles in Digital Circuitry—Scanner-Monitor Digital-Logic Section Checks—Positive Logic and Negative Logic—Applications of Logic Current Tracer—Equivalent Gates in Digital Logic Circuits—Common Causes for Puzzling Observations—Sensitivity Control Settings—Digital IC Failure Modes—Waveform Checks in Dedicated Digital Equipment—Digital Pulse Voltage Tolerance—Level Indicators—Current and Voltage in Failed ICs—In-Circuit Versus Out-of-Circuit Tests—Fan-In/Fan-Out Principles—Glitches Caused by Baces at Gate Inputs—Noise Glitches in Digital | 9 |
|---|---|
| Tests—Fan-In/Fan-Out Principles—Glitches Caused by Races at Gate Inputs—Noise Glitches in Digital Waveforms | |

| ADDERS AND SUBTRACTERS |
|---|
| Half-Adder Operation—Operation of Basic Full |
| Adder—Subtraction by Full Adders—Parallel Adder |
| Function—Sign-Magnitude Adder/ Subtracter |

In this book, no previous experience with digital circuitry is assumed. The coverage starts with simple gates, illustrates commercial IC package pinouts, and introduces the reader to truth tables. Test procedures are initially concerned with verifying device input/output relations as specified in the associated truth table. Of course, not all digital trouble symptoms are caused by IC faults—poor contacts, solder "whiskers," or broken pc conductors may also cause trouble symptoms. Suitable follow-up tests are often required to pinpoint the trouble to device failure or to external circuitry. We have attempted to anticipate all of the pitfalls that lie in wait for the beginner. It is sometimes remarked that a digital troubleshooter need pay attention only to the IC package pinout and to its truth table. However, this is somewhat of an oversimplification. As in television troubleshooting procedures, the technician will be called upon to reason back from symptom to cause, and to systematically eliminate various possibilities on the basis of tests and measurements.

Electronics technology is becoming increasingly advanced and sophisticated. We must keep up with these advances if we are to remain competitive. Unless the full capabilities of the logic probe, pulser, current tracer, logic clip, comparator, and oscilloscope are clearly understood, it will become much more difficult in the future to properly service modern electronic circuitry.

In preparing this new working handbook, I have recognized the current need, and have made a dedicated effort to meet it. It is my firm belief and sincerest hope that this book will be a valuable addition to the libraries of all present and future electronic service technicians.

ROBERT G. MIDDLETON

| PARITY GENERATOR/CHECKERS |
|---|
| Section 10 |
| SCHMITT TRIGGERS AND MONOSTABLE MULTIVIBRATORS135 Monostable Multivibrators—Monostable Multivibrator Applications |
| Section 11 |
| EXPANDABLE GATES AND DIGITAL LOGIC DIAGRAMS |
| Section 12 |
| INVERTERS, BUFFERS, AND DRIVERS |
| Section 13 |
| MEMORIES149 |
| Section 14 |
| MISCELLANEOUS DIGITAL TESTS |

| Feed-Through Latch—Operation of a Delay (D) Latch—One-Pulse Circuit—Edge-Triggered Flip- Flops—Clock, Preset, and Clear Signals—Operation of a D Flip-Flop—Operation of a JK Flip-Flop—Flip- Flop Family Relations—Logic Probe, Pulser, and Current Tracer in JK Flip-Flop Troubleshooting | |
|--|--|
| Section 4 | |
| SHIFT REGISTERS | |
| Section 5 | |
| COUNTERS | |
| Section 6 | |
| Priority Encoder—MSB and LSB—Digital Clock Signals | |
| Section 7 | |
| MULTIPLEXERS | |
| Section 8 | |
| COMPARATORS | |
| | |

| 15-25. | Oscilloscope |
|------------------|---|
| 15-26. 15-27. | |
| 15-28. | Oscilloscope |
| 15-26. | |
| | Section 16 |
| ADDE | RS189 |
| 16-1. | To Check a Dual Carry/Save Full Adder |
| 16-2. 16-3. | To Check the Operation of a 2-Bit Full Adder189 To Check the Operation of a 4-Bit Full Adder191 |
| 16-4. | To Check the Operation of a Dual Carry |
| 16-5. | Dependent Full Adder |
| | Section 17 |
| LATCH | IES AND FLIP-FLOPS |
| 17-1. | To Check the Operation of a 4-Bit Latch |
| 17-2. | To Check the Operation of a JK Master/Slave Flip-Flop |
| 17-3. | To Check the Operation of a JK Master/Slave |
| 17-4. | Flip-Flop With AND-OR Inputs |
| | Flip-Flop With AND Inputs205 |
| 17-5. 17-6. | To Check a D-Type Edge-Triggered Flip-Flop206 To Check the Operation of a JK Master/Slave |
| 17 0. | Flip-Flop With Separate Presets, Clears, |
| | and Clocks |
| | Section 18 |
| SHIFT | REGISTERS213 |
| 18-1. | To Check the Operation of a 5-Bit Shift |
| 18-2. | Register |
| | Register |
| 18-3. | To Check the Operation of an 8-Bit Bidirectional Shift Register214 |
| 18-4. | To Check the Operation of a Shift Register With a Logic Comparator |

| 18-5. | To Check the Operation of a Shift Register With a Logic Clip219 |
|----------------|--|
| | Section 19 |
| COUN | TERS221 |
| 19-1. | To Check the Operation of a 4-Bit Binary Counter221 |
| 19-2. 19-3. | To Check the Operation of a Decade Counter221 To Check the Operation of a Divide-by-12 |
| 19-4. | Counter |
| 19-5. | With Strobe Input |
| 19-6. | To Check the Operation of a Counter With a Logic Comparator |
| | Logic Comparator |
| | Section 20 |
| DECO | DERS AND ENCODERS229 |
| 20-1. 20-2. | To Check the Operation of a 1-of-10 Decoder/Driver |
| 20-3. | To Check the Operation of a BCD to 7-Segment Decoder |
| 20-4. | To Check the Operation of a Nixie 1-of-10 Decoder/Driver |
| 20-5. | To Check the Operation of a Decoder With a Logic Comparator |
| 20-6. | To Check the Operation of an Eight-Input Priority Encoder |
| 20-7. | To Check the Operation of an Encoder With a Logic Comparator234 |
| | Section 21 |
| MIIITI | PLEXERS |
| 21-1. | To Check the Operation of a Dual Four-Input |
| = 1 3A | Multiplexer241 |
| 21-2. | To Check the Operation of a Quad Two-Input Multiplexer241 |

| 21-3. | To Check the Operation of an Eight-Input |
|----------------|--|
| 21-4. | Multiplexer242 To Check the Operation of a 16-Input |
| Z 1-4. | Multiplexer245 |
| 21-5. | To Check the Operation of a Multiplexer With |
| | a Logic Comparator245 |
| | Section 22 |
| COMF | PARATORS251 |
| 22-1. | To Check the Operation of a 4-Bit Quad |
| | Exclusive-NOR Comparator251 |
| 22-2. | To Check the Operation of a 5-Bit Comparator251 |
| | Section 23 |
| DA DIT | Y GENERATOR/CHECKERS255 |
| | SE SECTION OF THE SEC |
| 23-1. 23-2. | To Test an 8-Bit Parity Generator/Checker255 To Test a 9-Bit Parity Generator/Checker255 |
| 23-2. 23-3. | To Test a 12-Input Parity Generator/Checker258 |
| 23-4. | To Test a Parity Generator/Checker With a |
| | Logic Comparator258 |
| | Section 24 |
| SCHN | IITT TRIGGERS AND MONOSTABLES261 |
| 24-1. | To Check the Operation of a Dual Four-Input |
| | NAND Schmitt Trigger261 |
| 24-2. | To Check the Operation of a Monostable |
| 24-3. | Multivibrator |
| 24-3. | Monostable Multivibrator264 |
| 24-4. | To Check the Operation of a Retriggerable, |
| | Resettable Monostable Multivibrator265 |
| | Section 25 |
| EXPA | NDABLE GATES267 |
| 25-1. | To Check the Operation of an Expandable |
| | Two-Wide, Two-Input AND-OR-INVERT Gate267 |
| 25-2. | To Check the Operation of a Dual Four-Input |
| | Expander |

| 25-3. | To Check the Operation of an Expandable 2-2-2-3-Input AND-OR Gate | 8 |
|----------------|---|-----|
| | | |
| | Section 26 | |
| INVEF | RTERS, BUFFERS, AND DRIVERS27 | '1 |
| 26-1. | To Check the Operation of a Hex Inverter | |
| 20-1. | Buffer/Driver | 1 |
| 26-2. | To Check the Operation of a Quad Two-Input | |
| 26-3. | NAND Buffer | 1 |
| 20-3. | Interface Element27 | '3 |
| 26-4. | To Check the Operation of a Dual Two-Input | |
| 00.5 | Compatible Interface | 4 |
| 26-5. | Driver | '5 |
| 26-6. | To Check the Operation of a Tri-State Bus | |
| 00.7 | Driver | 5 |
| 26-7. 26-8. | To Check a Triple EIA RS-232-C Line Driver27 To Check the Operation of a Triple EIA | Ь |
| 20 0. | RS-232-C Line Receiver27 | '9 |
| 26-9. | To Check the Operation of a Dual Differential | |
| 26-10. | Line Driver | 9 |
| 20-10. | Zero/One Element27 | '9 |
| | | |
| | | |
| | Section 27 | |
| MEMO | DRIES | 7 |
| 27-1. | To Check the Operation of a 256-Bit | |
| | Read/Write Memory and Decoder Driver28 | 17 |
| 27-2. | To Check the Operation of a 64-Bit Fully Decoded Read/Write Memory | 17 |
| 27-3. | To Check the Operation of a 1024-Bit Read | |
| | Only Memory | 0 |
| 27-4. | To Check the Operation of a 16-Bit Coincident | ٠, |
| 27-5. | Select Read/Write Memory29 To Check the Operation of a 1K \times 1-Bit | U |
| | Static RAM | 0 |
| 27-6. | To Check the Operation of a 4096 × 1-Bit | . ~ |
| | Dynamic RAM29 | J |

| MISCE | LLANEOUS DIGITAL TESTS299 |
|--------|---|
| | To Map the Trouble Area in a Digital System299 To Make a Temperature Test of an IC299 |
| | To Identify a Defective IC by Voltage |
| 28-4. | Measurements |
| 20-4. | Milliohmmeter |
| 28-5. | Checking Circuit Action by Pin Lifting300 |
| 28-6. | Trouble Analysis by Card-Swapping |
| 28-7. | Troubleshooting by Comparative Tests301 |
| 28-8. | To Check the Output from a Logic Pulser302 |
| 28-9. | To Measure Propagation Delay303 |
| 28-10. | To Check the Output from a Digital Word |
| | Generator303 |
| 28-11. | To Check Master and Subordinate Clock Signals303 |
| Index | |