

Switching and Linear Power Supply, Power Converter Design

ABRAHAM I. PRESSMAN

Switching and Linear Power Supply, Power Converter Design

ABRAHAM I. PRESSMAN



HAYDEN BOOK COMPANY, INC.

— Rochelle Park, New Jersey

To
ANNE
Norman, Daniel, Eric, Dotty
Jeremy and Julie

Library of Congress Cataloging in Publication Data

Pressman, Abraham I

Switching and linear power supply, power converter
design.

Includes Index.

1. Electronic apparatus and appliances—Power
supply. 2. Voltage regulators. 3 Electric current
converters. I. Title.

TK7868.P6P74

621.3815'37

77-14639

ISBN 0-8104-5847-0

Copyright © 1977 by HAYDEN BOOK COMPANY, INC. All rights reserved.
No part of this book may be reprinted, or reproduced, or utilized in any
form or by any electronic, mechanical, or other means, now known or
hereafter invented, including photocopying and recording, or in any infor-
mation storage and retrieval system, without permission in writing from
the Publisher.

Printed in the United States of America

1	2	3	4	5	6	7	8	9	PRINTING
77	78	79	80	81	82	83	84	85	YEAR

Preface

It is widely experienced throughout the electronics/aerospace industry that power supplies give rise to more problems in design and reliability than the complex systems which they power. This book seeks to remedy that situation. It deals with all aspects of power supply design—from the initial block diagram systems alternatives to the detailed circuit design of all the electronics within the blocks. Written for both design engineer and undergraduate with little or no knowledge of the power supply field and the available design alternatives, this text should enable them first to make the best decision on a system block diagram concept and then to implement it with detailed circuits, magnetics, and a safe thermal design.

Switching regulators—which are in the process of revolutionizing the power supply industry because of their low internal losses, small size, and weight and costs competitive with conventional series-pass or linear power supplies—are covered fully. Half-cycle width-modulated dc/dc converters, dc/dc voltage down chopping, voltage up chopping, and transformer-coupled flyback regulators are detailed. Design equations for critical components are derived and typical designs presented. The dc/dc square-wave converters, used so frequently with switching regulators in modern power supply systems, are treated in depth.

For the present, series-pass regulators remain the major design approach in the industry; these are discussed at length along with their fields of application, advantages, capabilities, and disadvantages. Logical, step-by-step design procedures are offered, and combinations of series-pass and -switching regulators that retain the best capabilities of each type in a complex system are demonstrated. Efficiencies of various combinations are calculated.

Extensive discussion is devoted to magnetics—transformer and inductor design for high-frequency switching regulators. Design equations for transformer core selection for a given power level, frequency, and magnetic flux density are derived and typical designs shown. Design of inductors with air gaps or molypermalloy powder cores to avoid saturation in usual switching regulator usages is also presented.

Elements of thermal design and heat-sink performance are evaluated, with design equations and graphs showing temperature rise as a function of power level, area, and air flow. Feedback loop stability is treated in detail. Throughout, graphs are presented which permit gain and phase-shift calculations in the usual switching regulator elements—the LC filter and operational amplifiers with RC feedback. Tailoring the gain-phase characteristic to achieve loop stability is also discussed, along with commonly occurring problems in circuits and subtle failure modes in switching and series-pass power supplies.

The electronics industry has long had a vital need for a textbook on the reliable design of all the complex electronics in a modern society—computers, communications equipment, weapons systems and satellites, industrial control, and consumer electronic equipment. It is hoped that this book will fulfill the need for a comprehensive treatment of this significant element in our modern electronic world.

ABRAHAM I. PRESSMAN

Waban, Massachusetts

Contents

1	Basic Voltage Regulators, Power Converters	1
1.0	Introduction	1
1.1	DC Voltage Regulators	1
	<i>Series-Pass Regulators, 1 Series-Pass Regulator Efficiency, 3</i>	
1.2	Pulse-Width-Modulated Series-Switch Step-Down Converter	5
	<i>Pulse-Width-Modulated Voltage Converter Efficiency, 6 Pulse-Width-Modulated Series-Switch Step-Down Regulator, 7</i>	
1.3	Pulse-Width-Modulated Step-Up Converter/Regulator	9
	<i>Pulse-Width-Modulated Step-Up Converter Efficiency, 10 Input-Output Voltage Relationship, 11 Pulse-Width-Modulated Shunt-Switch Step-Up Regulator, 11</i>	
1.4	Pulse-Width-Modulated, Single-Ended, Transformer-Coupled Energy Storage Converter/Regulator	12
	<i>Input-Output Voltage Relationship, 13 Single-Ended Transformer-Coupled Regulator, 14</i>	
1.5	Zener Diode Regulators	15
	<i>Zener Voltage-Current Characteristics, 15 Zener Diode Output Impedance, 16 Zener Diode Temperature Coefficients, 19 Operating Point Selection for Zener Diode Regulators, 20 Temperature-Compensated Zener Reference Elements, 24</i>	
1.6	Zener Diode-Emitter Follower Regulator	24
	<i>Typical Example of Zener Diode-Emitter Follower Regulator, 25 Collector Leakage and Minimum Output Currents, 29 Sensitivity to Collector Voltage Variations, 29 Zener and Emitter Follower Power Dissipations, 31 Problems, 32</i>	
2	Basic Square-Wave Power Converters, Regulators	34
2.0	Introduction	34
2.1	Driven Push-Pull Converters	34
	<i>Basic Circuit, 34 Generation of Multiple-Output Voltage from a Single dc Source, 35 Converter Efficiencies, 36 Filtering of Square-Wave Voltages, 38 Input-Output Voltage Relationship, 39 Output Impedance, 39 High-Frequency Operation, 40 Transformer Core-Material Selection, 42 Converter Transistor Selection, 45</i>	
2.2	Driven Bridge Converters	55
2.3	Driven Half-Bridge Converters	56
2.4	Square-Wave Oscillator Converters	58
	<i>Relative Merits of Driven and Square-Wave Oscillator Converters, 58 Single-Transformer, Square-Wave Power Oscillator</i>	

	<i>Converter, 58 Two-Transformer, Square-Wave Power Oscillator, 62</i>	
2.5	Half-Cycle, Width-Modulated Converters	68
	<i>Half-Cycle, Width-Modulated Converter Regulator, 71 Half-Cycle, Width-Modulated Regulator Advantages, 71 Problems, 72</i>	
3	Building Block Assembly of Compound Regulating Systems	74
3.0	Introduction	74
3.1	General Classes of Regulating Systems	75
	<i>Preregulator-Driven dc/ac Converter with Open-Loop Secondary Outputs, 75 Preregulator-Driven dc/ac Converter with Rectified Secondary Feedback, 76 Unregulated dc/ac Converter with Postregulators Following Secondary Rectification, 78 Preregulator-Driven Converter with Postregulation Following Secondary Rectification, 81 Half-Cycle, Width-Modulated Inverter with Rectified Secondary Feedback and Line-Only Regulated Slave Outputs, 83 Half-Cycle, Width-Modulated Inverter with Rectified Secondary Feedback and Postregulated Slave Outputs, 84</i>	
3.2	Building Block Combinations of Preregulated dc/dc Converters with Open-Loop Secondary Outputs	84
	<i>Series-Pass, 84 Series-Switch Step-Down, 89 Shunt-Switch Step-Up, 91 Width-Modulated Inverter, 93</i>	
3.3	Building Block Combinations of Preregulated Converters with Rectified Secondary Feedback	94
3.4	Building Block Combinations of Unregulated dc/dc Converter with Postregulated Secondary Outputs	94
	<i>Series-Switch Step-Down, 94 Series-Pass Postregulator, 95</i>	
3.5	Building Block Combinations of Preregulated dc/dc Converters with Postregulated Secondary Outputs	96
	<i>Series-Switch Step-Down Preregulator with Series-Pass Postregulator, 96 Series-Switch Step-Down Preregulator with Series-Switch Step-Down Postregulator, 98</i>	
3.6	Building Block Combinations of Half-Cycle, Width-Modulated Inverters with Line-Only-Regulated Slave Outputs	98
3.7	Building Block Combinations of Half-Cycle, Width-Modulated Inverters with Postregulated Slave Outputs	98
	<i>Series-Pass Postregulators, 98 Series-Switch Step-Down Postregulators, 98</i>	
3.8	DC Prime Power Systems	99
3.9	Prime Power Systems with 400-Hz Line Frequency	101
	<i>Transformer-Isolated Series-Switch Step-Down Regulators, 101 Power Transformer-Rectifier-Driven Series-Pass Preregulator with a dc/dc Converter with Open-Loop Secondaries, 102 Problems, 103</i>	

4	Elements of Thermal Design	105
4.0	Introduction	105
4.1	Maximum Permissible Temperature and Temperature Deratings	105
4.2	Temperature Calculations and Thermal Resistance Concept	107
4.3	Transistor Junction Temperature Calculations	109
	<i>Junction Temperatures for Heat-Sink-Mounted Transistors, 109 Thermal Resistance/Thermal Conductivity/Geometry Relationships, 111 Thermal Resistance Calculation for a Potted Toroidal Core Transformer in a Cylindrical Hole in a Heat Sink, 113 Thermal Resistance of TO3 Transistor on L-Shaped Aluminum Mounting Bracket, 114 Thermal Resistance of a 2-Mil Mica-Insulating Washer for a TO3 Case, 115</i>	
4.4	Heat Sink Fundamentals	116
	<i>Thermal Resistance/Heat Sink Area Relationship, 116 Thermal Resistance/Heat Sink Power Level Relationship, 118 Forced Convection Cooling of Heat Sinks, 119 Heat Sink Thermal Resistance/Volume Relationship, 121</i>	
4.5	Transistor Power Dissipation Ratings	122
	<i>Junction-to-Ambient Air Thermal Resistance, 123</i>	
4.6	Power Transistor Insulating Washers	124
4.7	Temperature Rise/Air-Flow Rate Calculations for Fan Cooling of Power Supply Cabinets	124
	<i>Problems, 125</i>	
5	Elements of Rectifier Design	127
5.0	Introduction	127
5.1	Rectifier Circuits and Output-Input Relationships for Resistive Loads	129
5.2	Capacitive Input Filters	130
	<i>Output Ripple/Filter Capacitance and Load-Current Relationship, 131 Filter Capacitance Proportional to Load Current, 132</i>	
5.3	Rectifier Diode Characteristics and Ratings	133
	<i>Peak Repetitive Reverse Voltage Rating (V_{rm}) and Input Transients, 133 Rectifier Peak Reverse Voltages with Capacitive Input Filters, 137 Maximum Average Forward-Rectified Current (I_o), 137 Rectifier Diode Dissipation with Capacitive Input Filters and Sine-Wave Power Input, 138 Nonrepetitive Peak Surge Current [$I_{fm(surge)}$], 141 I^2t rating, 142</i>	
5.4	Circuit Considerations	142
	<i>Bridge Versus Center-Tap Rectifiers, 142 Three-Phase, Full-Wave Versus Half-Wave, Line-to-Neutral "Wye" Circuits, 143 Peak and Valley dc Output Voltages for Various Rectifiers with Capacitive Input Filters, 143 Rectifier Circuits for Various Output Voltage Combinations, 144</i>	

5.5	Multiplier Circuits	146
	<i>Selection of Multiplication Ratio, 148 Resistive Isolation of Multiplier Capacitor Ladder, 148 Problems, 148</i>	
6	Series-Pass Regulators	149
6.0	Introduction	149
6.1	Line-Voltage-Regulation Calculation	149
	<i>Operating Point Effect on Line Regulation, 151 Line-Voltage Regulation with Darlington Series-Pass Element, 152</i>	
6.2	Load-Current-Regulation Calculation	153
6.3	Series-Pass Regulator Efficiency with Rectified ac Input Voltage	154
	<i>Selection of Transformer Secondary Voltage for a Maximum Efficiency Pass Regulator for Fixed Output Voltage, 156</i>	
6.4	Series-Pass Transistor Configurations	159
	<i>Single-Transistor Series-Pass Elements, 159 Base Drive Problems with Single-Transistor Series-Pass Elements, 160 Improved Current Source Drive for Series-Pass Elements, 161 Constant-Current Transistor Drive for Series-Pass Elements, 162 Complementary Transistor Drive for Series-Pass Elements, 164</i>	
6.5	Difference Amplifiers	166
	<i>Two-Transistor, Emitter-Coupled Difference Amplifier, 167 Transconductance and Gain in the Emitter-Coupled Difference Amplifier, 169 Difference Amplifier Transconductance from a Circuits Viewpoint, 171 Alternative Difference Amplifiers, 172</i>	
6.6	Drift in Regulated Output Voltage	174
	<i>Single- and Double-Ended Difference Amplifier Drift, 174 Difference Amplifier "Offset" Voltage Drift, 177 Difference Amplifier Offset Current Drift, 179 Reference Voltage Drift, 179</i>	
6.7	Feedback Amplifier Configurations	180
	<i>Feedback Amplifiers with Double-Ended Difference Amplifier Output, 180 Feedback Amplifiers with Single-Ended Difference Amplifier Output, 182</i>	
6.8	Protection Circuits	182
	<i>Overcurrent Protection, 183 Constant-Current Overcurrent/Short-Circuit Protection, 184 Current Foldback Overcurrent Protection, 184 Constant-Current Circuit Implementation, 186 Current Foldback Circuit Implementation, 187 Quantitative Relations in the Current Foldback Overcurrent Protection Circuit, 188 Magnitude of Short-Circuit Foldback Current, 190 Latch-Up in Overcurrent Protection Circuits, 191</i>	
6.9	Overvoltage Protection	193
	<i>Overvoltage Protection Circuits, 195 Overvoltage Protection Situations, 199</i>	

6.10	Thermal Calculations Problems, 201	200
7	Integrated-Circuit Voltage Regulators	203
7.0	Introduction	203
7.1	Fairchild 723 Integrated-Circuit Voltage Regulator <i>Internal Circuit Details, 205 Integrated Regulator Applications Using the 723, 215</i>	204
7.2	National Semiconductor Integrated Voltage Regulators <i>LM105 Integrated-Circuit Voltage Regulator, 219</i>	219
7.3	Motorola Integrated Voltage Regulators <i>MC1561 Integrated-Circuit Voltage Regulator, 225</i>	225
8	DC/DC Square-Wave Converter Design	230
8.0	Introduction	230
8.1	Transformer Core Geometry, Hysteresis Loss, and Peak Flux Density	230
8.2	Transformer Core Selection: Core Geometry Versus Power-Handling Relationships	236
8.3	Selection of Number of Turns per Winding	245
8.4	Winding Copper Losses	245
8.5	Transformer Thermal Design <i>Thermal Resistance of a Typical Ferrite Cup Core Transformer, 249 Winding Temperature Rise in a Typical Cup Core Transformer, 252 Winding Fit within Available Winding Space, 253 Coil Temperature Rise in Unpotted Transformers without Heat Sink, 254 Coil Temperature Rise Measurements, 254 Temperature Limitations, 257</i>	249
8.6	Transistor-Type Selections and Circuit Decisions	257
8.7	Recurrent Circuit Problems in Converter Designs <i>Simultaneous Inverter Conduction, 259 Capacitive Load Problems, 262 Overcurrent Protection, 263 Collector Spike Problems, 265 High-Voltage, High-Current Overlap at Turn-On/Turn-Off Transitions, 266 Power Transformer Vertical Drift along Its Hysteresis Loop, 266 Switching Noise Voltage on Power Supply Chassis, 268</i>	259
8.8	Typical dc/dc Converter Designs <i>Design of a 400-W dc/dc Converter with Rectified Preregulated Line Voltage Input and Five Output Voltages, 269 Design of Power Transformer, 270 Power Transistor Selection, 274 Output Rectifier Dissipation, 283 Output Filters, 285 Output Line and Load Regulation, 287 Problems, 287</i>	269

- 9.1 Width-Modulated, Step-Down Switching Regulator 289
Voltage and Current Waveforms in Step-Down Switching Regulator, 289 Minimum Load Current in Step-Down Switching Regulator, 293 Input and Output Currents and Dissipation, 294 Switching Regulator Efficiency, 294 Filter Inductance Calculation, 294 Filter Capacitance Calculation, 296 Design of Input, Filter, and Power Components for a Typical Off-the-ac-Line Step-Down Switching Regulator, 298 Output Filter Inductance Design for Direct Current in Inductor, 305
- 9.2 Circuit Considerations in Step-Down Switching Regulators 316
Pulse-Width-Modulator Circuit, 316 Voltage Gain through Switch and Width Modulator, 319 Total Open-Loop dc Voltage Gain and Line Voltage Regulation, 320 Switch Base Drive Circuits, 321 Emitter- Versus Collector-Loaded Switches, 325 Optoelectronic Couplers, 327 Gain, Phase Margin, and Loop Stability in Step-Down Switching Regulators, 330
- 9.3 Turn-On and Turn-Off Problems in Switching Regulators 348
- 9.4 Width-Modulated dc/dc Converters 349
- 9.5 Width-Modulated Step-Up Switching Converters 350
Critical Waveforms in Step-Up Switching Converters, 350 Selection of Output Filter Capacitor, 351 Selection of Energy Storage Inductor, 351 Transistor Voltage and Current and Power Stresses, 353 Avoiding Switching Inductor Saturation, 353 Width-Modulated, Step-Up Regulator, 353
- 9.6 Integrated-Circuit Building Blocks for Control Circuitry in Pulse-Width-Modulated dc/dc Converters 353
Motorola MC3420 Switching-Regulator Control Circuit Module, 356 Silicon General SG1524 Switching-Regulator Control Circuit Module, 359 Problems, 363

Index 366

1

Basic Voltage Regulators, Power Converters

1.0 Introduction

The voltage regulators considered herein generate single or multiple output dc voltages whose magnitudes are substantially constant for any value of static or dynamic load currents or input voltage within their specified limits.

Input voltages can be dc or single- or multiple-phase ac at any of the usual power line frequencies, generally ranging between 50 and 800 Hz. Magnitudes of the dc or rms ac input voltages can be higher or lower than the desired output voltages. Output voltages must remain constant to the specified accuracy with input voltages generally varying from ± 5 to $\pm 15\%$ around their nominal values and load currents varying from 0 to 100% of maximum at each output. Often, the supplies must cope with transient input voltage changes in excess of the ± 5 to $\pm 15\%$ steady-state variations. Duration of such transients may range from less than one to several hundred milliseconds.

Supplies are often required to have protective features such as the ability to survive short-circuited outputs or output voltage limiting above specified values. Limits on power supply efficiency, weight, size, cost, and audio and rf noise outputs are almost always specified.

The various ways to design power supplies to meet such specifications will be dealt with in this book. In this chapter, the basic regulating and power-converting techniques available to the designer will be presented in general terms without going into detailed circuit designs. In the following chapter, systems combinations of these individual regulating schemes will be taken up in block diagram form. Finally, subsequent chapters will go into detailed circuit designs of individual regulators and combinations of regulator types comprising whole power supply systems.

1.1 DC Voltage Regulators

1.1.1 Series-Pass Regulators

The series-pass regulator is the simplest, most frequently used but least efficient regulating technique. Until the appearance of high-current, low-forward-drop transistors, usable as high-frequency single-pole switches, it was the main

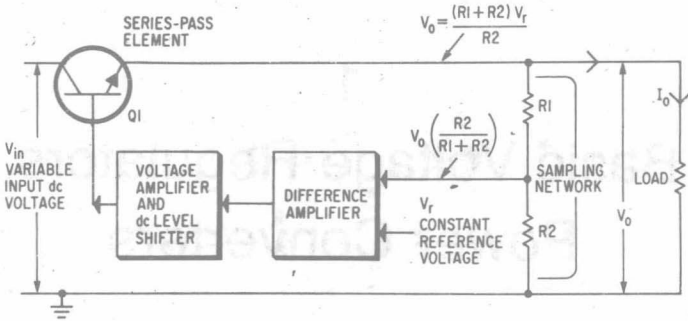


Fig. 1-1. Basic series-pass voltage regulator. Q1 is an electronically controlled variable resistance in series with the load.

and practically the only voltage-regulating technique up to power levels of 1,000 W. Techniques using constant voltage transformers and phase-controlled silicon-controlled rectifiers (SCR) have certain fields of application but are slow in response to line and load changes and will not be considered herein.

The basic series-pass regulator is shown in Fig. 1-1. It converts a variable higher voltage dc to a constant lower voltage dc. Input is dc—either from a battery source, which decreases in output as it discharges, or from a rectifier directly off an ac line source or from a rectifier following a step-up or step-down transformer.

In either of the latter cases, the rectified dc output is proportional to ac line input and will thus vary by the same ± 5 to $\pm 15\%$ usually specified for ac line sources. Further, usual rectifier outputs will have a large-amplitude ripple voltage at some harmonic of the line frequency superimposed on the rectified dc. The series-pass regulator will eliminate both the line harmonic ripple and the slower dc variations proportional to line changes, yielding a constant output voltage. Output voltage can be made as constant as desired, limited only by the stability of the reference sources, drift in the difference amplifier, and gain in the feedback loop.

In Fig. 1-1, the output is kept constant by using the series-pass element consisting of one or a number of paralleled transistors as a variable resistance device. As the input rises or falls, the effective resistance of the series element is increased or decreased so that it, rather than the output load, absorbs the input voltage change. The series element is controlled to give a constant output voltage by the negative-feedback loop composed of the resistor sampling chain, the difference amplifier, and voltage amplifier-level shifter.

A fraction of the output voltage, $[R2/(R1 + R2)] V_o$, is sampled and compared to a constant reference voltage, V_r . The difference amplifier yields a voltage proportional to the difference between V_r and the output sample. The amplified difference voltage is further amplified and the dc level shifted to drive the input terminal of the series element. Voltage polarities are such that a small increase or decrease in output voltage resulting from line or load changes causes the correct increase or decrease, respectively, in series element impedance to keep the output constant. The output adjusts itself so that the sampled fraction $V_o R2/(R1 + R2)$ is very closely equal to the reference voltage.

It is obvious from Fig. 1-1 that all of the output load current must flow through the series-pass element at a dc voltage drop of $V_{in} - V_o$. The minimum efficiency occurs at maximum input voltage and is equal to $P_o/P_{in} = V_o I_o \div V_{in(max)} I_o = V_o/V_{in(max)}$. The larger the difference between input and output voltage, the larger the internal dissipation for a given load current. Any dc voltage can be dropped down and regulated to any lower voltage, but the series-pass element must be capable of absorbing the maximum dissipation at its maximum voltage drop.

Thus, the series-pass regulator of Fig. 1-1 is seen to be simple, comprised only of a series voltage dropping element, resistor voltage sampling chain, difference amplifier, and voltage amplifier-level shifting device. But the relatively high dissipation across the series element at the maximum input voltage results in low output-input power efficiency.

1.1.2 Series-Pass Regulator Efficiency

In the usual power supply, whose prime input is ac line power, efficiency calculations must consider rectifier drop, ripple, transformer regulation, and transformer losses. But here, to start with, maximum attainable efficiencies will be calculated for sources with totally ripple-free dc output voltage whose magnitude can be set at any desired value to maximize regulator efficiency.

Such efficiencies will be the highest achievable for a given output voltage. Practical efficiencies for regulators with optimum ac inputs and realistic ripple voltage at regulator input terminal will be calculated in Chap. 6.

The usual series-pass element, npn or pnp power transistor, has a knee in its I_c - V_c curve at about 2.0 V (Fig. 1-2A). Although operation below the knee is possible, gain is low and a larger fraction of input changes would be transmitted to the output if operation below the knee were permitted.

Thus, in Fig. 1-1 with output taken from the emitter, the minimum input voltage permissible at the collector when the input is at its low tolerance limit is $(V_o + 2)$ volts. For a nominal input voltage of V_n and tolerances of $\pm T$ percent, minimum and maximum input voltages are then $(1 - 0.01T)V_n$ and $(1 + 0.01T)V_n$. Since the minimum input voltage must be no less than $V_o + 2$, then

$$(1 - 0.01T)V_n = V_o + 2$$

and maximum input voltage is

$$(1 + 0.01T)V_n = \left(\frac{1 + 0.01T}{1 - 0.01T} \right) (V_o + 2)$$


And minimum efficiency, which occurs at maximum input voltage, is

$$V_o/V_{in(max)} = \frac{V_o}{\left(\frac{1 + 0.01T}{1 - 0.01T} \right) (V_o + 2)}$$


or

$$\text{Minimum efficiency} = \left(\frac{1 - 0.01T}{1 + 0.01T} \right) \left(\frac{V_o}{V_o + 2} \right) \quad (1-1)$$

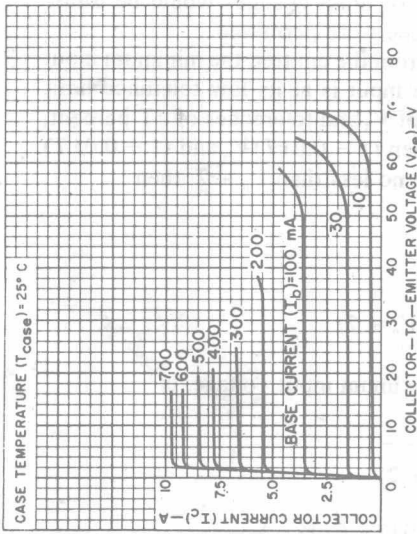
Efficiencies calculated from Eq. 1-1 are plotted in Fig. 1-3 for input tolerances of ± 5 , ± 10 , and $\pm 15\%$. Such efficiencies are realizable from dc sources having no ripple and at output voltages 2 V below the minimum dc input. It will



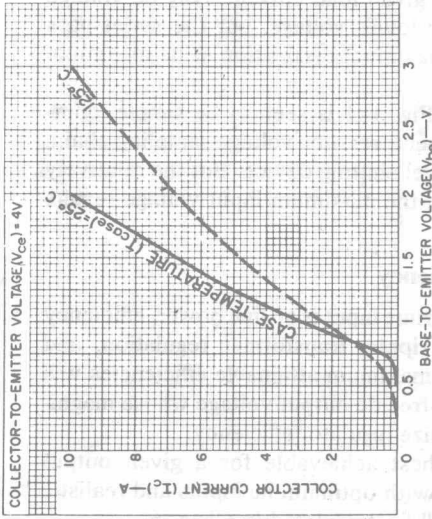
(A) — Typical output characteristics for type 2N3055.



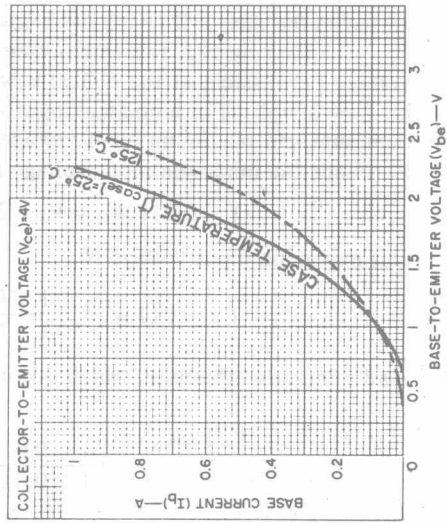(B) — Typical transfer characteristics for types 2N6253 and 2N3055.



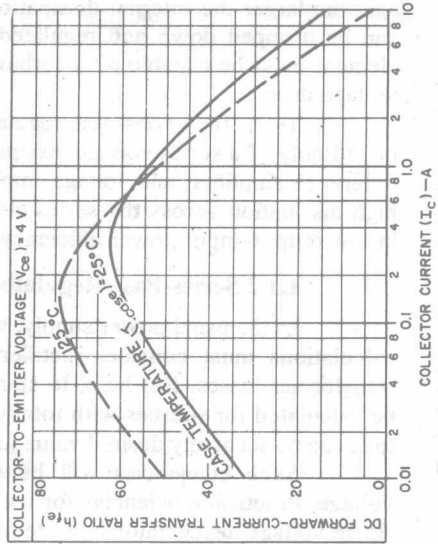(C) — Typical input characteristics for type 2N3055.



(D) — Typical dc-beta characteristics for type 2N3055.

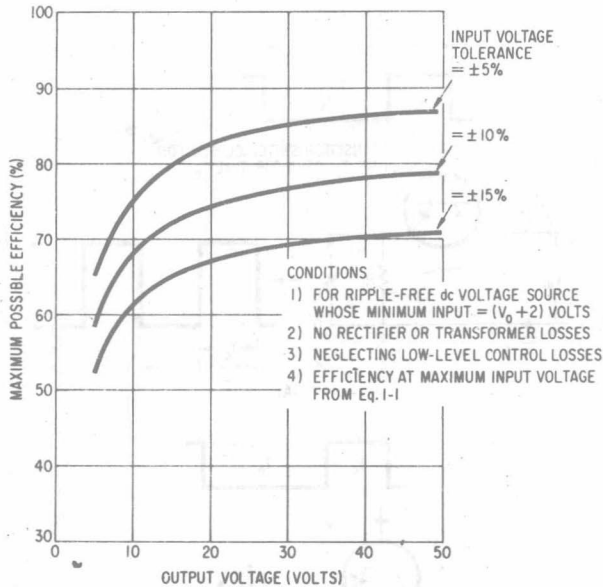


Fig. 1-3. Maximum possible efficiency versus output voltage for a series-pass voltage regulator.

be seen in Chap. 6 that when the input source is the rectified output of a transformer and when the effect of transformer losses, rectifier-output ripple, and rectifier losses are considered, efficiencies considerably less than shown in Fig. 1-3 result.

1.2 Pulse-Width-Modulated Series-Switch Step-Down Converter

Figure 1-4 shows a far superior way of obtaining a lower voltage from a higher one. Instead of absorbing the difference between the input and desired output with a power-dissipating element, a low-impedance transistor switch is made to open and close periodically between input and output. If the switch S1 has zero voltage drop in its closed position, the output shown in Fig. 1-4A varies periodically between zero volts and the input voltage. The average or dc value of this waveform is $V_o = V_{in}T_c/T$, where T_c is the switch-closed time and T is the switching period. This is the voltage that would be read with a dc voltmeter at the output terminals. The ripple component has a peak-to-peak value of V_{in} volts and would, of course, not be observed by a dc voltmeter.

By adding the L1-C1 filter as shown in Fig. 1-4B, the ripple component can be reduced to any desired value, yielding a clean dc voltage of magnitude $V_o = V_{in}(T_c/T)$. By going to high switching rates permitted by transistor switches (5-50 kHz), the filter components L1 and C1 become quite small.

Fig. 1-2. Characteristics of an often-used series-pass transistor. (Courtesy RCA)

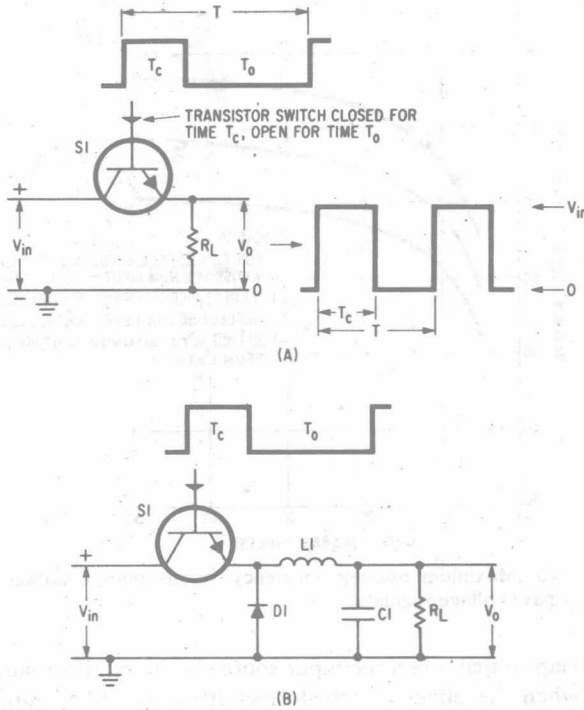


Fig. 1-4. (A) Switching voltage converter average output voltage at $V_o = V_{in}(T_c/T)$. (B) Switching voltage converter with LC filter and diode for eliminating ripple.

Any desired output voltage lower than the input can be obtained by varying the width of the "on" time T_c or the ratio T_c/T . Such a voltage stepdown is achieved at very high efficiency, since the only losses in such a stepdown are those primarily in the switch SI when it is closed. Using a transistor switch, the voltage drop with the switch in the closed position can be as low as 1 V. During the time the switch is open, the full input voltage is absorbed, but since no current flows in it, there is no power dissipation.

During the transition between open-switch and closed-switch times or vice versa, there is a momentary overlap of high voltage and current, which does yield some losses. Even with such switching losses, efficiencies of 95% are achievable.

1.2.1 Pulse-Width-Modulated Voltage Converter Efficiency

The circuit has the interesting properties of a step-down transformer. With a relatively large inductance for L1, the current in L1 remains constant during the switch-open time. As the switch opens, there is an inductive "kick" across L1 with its input end going negative, since current in an inductor cannot change instantaneously. It goes negative until diode D1 (often referred to as a "free-wheeling" diode) latches on and starts conducting with its cathode one