

ELECTRONIC DEVICES AND CIRCUITS



Michael **HASSUL**
Don **ZIMMERMAN**

Library of Congress Cataloging-in-Publication Data

Hassul, Michael.

Electronic devices and circuits / Michael Hassul, Donald E. Zimmerman.

p. cm.

Includes index.

ISBN 0-13-500869-7

1. Electronic circuits. 2. Electronic apparatus and appliances.

I. Zimmerman, Donald E. II. Title.

TK7867.H367 1997

621.3815—dc20

96-30563

CIP

Cover Photo: Telegraph Color Library/FPG Int'l

Editor: Linda Ludewig

Production Editor: Mary M. Irvin

Design Coordinator: Julia Zonneveld Van Hook

Cover Designer: Russ Maselli

Production Manager: Pamela D. Bennett

Marketing Manager: Debbie Yarnell

Production Coordinator: Proof Positive/Farrowlyne Associates, Inc.

This book was set in Times Roman by The Clarinda Company and was printed and bound by Von Hoffmann Press, Inc. The cover was printed by Von Hoffman Press, Inc.



© 1997 by Prentice-Hall, Inc.

Simon & Schuster/A Viacom Company

Upper Saddle River, New Jersey 07458

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

ISBN: 0-13-500869-7

Prentice-Hall International (UK) Limited, *London*

Prentice-Hall of Australia Pty. Limited, *Sydney*

Prentice-Hall of Canada, Inc., *Toronto*

Prentice-Hall Hispanoamericana, S.A., *Mexico*

Prentice-Hall of India Private Limited, *New Delhi*

Prentice-Hall of Japan, Inc., *Tokyo*

Simon & Schuster Asia Pte. Ltd., *Singapore*

Editora Prentice-Hall do Brasil, Ltda., *Rio de Janeiro*

CONTENTS

1	1.1	ELECTRONICS TODAY	4
Introduction to Electronics 2	1.2	THE STUDY OF ELECTRONICS	6
		Multiple Small Exposures 6	
		Study Techniques 8	
	1.3	A WORD ABOUT CURRENT	8
	1.4	COMPUTER SIMULATION	10
		Sample Circuit Simulation Programs 11	
		Using Computer Programs 13	
PART 1 ■ DIODES			15
2	2.1	INTRODUCTION	18
The Ideal Diode 16	2.2	THE IDEAL DIODE	19
	2.3	DIODE-RESISTOR CIRCUITS	20
		Example 2.1 Simple Diode-Resistor Circuits 22	
		Example 2.2 Single Loop Circuit 23	
		Example 2.3 Multiple Resistor Circuit 24	
	2.4	IS A DIODE ON OR OFF?—TWO APPROACHES	25
		Current Test 26	
		Voltage Test 26	
		Example 2.4 Diode Test 27	
	2.5	CURRENT TRAFFIC CONTROL—DIODE LOGIC	28
	A Diode Logic Circuit 28		
2.6	AC TO DC CONVERSION—THE HALF-WAVE RECTIFIER	30	
	Example 2.5 Half-Wave Rectifier Examples 31		
	AC-DC Conversion 32		
	Example 2.6 Finding DC Values 33		
2.7	AC TO DC CONVERSION—THE FULL-WAVE RECTIFIER	34	
	The Diode Bridge Circuit 34		
2.8	DIODE LIMITERS (CLIPPERS)	35	
	Top Clipping 36		
	Example 2.7 Diode Limiters—Top Clipping 38		
	Bottom Clipping 38		
	Example 2.8 Diode Limiters—Bottom Clipping 39		
	Symmetric Clipping 39		
	Example 2.9 Symmetric Clipping Circuits 40		
3	3.1	INTRODUCTION	48
The Real Diode 46	3.2	DIODE CURRENT AND VOLTAGE (THE I-V CURVE)	48
	3.3	THE REAL DIODE	51
		The Improved Diode Model 53	
	An Important Note 53		

	Current Test	53
	Example 3.1 The Current Test I	54
	Example 3.2 The Current Test II	54
	Voltage Test	55
	Example 3.3 The Voltage Test	55
3.4	DIODE CIRCUITS WITH REAL DIODES	56
	The Half-Wave Rectifier Circuit	56
	Example 3.4 The Half-Wave Rectifier	57
	The Full-Wave Rectifier	59
	Example 3.5 The Full-Wave Rectifier	60
	The Clipping Circuit	61
	Example 3.6 Two-Sided Limiting with Real Diodes	61
3.5	DIODE RESISTANCE	62
3.6	DIODE RATINGS—THE BREAKDOWN REGION	64
	The ON Diode	64
	Example 3.7 Approximating Power	65
	The Breakdown Region	66
	Example 3.8 Breakdown	67
3.7	COMMERCIALLY AVAILABLE DIODES—THE DIODE DATA SHEET	69
	Catalog Data	69
	Example 3.9 Diode Selection	69
	Diode Data Sheets	70
	The Diode Reverse Current	73
	Reverse Recovery Time	74
	Example 3.10 Using the Data Sheet	74
3.8	DIODE TESTING	75
	A Bad Diode (Using the VOM)	75
	A Bad Diode (Using the DMM)	76
3.9	DIODE CIRCUIT TROUBLESHOOTING	76
	Example 3.11 Troubleshooting the Diode Limiter	78
	Multimeter Testing	78
4		
	4.1 INTRODUCTION	88
	4.2 THE CAPACITOR AS BATTERY	88
	Example 4.1 Capacitor Discharge	89
	4.3 HALF-WAVE RECTIFIER WITH CAPACITOR	90
	Ripple	90
	Example 4.2 Half-Wave Rectifier with Capacitor I	92
	Example 4.3 Half-Wave Rectifier with Capacitor II	93
	rms Ripple Factor	93
	4.4 THE FULL-WAVE RECTIFIER WITH CAPACITOR	94
	Example 4.4 Full-Wave Rectifier with Capacitor	95
	Rectifier with Transformer	95
	Example 4.5 Bridge Rectifier with Transformer	96
	The Center-Tapped Transformer	96
	Example 4.6 Center-Tapped Transformer Rectifier	97
	4.5 DIODE CURRENT RATINGS	97
	Half-Wave Rectifier	97
	Example 4.7 Diode Currents	98
	Example 4.8 Determining the Diode On-Time	99
	Full-Wave Rectifiers	99
	Diode Current Ratings	100

Diode—Reactive Circuits 86

	4.6 THE PEAK DETECTOR	101
	Example 4.9 Peak Detector	101
	4.7 THE DIODE AM DEMODULATOR	102
	Example 4.10 AM Demodulation	104
	4.8 DIODE CLAMPING CIRCUITS	105
	Example 4.11 Clamping Circuits	107
	4.9 THE VOLTAGE DOUBLER	108
	4.10 DIODE-INDUCTOR CIRCUIT (FLYBACK)	109
	Flyback Prevention	111
	4.11 TROUBLESHOOTING DIODE-CAPACITOR CIRCUITS	112
	The Capacitor	112
	Example 4.12 Troubleshooting I	112
	Example 4.13 Troubleshooting II	113
5	5.1 INTRODUCTION	122
	5.2 THE ZENER DIODE	123
	Zener Diode Basics	123
	The Real Zener Diode	125
	5.3 ZENER DIODE CIRCUITS	126
	Example 5.1 Zener Circuit	127
	Zener Diode-Resistor Load Circuit	128
	Is the Zener Diode in Breakdown?—An Alternate Approach	129
	Example 5.2 Zener Diode—Resistor Circuit I	129
	Minimum Load Resistance	130
	Example 5.3 Zener Diode—Resistor Circuit II	130
	5.4 ZENER CLIPPER CIRCUITS	131
	Example 5.4 Zener Clipper	133
	5.5 ZENER VOLTAGE REGULATOR CIRCUIT	134
	Example 5.5 Zener Regulator—Minimum Load	135
	Example 5.6 Zener Regulator—Regulator Resistor	135
	5.6 INTEGRATED CIRCUIT VOLTAGE REGULATORS	136
	5.7 TROUBLESHOOTING ZENER DIODES AND CIRCUITS	137
	Example 5.7 Troubleshooting a Zener Diode Circuit	139
6	6.1 INTRODUCTION	148
	Specialized Diodes	148
	Troubleshooting Specialized Diodes	148
	6.2 THE GERMANIUM DIODE	148
	Example 6.1 The Germanium Diode	149
	6.3 THE SCHOTTKY DIODE	150
	Example 6.2 The Schottky Diode	151
	6.4 THE TUNNEL DIODE	152
	Example 6.3 The Tunnel Diode Circuit	153
	6.5 THE VARACTOR DIODE	155
	Example 6.4 The Varactor Diode	156
	6.6 THE PHOTO DIODE	157
	The Photoconductive Mode	157
	Example 6.5 The Photoconductive Cell	158
	The Light Spectrum	159
	Example 6.6 Frequency and Wavelength	160
The Zener Diode—Voltage Regulation		120
Special-Purpose Diodes and Opto-Electrical Devices		146

	Commercial Photo Diodes Data Sheets	161
	The Photovoltaic Mode	163
	Example 6.7 The Photovoltaic Mode	164
6.7	THE PHOTORESISTOR (PHOTOCONDUCTIVE CELL)	165
	Example 6.8 The Photoresistor	167
6.8	LIGHT-EMITTING DIODES (LED)	167
	LED Basics	167
	Example 6.9 A Bad LED Design	169
	The Seven-Segment Display	170
6.9	THE PHOTO TRANSISTOR AND OPTO-ISOLATOR	172
	The Photo Transistor	172
	The Opto-Isolator (Opto-Coupler)	172
	Fiber Optics	174

PART 2 ■ BIPOLAR JUNCTION TRANSISTORS (BJT) 179

7 The NPN Bipolar Junction Transistor 180	7.1	INTRODUCTION	182
	7.2	BJT STATES OF OPERATION	183
		Overview	184
		The Active State	184
		Example 7.1 Transistor Current Gain, β	186
		Example 7.2 Emitter Current-Collector Current Relations	187
	7.3	TRANSISTOR RATINGS	188
		Transistor Power	188
		Base Collector Breakdown (V_{CBO})	189
	7.4	SIMPLE DC TRANSISTOR CIRCUITS (I_B CONTROL)	189
		Example 7.3 I_B Control with Base Resistor	192
		Example 7.4 I_B Control with Base Supply Voltage	193
	7.5	THE COLLECTOR RESISTOR	196
		Example 7.5 Collector Resistor	197
	7.6	THE CUT-OFF AND SATURATION STATES	199
		CUT-OFF	199
	SATURATION	200	
	Example 7.6 Base Supply Voltage and Saturation I	202	
	Example 7.7 Base Supply Voltage and Saturation II	203	
	Example 7.8 Base Resistor and Saturation I	205	
	Example 7.9 Base Resistor and Saturation II	206	
	Example 7.10 Collector Resistor and Saturation I	207	
	Example 7.11 Collector Resistor and Saturation II	208	
	Example 7.12 Collector Supply Voltage and Saturation I	209	
	Example 7.13 Collector Supply Voltage and Saturation II	210	
7.7	DETERMINING THE STATE OF A TRANSISTOR	212	
	Example 7.14 Determining the State of a Transistor I	212	
	Example 7.15 Determining the State of a Transistor II	213	
	Example 7.16 Determining the State of a Transistor III	215	
7.8	DC TRANSISTOR DATA SHEET	216	

8

Troubleshooting
222

8.1	INTRODUCTION	224
	Temporary Breadboard Building	224
	Prototype Building	224
	Repairing a Circuit That Once Worked	224
8.2	DC TROUBLESHOOTING, BRIEFLY	225
	Recording the Estimated and Measured Voltages	226
	Example 8.1 Recording Estimated Voltages	227
	Example 8.2 Recording the Measured Voltages	228
8.3	THE COMPLETE DC TROUBLESHOOTING PROCEDURE	229
	Troubleshoot the Circuit	229
	Locate the Problem	230
	Example 8.3 DC Troubleshooting I	230
	Example 8.4 DC Troubleshooting II	231
	Example 8.5 DC Troubleshooting III	232
	Example 8.6 DC Troubleshooting IV	232
	Example 8.7 DC Troubleshooting V	233
	Summary of Examples	234
8.4	TYPES OF COMPONENT FAILURES	235
	Resistor Failures	235
	Transistor Failures	235
	Open Circuit Failures in Transistors	236
	Short Circuit Failures in Transistors	236
8.5	THE UNIVERSAL TRANSISTOR TEST CIRCUIT (UTTC)	237
	Determining if a Transistor Is Good or Bad with the UTTC	238
	Finding β with the UTTC	239
8.6	DC TROUBLESHOOTING EXAMPLES	239
	Example 8.8 DC Troubleshooting VI	239
	Example 8.9 DC Troubleshooting VII	240
	Example 8.10 DC Troubleshooting VIII	241
	Example 8.11 DC Troubleshooting IX	241
	Example 8.12 DC Troubleshooting X	242
8.7	TROUBLESHOOTING IN THE LABORATORY	244
	Why Not Current Measurements?	245
	Tips on Using the Temporary Breadboard in the Lab	246
	Common Problems in Using the Temporary Breadboards	247
8.8	DC TROUBLESHOOTING ON THE JOB	249
	Obtaining the Circuit Diagram	249
	Making Enough Copies of the Circuit Diagram	250
9	INTRODUCTION	258
	BASE VOLTAGE BIASING (V_B CONTROL)	259
	Example 9.1 V_B Control	262
	THE COLLECTOR RESISTOR	263
	Example 9.2 V_B Control with Collector Resistor	264
	Example 9.3 Comparison of I_B and V_B Control	266
	Example 9.4 V_B Control, R_C Variations	267
	Example 9.5 Variable Base Voltage Biasing	269
	THE VOLTAGE DIVIDER	270
	Example 9.6 The Voltage Divider	271
	Example 9.7 Approximate Voltage Divider with Load	272

9

Biasing for
Linear
Applications
256

	9.5 SELF-BIASING THE TRANSISTOR	274
	Example 9.8 Self-Biasing Circuit	275
	9.6 VOLTAGE AMPLIFICATION	278
	Example 9.9 Voltage Amplification	280
	Example 9.10 Effect of R_C on Voltage Amplification	282
	9.7 EXACT BASE VOLTAGE CALCULATIONS	284
	The Thevenin Approach	284
	Example 9.11 Thevenin Equivalent I	286
	Example 9.12 Thevenin Equivalent II	287
	Voltage Divider Versus the Exact Thevenin Approach	288
	9.8 DC TROUBLESHOOTING	289
	Voltage Divider Problems	289
	V_B -Control Transistor Problems	290
	Transistor Failures	292
	Example 9.13 DC Troubleshooting	294
10	10.1 INTRODUCTION	306
	Example 10.1 DC and AC Signal Components	307
	10.2 DC BIAS LEVELS	308
	Biasing	308
	Example 10.2 Bias Level Determination	310
	DC Bias and Output Voltage Limits	311
	Example 10.3 Maximum Voltage Swing I	313
	Example 10.4 Maximum Voltage Swing II	314
	10.3 THE AC BEHAVIOR OF THE TRANSISTOR	315
	Example 10.5 Small-Signal AC Emitter Resistor	318
	10.4 THE COMMON-EMITTER AMPLIFIER	319
	Example 10.6 The Common-Emitter Amplifier I	321
	Example 10.7 The Common-Emitter Amplifier II	322
	10.5 THE EMITTER BYPASS CAPACITOR	323
	The Capacitor	323
	The Emitter Bypass Capacitor	324
	Example 10.8 The Emitter Bypass Capacitor	326
	10.6 INPUT CAPACITOR COUPLING—THE SELF-BIASED CIRCUIT	327
	Example 10.9 The Input Coupling Capacitor	329
	10.7 THE LOAD RESISTOR	330
	Example 10.10 The Load Resistor	333
	10.8 TROUBLESHOOTING	334
	Example 10.11 Troubleshooting I	336
	Example 10.12 Troubleshooting II	337
	Example 10.13 Troubleshooting III	338
	Example 10.14 Troubleshooting IV	339
	Example 10.15 Troubleshooting V	340
11	11.1 INTRODUCTION	350
	11.2 THE BOX MODEL	351
	The Load Resistor	352
	Example 11.1 The Load Resistor I	352
	Example 11.2 The Load Resistor II	354
	Load Power	355
The Common-Emitter Amplifier	304	
The Box Model	348	

	The Source Resistor	355	
	Example 11.3 The Source Resistance I	356	
	Example 11.4 The Source Resistance II	357	
	The Complete System	358	
	Example 11.5 The Total System	359	
11.3	THE COMMON-EMITTER AMPLIFIER		360
	No-Load Gain	361	
	Output Resistance	362	
	Input Resistance	363	
	General Derivation of R_{base}	363	
	Formal Derivation of R_{base}	364	
	Example 11.6 Box Model of the Common-Emitter Amplifier	366	
	Example 11.7 Box Model of the Bypassed Common-Emitter Amplifier	367	
11.4	COMMON-EMITTER AMPLIFIER WITH LOAD AND SOURCE RESISTORS		369
	Load Resistor	369	
	Example 11.8 Load Resistor	370	
	Source Resistor	372	
	Example 11.9 Source Resistor	372	
	The Complete Common-Emitter Amplifier	374	
	Example 11.10 The Complete Amplifier	375	
11.5	MULTISTAGE AMPLIFIER		376
	Example 11.11 Two-Stage Amplifier	379	
12			
The Emitter Follower (The Common-Collector Amplifier)		388	
12.1	INTRODUCTION—THE BUFFER AMPLIFIER		390
	Example 12.1 The Buffer	392	
	Example 12.2 Buffer Design	393	
12.2	THE EMITTER FOLLOWER (COMMON-COLLECTOR AMPLIFIER)		395
	No-Load Gain	395	
	Example 12.3 Emitter-Follower Box Model Gain	396	
	Input Resistance	398	
	Example 12.4 Emitter Follower Input Resistance	399	
	Output Resistance	400	
	Example 12.5 Emitter-Follower Output Resistance	402	
	The Complete Box Model	403	
	Example 12.6 The Complete Emitter Follower	404	
12.3	THE EMITTER FOLLOWER AS A CURRENT BUFFER		406
	Example 12.7 The Current Buffer	407	
12.4	ZENER VOLTAGE REGULATION AND THE CURRENT BUFFER		408
	Example 12.8 Zener Regulation	409	
12.5	TROUBLESHOOTING		411
	Shorted C_L	411	
	Open C_L	412	
13			
Improved BJT AC Models		418	
13.1	INTRODUCTION		420
13.2	BJT TRANSISTOR CHARACTERISTIC CURVES		420
13.3	THE SIMPLE BJT MODEL		423
	Example 13.1 The Simple BJT AC Model	424	

14

The PNP
Transistor 442

13.4	THE HYBRID-PI BJT MODEL	425
	The Hybrid-Pi Model 425	
	Example 13.2 The Early Voltage and r_o 427	
	Example 13.3 The Hybrid-Pi Model 427	
	Example 13.4 The Hybrid-Pi Model with r_o 428	
	Alternate Hybrid-Pi Model 429	
13.5	THE H-PARAMETER BJT MODEL	430
	Example 13.5 h-Parameter Model 431	
	Example 13.6 The BJT h-Parameter Model 432	
13.6	MODEL COMPARISONS	433
	Simple Model \longleftrightarrow Hybrid-Pi Model 433	
	Hybrid-Pi Model \longleftrightarrow h-Parameter Model 434	
13.7	BJT DATA SHEETS	435
	Interpreting Data Sheets 435	
	Determining the Early Voltage 435	
14.1	INTRODUCTION	444
14.2	V_B CONTROL OF PNP TRANSISTORS	446
	Example 14.1 V_B Control I 449	
	Example 14.2 V_B Control II 450	
14.3	DOUBLE-SIDED SUPPLY BIASING	451
	Example 14.3 Double-Sided Supply Voltages 452	
14.4	THE PNP COMMON-EMITTER AMPLIFIER	453
	DC Bias Analysis 453	
	AC Analysis—The Box Model 454	
	Gain 455	
	Input Resistance 455	
	Output Resistance 455	
	System Gain 456	
	Example 14.4 The PNP Common-Emitter Amplifier 456	
14.5	THE PNP EMITTER FOLLOWER (COMMON-COLLECTOR)	458
	DC Bias Analysis 458	
	AC Analysis—The Box Model 458	
	Gain 459	
	Input Resistance 459	
	Output Resistance 460	
	System Gain 460	
	Example 14.5 The PNP Emitter Follower 460	
14.6	I_B CONTROL	462
	Example 14.6 Comparison of the NPN and PNP Inverters 463	
14.7	COMBINED NPN-PNP CIRCUITS	465
	V_B Control 465	
	I_B Control 466	
	Current Gain 467	
14.8	TROUBLESHOOTING	468
	Bad Connections 468	
	Transistor Open Failures 469	
	Transistor Short Failures 469	
	AC Signal Tracing 470	
	Example 14.7 Troubleshooting 470	

15**The Common-Base Amplifier 480**

15.1	INTRODUCTION	482
15.2	DC BIASING OF THE COMMON-BASE AMPLIFIER	482
	The NPN Common-Base Amplifier	482
	The PNP Common-Base Amplifier	484
	Example 15.1 DC Bias Levels in the Common-Base Amplifier	485
15.3	AC BEHAVIOR OF THE COMMON-BASE AMPLIFIER—BOX MODEL	486
	Gain	487
	Output Resistance	488
	Input Resistance	488
	Example 15.2 Box Model of the Common-Base Amplifier	489
15.4	THE COMPLETE COMMON-BASE AMPLIFIER	490
	Example 15.3 Complete AC Analysis of the Common-Base Amplifier	491
15.5	AMPLIFIER COMPARISONS	492
15.6	TROUBLESHOOTING	492
	Example 15.4 DC Troubleshooting the Common-Base	493
	Example 15.5 AC Signal Tracing in the Common-Base Amplifier	494

16**Specialized Transistor Circuits 500**

16.1	INTRODUCTION	502
16.2	THE DARLINGTON CONNECTION	502
	Equivalent AC Emitter Resistance	503
16.3	DARLINGTON COMMON-EMITTER AMPLIFIER	504
	DC Bias Levels	504
	AC Analysis—the Box Model	505
	Example 16.1 The Darlington Common-Emitter Amplifier	506
16.4	THE CASCODE AMPLIFIER	508
	DC Analysis	508
	Example 16.2 DC Analysis of the Common-Base Amplifier	510
16.5	THE CASCODE AMPLIFIER—AC ANALYSIS	512
	Example 16.3 Cascode Amplifier—AC Analysis	514
16.6	COLLECTOR-FEEDBACK BIASING	515
	Example 16.4 Collector-Feedback Biasing	516
16.7	ANALYSIS OF COLLECTOR-FEEDBACK BIASING—THE MILLER EFFECT	517
	Input Resistance—The Miller Effect	518
	Example 16.5 Collector Feedback—AC Analysis	520

17**The Differential Amplifier 526**

17.1	INTRODUCTION	528
17.2	BIASING THE DIFFERENTIAL AMPLIFIER	530
	Example 17.1 NPN Differential Amplifier Biasing	531
	Example 17.2 Current Source Biasing	533
	Example 17.3 PNP Differential Amplifier Biasing	533
17.3	THE DIFFERENTIAL MODE	535
	Example 17.4 Differential-Mode Gain	538
	The Differential-Mode Box Model	539
	Limits on Input Voltage Difference	540

18**Current Sources
562**

17.4	COMMON-MODE GAIN	541
	Example 17.5 Common-Mode Gain	544
17.5	THE GENERAL DIFFERENTIAL AMPLIFIER	545
	Example 17.6 General Differential Amplifier Response	546
17.6	INTEGRATED CIRCUIT DIFFERENTIAL AMPLIFIERS	548
	Example 17.7 Instrumentation Amplifiers	551
17.7	TROUBLESHOOTING	552
	Open Failures	552
	Short Failures	553
	Example 17.8 Troubleshooting Differential Amplifier Circuits	554
	Troubleshooting Integrated Circuit Amplifiers	554
18.1	INTRODUCTION	564
18.2	THE BASIC NPN TRANSISTOR CURRENT SOURCE	565
	V_B Control	565
	Example 18.1 The NPN Current Source	566
	Maximum Load Voltage and Resistance	567
	Example 18.2 Maximum Load Voltage and Current	568
18.3	THE BASIC PNP TRANSISTOR CURRENT SOURCE	568
	V_B Control	569
	Maximum Load Voltage and Resistance	569
	Example 18.3 The PNP Current Source	570
18.4	NEGATIVE VOLTAGE SUPPLY CURRENT SOURCES	571
	NPN	571
	Example 18.4 Negative Voltage Supply NPN Current Source	572
	PNP	573
	Example 18.5 Negative Voltage Supply PNP Current Source	573
18.5	TEMPERATURE COMPENSATION	575
	Example 18.6 Temperature Compensation	576
18.6	THE CURRENT MIRROR	578
	Example 18.7 Negative Supply NPN Current Mirror	580
	Example 18.8 PNP Current Mirror	580
18.7	CURRENT SOURCE BIASING OF DIFFERENTIAL AMPLIFIERS	581
	DC Bias	582
	Box Model	582
	Common-Mode Rejection Ratio	583
	Current Source Output Resistance	583
	Example 18.9 Differential Amplifier	583

19**Power Amplifiers
590**

19.1	INTRODUCTION	592
19.2	THE COMMON-EMITTER AMPLIFIER—MAXIMUM VOLTAGE SWING	593
	Symmetrical Swing	594
	Example 19.1 Maximum Symmetrical Swing	595
	Example 19.2 Maximum Swing—Common-Emitter Amplifier	597
	Capacitor Coupling and the Bypass Capacitor	598
	Example 19.3 Common Emitter with Capacitors I	599
	Example 19.4 Common Emitter with Capacitors II	599

19.3	THE EMITTER FOLLOWER—MAXIMUM VOLTAGE SWING	601
	Example 19.5 Emitter Follower—Maximum Swing	601
19.4	CLASS A POWER CONSIDERATIONS	603
	Example 19.6 Power Calculations for the Class A Amplifier	605
19.5	TRANSFORMER COUPLING	607
	Analysis of the Transformer-Coupled Amplifier	608
	Power Calculations	610
	Example 19.7 Transformer-Coupled Class A Amplifier	611
19.6	THE CLASS B AMPLIFIER	612
	Operation	612
	Power Considerations	614
	Example 19.8 Class B Maximum Power Calculations	616
	Example 19.9 Class B Power Calculations	617
	Distortion in the Class B Amplifier	618
19.7	PUSH-PULL AMPLIFIER BIASING	619
	Example 19.10 Class B Biasing	620
	Diode Biasing	621
	Single-Supply Biasing	622
	Example 19.11 Single-Supply Diode Biasing	622
	The Bridge Amplifier and Phase Splitter	623
19.8	TROUBLESHOOTING	624
	Short Circuit Failures	625
	Example 19.12 Q_2 Short Failures	626
	Open Circuit Failures	626

PART 3 ■ FIELD EFFECT TRANSISTORS (FET)**637****20****The Field Effect Transistor 638**

20.1	INTRODUCTION	640
20.2	THE JUNCTION FIELD EFFECT TRANSISTOR (JFET)	641
	JFET Operating States	644
	Example 20.1 Determining the Pinch-Off Voltage	644
	BJT SATURATION Region—JFET OHMIC Region	645
	Example 20.2 The OHMIC Region	646
20.3	ACTIVE REGION DRAIN CURRENT VS. GATE VOLTAGE (I_D-V_{GS})	647
	The I_D - V_{GS} Curve	647
	Example 20.3 Constructing the I_D - V_{GS} Curve	648
	The CUT-OFF, PINCH-OFF Confusion	649
20.4	BASIC N-CHANNEL JFET BIASING	650
	Example 20.4 N-Channel JFET Biasing	651
	Example 20.5 The OHMIC Region	652
20.5	SINGLE-SOURCE JFET BIASING (GRAPHICAL)	653
	Determining the Q-Point	653
	Example 20.6 Graphical Bias Calculations	655
	But I Can't Find the JFET I-V Curve!	656
	Example 20.7 Constructing the JFET I-V Curve	657
20.6	SINGLE-SOURCE JFET BIASING (ANALYTICAL)	657
	Example 20.8 Analytical Bias Calculation	658
20.7	VOLTAGE DIVIDER BIASING	659
	Example 20.9 Voltage Divider Biasing	661

	Analytical Calculation of Bias Levels	661
	Example 20.10 Voltage Divider Biasing—Analytical Calculation	662
	The Universal JFET I-V Curve	662
20.8	THE P-CHANNEL JFET	663
	Finding Bias Values	663
	Example 20.11 P-Channel Biasing ($V_G = 0V$)	664
	Example 20.12 Voltage Divider P-Channel Biasing	665
	Analytical Calculations	667
	Example 20.13 Analytical Bias Calculation ($V_G = 0V$)	667
	Example 20.14 Voltage Divider Biasing—Analytical	668
20.9	JFET DATA SHEETS AND COMPUTER MODELS	668
	JFET Specifications	670
	JFET Computer Model	670
	Example 20.15 Data Sheet Parameters and Computer Model Parameters	671
20.10	TROUBLESHOOTING THE JFET	672
	Out-of-Circuit Tests	672
	DC Troubleshooting of JFET Circuits	673
	Example 20.16 DC Troubleshooting	674
21.1	INTRODUCTION	684
21.2	THE N-CHANNEL D-MOSFET	684
	Structure and Function	684
	Example 21.1 Biasing the D-MOSFET, Depletion Region	686
	Example 21.2 Biasing the D-MOSFET, Enhancement Region	687
	Example 21.3 D-MOSFET Biasing, Analytical Method	688
	The Almost Universal N-Channel D-MOSFET I-V Curve	688
21.3	THE P-CHANNEL D-MOSFET	689
	Structure and Function	689
	Example 21.4 Biasing the P-Channel D-MOSFET	690
	Example 21.5 P-Channel D-MOSFET Biasing, Analytical Method	691
	The Almost Universal P-Channel D-MOSFET I-V Curve	692
21.4	THE N-CHANNEL E-MOSFET	692
	Structure and Function	692
	Example 21.6 N-Channel E-MOSFET Biasing	693
	Analytical N-Channel E-MOSFET Biasing	694
	Example 21.7 N-Channel E-MOSFET Biasing, Analytical Method	695
	The Almost-Universal N-Channel E-MOSFET I-V Curve	695
21.5	THE P-CHANNEL E-MOSFET	696
	Structure and Function	696
	Example 21.8 P-Channel E-MOSFET Biasing	696
	Analytical P-Channel E-MOSFET Biasing	697
	Example 21.9 P-Channel E-MOSFET Biasing, Analytical Method	698

21

The MOSFET 682

22

FET AC Behavior and Applications 716

	The Almost Universal P-Channel E-MOSFET I-V Curve 698	
21.6	MOSFET DATA SHEETS AND COMPUTER MODELS 699	699
	Data Sheets 699	
21.7	THE COMPLEMENTARY MOSFET (CMOS)—AN INVERTER	703
21.8	OTHER MOSFETs 704	704
	Power FETs 705	
	Dual-Gate MOSFETs 705	
	The MESFET 705	
21.9	DC TROUBLESHOOTING MOSFET CIRCUITS 705	705
	DC Troubleshooting the D-MOSFET 705	
	Open Failures 706	
	Short Failures 707	
	DC Troubleshooting the E-MOSFET 707	
22.1	INTRODUCTION	718
22.2	FET AC MODEL 718	718
	Determining g_m for the JFET and D-MOSFET 719	
	Example 22.1 Finding g_m for the JFET 720	
	Determining g_m for the E-MOSFET 720	
	Example 22.2 Finding g_m for the E-MOSFET 721	
	FET Data Sheets and AC Parameters 721	
	FET OHMIC Region Resistance 724	
22.3	THE COMMON-SOURCE FET AMPLIFIER 725	725
	Common Source Box Model Parameters 725	
	Example 22.3 The Common-Source Amplifier 726	
22.4	ADDITIONAL FET CIRCUITS 728	728
	Example 22.4 The FET Follower 729	
22.5	FET-BJT CIRCUITS	731
22.6	THE VOLTAGE VARIABLE RESISTOR 732	732
	Resistance of FET 733	
	Example 22.5 The FET as a Voltage Variable Resistor 733	
	Automatic Gain Control (AGC) 734	
22.7	CMOS LOGIC CIRCUITS 735	735
	Inverter 735	
	NAND Gate 736	
	NOR Gate 737	
	Special Topic FET Modeling 739	
	BJT Models 739	
	FET Models 740	

PART 4 ■ THE OPERATIONAL AMPLIFIERS

745

23

The Operational Amplifier (OP-AMP) 746

23.1	INTRODUCTION	748
23.2	THE OPERATIONAL AMPLIFIER (OP-AMP)	748
23.3	NEGATIVE FEEDBACK 750	750
	Talking Around the Loop 751	
	The General Negative Feedback Amplifier 753	
	Example 23.1 Closed-Loop Gain 754	
	High Forward Gain 755	

	23.4 THE NON-INVERTING AMPLIFIER—TALKING AROUND THE LOOP	756
	The Unity-Gain Amplifier (Buffer Amplifier) 756	
	Example 23.2 The Unity-Gain (Buffer) Amplifier 757	
	The Non-Inverting Amplifier 758	
	Example 23.3 The Non-Inverting Amplifier 759	
	Example 23.4 Non-Inverting Amplifier Design 760	
	23.5 THE INVERTING AMPLIFIER—TALKING AROUND THE LOOP	760
	Example 23.5 The Inverting Amplifier 762	
	Example 23.6 The Inverting Amplifier, Design 762	
	23.6 THE IDEAL OP-AMP	763
	Non-Inverting Amplifier 764	
	Example 23.7 The Non-Inverting Amplifier 765	
	Inverting Amplifier 766	
	Example 23.8 The Inverting Op-Amp Amplifier 767	
	23.7 THE REAL OP-AMP	768
	Input Bias Current 769	
	Example 23.9 The Non-Inverting Amplifier 770	
	Input Offset Voltage 771	
	Bandwidth (Gain-Bandwidth Product) 771	
	Example 23.10 Bandwidth and Gain-Bandwidth Product 772	
	Rise Time and Slew Rate 772	
	Op-Amp Data Sheets 773	
	23.8 INSTRUMENTATION AMPLIFIERS	776
	23.9 TROUBLESHOOTING OP-AMP CIRCUITS	778
	Example 23.11 Op-Amp Troubleshooting 778	
24	24.1 INTRODUCTION	790
	Non-Inverting Amplifier 790	
	Unity-Gain Buffer Amplifier 790	
	Inverting Amplifier 791	
	Op-Amp Analysis Procedure 792	
	Troubleshooting 792	
	24.2 SUMMING AMPLIFIERS	792
	Inverting Summer 792	
	Example 24.1 The Inverting Summer 794	
	Example 24.2 Digital-to-Analog Converter (DAC) 795	
	Inverting Amplifier with Buffers 796	
	Non-Inverting Summer 796	
	Example 24.3 Non-Inverting Amplifier 797	
	Example 24.4 Non-Inverting Summing Amplifier 798	
	Troubleshooting 799	
	24.3 DIFFERENCE (DIFFERENTIAL) AMPLIFIER	800
	Differential Amplifier 801	
	The Bridge Amplifier 802	
	Example 24.5 Bridge Amplifier 802	
	Troubleshooting 803	
	24.4 DIFFERENTIATION AND INTEGRATION	804
	Differentiation 804	
	A Note of Caution 806	
	Example 24.6 Differentiation 806	
Operational Amplifier Circuits 788		

25

Non-Linear
Operational
Amplifier
Circuits 820

	Integration	807	
	Example 24.7 Op-Amp Integration	808	
	Troubleshooting	809	
24.5	IMPROVED VOLTAGE REGULATION		809
	Example 24.8 Buffered Zener with Voltage Divider	810	
	Troubleshooting	811	
25.1	INTRODUCTION		822
25.2	RECTIFIERS		823
	Simple Inverting Rectifier	823	
	Example 25.1 Simple Inverting Rectifier	824	
	Precision Rectifiers	824	
	Non-Inverting Precision Rectifier	824	
	Example 25.2 Non-Inverting Rectifier	825	
	Inverting Precision Rectifier	826	
	Example 25.3 Inverting Precision Rectifier	827	
	Troubleshooting	828	
25.3	LIMITERS		829
	Op-Amp Limiter Circuit	829	
	Example 25.4 Op-Amp Limiter	830	
	Troubleshooting	830	
25.4	ZERO-CROSSING DETECTOR		831
	Example 25.5 Zero-Crossing Detector	833	
25.5	COMPARATORS (LEVEL DETECTORS)		833
	The Non-Inverting Comparator	834	
	Example 25.6 Non-Inverting Comparator	834	
	Voltage Divider Reference Voltage for Comparator	835	
	The Inverting Comparator	835	
	Example 25.7 Voltage Level Indicator	835	
	Troubleshooting	837	
25.6	SCHMITT TRIGGER		837
	Positive Feedback	837	
	Example 25.8 The Schmitt Trigger	839	
	Troubleshooting	841	

PART 5 ■ ADVANCED TOPICS RESPONSE AND FILTERS**849**

26

Frequency
Response 850

26.1	INTRODUCTION		852
26.2	THE GAIN RESPONSE		853
	Amplifier Gain	853	
	Bandwidth	853	
	Example 26.1 Half-Power Frequencies—Band-Pass Response	855	
	Example 26.2 Half-Power Frequency—Low-Pass Response	855	
	Example 26.3 Half-Power Frequency—High-Pass Response	856	
26.3	THE BODE GAIN PLOT		857
	Example 26.4 Log f Scale—Decades	858	
	Example 26.5 Log f Scale—Octaves	858	
	Example 26.6 3-dB Frequencies—Band-Pass Response	860	