

ANALYSIS OF ELECTRICAL NETWORKS

SHLOMO KARNI

ANALYSIS OF ELECTRICAL NETWORKS

SHLOMO KARNI

University of New Mexico

JOHN WILEY & SONS

New York Chichester Brisbane Toronto Singapore

Copyright © 1986, by John Wiley & Sons, Inc

All rights reserved Published simultaneously in Canada

Reproduction or translation of any part of
this work beyond that permitted by Sections
107 and 108 of the 1976 United States Copyright
Act without the permission of the copyright
owner is unlawful Requests for permission
or further information should be addressed to
the Permissions Department, John Wiley & Sons

Library of Congress Cataloging in Publication Data:

Karni, Shlomo, 1932-

Analysis of electrical networks.

Includes indexes

1. Electric network analysis I Title

TK454.2.K27 1986 621.319'2 85-12206

ISBN 0-471-80268-9

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

ABOUT THE AUTHOR

Shlomo Karni was born in Poland in 1932. He received his BSEE degree (cum laude) from the Technion, Israel Institute of Technology, in 1956; his M.E. from Yale University in 1957, and a Ph.D. in electrical engineering from the University of Illinois, Urbana, in 1960.

Since 1961 he has been with the Department of Electrical and Computer Engineering at the University of New Mexico in Albuquerque, New Mexico, where he is a Professor and the Director of Graduate Studies. During 1954–1956, Professor Karni was employed by the Palestine Power Company, Haifa, Israel; 1956–1957 was spent as a teaching assistant at Yale University. From 1957 to 1961, he was Instructor, then Assistant Professor, at the University of Illinois. He was Visiting Professor, Department of Electrical Engineering, University of Hawaii, during 1968–1969; a Visiting Professor and the first Acting Dean at the School of Engineering, Tel Aviv University, 1970–1971; and a Visiting Professor at the Technion, Israel Institute of Technology, during the summer of 1977.

Professor Karni has served as a consultant to Westinghouse Learning Corporation, Gulton Electronics Industries, the Air Force Weapons Labs, and the Los Alamos ERDA (now DOE) Labs.

Professor Karni was on the editorial board of the *IEEE Spectrum* (1969–1972) as Associate Editor and is currently Editor of the *IEEE Magazine on Circuits and Systems*. He has also served as a consultant to major publishing houses (John Wiley & Sons, McGraw-Hill, Prentice-Hall, Houghton Mifflin, Addison-Wesley, and others).

He is the author of three books: *Network Theory: Analysis and Synthesis*, (Boston: Allyn & Bacon, 1966; Russian translation: Moscow: Svyaz Publishing Co., 1973); *Intermediate Network Analysis*, (Boston: Allyn & Bacon, 1971); and *Analysis of Continuous and Discrete Systems*, with W. Byatt (Holt, Rinehart & Winston, 1981). In addition, he has written over 60 technical articles.

Dr. Karni is a Fellow of the IEEE, and a member of Tau Beta Pi (board of directors, 1972–1976); the New York Academy of Science (1970); Eta Kappa Nu; and The Academy of Hebrew Languages, Jerusalem, (correspondent, 1970).

PREFACE

This book is intended for a one-semester (or two-quarter) second course in circuit analysis. The student is expected to have had the following topics as prerequisites: R , L , M , and C as circuit elements, analysis of resistive networks via node and loop equations, dc Thévenin and Norton equivalent circuits, power and energy, superposition, classical solutions of first-order (RL , RC) circuits and of second-order (RLC) circuits, simple operational amplifier circuits, and sinusoidal steady-state (phasor) analysis.*

To help the student and the instructor in the review of some of this material, Chapter 1 provides a summary leading to the general time-domain formulation of dynamic equations for RLC networks. Appendix A contains the essentials of linear algebraic equations, matrices, and determinants. In Appendix B, a brief survey is given of the op-amp, together with some of its common circuits. Students and instructors should use their discretion in studying this review material and referring to it as needed. Appendix C, on scaling, may be conveniently studied or reviewed at this early stage.

The rest of the book is devoted to more advanced topics in circuit analysis. Interconnections of networks, topology, and signal flow graphs (Appendix D) stress the uniformity and the organized formulation of network equations. Convolution reiterates the principle of superposition. The Laplace transform and the Fourier transform serve as powerful tools in the solution of network equations; in addition, they provide the necessary tools for many related subjects, such as stability and frequency response. State variable analysis and solution give us, in addition to mathematical elegance, a deep insight into the physical behavior of networks. The last chapter gives a brief introduction to linear, time-varying networks.

Throughout the text, the following features are used:

1. Problems relevant to a particular topic are listed by number next to the discussion of that topic. It is hoped that such an arrangement will make the learning of the material more systematic and more helpful.
2. Topics which are more advanced are marked with an asterisk (*) at the beginning of the appropriate section. They may be skipped during the first reading without loss of continuity. Later, the student and the instructor are encouraged to return and integrate them into the study.
3. Examples are marked clearly with a title ("Example 3") and with a square mark (\square) at the end, all between two thick lines.
4. In Appendix F, selected solutions and hints to problems are given. The student should use these judiciously as a helpful tool, not as a substitute for thinking and

* See, for example, R. E. Thomas and A. J. Rosa, *Circuits and Signals*. New York: John Wiley & Sons, 1984, and D. F. Mix and N. M. Schmitt, *Circuit Analysis for Engineers: Continuous and Discrete-Time Systems*. New York: John Wiley & Sons, 1985.

working! A more complete Solutions Manual is available to instructors upon adoption.

5. References and bibliographical listings at the end of each chapter are kept to a minimum. Too many references may look impressive, but they tend to discourage, by their sheer numbers, even the most well-intended student. This is not to say, however, that a resourceful instructor should not encourage the better students to read additional material. The given lists are a good start in that direction.

I gratefully acknowledge the help of Robin Morel, Ireena Erteza, and Sabina Erteza, who helped me in the preparation of Appendix E. My secretary, Mrs. Joan Lillie, typed the final manuscript and managed the administrative aspects of my work. My editors at John Wiley & Sons, along with the staff, provided prompt, courteous, and efficient assistance throughout the stages of this project. My sincere thanks go to them.

Albuquerque, New Mexico
August 1985

Shlomo Karni

CONTENTS

CHAPTER 1 Introduction	1
1-1 Systems and Networks	1
1-2 Some Characteristics of Electrical Networks	1
1-3 Elements and Sources	4
1-4 Linearity and Superposition	12
1-5 Kirchhoff's Laws: Loop and Node Equations	13
Problems	16
 CHAPTER 2 The Laplace Transform	 20
2-1 The Unit Step Function	20
2-2 The Laplace Transform	28
2-3 Properties of the Laplace Transform	33
Problems	46
 CHAPTER 3 Laplace Transform in Circuit Analysis	 53
3-1 Loop and Node Equations	53
3-2 Transform Diagrams—Loop Equations	56
3-3 Transform Diagrams—Node Equations	60
3-4 Summary	63
3-5 Rational Functions: Poles and Zeros	64
3-6 Partial Fraction Expansion	66
Problems	78
 CHAPTER 4 External Characterization of Networks	 85
4-1 N-Port and N-Terminal Networks	85
4-2 The One-Port (1-P) Network	86
4-3 The 2-P Network and Its Open-Circuit Parameters	91
4-4 A Neat Method: Matrix Partitioning	96
4-5 The 2-P Network and Its Short-Circuit Parameters	98
4-6 The 2-P Network and Its Hybrid Parameters	101
4-7 The 2-P Networks and Its Chain Parameters	103
4-8 The N-T Network and the Indefinite Admittance Matrix	104
Problems	111
 CHAPTER 5 Interconnections of Networks	 118
5-1 Series Connection of 2-P Networks	118
5-2 Parallel Connection of 2-P Networks	123

viii Contents

5-3	Series-Parallel Connection of 2-P Networks	125
5-4	Parallel-Series Connection of 2-P Networks	127
5-5	The Chain Connection of 2-P Networks	127
5-6	Parallel Connection of N-T Networks	128
	Problems	130
CHAPTER 6 Network Topology		134
6-1	Basic Properties and Definitions	135
6-2	The Incidence Matrix. Cut-Sets	140
6-3	The Circuit Matrix	146
6-4	Transformation of Variables: Loop and Node Equations	152
6-5	Power and Energy: Passive and Active Elements	160
	Problems	163
CHAPTER 7 Network Functions and Responses		167
7-1	Network Functions: Definitions and Derivations	167
7-2	Driving-Point Functions	169
7-3	Transfer Functions	176
7-4	Properties of Network Functions: Poles and Zeros and Parts of $H(s)$	179
7-5	Natural Frequencies and the Characteristic Equation	186
7-6	Network Functions and the Impulse Response	190
7-7	Complete Response	192
	Problems	196
CHAPTER 8 Convolution and Superposition		203
8-1	Superposition	203
8-2	Graphical Convolution	209
8-3	Numerical Convolution	210
8-4	Laplace Transform of the Convolution	213
	Problems	216
CHAPTER 9 Frequency Response and Graphical Methods		220
9-1	Magnitude and Phase: Rectangular and Polar Plots	221
9-2	A Graphical Method: Zero Lines and Pole Lines	226
9-3	Bode Plots	231
	Problems	241
CHAPTER 10 State Variables I: Formulation		246
10-1	Introductory Example	246
10-2	Independent Initial Conditions and the Order of Complexity of the Network	248

10-3	Formulation of the State Equations: Linear, Constant, Passive Networks	253
10-4	Networks Containing Transformers, Gytrators, and Controlled Sources	258
10-5	Formulation of the State Equations: Time-Varying and Non-Linear Networks	262
	Problems	266
CHAPTER 11 State Variables II: Solution		271
11-1	Introductory Example	271
11-2	Time Domain Solutions of the State Equations	273
11-3	Frequency Domain Solution of the State Equations	283
11-4	Simulation Diagrams	288
	Problems	303
CHAPTER 12 Stability		308
12-1	Zero-Input Stability and the Characteristic Equation	308
12-2	Hurwitz Polynomials: The Routh Criterion and the Hurwitz Test	310
12-3	A Graphical Method: The Encirclement Theorem	322
12-4	Zero-State (BIBO) Stability	327
12-5	BIBO Stability and the Network Function $H(s)$	328
12-6	Conclusion	330
	Problems	331
CHAPTER 13 Periodic Waveforms and the Fourier Series		334
13-1	The Laplace Transform Revisited	334
13-2	The Fourier Series	337
13-3	Evaluation of the Fourier Coefficients	339
13-4	Convergence of the Fourier Series	342
13-5	The Cosine Form of the Fourier Series	345
13-6	Fourier Series, Superposition, and Phasors	347
13-7	The Exponential Fourier Series	350
13-8	Power Relationships	353
13-9	Discrete Spectra	354
	Problems	359
CHAPTER 14 The Fourier Transform		363
14-1	The Square Pulse Revisited	363
14-2	The Fourier Integral and Transform	365
14-3	Properties of the Fourier Transform	368
14-4	Applications to Circuits	372

x Contents

14-5 Parseval's Theorem and the Energy Spectrum	377
14-6 Comparisons between the Fourier and the Laplace Transforms	378
Problems	382
 CHAPTER 15 Time-Varying Networks	 387
15-1 Applications of the Laplace Transform	387
15-2 Impulse Response and Convolution	389
15-3 Network Functions	392
15-4 State Variables	396
Problems	400
 APPENDIX A Matrices	 405
APPENDIX B The Operational Amplifier	417
APPENDIX C Magnitude and Frequency Scaling	421
APPENDIX D Signal Flow Graphs	424
APPENDIX E Computer Programs	437
APPENDIX F Hints and Solutions to Selected Problems	447
 INDEX	 463

INTRODUCTION

In this chapter, we review the basic properties of network elements and the formulation of loop equations and node equations.

1-1 SYSTEMS AND NETWORKS

In its broadest sense, a *system* can be defined as a group, or collection, of components, each with its specific characteristics, interacting in some prescribed manner. So, an automobile with all its parts, a generating station supplying electric power to customers through transmission lines, the nerves of a living organism, a group of people with certain mutual interests—all are examples of systems. In fact, any conceivable group of entities, interrelated in some fashion can be called a system.

In particular, an electrical network is a system, consisting of *elements* (components) such as resistors, capacitors, voltage and current sources, transistors, diodes, etc. Our aim in this book is the analysis of electrical networks, that is the development of the mathematical relations among the variables that describe the behavior of the network.

1-2 SOME CHARACTERISTICS OF ELECTRICAL NETWORKS

In certain cases, it will be useful to represent a network by the classical “black box.” See Fig. 1-1. It has, in general, m inputs (excitations), $x_1(t), x_2(t), \dots, x_m(t)$ and n outputs (responses), $y_1(t), y_2(t), \dots, y_n(t)$.[†] Note that, in general, m is not equal to n . We use the notation

$$S\{x_1, x_2, \dots, x_m\} = \{y_1, y_2, y_3, \dots, y_n\} \quad (1-1a)$$

[†] These are general symbols; others are $e(t)$ for excitation and $r(t)$ for response. Specific excitations and responses will be denoted by appropriate symbols such as $i(t)$ for a current, $v(t)$ for a voltage, etc.

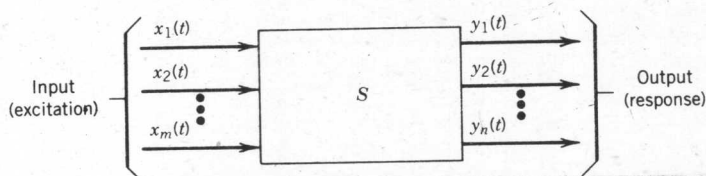


FIGURE 1-1. A "black box."

or

$$\{x_1, x_2, \dots, x_m\} \xrightarrow{S} \{y_1, y_2, y_3, \dots, y_n\} \quad (1-1b)$$

to mean, "the inputs x_1, x_2, \dots, x_m to network S produce the outputs y_1, y_2, \dots, y_n ." In network analysis, we deal in general with the following problems.

1. Given the network S , obtain the input-output relations in the mathematical form. In other words, find the explicit form of Eq. (1-1) for a given network.
2. Having obtained the equations for the given network, solve them to obtain the outputs corresponding to given inputs.
3. Discuss the mathematical properties of the equations of a network, and, hence, certain properties of the network.

A *continuous-time* network is characterized by inputs and outputs which are functions of the *continuous variable* t . In a *discrete-time* network, they vary only at discrete values of time. In the former case we designate these inputs and outputs as $x(t)$ and $y(t)$, whereas in the latter case they are denoted by $x(n)$ and $y(n)$, where $n = 1, 2, 3, \dots$.

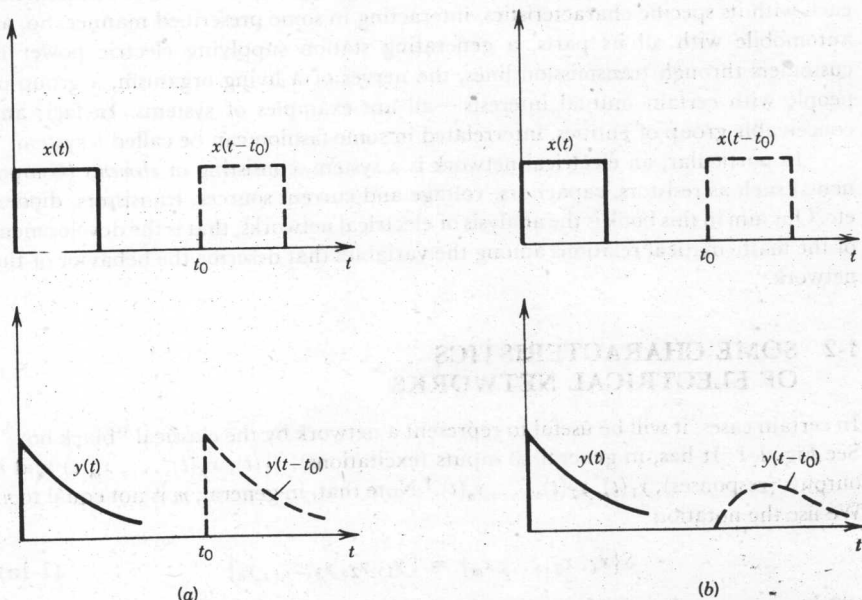


FIGURE 1-2. (a) A constant network; (b) A time-varying network.

are the discrete points on the time axis. Continuous-time networks can be described, in general, by *differential equations*, and discrete-time networks by *difference equations*.

A *constant (time-invariant)* network is one whose response has a *shape* depending only on the *shape* of the excitation and not on the time of application of the excitation (see Fig. 1-2). Mathematically, this can be expressed as follows: with all initial conditions zero, if

$$S\{x(t)\} = y(t) \quad (1-2a)$$

then

$$S\{x(t - t_0)\} = y(t - t_0) \quad (1-2b)$$

where the notation of Eq. (1-1) is used. In other words: a time-shift t_0 in the input produces an identical time-shift in the output.

In a *time-varying* network, Eq. (1-2b) does not hold. Typically, the parameters of a time-invariant network will be constants, and those of a time-varying network will be functions of time.

Example 1

A (hypothetical) network is described by the equation $v(t) = i(t/2)$, where v is the output voltage and i is the input current. Applying Eq. (1-2), we obtain

$$S\{i(t - t_0)\} = i[\tfrac{1}{2}(t - t_0)]$$

but on the other hand,

$$v(t - t_0) = i(\tfrac{1}{2}t - t_0)$$

obviously, $i(t/2 - t_0) \neq i[1/2(t - t_0)]$, and, therefore, the network is time-varying. \square

Example 2

The output current of a certain network is given by $i(t) = [v(t)]^2$, where v is the input voltage. With Eq. (1-2), we obtain

$$S\{v(t - t_0)\} = [v(t - t_0)]^2$$

on one hand, and

$$i(t - t_0) = [v(t - t_0)]^2$$

on the other. This network, then, is constant. \square

A lumped element has physical dimensions which do not affect its describing equation. More precisely, if d is the largest dimension of the element, and λ is the wavelength of the signal, then a lumped element satisfies

$$d \ll \lambda \quad (1-3a)$$

4 1 Introduction

The wavelength λ is given by

$$\lambda = \frac{c}{f} \quad (1-3b)$$

where $c = 3 \times 10^8$ m/s = velocity of electromagnetic waves (velocity of light), and f , in Hertz, is the frequency of the signal. *Total* differential equations describe a network made up of lumped elements. In a distributed network, variations with respect to, say, the length of the components *are* important; such a network is described by partial differential equations, involving space variation as well as time variation.

Example 3

At audio frequencies, with $f = 1,000$ Hz, $\lambda = 3 \times 10^5$ meters \approx 186 miles. At typical microwave frequencies, $f = 10^{10}$ Hz, then $\lambda = 3$ cm \approx 1.2 inches. Thus, for audio circuits, all elements are considered lumped. In microwave circuits, elements such as waveguides are distributed and their describing equations will involve space variations as well as time variations.

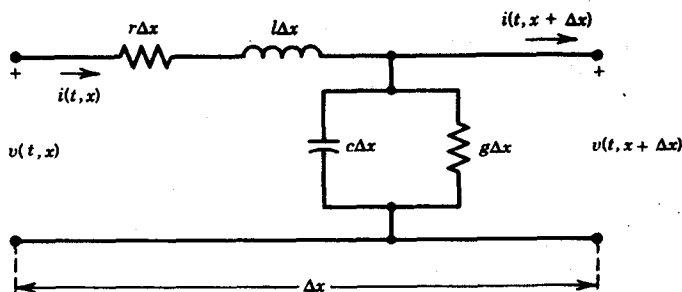


FIGURE 1-3. A model of a distributed network.

The model of the transmission line, Fig. 1-3, is that of a distributed network, since its equations are¹

$$\begin{aligned} -\frac{\partial v(t, x)}{\partial x} &= ri(t, x) + l \frac{\partial i(t, x)}{\partial t} \\ -\frac{\partial i(t, x)}{\partial x} &= gv(t, x) + c \frac{\partial v(t, x)}{\partial t} \end{aligned}$$

showing dependence on time and position; voltage and current at a given time will vary along the length of transmission line. □

1-3 ELEMENTS AND SOURCES

It is both an amazing and a comforting fact that we can model, analyze, and design the most complicated electrical networks using only a few basic elements. Let us

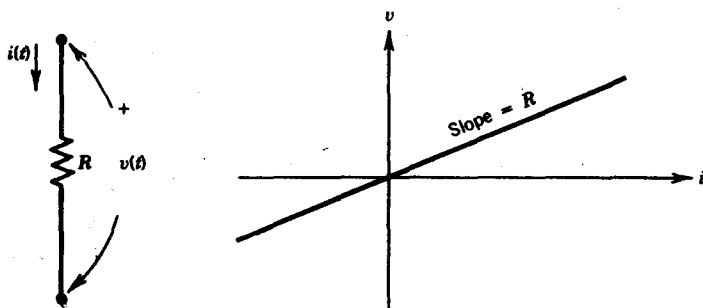


FIGURE 1-4. A constant resistor and its v - i characteristic.

review their properties and introduce certain additional concepts associated with them.

The Resistor

A lumped, time invariant, *linear* resistor is defined by its voltage-current relation

$$v(t) = Ri(t) \quad (1-4a)$$

as shown in Fig. 1-4. The voltage $v(t)$ and the current $i(t)$ have their reference signs as indicated.[†] The units of $v(t)$ are *volts* (V), of $i(t)$ are *amperes* (A), and the resistance R is in *ohms* (Ω).

The inverse relationship, i in terms of v , is, of course,

$$i(t) = \frac{1}{R} v(t) = Gv(t) \quad (1-4b)$$

where G , the *conductance*, is in *mhos* (\mathcal{S}).

The relationships in Eq. (1-4) indicate that the output of a resistor, either v or i , depends, at any time $t = t_0$, only on the input, i or v , respectively, at that time $t = t_0$, and not on past values of the input. Such an element is called *instantaneous* (*memoriless*).

The Capacitor

A constant, lumped, linear capacitor is defined by its charge-voltage relation

$$q(t) = Cv(t) \quad (1-5)$$

as shown in Fig. 1-5. The charge $q(t)$ is measured in *coulombs* and the capacitance C is in *farads* (F). In network analysis, we are interested in the relations between currents and voltages; therefore, we recall the basic relation between current and charge

$$i(t) = \frac{dq(t)}{dt} \quad (1-6)$$

[†] Throughout this book, lower case letters will denote functions of time, for example, $v(t)$, $i(t)$. Sometimes the parenthetical t may be omitted for convenience.

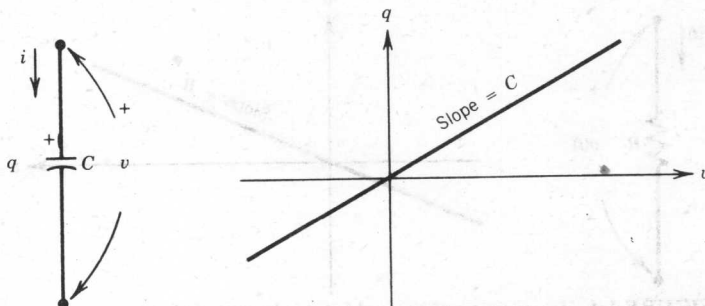


FIGURE 1-5. A constant capacitor and its q - v characteristic.

and differentiate Eq. (1-5). The result is

$$\frac{dq(t)}{dt} = i(t) = C \frac{dv(t)}{dt} \quad (1-7a)$$

and it provides the i - v relationship for the capacitor.

The inverse relationship, v in terms of i , is obtained from Eq. (1-5) and by integrating Eq. (1-7a):

$$\frac{q(t)}{C} = v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx \quad (1-7b)$$

The integral of i , from $-\infty$ to any time t , represents the total charge on the capacitor at time t . The dummy variable x is used in the integrand in order not to confuse it with t .

Unlike the resistor, the capacitor has a *memory*: past values of the input (i) also affect the output (v), as seen in Eq. (1-7b). Such an element, where the output at $t = t_0$ depends on present *and* on past values of the input, is called *dynamic*.

Finally, it will be convenient for us to rewrite Eq. (1-7b) by expressing the integral as a sum of two integrals:

$$\int_{-\infty}^t i(x) dx = \int_{-\infty}^0 i(x) dx + \int_0^t i(x) dx = q(0) + \int_0^t i(x) dx \quad (1-8)$$

where $t = 0$ is some convenient *initial* time, and $q(0)$ is the initial charge (initial condition) on the capacitor. Then Eq. (1-7b) becomes

$$v(t) = \frac{q(0)}{C} + \frac{1}{C} \int_0^t i(x) dx \quad (1-9)$$

that is,

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(x) dx \quad (1-10)$$

with $v(0)$ the initial voltage across the capacitor.

The Inductor

A constant, lumped, linear inductor is defined by its flux-current relation

$$\phi(t) = Li(t) \quad (1-11)$$

as shown in Fig. 1-6. The flux $\phi(t)$ is measured in webers and the inductance L in henries (H).

In order to obtain the v - i relations, we recall that, according to experimental observations (of Faraday, Lenz, and others)

$$v(t) = \frac{d\phi(t)}{dt} \quad (1-12)$$

and differentiate Eq. (1-11)

$$\frac{d\phi(t)}{dt} = v(t) = L \frac{di(t)}{dt} \quad (1-13a)$$

This is the desired v - i relationship for the inductor. It is interesting and instructive to recognize that Eqs. (1-7a) and (1-13a) are of identical form, but with voltage and current exchanging places; that is, for the capacitor

$$i_C(t) = C \frac{dv_C(t)}{dt} \quad (1-7a)$$

while for the inductor

$$v_L(t) = L \frac{di_L(t)}{dt} \quad (1-13a)$$

Here we have added the subscripts C and L for clarity. Such relationships, where elements obey the same equation in form but with v and i replaced, are called *duals*. The principle of duality will be very useful to us.

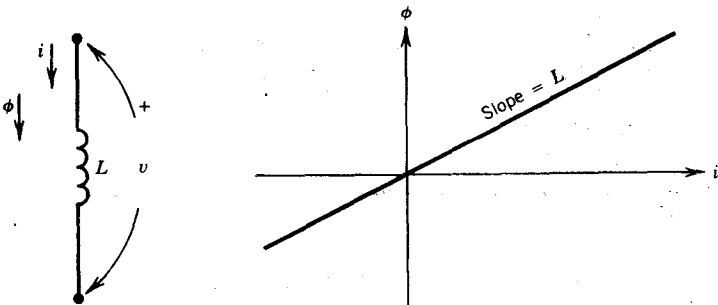


FIGURE 1-6. A constant inductor and its ϕ - i characteristic.