

**Microwave  
Transmission  
Line Filters**

**J.A.G.  
Malherbe,  
Ph.D.**

73.4216  
M200

# Microwave Transmission Line Filters

J.A.G.  
Malherbe,  
Ph.D.



5505742

5505742

Copyright © 1979  
ARTECH HOUSE, INC.  
610 Washington Street  
Dedham, Massachusetts 02026

ZD80/21

Printed and bound in the United States of America  
All rights reserved. No part of this book may be reproduced or utilized in any form or by any means, electronic or mechanical, including photocopying, recording, or by any information storage and retrieval system, without permission in writing from the publisher.  
Library of Congress Card Catalog Number: 78-31243  
Standard Book Number: 0-89006-063-0

# Preface

This book concerns microwave filters constructed of transmission-lines or coupled transmission lines, a field in which considerable advances have been made during the last decade, specifically in exact filter design methods. Much of this material has not been available in textbook form, presenting the novice with the task of collecting and evaluating material of which he has as yet little knowledge or experience. It is the purpose of this book, therefore, to provide a unified treatment of the most relevant material, both old and new. Students at graduate level (the text is based on part of a one semester course in microwave networks at Stellenbosch University) or practicing engineers interested in entering the field should therefore find the book of value.

One obvious omission is that of filter approximation theory. However, there are a large number of excellent texts on filters and modern network theory to which the reader can refer; only in a number of special cases where the treatment for microwave filters differs from that for conventional (lumped element) filters will approximation theory be considered. Simultaneously it is assumed that the reader is familiar with such basic concepts as maximally flat and equiripple prototypes, scaling, and so forth.

The microwave filter principles are introduced as first principles so that the reader need not be equipped with any knowledge in the field other than basic transmission-line theory and high-frequency methods in general. Extensive use is made of a series of equivalent circuits or network models of coupled line circuits and circuit transforms which are developed in the first chapter. The treatment is purposely complete so that the principles can be applied to material outside the contents of this book. In addition,

5505742

references and suggestions for further reading are included at the end of each chapter.

Chapters 2 and 3 are devoted to the study of bandstop filters using lumped element prototypes: Butterworth and Chebyshev in Chapter 2 and elliptic function prototypes in Chapter 3. Similarly, band-pass filters using lumped element prototypes are treated in Chapters 4 and 5.

Nonredundant filter synthesis in both the S- and Z-planes is described in Chapter 6, a necessary amount of approximation theory being included. The design procedures described in Chapters 2 to 6 are applied to the design of multiplexers in Chapter 7 while Chapter 8 describes linear phase filters. It should be noted that most of Chapter 7 can be covered should the reader prefer to omit Chapter 6.

Simple computer analysis methods are described in Appendix A while Appendix B is a convenient summary of design formulae used in Chapters 1 to 5.

The author remains indebted to Mr. J.H. Cloete for his constructive criticism and the use of his design example and advice in Chapter 8, and to Mrs. M.M. Kruger for an exceptional effort in typing the manuscript.

J.A.G. Malherbe  
Stellenbosch  
1 November 1977

# Contents

INTRODUCTION

PREFACE

## 1

TEM NETWORK ELEMENTS 1

- 1.1 Richards' Transform 1
- 1.2 Characteristic Impedance 6
- 1.3 Coupled Lines 9
- 1.4 General Network Transforms 25
- 1.5 An N-Line Network Model 38
- References 46

## 2

BUTTERWORTH AND CHEBYSHEV  
BANDSTOP FILTERS 49

- 2.1 Prototypes and Scaling 49
- 2.2 Redundant Synthesis using Kuroda's Transform 54
- 2.3 Bandstop Elements 56
  - 2.3.1 Coaxial Lines and Round Center Conductors Between Parallel Plates 56
  - 2.3.2 MPC Stripline 60
  - 2.3.3 Machined Stripline with Thick Center Conductors 64
- 2.4 Design Example 65
- References 69

## 3

ELLIPTIC FUNCTION BANDSTOP FILTERS 71

- 3.1 Digital Elliptic Filters 73
  - 3.1.1 Prototype and Scaling 73
  - 3.1.2 Dimensions 73
  - 3.1.3 Construction and Bandwidth 78
  - 3.1.4 Design Example 78
- 3.2 Redundant Synthesis using the Kuroda-Levy Transform: Parallel and Series Foster Circuits 80
  - 3.2.1 Prototypes 80
  - 3.2.2 Foster Sections Without Unit Elements 84

- 3.2.3 Design Example 89
- 3.2.4 Foster Sections with Unit Elements 89
- 3.2.5 Design Example 95
- 3.3 Redundant Synthesis using a Noncommensurate Line Approximation 97
  - 3.3.1 A Noncommensurate Transform 97
  - 3.3.2 Noncommensurate Bandstop Filters 100
  - 3.3.3 Design Example 104
- 3.4 Microwave Brune Sections 104
- References 108

## **4**

### **BUTTERWORTH AND CHEBYSHEV BANDPASS FILTERS 111**

- 4.1 Bandpass Section Properties 111
- 4.2 Prototypes with Inverters 118
- 4.3 Shunt Shorted or Series Open Circuit Stub Filters 123
- 4.4 SCTL Interdigital Filter 124
- 4.5 Parallel-Coupled Line Filters 125
- 4.6 OCTL Interdigital Filters 127
- 4.7 Non-Redundant Interdigital 130
- 4.8 Compline Filters 132
- 4.9 Hairpin-Line Filters 136
- 4.10 Design Examples 142
  - 4.10.1 Shunt Shorted Stub Filter 142
  - 4.10.2 SCTL Interdigital Filter 144
  - 4.10.3 Compline Filter 144
  - 4.10.4 Hairpin Line Filter 146
- References 152

## **5**

### **ELLIPTIC FUNCTION BANDPASS FILTERS 155**

- 5.1 Digital Elliptic Construction 155
- 5.2 Interdigital Elliptic Construction 158
- 5.3 Prototypes for Narrow Bandwidths 160
- 5.4 Stepped Digital Elliptic Filter 163
  - 5.4.1 Quarter-Wave Stepped Filter 163
  - 5.4.2 Design Example 170
  - 5.4.3 Half-Wave Stepped Filter 172
  - 5.4.4 Design Considerations 172
- 5.5 Narrowband Filters With Stubs 178
  - 5.5.1 Commensurate Realization 178
  - 5.5.2 Design Example 183

- 5.5.3 Noncommensurate Form 183
- 5.6 Combine Elliptic Filters 187
- References 191

## 6

### NON-REDUNDANT FILTER SYNTHESIS 193

- 6.1 Equiripple Responses 193
- 6.2 Synthesis in the S-Plane 197
  - 6.2.1 Transfer Functions 197
  - 6.2.2 Synthesis Procedure 198
  - 6.2.3 Design Example 200
  - 6.2.4 Design Considerations 204
- 6.3 Synthesis in the Z-Plane 207
  - 6.3.1 Synthesis Procedure 208
  - 6.3.2 Design Example 211
  - 6.3.3 Calculation of Necessary Order 212
- 6.4 The Capacitively Loaded Interdigital Filter 214
  - 6.4.1 Design Example 218
- 6.5 Combine Filters 222
- 6.6 Maximally Flat Responses 225
- References 228

## 7

### MULTIPLEXERS

- 7.1 Complementary Filters 232
  - 7.1.1 Admittance Properties 232
  - 7.1.2 Redundant (Exact) Design 234
  - 7.1.3 Non-Redundant Synthesis 235
  - 7.1.4 Approximate Designs 237
- 7.2 Pseudo-Complementary Filters 241
  - 7.2.1 Admittance Properties 241
  - 7.2.2 Chebyshev Response 244
  - 7.2.3 Elliptic Function Response 244
  - 7.2.4 Design Examples 246
- 7.3 Multiplexers 249
  - 7.3.1 Cascaded Diplexers 249
  - 7.3.2 Direct Multiplexers 251
  - 7.3.3 Multiplexer Example 255
- References 260



# 8

## LINEAR PHASE FILTERS 263

- 8.1 Linear Phase Lowpass Prototype 263
  - 8.1.1 The Periodic Phase Delay/Amplitude Transfer Function Prototype 267
  - 8.1.2 Prototype Obtained by means of the Arbitrary Phase Polynomials 269
- 8.2 Prototype Element Value Synthesis 273
- 8.3 Physical Realization 274
- 8.4 Mapping 281
- 8.5 Physical Dimensions 283
- 8.6 Design Examples 286
  - 8.6.1 Periodic Phase Delay Prototype 286
  - 8.6.2 Arbitrary Phase Polynomial Prototype 291
- References 296

## APPENDIX A: FILTER ANALYSIS 299

## APPENDIX B: COLLECTED EQUATIONS 313

## INDEX 335

# Chapter 1

## TEM

### Network Elements

The study of transmission-line filters introduces a number of new and physically different principles to the field of conventional lumped element network theory. These concepts are so basic to the theory and practice of TEM (Transverse Electro-Magnetic) filters that it is necessary to first consider them in detail. The transform proposed by Richards<sup>[1-1]</sup> in 1948 forms the basis of the TEM network theory, and although specific filter designs will only be studied in Chapter 2, an example is introduced in the first paragraph to at least partially motivate the long excursion into TEM network elements, of which the basis are sections of transmission-line, single or coupled.

#### 1.1 RICHARDS' TRANSFORM

At frequencies in the kilohertz or lower Megahertz region, the change in phase due to the finite propagation velocity of an electrical signal is usually so small as to be considered negligible for most physical structures. At these frequencies the networks are termed lumped element (LE) networks. At high (radio) frequencies, however, the distributed nature of a physical structure is taken into consideration, leading to the well known transmission-line theory. The driving-point impedance of a transmission-line of characteristic impedance  $Z_0$  and length  $\ell$  is given by

$$Z_s = Z_0 \frac{Z_L \cosh \gamma \ell + Z_0 \sinh \gamma \ell}{Z_0 \cosh \gamma \ell + Z_L \sinh \gamma \ell}$$

where  $Z_0$  and  $\gamma$  are given by

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad \gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

and  $R$ ,  $L$ ,  $G$  and  $C$  are the distributed parameters resistance, inductance, conductance and capacitance per meter of the line. For electrically short linelengths at very high frequencies,  $R \ll \omega L$ ,  $G \ll \omega C$  so that, for  $\alpha = 0$ ,

$$Z_0 \approx \sqrt{\frac{L}{C}} = \frac{1}{vC}, \beta = \omega\sqrt{LC}, v = \frac{1}{\sqrt{LC}}.$$

Consider a capacitor made up of two long strips of foil, separated by a dielectric. The input admittance of such a line will be given by

$$Y = jvC \tan \beta\ell.$$

At low frequencies,  $\beta\ell$  is small so that  $\tan \beta\ell \approx \beta\ell$ , and

$$Y = jvC\beta\ell = jvC \frac{\omega}{v} \ell = j\omega C\ell.$$

that is, the structure behaves as a capacitor of capacitance  $C\ell$ . At high frequencies the input admittance is given by

$$\begin{aligned} Y_{oc} &= \frac{j}{Z_0} \tan \beta\ell \\ &= \frac{j}{Z_0} \tan \left( \frac{\pi}{2} \frac{\omega}{\omega_0} \right) \end{aligned}$$

where  $\omega_0$  is defined as the frequency at which  $\ell = \lambda_0/4$ . The transform proposed by Richards states that, if

$$\dot{S} = j\Omega = j \tan \left( \frac{\pi}{2} \frac{\omega}{\omega_0} \right), \quad (1-1)$$

then

$$Y_{oc} = j\Omega/Z_0 = j\Omega C' ,$$

that is, the open-circuited transmission-line behaves as a capacitor in the S-plane. For the case of a short circuited line,

$$\begin{aligned} Z_{sc} &= jZ_0 \tan \left( \frac{\pi}{2} \frac{\omega}{\omega_0} \right) \\ &= j\Omega Z_0 = j\Omega L' . \end{aligned}$$

Under Richards' transform, open circuited transmission-lines map into capacitors, while short circuited lines become inductors. This is shown graphically in Figure 1.1.

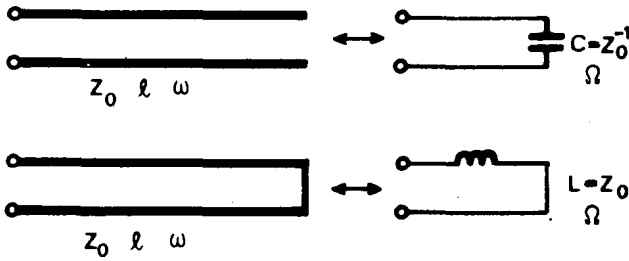


Figure 1.1. Richards' transform.

In order to indicate the application and to illustrate the shortcomings of Richards' transform, it is necessary to consider the performance of a simple lumped element filter, as shown in Figure 1.2 (a) for a 3<sup>rd</sup> order Butterworth lowpass prototype, with the frequency response as shown in Figure 1.2 (b). Applying Richards' transform, the network of Figure 1.2 (c) results, after replacing capacitors by open circuit lines, and inductors by short circuit lines.

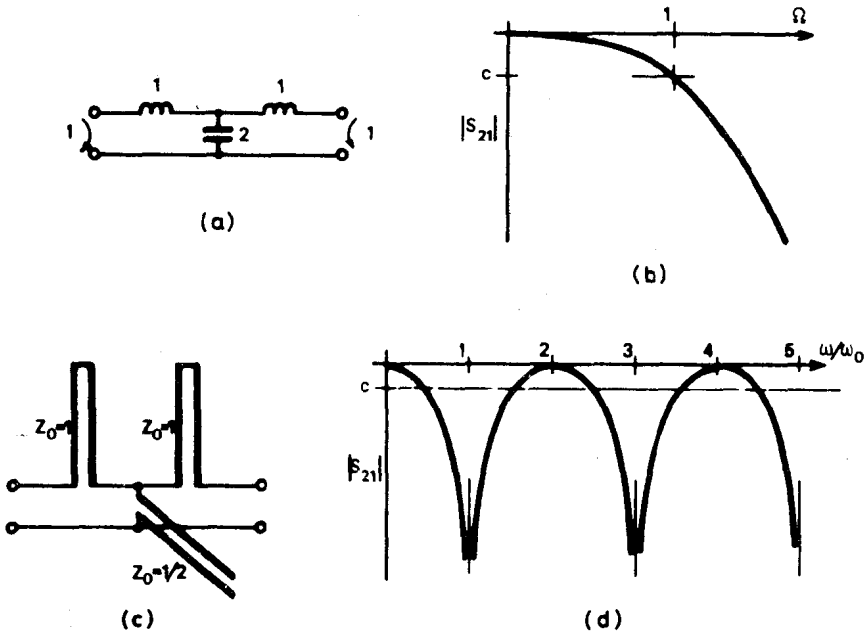


Figure 1.2. Application of Richards' transform to filter synthesis. (a): lumped element prototype with frequency response shown in (b); (c): transmission-line filter with harmonic response, (d).

Now the frequency variable  $\Omega$  varies as  $\tan\left(\frac{\pi}{2} \frac{\omega}{\omega_0}\right)$ , so that for  $\omega = n\omega_0$ ,  $n$  odd, a singularity in  $\Omega$  results. Therefore, as  $\omega$  increases from zero to  $\omega_0$ ,  $\Omega$  changes through all values from zero to infinity, and must consequently cause the full response (all the way to infinity) of Figure 1.2 (b) to be compressed between zero and  $\omega_0$ . As  $\omega$  exceeds  $\omega_0$  for the first time, the sign of  $\Omega$  changes, and  $\Omega$  decreases from negative infinity to zero as  $\omega$  approaches  $2\omega_0$ . This causes the mirror image of the first response to be plotted between  $\omega_0$  and  $2\omega_0$ . This process is repeated between  $2\omega_0$  and  $4\omega_0$ , and so on, resulting in the odd harmonic response shown in Figure 1.2 (d). It should also be noted that the lowpass response has been mapped into a bandstop response in exactly the same way a highpass response maps into a bandpass response. If the initial prototype had had a Chebyshev rather than Butterworth response, the ripples occurring in the band  $0 \leq \omega \leq 1$  would also have appeared in the frequency bands  $0 \leq \omega \leq \omega_0/2$ ,

$1.5 \omega_0 \leq \omega \leq 2\omega_0, 2\omega_0 \leq \omega \leq 2.5 \omega_0 \dots$ . In both cases the response would also be Butterworth or Chebyshev in the sense of being maximally flat or equal ripple.

The purpose of the transform has been shown; it remains to be stated that, as such, it has extremely limited application because the filter of Figure 1.2 (c) cannot be physically constructed, due to the series connected stubs. (The parallel, open circuit stub would present no problem.) At this stage, an element without equivalent under the inverse of Richards' transform is introduced: the *Unit Element* (U), which consists simply of a length  $\lambda_0/4$  of transmission-line  $Z_0$ . The unit element is readily described in matrix form as

$$[Z] = \frac{Z_0}{S} \begin{bmatrix} 1 & \sqrt{1-S^2} \\ \sqrt{1-S^2} & 1 \end{bmatrix} \quad (1-2a)$$

$$[Y] = \frac{1}{SZ_0} \begin{bmatrix} 1 & -\sqrt{1-S^2} \\ -\sqrt{1-S^2} & 1 \end{bmatrix} \quad (1-2b)$$

$$\begin{bmatrix} AB \\ CD \end{bmatrix} = \frac{1}{\sqrt{1-S^2}} \begin{bmatrix} 1 & Z_0 S \\ \frac{S}{Z_0} & 1 \end{bmatrix} \quad (1-2c)$$

The basic TEM network elements can be summarized as in Figure 1.3 below.

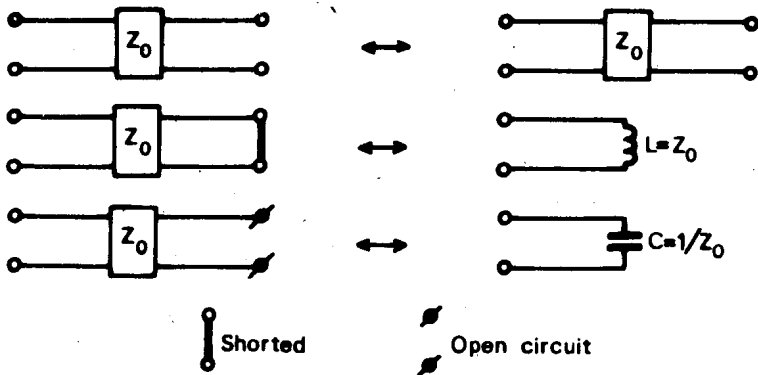


Figure 1.3. TEM Network Elements.

Consider again the transmission-line filter of Figure 1.2 (c). Extending the connection lines on both sides of the filter will leave the amplitude response of the network invariant (although the phase response does change) providing the extending line is of the same characteristic impedance as the generator or load into which the filter operates. It is acceptable therefore to introduce any number of unit elements to each port of the filter, without changing its performance. In that case, if one unit element is added to each port, it would be possible to construct the series lines as series internal coaxial stubs, making the network realizable. Such a form of construction is shown below in Figure 1.4.

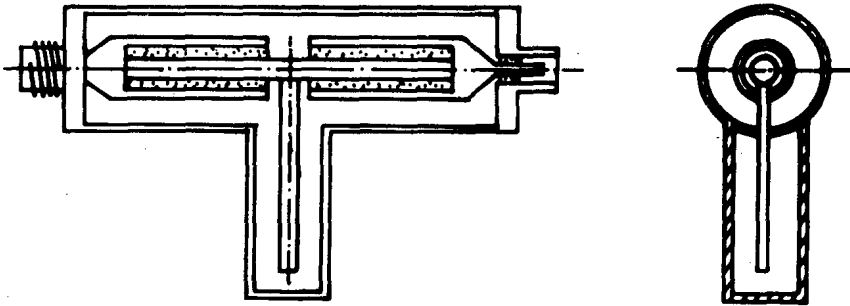



Figure 1.4. Coaxial construction of 3<sup>rd</sup> order Butterworth bandstop filter.

At this point the range of realizable filter structures is very limited; prototypes of different order are freely available but the limitations of physical construction prohibit their use. For this reason, transforms will be developed to introduce unit elements deeper into more complex networks, and exact synthesis methods for the optimal use of such elements investigated. The range of useful networks will also be vastly extended by the use of coupled lines.

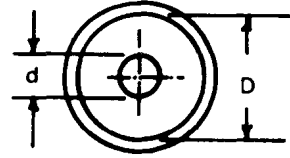
## 1.2 CHARACTERISTIC IMPEDANCE

Characteristic impedance is viewed as being of prime importance in the design of transmission-line filters. Some of the more important types of transmission-line are mentioned here without going into derivations of the equations. For further reference the reader should consult the bibliography at the end of this chapter. The most common forms of TEM line cross section using round cylindrical center conductors are shown in Figure 1.5.

$$Z_0 = \frac{60}{\sqrt{\epsilon_r}} \ln D/d$$


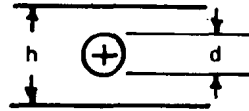
$$Z_0 = \frac{138}{\sqrt{\epsilon_r}} \log \frac{4h}{\pi d}, \text{ if } d/h < 0.75$$



$$Z_0 \approx (138 \log_{10} q + 6.48 - 2.34A - 0.48B - 0.12C) \epsilon^{-1/2}$$

where  $q = D/d$

$$A = (q^4 + 0.405) / (q^4 - 0.405)$$

$$B = (q^8 + 0.163) / (q^8 - 0.163)$$

$$C = (q^{12} + 0.067) / (q^{12} - 0.067)$$

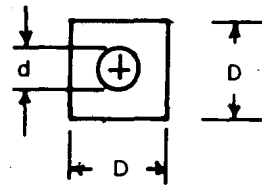


Figure 1.5. Characteristic Impedance.

Lines with rectangular or square center conductor cross sections are generally classified as striplines. Figure 1.6 shows a typical cross section, the capacitance being made up out of the parallel-plate components  $c_{p1}$  and  $c_{p2}$  and the fringe-fields  $c_{f1}$  and  $c_{f2}$ . The total capacitance is given by

$$c/\epsilon = c_{p1}/\epsilon + c_{p2}/\epsilon + 2c_{f1}/\epsilon + 2c_{f2}/\epsilon,$$

and

$$Z_0 = \frac{1}{\sqrt{c}} = \frac{\eta}{\sqrt{\epsilon_r}} \frac{1}{c/\epsilon}.$$

Cohn<sup>[1-2]</sup> gives the fringe-field capacitance as

$$c_f/\epsilon = \frac{1}{\pi} [2\xi \ln(\xi + 1) - (\xi - 1) \ln(\xi^2 - 1)],$$



$$\xi = \begin{cases} \frac{1}{1 - t/(b-s)} \dots (c_{f1}) \\ \frac{1}{1 - t/(b+s)} \dots (c_{f2}) \end{cases} \quad (1-3)$$

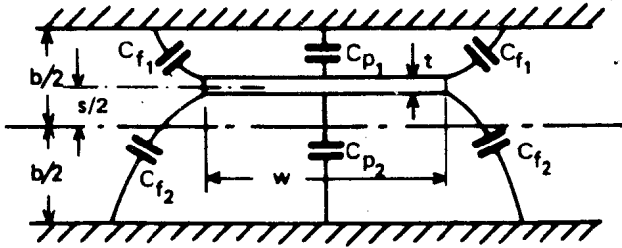


Figure 1.6. Stripline cross section.

The parallel-plate capacitance values are given by

$$c_{p1}/\epsilon = \frac{2w/(b-s)}{1 - t/(b-s)}$$

$$c_{p2}/\epsilon = \frac{2w/(b+s)}{1 - t/(b+s)}$$

For symmetrically spaced stripline, the equation for  $Z_0$  simplifies to

$$Z_0 = \frac{\eta}{4\sqrt{\epsilon_r}} \left( \frac{w/b}{1 - t/b} + c_f/\epsilon \right)^{-1} \quad (1-4)$$

In cases where the normalized width,  $w/(b-t) \leq 0.35$ , the line-width must be compensated because of the loss of fringe field capacitance. According to Getsinger<sup>[1.3]</sup> the new width must be

$$w'/b = [0.07(1 - t/b) + w/b] \div 1.2. \quad (1-5)$$