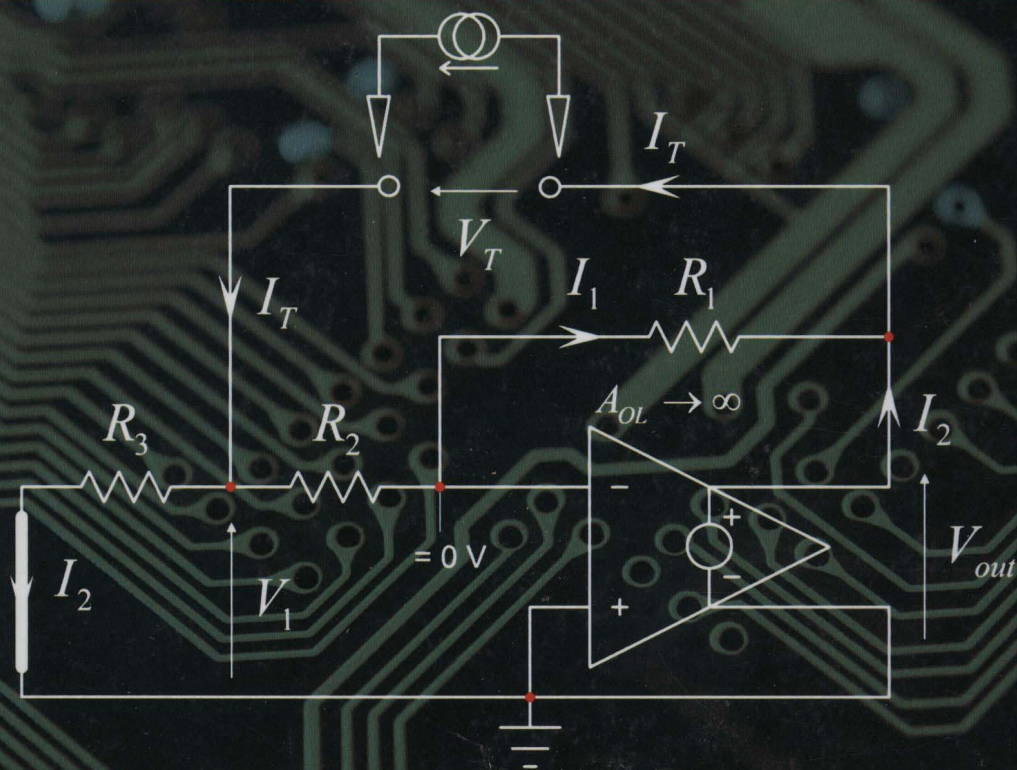


LINEAR CIRCUIT TRANSFER FUNCTIONS

AN INTRODUCTION TO FAST ANALYTICAL TECHNIQUES



CHRISTOPHE P. BASSO

IEEE PRESS

WILEY

LINEAR CIRCUIT TRANSFER FUNCTIONS

AN INTRODUCTION TO FAST ANALYTICAL TECHNIQUES

Christophe P. Basso

ON Semiconductor, Toulouse, France


IEEE PRESS

WILEY

This edition first published 2016
© 2016 John Wiley & Sons, Ltd

Registered office

John Wiley & Sons Ltd, The Atrium, Southern Gate, Chichester, West Sussex, PO19 8SQ, United Kingdom

For details of our global editorial offices, for customer services and for information about how to apply for permission to reuse the copyright material in this book please see our website at www.wiley.com.

The right of the author to be identified as the author of this work has been asserted in accordance with the Copyright, Designs and Patents Act 1988.

All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted, in any form or by any means, electronic, mechanical, photocopying, recording or otherwise, except as permitted by the UK Copyright, Designs and Patents Act 1988, without the prior permission of the publisher.

Wiley also publishes its books in a variety of electronic formats. Some content that appears in print may not be available in electronic books.

Designations used by companies to distinguish their products are often claimed as trademarks. All brand names and product names used in this book are trade names, service marks, trademarks or registered trademarks of their respective owners. The publisher is not associated with any product or vendor mentioned in this book.

Limit of Liability/Disclaimer of Warranty While the publisher and author have used their best efforts in preparing this book, they make no representations or warranties with respect to the accuracy or completeness of the contents of this book and specifically disclaim any implied warranties of merchantability or fitness for a particular purpose. It is sold on the understanding that the publisher is not engaged in rendering professional services and neither the publisher nor the author shall be liable for damages arising herefrom. If professional advice or other expert assistance is required, the services of a competent professional should be sought

Library of Congress Cataloging-in-Publication Data

Names: Basso, Christophe P., author.

Title: Linear circuit transfer functions : an introduction to fast analytical techniques / Christophe Basso.

Description: Chichester, West Sussex ; Hoboken, NJ : Wiley, 2016. | Includes index.

Identifiers: LCCN 2015047967 | ISBN 9781119236375 (cloth) | ISBN 9781119236351 (epub)

Subjects: LCSH: Transfer functions. | Electric circuits, Linear.

Classification: LCC TA347.T7 B37 2016 | DDC 621.3815-dc23 LC record available at <http://lccn.loc.gov/2015047967>

A catalogue record for this book is available from the British Library.

ISBN: 9781119236375

Set in 9.5/11.5 pt TimesLTStd-Roman by Thomson Digital, Noida, India
Printed and bound in Malaysia by Vivar Printing Sdn Bhd

LINEAR CIRCUIT TRANSFER FUNCTIONS



About the Author

Christophe Basso is a Technical Fellow at ON Semiconductor in Toulouse, France, where he leads an application team dedicated to developing new offline PWM controller's specifications. He has originated numerous integrated circuits among which the NCP120X series has set new standards for low standby power converters.

Further to his 2008 book *Switch-Mode Power Supplies: SPICE Simulations and Practical Designs*, published by McGraw-Hill, he released a new title in 2012 with Artech House, *Designing Control Loops for Linear and Switching Power Supplies: a Tutorial Guide*. He holds 17 patents on power conversion and often publishes papers in conferences and trade magazines including How2Power and PET.

Christophe has over 20 years of power supply industry experience. Prior to joining ON Semiconductor in 1999, Christophe was an application engineer at Motorola Semiconductor in Toulouse. Before 1997, he worked at the European Synchrotron Radiation Facility in Grenoble, France, for 10 years. He holds a BSEE equivalent from the Montpellier University (France) and a MSEE from the Institut National Polytechnique of Toulouse (France). He is an IEEE Senior member.



When he is not writing, Christophe enjoys snowshoeing in the Pyrenees.

Preface

First as a student and later as an engineer, I have always been involved in the calculation of transfer functions. When designing power electronics circuits and switch mode power supplies, I had to apply my analytical skills on passive filters. I also had to linearize active networks when I needed the control-to-output dynamic response of my converter. Methods to determine transfer functions abounded and there are numerous textbooks on the subject. I started in college with mesh-node analysis, and at some point ended up using state variables. If all paths led to the correct result, I often struggled rearranging equations to make them fit a friendly format. Matrices were useful for immediate numerical results but, when trying to extract a meaningful symbolic transfer function, I was often stuck with an intractable result. What matters with a transfer function formula is that you can immediately distinguish poles, zeros and gains without having to rework the expression. This is the idea behind the term *low-entropy*, a concept forged by Dr. Middlebrook.

Simulation gives you an idea where poles and zeros hide by interpreting the phase and magnitude plots with minimum-phase functions. However, inferring which terms really affect a pole or a zero position from a Bode plot is a different story. Fortunately, if the transfer function is written the right way, then you can immediately identify which elements contribute to the roots and assess how they impact the dynamic response. As some of these parasitics vary in production or drift with temperature, you have to counteract their effects so that reliability is preserved during the circuit's life. The typical example is when you are asked to assess the impact of a parasitic term variation on a product you have designed: if a new capacitor or a less expensive inductor is selected by the buyers, will production be affected? Is there a chance that stability will be jeopardized in some operating conditions? Implementing the classical analysis method will surely deliver a result describing the considered circuit, but extracting the information you need from the final expression is unlikely to happen if the equations you have are disorganized or in a *high-entropy* form.

This is where Fast Analytical Circuit Techniques (FACTs) come into play. The acronym was formed by Dr. Vatché Vorpérian, who formalized the technique you are about to discover here. Before him, Dr. Middlebrook published numerous papers and lectured on his Extra-Element Theorem (EET), later generalized to the N extra-element theorem by one of his alumni. Since Hendrik Bode in the 40's, authors have come up with techniques aiming to simplify linear circuit analysis through various approaches. All of them were geared towards determining the transfer function at a pace quicker than what traditional methods could provide. Unfortunately, while traveling and visiting customers world-wide, I have found that, despite all the available documentation, FACTs were rarely adopted by engineers or students. When describing examples in my seminars and showing the method at work in small-signal analysis, I could sense interest from the audience through questions and comments. However, during the discussions I had later on with some of the engineers or students, they confessed that they tried to acquire the skill but gave up because of the

intimidating mathematical formalism and the complexity of the examples. If one needs to be rigorous when tackling electrical analysis, perhaps a different approach and pace could make people feel at ease when learning the method. This is what I strived to do with this new book, modestly shedding a different light on the subject by progressing with simple-to-understand examples and clear explanations. As a student, I too struggled to apply these fast analytical circuits techniques to real-world problems; as such, I identified the obstacles and worked around them with success. Thus, the seeds for this book were sown.

This book consists of five chapters. The first chapter is a general introduction to the technique, explaining what transfer functions are and how time constants characterize a circuit. The second chapter digs into transfer function definitions and polynomial forms, introducing the low- Q approximation, and how to organize 2nd and 3rd-order denominators or numerators. The third chapter uses the superposition theorem to gently introduce the extra-element theorem. Numerous examples are given to illustrate its usage in different 1st-order configurations. The fourth chapter deals with the 2-extra element theorem, generalized and applied to 2nd-order networks. Numerous examples illustrated with Mathcad® and SPICE punctuate the explanations. Finally, the fifth chapter tackles 3rd- and 4th-order circuits, all illustrated with examples. Each chapter ends with 10 fully documented problems. There is no secret; mastering a technique requires patience and practice, and I encourage you to test what you have learned after each chapter through these problems.

I have adopted the same casual writing style already used in my previous books, as readers' comments show that the way I present things better explains complex matters. Please let me know if my approach still applies here and if you enjoy reading this new book. As usual, feel free to send me your comments or any typos you may find at cbasso@wanadoo.fr. I will maintain an errata list in my personal webpage as I did for the previous books (<http://cbasso.pagesperso-orange.fr/Spice.htm>). Thank you, and have fun determining transfer functions!

Christophe Basso
May 2015

Acknowledgement

A book like this one could not have been written and published without the help of many contributing friends. My warmest thanks and love first go to my sweet wife Anne who endured my ups and downs when determining some of the book transfer functions: equations time is over and we can now enjoy the long and warm evenings of summer to come!

I was fortunate to share my work with my ON Semiconductor colleagues and friends who played a crucial role in reviewing my pages and challenging the method. Stéphanie Cannenterre reviewed and practiced numerous book exercises. She now masters the method: well done! Dr. José Capilla raced with me several times to determine a transfer function with his Driving Point Impedance method and I recognize his skills in doing so. Special thanks go to my friend Joël Turchi with whom I spent endless hours debating the method or discussing the validity of an equation. Merci Joël for your kindness and invaluable support for this book!

Two people did also accompany me from the beginning of the writing process. Mon ami Canadien Alain Laprade from ON Semiconductor in East Greenwich who developed an addicted relationship to the FACTs and kindly reviewed all my work. Monsieur Feucht from Innovatia did also a tremendous work in correcting my pages but also kindly polished my English. I am not exactly a novelist and cannot hide my French origins Dennis!

I want to warmly thank the following reviewers for their kind help in reading my pages during the 2015 summer: Frank Wiedmann (Rhode & Schwarz), Thierry Bordignon, Doug Osterhout (both are with ON Semiconductor), Tomas Gubek – děkuji! (FEI), Didier Balocco (Fairchild), Jochen Verbrugghe, Bart Moeneclaey (both are with Ghent University), Bruno Allard (INSA Lyon), Vatché Vorpérian (JPL), Luc Lasne (Bordeaux University) and Garrett Neaves (Freescale Semiconductor).

Last but not least, I would like to thank Peter Mitchell at Wiley & Sons UK for giving me the opportunity to publish my work.

Contents

About the Author	ix
Preface	xi
Acknowledgement	xiii
1 Electrical Analysis – Terminology and Theorems	1
1.1 Transfer Functions, an Informal Approach	1
1.1.1 <i>Input and Output Ports</i>	3
1.1.2 <i>Different Types of Transfer Function</i>	6
1.2 The Few Tools and Theorems You Did Not Forget . . .	11
1.2.1 <i>The Voltage Divider</i>	11
1.2.2 <i>The Current Divider</i>	12
1.2.3 <i>Thévenin's Theorem at Work</i>	14
1.2.4 <i>Norton's Theorem at Work</i>	19
1.3 What Should I Retain from this Chapter?	25
1.4 Appendix 1A – Finding Output Impedance/Resistance	26
1.5 Appendix 1B – Problems	37
Answers	39
2 Transfer Functions	41
2.1 Linear Systems	41
2.1.1 <i>A Linear Time-invariant System</i>	43
2.1.2 <i>The Need for Linearization</i>	43
2.2 Time Constants	44
2.2.1 <i>Time Constant Involving an Inductor</i>	47
2.3 Transfer Functions	49
2.3.1 <i>Low-entropy Expressions</i>	54
2.3.2 <i>Higher Order Expressions</i>	59
2.3.3 <i>Second-order Polynomial Forms</i>	60
2.3.4 <i>Low-Q Approximation for a 2nd-order Polynomial</i>	62
2.3.5 <i>Approximation for a 3rd-order Polynomial</i>	68
2.3.6 <i>How to Determine the Order of the System?</i>	69
2.3.7 <i>Zeros in the Network</i>	76
2.4 First Step Towards a Generalized 1 st -order Transfer Function	78
2.4.1 <i>Solving 1st-order Circuits with Ease, Three Examples</i>	82

2.4.2	<i>Obtaining the Zero with the Null Double Injection</i>	89
2.4.3	<i>Checking Zeros Obtained in Null Double Injection with SPICE</i>	94
2.4.4	<i>Network Excitation</i>	95
2.5	What Should I Retain from this Chapter?	100
	References	101
2.6	Appendix 2A – Problems	102
	Answers	105
3	Superposition and the Extra Element Theorem	116
3.1	The Superposition Theorem	116
3.1.1	<i>A Two-input/Two-output System</i>	120
3.2	The Extra Element Theorem	126
3.2.1	<i>The EET at Work on Simple Circuits</i>	130
3.2.2	<i>The EET at Work – Example 2</i>	132
3.2.3	<i>The EET at Work – Example 3</i>	137
3.2.4	<i>The EET at Work – Example 4</i>	138
3.2.5	<i>The EET at Work – Example 5</i>	140
3.2.6	<i>The EET at Work – Example 6</i>	146
3.2.7	<i>Inverted Pole and Zero Notation</i>	150
3.3	A Generalized Transfer Function for 1 st -order Systems	153
3.3.1	<i>Generalized Transfer Function – Example 1</i>	156
3.3.2	<i>Generalized Transfer Function – Example 2</i>	159
3.3.3	<i>Generalized Transfer Function – Example 3</i>	163
3.3.4	<i>Generalized Transfer Function – Example 4</i>	170
3.3.5	<i>Generalized Transfer Function – Example 5</i>	174
3.4	Further Reading	180
3.5	What Should I Retain from this Chapter?	180
	References	182
3.6	Appendix 3A – Problems	183
	Answers	185
	References	218
4	Second-order Transfer Functions	219
4.1	Applying the Extra Element Theorem Twice	219
4.1.1	<i>Low-entropy 2nd-order Expressions</i>	227
4.1.2	<i>Determining the Zero Positions</i>	231
4.1.3	<i>Rearranging and Plotting Expressions</i>	233
4.1.4	<i>Example 1 – A Low-Pass Filter</i>	235
4.1.5	<i>Example 2 – A Two-capacitor Filter</i>	241
4.1.6	<i>Example 3 – A Two-capacitor Band-stop Filter</i>	245
4.1.7	<i>Example 4 – An LC Notch Filter</i>	248
4.2	A Generalized Transfer Function for 2 nd -Order Systems	255
4.2.1	<i>Inferring the Presence of Zeros in the Circuit</i>	256
4.2.2	<i>Generalized 2nd-order Transfer Function – Example 1</i>	257
4.2.3	<i>Generalized 2nd-order Transfer Function – Example 2</i>	262
4.2.4	<i>Generalized 2nd-order Transfer Function – Example 3</i>	266
4.2.5	<i>Generalized 2nd-order Transfer Function – Example 4</i>	273

4.3	What Should I Retain from this Chapter ?	277
	References	279
4.4	Appendix 4A – Problems	279
	Answers	282
	References	311
5	N^{th}-order Transfer Functions	312
5.1	From the 2EET to the NEET	312
5.1.1	<i>3rd-order Transfer Function Example</i>	317
5.1.2	<i>Transfer Functions with Zeros</i>	320
5.1.3	<i>A Generalized N^{th}-order Transfer Function</i>	327
5.2	Five High-order Transfer Functions Examples	335
5.2.1	<i>Example 2: A 3rd-order Active Notch Circuit</i>	341
5.2.2	<i>Example 3: A 4th-order LC Passive Filter</i>	349
5.2.3	<i>Example 4: A 4th-order Band-pass Active Filter</i>	355
5.2.4	<i>Example 5: A 3rd-order Low-pass Active GIC Filter</i>	368
5.3	What Should I Retain from this Chapter ?	383
	References	385
5.5	Appendix 5A – Problems	385
	Answers	388
	References	431
	Conclusion	433
	Glossary of Terms	435
	Index	439

1

Electrical Analysis – Terminology and Theorems

This first chapter is an introduction to some of the basic definitions and terms you must understand in order to perform electrical analysis with efficiency and speed. By electrical analysis, I imply finding the various relationships that characterize a particular electrical network. To excel in this field, as in any job, you need to master a few tools. Obviously, they are innumerable and I am sure you have learned a plethora of theorems during your student life. Some names now seem distant simply because you never had a chance to exercise them. Or you actually did but implementation was so obscure and complex that you left quite a few of them aside. This situation often happens in an engineer's life where real-case experience helps clean up what you have learned at school to only retain techniques that worked well for you. Sometimes, when what you know fails to deliver the result, it is a good opportunity to learn a new procedure, better suited to solve your current case. In this chapter, I will review some of the founding theorems that I extensively use in the examples throughout this book. However, before tackling definitions and examples, let us first understand what the term *transfer function* designates.

1.1 Transfer Functions, an Informal Approach

Assume you are in the laboratory testing a circuit encapsulated in a box featuring two connectors: one for the input, the second for the output. You do not know what is inside the box, despite the transparent case in the picture! You now inject a signal with a function generator to the input connector and observe the output waveform with an oscilloscope. Using the right terminology, you *drive* the circuit input and observe its *response* to the stimulus. The input waveform represents the *excitation* denoted u and it generates a *response* denoted y . In other words, the excitation variable propagates through the box, undergoes changes in phase, amplitude, perhaps induces distortion etc. and the oscilloscope reproduces the response on its screen.

The waveform displayed by the oscilloscope is a *time-domain* graph in which the horizontal axis x is graduated in seconds while the vertical axis y indicates the signal *amplitude* (positive or negative). Its dimension depends on the observed variable (volts, amperes and so on). The input waveform is denoted in lower case as it is an *instantaneous* signal, observed at a time – the *instant* t – $u(t)$. A similar notation applies to the output signal, $y(t)$. In Figure 1.1, you see a low duty ratio square-wave injected in the box engendering a rather distorted waveform on the output.

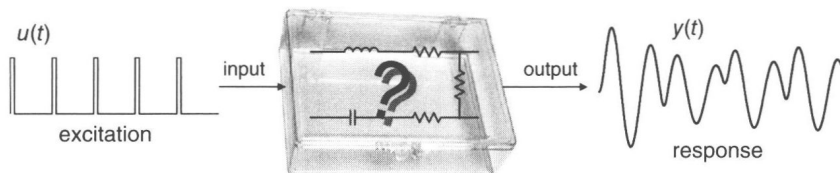


Figure 1.1 A black box featuring an input and an output signal. What is the relationship linking output and input waveforms?

This ringing signal tells us that the box could associate resonant elements, probably capacitors and inductors but not much more than that. If we change the excitation, what type of shape will we obtain? Knowing what is inside the box will let us predict its response to various types of excitation signals.

There are several available ways to characterize an electrical linear circuit. One of them is called *harmonic analysis*. The input signal is replaced by a sinusoidal waveform and you observe how the stimulus propagates through the box to form the response. This is shown in Figure 1.2:

The excitation level must be of reasonable amplitude – understand *small* – so that the response signal is not distorted. The input signal dc bias must also be set accounting for the physical constraints imposed by the active circuit so that upper- or lower-rail saturation is avoided. In other words, the box internal circuitry is not *overdriven* and remains *linear* during the analysis. Linearity is confirmed if the output signal is sinusoidal with the same frequency as the input sine and only varies in amplitude and phase while you ac-sweep the network. This is a so-called *small-signal* analysis. In the Laplace domain, you perform such harmonic analysis when you set $s = j\omega$ in which $\omega = 2\pi f$ represents the angular frequency expressed in radians per seconds (rads/s). Laplace analysis with $s = j\omega$ applies to linear circuits only.

Should you increase the input signal amplitude or change the operating bias point, slewing or clipping may happen. In this case, you explore the box *large-signal* or *nonlinear* response. This is a characterization different than the small-signal approach and it offers another insight into the circuit operation. Let us keep linear and once the right input amplitude is found, i.e. a signal of comfortable amplitude is observed on the oscilloscope screen, the frequency is varied step by step while output amplitude/phase couples are recorded in an array. At each frequency point f , we store the ratio of the response amplitude $Y(f)$ in volts to the excitation amplitude $U(f)$ in volts also. At each frequency point f , we save the phase information linking both input and output waveforms. As U and Y are complex variables affected by a magnitude and a phase, we can write:

$$A_v(s) = \frac{Y(s)}{U(s)} \quad (1.1)$$

A_v represents a *transfer function*, a mathematical relationship linking a response signal Y to an excitation signal U . Please note that the excitation signal U resides in the transfer function

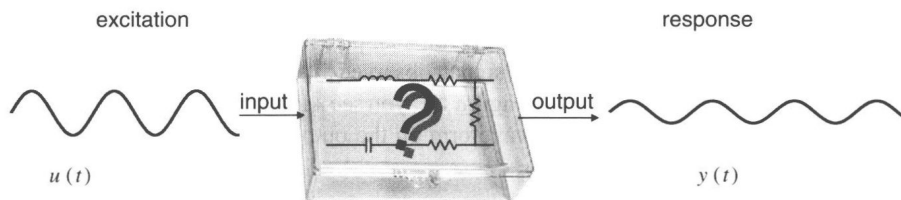


Figure 1.2 The black box is now driven by a sinusoidal stimulus for a small-signal analysis.