

电工电子技术与EDA基础

(上)

Electrical Engineering and EDA Fundamentals

Volume I

段玉生 王艳丹 何丽静 主编

Duan Yusheng Wang Yandan He Lijing

杨福生 主审

Yang Fusheng



清华大学出版社



Springer

电工电子技术 与 EDA 基础（上）

Electrical Engineering and EDA Fundamentals Volume I

编者 段玉生（清华大学电机系）
王艳丹（清华大学电机系）
何丽静（清华大学电机系）
侯世英（重庆大学电气工程学院）
许怡生（北京工业大学电控学院）
李钊年（青海大学水电系）

译审 杨福生（清华大学电机系）



清华大学出版社
北京



Springer

版权所有，翻印必究。

本书封面贴有清华大学出版社激光防伪标签，无标签者不得销售。

图书在版编目(CIP)数据

电工电子技术与 EDA 基础(上)/段玉生,王艳丹,何丽静等编著. —北京: 清华大学出版社, 2004

ISBN 7-302-07818-1

I . 电… II . ①段… ②王… ③何… III . ①电工电子—高等学校—教材 ②电子电路—电路设计：
计算机辅助设计—高等学校—教材 IV . ①TM1 ②TN702

中国版本图书馆 CIP 数据核字(2003)第 117306 号

出版者: 清华大学出版社 **地 址:** 北京清华大学学研大厦

<http://www.tup.com.cn> **邮 编:** 100084

社总机: 010-62770175 **客户服务:** 010-62776969

责任编辑: 王一玲

版式设计: 刘祎森

印 刷 者: 北京四季青印刷厂

装 订 者: 北京市密云县京文制本装订厂

发 行 者: 新华书店总店北京发行所

开 本: 185×230 **印张:** 25 **字数:** 497 千字

版 次: 2004 年 5 月第 1 版 2004 年 5 月第 1 次印刷

书 号: ISBN 7-302-07818-1/TM · 47

印 数: 1 ~ 3000

定 价: 29.80 元(附光盘 1 张)

本书如存在文字不清、漏印以及缺页、倒页、脱页等印装质量问题,请与清华大学出版社出版部联系
调换。联系电话: (010)62770175-3103 或(010)62795704

前 言

“电工电子技术”(电工学)是高等学校理工科非电类专业本科学生的技术基础课。从我国高等学校开设电工学课程以来,随着新技术和新器件的出现,课程内容进行了多次改革,例如 70 年代末引入了模拟和数字集成电路,90 年代初引入了可编程控制器等。进入 21 世纪后,电子设计自动化 EDA(Electronics Design Automation)技术在我国逐渐得到推广应用。它以计算机为工作平台,以硬件描述语言为电路和器件设计的基础,结合相应的 EDA 开发软件,使电子系统的设计产生了质的飞跃,系统的功能验证日趋完善,硬件实现的速度大大提高。当前飞速发展的科技形势对科技工作者提出了新的要求及挑战,掌握和应用 EDA 技术,已经成为每位工程技术人员需要具备的一种技能。为了适应科技发展与教学改革的需要,将 EDA 技术引入“电工学”教学已成当务之急。

本套教材分为上、下两册:上册的主要内容为电工技术与相关的 EDA 知识;下册的主要内容为电子技术与相关的 EDA 知识。两册可以配套使用,也可以单独选用。

本教材根据课程的性质和实际应用情况,对传统的教学内容进行了精选及补充。上册内容包括电路的基本理论和分析方法、EDA 基础知识(SPICE)、磁路与变压器、电动机的原理及应用、继电器-接触器控制和可编程控制器(PLC)等内容;下册内容包括模拟电子电路、数字电子电路、电路的设计与仿真、VHDL 语言、可编程器件等内容。各章都对所选用的教学内容进行了深入细致的分析,努力做到概念准确、重点突出、叙述精练、通俗易懂,便于读者自学。书中配有较多的例题及习题,通过这些练习,读者会加深对课程内容的理解。

电工学课程的发展趋势必然是软硬结合,据此我们在教学内容中加入了 EDA 技术,并将其放在了较重要的位置。有关 EDA 技术部

分,在电工技术和模拟电路中,以电路仿真程序 SPICE 语言为重点;在数字电路中,以硬件描述语言 VHDL 为重点。SPICE 和 VHDL 是目前 EDA 技术中最基础的标准语言,在元件建模、电路的分析仿真等方面具有其他语言无法替代的作用。本册在对电路的基本概念和分析方法做了介绍之后,从第 2 章开始便引入了 SPICE 基本知识,并在以后各章根据其具体内容,对 SPICE 的语法结构、语句格式以及电路仿真过程等做了进一步介绍。也就是说,采用“结合使用,循序渐进”的方法,将 EDA 内容引入到教材中,这样安排既可以避免冗长繁琐的讲解,又可将其和传统的教学内容有机地结合起来,更便于读者学习。在以往的教学中,我们按此思路已进行过数次试验,得到了学生的一致好评。

教学内容和学时是有限的,很多需要学习的内容不可能全部安排在课堂上进行讲授,有些内容可以选学或课外自学。我们把不少相关内容放在附录中,将一些常用的应用软件(学生版或演示版)放到光盘中,为学生提供了更大的学习空间。如本册的光盘中,附有电路仿真软件 Multisim 的评估版,并在书后的附录中对该软件的使用作了说明。Multisim 功能强大,具有模拟/数字/VHDL/Verilog 混合仿真能力,而且界面友好、易学易用。Multisim 是以 SPICE 为内核的电路仿真软件,学好 SPICE 对 Multisim 软件的应用(特别是高级应用)将会有很大的帮助,读者掌握了 SPICE 内容后可以自己练习使用 Multisim 进行电路分析。

可编程控制器(PLC)现在已是电工技术教学中不可或缺的内容。根据近几年我国 PLC 的使用情况,西门子公司生产的可编程控制器占有较大市场,而且其系统性能、网络特性等都比较好。因此,本册在讲授可编程控制器时,采用了西门子的产品为介绍对象。因为不同的 PLC 产品,在编程语言和使用方法等方面多有类似之处,所以熟悉和掌握西门子的 PLC 产品,也有利于对其他品牌产品的学习和使用。

本套教材的教学内容,主要适用于多学时类型的电工学课程,其他相关类型课程也可选用。各位老师在选用该教材时,可不受学时数的限制,根据本校的实际情况,对教学内容进行安排或取舍。

本书的编写以清华大学的几位老师为主,同时还有北京工业大学、重庆大学、青海大学等高校的有丰富教学经验的老师参加。书中内容凝聚了清华大学电工学及应用电子学教研组很多老师的心血,在

这里向所有为本书做出贡献的老师、同行表示深深的谢意！

本册共分 10 章,第 1,6 章由何丽静编写,第 2,5 章由段玉生编写,第 3,4,9 章由王艳丹编写,第 7 章由李钊年编写,第 8 章由许怡生编写,第 10 章和附录 D 由侯世英编写。全书内容编排以及目录、附录(除附录 D)、附带光盘的内容、SPICE 软件的使用等全部由段玉生负责。本书的统稿工作由段玉生、王艳丹、何丽静共同完成。本书的主审是杨福生教授,他对本书进行了认真审查,严格把关,对本教材的成稿起了关键作用。

由于时间仓促,编者的知识水平有限,书中难免存在不妥和错误之处,真诚希望广大读者特别是从事“电工电子技术”教学的同仁批评、指正!

编 者

2004 年 3 月于清华大学

目 录

第 1 章 电路的基本概念和分析方法	1
1.1 电路中的物理量及其正方向	2
1.1.1 电路中物理量的实际方向	2
1.1.2 电路分析中的假设正方向	3
1.1.3 电功率	4
1.2 电路元件	5
1.2.1 无源元件	5
1.2.2 有源元件	8
1.3 电路的基本定律	14
1.3.1 欧姆定律	14
1.3.2 克希荷夫定律	15
1.4 电路的两种基本分析方法	17
1.4.1 支路电流法	18
1.4.2 节点电位法	20
1.5 线性电路中的两个重要定理	23
1.5.1 叠加定理	23
1.5.2 等效电源定理	25
1.6 受控源电路及分析	34
1.6.1 受控源的概念	34
1.6.2 受控源的类型及符号	34
1.6.3 含受控源电路的分析	35
本章小结	39
习题	40

第 2 章 电路仿真程序 SPICE 入门	46
2.1 SPICE 简介	46
2.2 SPICE 电路文件	48
2.2.1 在 SPICE 中怎样描述电路	48
2.2.2 元件值的写法	49
2.2.3 电路文件的编辑与运行	50
2.3 元件语句	50
2.3.1 电阻、电容和电感	50
2.3.2 电源	50
2.4 直流分析语句	52
2.5 输出语句	54
2.6 子电路的定义和调用	54
2.7 .model 语句与二极管、开关在 SPICE 中的表示法	55
2.7.1 .model 语句	55
2.7.2 开关模型	56
2.7.3 二极管模型	57
2.8 用 SPICE 分析直流电路举例	58
本章小结	61
习题	61
第 3 章 正弦交流电路	64
3.1 概述	64
3.2 正弦量的数学描述	65
3.2.1 正弦量的三要素	65
3.2.2 同频率正弦量作加减运算的特点	68
3.2.3 正弦量的相量表示法	69
3.3 单一参数的正弦交流电路	72
3.3.1 纯电阻电路	72
3.3.2 纯电感电路	74
3.3.3 纯电容电路	76
3.4 RLC 串联电路	79
3.4.1 RLC 串联电路中电压和电流的关系及阻抗	79
3.4.2 RLC 串联电路中的功率	81

目 录

3.5 交流电路的分析方法	83
3.5.1 阻抗的串并联	83
3.5.2 一般交流电路的分析方法	86
3.5.3 功率因数的提高	89
3.6 谐振现象与交流频率特性	92
3.6.1 串联谐振和并联谐振	92
3.6.2 电路的频率特性	99
3.7 SPICE 在正弦交流电路分析中的应用	106
3.7.1 SPICE 中正弦交流电源的表示方法	106
3.7.2 电阻、电感、电容在 SPICE 中的表示方法	107
3.7.3 SPICE 中的弛豫分析语句 .tran	108
3.7.4 交流分析语句 .ac	109
本章小结	113
习题	113
 第 4 章 三相交流电路	119
4.1 三相交流电源	119
4.1.1 三相电动势的产生	119
4.1.2 三相交流电源的连接	120
4.2 三相负载及三相电路的分析	122
4.2.1 负载星形连接及分析	123
4.2.2 负载三角形连接及分析	126
4.3 三相电路的功率	127
4.3.1 三相电路功率的计算	127
4.3.2 三相电路功率的测量	128
4.4 三相电路的相序	130
4.5 用 SPICE 分析三相交流电路	131
本章小结	133
习题	133
 第 5 章 非正弦周期交流电路	137
5.1 概述	137
5.2 非正弦周期交流信号的分解	138

5.3 非正弦周期交流电路的计算	141
5.4 有效值和平均功率的计算	143
5.4.1 有效值	143
5.4.2 平均功率	144
5.5 脉冲信号源在 SPICE 中的表示法与傅里叶分析(. Fourier)语句	145
5.5.1 脉冲信号源在 SPICE 中的表示法	145
5.5.2 SPICE 中的非线性受控源	146
5.5.3 SPICE 的傅里叶分析(. Fourier)语句	146
5.6 用 SPICE 分析非正弦电路举例	147
本章小结	150
习题	150

第 6 章 电路的过渡过程	154
6.1 概述	154
6.2 换路定理及起始值的确定	155
6.2.1 换路定理	155
6.2.2 起始值的确定	156
6.3 一阶电路过渡过程的分析方法	158
6.3.1 经典法	159
6.3.2 三要素法	162
6.3.3 用叠加法求一阶电路的响应	169
6.4 脉冲激励下的 RC 电路	171
6.4.1 微分电路	171
6.4.2 积分电路	172
6.4.3 序列脉冲作用下的 RC 电路	173
6.5 含有多个储能元件的一阶电路	175
6.5.1 多个储能元件可等效为一个储能元件的一阶电路	175
6.5.2 起始值不独立的一阶电路	175
6.5.3 实用电路举例——脉冲分压电路	178
6.6 二阶电路过渡过程简介	181
6.6.1 RLC 电路二阶过渡过程求解的简要说明	182
6.6.2 二阶过渡过程的特点	183
6.7 用 SPICE 分析电路的过渡过程举例	184

目 录

本章小结	186
习题	187
第 7 章 磁路与变压器	191
7.1 磁路	191
7.1.1 磁场的基本物理量	191
7.1.2 磁性材料的特点	193
7.1.3 磁路计算的基本定律	194
7.1.4 磁路的分析和计算方法	196
7.2 变压器的工作原理与应用	199
7.2.1 变压器的分类	199
7.2.2 互感与互感系数	200
7.2.3 变压器的工作原理	202
7.2.4 变压器的运行特性	204
7.2.5 变压器的使用	205
7.3 专用变压器	207
7.3.1 自耦变压器	207
7.3.2 仪用互感器	208
7.4 互感器和理想变压器在 SPICE 中的表示方法	209
7.4.1 互感器在 SPICE 中的表示方法	209
7.4.2 理想变压器在 SPICE 中的表示方法	209
7.5 用 SPICE 分析变压器电路举例	210
本章小结	213
习题	213
第 8 章 电动机	217
8.1 三相异步电动机	217
8.1.1 三相异步电动机的结构及转动原理	217
8.1.2 三相异步电动机的等效电路	223
8.1.3 三相异步电动机的电磁转矩和机械特性	225
8.1.4 三相异步电动机的铭牌数据及应用	229
8.2 单相异步电动机	235
8.2.1 单相异步电动机的结构和工作原理	235

8.2.2 单相异步电动机的启动	237
8.2.3 三相异步电动机的单相运行	238
8.3 直流电动机	239
8.3.1 直流电动机的主要结构	239
8.3.2 直流电动机的工作原理	240
8.3.3 机械特性	241
8.3.4 直流电动机的调速	243
8.3.5 直流电动机的使用	245
8.3.6 直流电动机的额定值	247
8.4 控制电动机	247
8.4.1 步进电动机	247
8.4.2 伺服电动机	250
本章小结	252
习题	252
第 9 章 继电器-接触器控制	254
9.1 常用低压电器	254
9.1.1 手动电器	254
9.1.2 自动控制电器	255
9.2 基本控制环节	259
9.2.1 直接启动停车控制	259
9.2.2 电动机正反转控制	261
9.2.3 行程开关和行程控制	262
9.2.4 时间继电器和延时控制	263
9.3 控制电路综合举例	265
本章小结	269
习题	270
第 10 章 可编程控制器	273
10.1 概述	273
10.1.1 可编程控制器的产生及发展	273
10.1.2 可编程控制器的组成与工作原理	274
10.1.3 西门子 S7-200 可编程控制器简介	280

10.2 S7-200 PLC 程序设计基础	281
10.2.1 可编程控制器的编程语言与程序结构	281
10.2.2 S7-200 PLC 存储器的数据类型与寻址方式	285
10.3 S7-200 PLC 的基本指令(SIMATIC 指令)	290
10.3.1 位逻辑指令	290
10.3.2 定时器指令	295
10.3.3 计数器指令	298
10.4 数字量小型 PLC 控制系统程序设计举例	299
10.4.1 PLC 控制系统设计的一般步骤	299
10.4.2 梯形图的经验设计方法	300
10.4.3 PLC 顺序功能图的设计方法简介	307
本章小结	307
习题	308
 附录 A AIM-SPICE 的使用方法	310
附录 B 混合电路仿真软件 SPICE OPUS 使用说明	321
附录 C Multisim V7 使用说明	326
附录 D STEP 7-Micro/WIN32 编程软件使用指南	337
附录 E 用电安全技术知识	352
附录 F 本书用到的 SPICE3F5 语句	357
附录 G 常用电工电子术语中英文对照表	365
 参考文献	377

Contents

Chapter 1	Fundamental Conceptions and Basic Methods of Circuit Analysis	1
1.1	Circuit Quantities and Polarities	2
1.1.1	Real Directions of Circuit Variables	2
1.1.2	Reference Directions	3
1.1.3	Electric Power	4
1.2	Circuit Elements	5
1.2.1	Passive Elements	5
1.2.2	Active Elements	8
1.3	Basic Laws in Circuit	14
1.3.1	Ohm's Law	14
1.3.2	Kirchhoff's Laws	15
1.4	Basic Methods of Circuit Analysis	17
1.4.1	Branch Current Method	18
1.4.2	Node Voltage Method	20
1.5	Circuit Theorems	23
1.5.1	Superposition Principle	23
1.5.2	Thevenin's Theorem and Norton's Theorem	25
1.6	Circuits Containing Dependent Sources	34
1.6.1	Concept of Dependent Sources	34
1.6.2	Dependent Sources and Their Symbols	34
1.6.3	Analysis Methods of Circuits Containing Dependent Sources	35
Summery		39
Problems		40

Chapter 2 SPICE Fundamentals	46
2.1 SPICE Introduction	46
2.2 SPICE Circuit File	48
2.2.1 How to Describe a Circuit in SPICE	48
2.2.2 Component Value in SPICE	49
2.2.3 Edit and Run Circuit Files	50
2.3 Element Statements	50
2.3.1 Resistors, Capacitors and Inductors	50
2.3.2 Sources	50
2.4 DC Analysis Statements	52
2.5 Output Statements	54
2.6 Sub-circuits	54
2.7 .model Statement , Diode and Switch	55
2.7.1 .model Statement	55
2.7.2 Switch Models	56
2.7.3 Diode Model	57
2.8 Examples	58
Summery	61
Problems	61
Chapter 3 Sinusoidal Steady-State Circuit Analysis	64
3.1 Introduction	64
3.2 Mathematical Description of a Sinusoidal Quantity	65
3.2.1 Three Factors of Sinusoidal Quantities	65
3.2.2 Addition-Subtraction Operations of Sinusoidal Quantities with a Same Frequency	68
3.2.3 Phasor	69
3.3 Simple Sinusoidal Circuits	72
3.3.1 Resistor Circuit	72
3.3.2 Inductor Circuit	74
3.3.3 Capacitor Circuit	76
3.4 RLC Series Circuit	79
3.4.1 The Relation of Voltage and Current and Impedance	79

3.4.2	Electric Power in <i>RLC</i> Series Circuit	81
3.5	Analysis Methods of Sinusoidal Circuit	83
3.5.1	Series and Parallel Impedances	83
3.5.2	Analysis Methods	86
3.5.3	Power Factor Correcting	89
3.6	Resonance and Frequency Response	92
3.6.1	Series Resonance and Parallel Resonance	92
3.6.2	Frequency Response	99
3.7	Sinusoidal Steady-State Circuit Simulation Using SPICE	106
3.7.1	Sinusoidal Source in SPICE	106
3.7.2	Resistor, Inductor, Capacitor in SPICE	107
3.7.3	.tran Statement	108
3.7.4	.ac Statement	109
Summery		113
Problems		113
Chapter 4	Three-Phase Circuit	119
4.1	Three-Phase Voltages	119
4.1.1	Generation of Three-Phase Electromotive Force	119
4.1.2	Connection of Three-Phase Voltages	120
4.2	Three-Phase Load	122
4.2.1	Wye-Connection Load	123
4.2.2	Delta-Connection Load	126
4.3	Three-Phase Power	127
4.3.1	Computational Method	127
4.3.2	Measurement of Three-Phase Power	128
4.4	Phase-Sequence	130
4.5	SPICE Example	131
Summery		133
Problems		133
Chapter 5	Nonsinusoidal Periodic Current Circuits	137
5.1	Introduction	137

5.2	The Fourier Series	138
5.3	Circuit Analysis of Nonsinusoidal Periodic Current Circuit	141
5.4	Effective Value and Averaging Power	143
5.4.1	Effective Value	143
5.4.2	Averaging Power	144
5.5	Pulse Source in SPICE and Fourier Analysis Statement (.Fourier)	145
5.5.1	Pulse Source Description in SPICE	145
5.5.2	Non-linear Dependent Sources	146
5.5.3	Fourier Analysis Statement (.Fourier)	146
5.6	SPICE Examples	147
	Summery	150
	Problems	150

Chapter 6 Transient Analysis 154

6.1	Introduction	154
6.2	Initial Conditions of Switched Circuits	155
6.2.1	Switching Theorems	155
6.2.2	Calculating the Initial Conditions	156
6.3	First Order Circuits	158
6.3.1	Classical Method	159
6.3.2	Three-Factor Method	162
6.3.3	Response Analysis of a First Order Circuit with Superposition Method	169
6.4	The Response of a RC Circuit to a Pulse Input	171
6.4.1	The Differential Circuit	171
6.4.2	The Integral Circuit	172
6.4.3	The Response of a RC Circuit to a Sequential Pulse Input	173
6.5	First Order Circuit Containing Several Storage Elements	175
6.5.1	First Order Circuit Containing Series and Parallel Storage Elements	175
6.5.2	Complex First-Order Circuit	175
6.5.3	Pulse Voltage Divider	178
6.6	Introduction to Second Order Circuits	181