
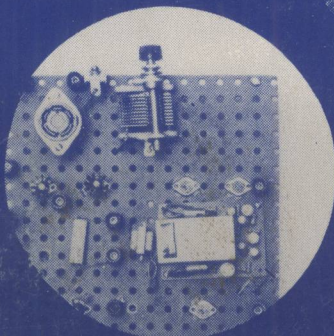
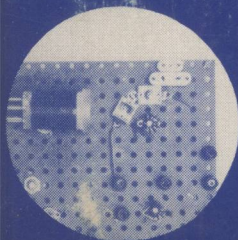
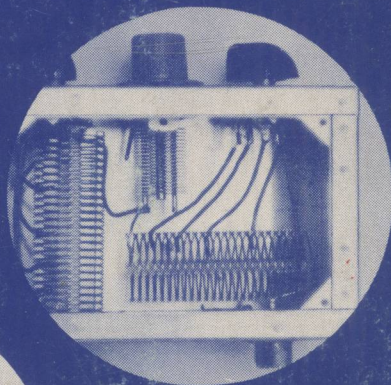
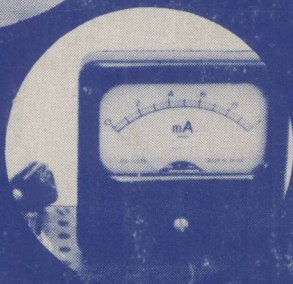
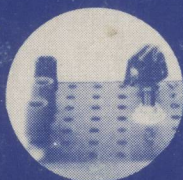


RADIO TRANSMITTER

PRINCIPLES and PROJECTS

by
**EDWARD
M. NOLL**

W3FQJ

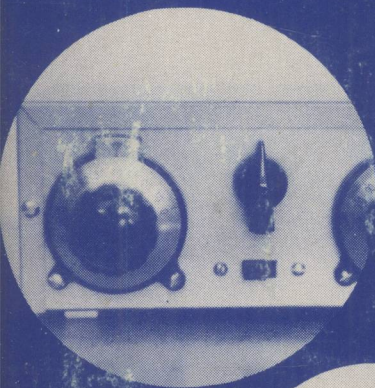

TN83
NI

7961236

Radio Transmitter

PRINCIPLES and PROJECTS

by Edward M. Noll, W3FQJ



E7961236



EDITORS and ENGINEERS

Division HOWARD W. SAMS & CO., INC.
INDIANAPOLIS, INDIANA 46268

FIRST EDITION

FIRST PRINTING—1973

Copyright © 1973 by Howard W. Sams & Co., Inc., Indianapolis, Indiana 46268. Printed in the United States of America.

All rights reserved. Reproduction or use, without express permission, of editorial or pictorial content, in any manner, is prohibited. No patent liability is assumed with respect to the use of the information contained herein. While every precaution has been taken in the preparation of this book, the publisher assumes no responsibility for errors or omissions. Neither is any liability assumed for damages resulting from the use of the information contained herein.

International Standard Book Number: 0-672-24031-9
Library of Congress Catalog Card Number: 73-78538



7961236



CONTENTS

CHAPTER 1

FET CW/A-M TRANSMITTER CIRCUITS	7
Field-Effect Transistor—RF Amplifier—Project 1: Output Indicator—Project 2: FET Crystal Oscillators—Project 3: One-Watt, Two-stage Multiband FET Transmitter—Project 4: Line Tuner and SWR Meter—Project 5: Multistage, Multiband Transmitter—Principles of Amplitude Modulation—Project 6: Solid-State A-M Modulator	

CHAPTER 2

BIPOLAR CW AND A-M TRANSMITTER CIRCUITS	37
Bipolar Transistor—Bipolar Class-B and Class-C Amplifiers—Project 7: Bipolar Crystal Oscillators—Project 8: Bipolar Two-Stage Transmitter—Project 9: Variable-Frequency Oscillator and Amplifier—Project 10: FET-Bipolar Hybrid Transmitter—Project 11: Bipolar Modulator—Project 12: Amplifier for TEN-TEC TX1 Transmitter	

CHAPTER 3

VACUUM-TUBE CW/A-M TRANSMITTER CIRCUITS	71
The Vacuum Tube—Class-C Amplifier Operation—Project 13: Vacuum-Tube Crystal Oscillator—Project 14: Vacuum-Tube Class-C Amplifier—Principles of Amplitude Modulation—Project 15: Vacuum-Tube Modulator	

CHAPTER 4

TRANSISTOR/TUBE TRANSMITTER CIRCUITS	107
Project 16: IC VFO—Project 17: 160-Meter IC and Vacuum-Tube Transmitter—Project 18: Universal Modulator—Project 19: Vacuum-Tube Crystal Oscillator and Untuned RF	

PREFACE

The explanations of principles and projects in this book are intended for both students and professional technicians. Each chapter begins with basic principles and advances to more detailed information. The projects are based on the basic principles and are designed to further the reader's understanding through actual experience.

The first three chapters contain information on electron devices—the FET, bipolar transistor, and the vacuum tube. Various modes of modulation—cw, a-m, f-m, dsb, and ssb—are discussed in other sections. Chapter 4 describes hybrid transmitter circuits using tubes and transistors. Double-sideband and single-sideband generation and circuits are included in Chapter 5. There is a chapter on linear amplifiers and mixers; another explains integrated circuits. The final three chapters detail vhf circuits, frequency modulation, and transmitter testing.

The radio transmitter projects are all low-power circuits that can serve as laboratory experiments in schools. The radio amateur will gain practical experience with all types of circuits and systems. It is hoped that the radio technician will find this book to be a helpful guide to modern transmitter principles, ideas, circuits, and techniques.

EDWARD M. NOLL, W3FQJ

Amplifier—Project 20: 10-15-20 FET VFO—Project 21:
10-160 Vacuum-Tube RF Amplifier

CHAPTER 5

BASIC PRINCIPLES OF SSB-DSB GENERATION127

Vector Relations—Power Relationships—Carrier Suppression
—Transistor and Tube Balanced Modulators—Beam-Deflec-
tion Modulator—Sideband Removal—Phasing Method—Proj-
ect 22: 40-80-160 DSB Generator—Project 23: Single-Side-
band Generator—Project 24: Utility Linear Amplifier and
Mixer—Project 25: Dual-FET Balanced Modulator

CHAPTER 6

BASIC PRINCIPLES OF LINEAR MIXERS AND AMPLIFIERS165

Linear Mixers—Linear Amplifiers—FET Linear Power Am-
plifier—Bipolar Linear Amplifiers—Project 26: Linear Am-
plifiers—Project 27: Linear Mixer and Heterodyne Oscillator
—Project 28: FET Linear Amplifier and Utility Oscillator-
Amplifier

CHAPTER 7

INTEGRATED CIRCUIT FUNDAMENTALS191

Basic Differential Amplifier—Stability—Constant-Current
Source—Darlington Configuration—A Basic IC—100-Milli-
watt IC RF Generator—Modulators and Demodulators—IC
RF Dividers—Simple Radio-Frequency Divider—Project 29:
IC DSB-SSB Generator—Project 30: 160-Meter Phasing SSB
Generator

CHAPTER 8

VHF/UHF TRANSMITTER CIRCUITS PRINCIPLES221

Basic Transmitter Plans—Modulation Methods—Typical Cir-
cuits—Project 31: Six-Meter Vacuum-Tube Transmitter—
Project 32: Two-Meter Transmitter—Project 33: Utility VHF
Amplifier—Project 34: FET Six-Meter QRPP Transmitter

CHAPTER 9

FREQUENCY MODULATION: GENERAL PRINCIPLES249

Direct and Indirect Frequency Modulation—Composition of F-M Wave—Typical Circuits—Voltage-Variable Capacitor—Project 37: VFO F-M Exciter and Utility Modulator—Project 38: FET F-M Exciter

CHAPTER 10

TEST EQUIPMENT AND PROCEDURES277

Frequency Meter—Tuning Indicators—Dip Oscillator—Power Output and Antenna Meters—Modulation Meters—Project 38: Digital Frequency Calibrator—Project 39: Digital IC HF/VHF Oscillator/Calibrator—Project 40: Direct-Conversion Test Receiver

APPENDIX314

INDEX315

CHAPTER 1

FET CW/A-M Transmitter Circuits

“Radio Transmitter Principles and Projects” has been written for the beginner, the oldtimer, and the experienced technician. Its approach can be summed up as “learn-and-do.” Principles are detailed and followed by construction projects that firm your knowledge of transmitter circuit operation. In the early fundamental chapters the projects are of step-by-step detail and include a series of suggested experimental procedures to follow which teach the underlying principles. The coverage provides an excellent introduction to solid-state and combined solid-state, vacuum-tube technology.

In the first three chapters the basic electron devices (FET, bipolar transistor, and vacuum tube) are covered. First you learn the principle of the device and then the fundamentals of the radio-frequency circuit with which the device can be associated. Then you will learn how the device can be amplitude-modulated. All sorts of devices in addition to the basic three are covered such as diode, voltage-variable capacitor diode, linear integrated circuits, digital integrated circuits, etc. Oscillators and all classes of amplifier operation A, AB, B, and C are covered. The transmitters include all modes of modulation, cw, a-m, dsb, ssb, and f-m.

The projects include small test units on up to complete transmitters that serve well as laboratory experiments or as actual parts

of an amateur radio station. Power levels range from QRPP to QRP (very low power to low power) and on up to a maximum of about 50 watts.

In the early fundamental chapters the projects are in the form of experiments that follow along with the text. Even though you do not perform the experiments, read right along with the copy, because the experiments are an inherent part of the chapter continuity. Performing the experiments, however, gives you that extra and very valuable practical experience with new devices and circuits.

FIELD-EFFECT TRANSISTOR

A field-effect transistor (FET) is a three-element device consisting of source, gate, and drain (Fig. 1-1). The source and drain elements


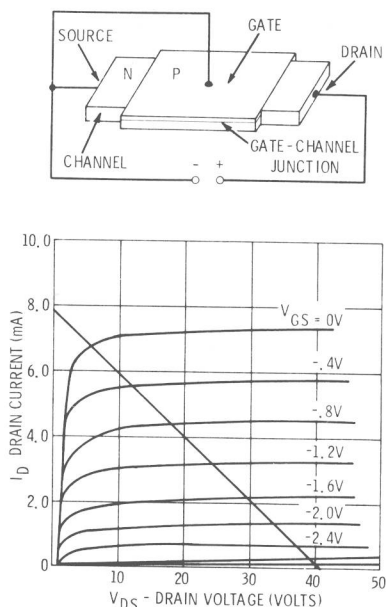


Fig. 1-1. Drawing of basic field-effect transistor.

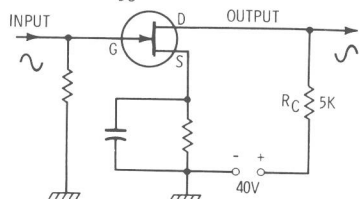

are positioned at the ends of a continuous semiconductor channel. The charge motion along the channel from source to drain depends on the conductivity of that channel. Conductivity is regulated by a third element, the gate, which surrounds all or part of the channel. A single semiconductor junction is present at the boundary between the gate and the channel. Normally this junction is reverse-biased just as the grid of a vacuum tube is biased negatively.

The gate actually has a capacitive influence on the channel. This capacitive effect is such that a charge depletion area extends into the channel. The amount of reverse biasing of the gate determines the extent of the depletion activity and therefore the conductivity of the channel. In turn, the conductivity of the channel determines the charge motion (current) between source and drain.

As the gate reverse bias is increased, the depletion area increases and lowers the conductance of the channel, thus increasing the channel resistance or decreasing the channel conductance. As a result the channel and output drain currents decrease. If the reverse-bias voltage is made to vary, there results a substantial change in the drain current. This substantial drain-current variation in the common-source circuit of Fig. 1-1 produces a substantial voltage variation across the output. Since the drain-voltage variation is greater than gate-voltage variation, the common-source stage has voltage gain.

A typical family of curves is also shown in Fig. 1-1, along with a load line. Note how similar the set of curves is to those of a pentode

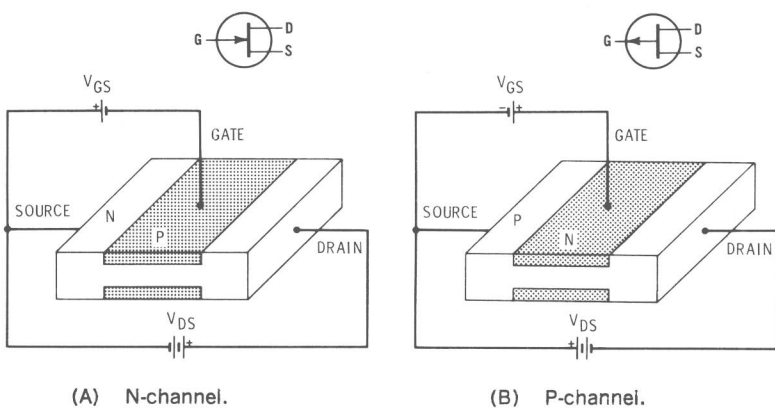


Fig. 1-2. N- and P-channel FETs.

vacuum tube. The lower the gate bias is, the greater is the drain current. Also over a substantial voltage range the drain current remains essentially constant for a given gate bias as the drain voltage is increased. This is characteristic of a high-resistance device. In fact, the input and output resistances of a field-effect transistor are high like those of a vacuum tube and are unlike the low resistances at the input and output of a conventional bipolar transistor. The field-effect transistor in simple circuits is less prone to distortion and the generation of spurious signal components, compared to a bipolar transistor.

There are two fundamental types of junction field-effect transistors, those with a p-channel and those with an n-channel (Fig. 1-2). An n-channel has a charge motion determined by free electrons. The gate which surrounds an n-channel is a p-type semiconductor material with its electric charge motion determined by free positive charges, or holes. The second type uses a p-type channel and an n-type gate. The only difference is the polarity of the biasing. Note that the drain of an n-channel type is positive with a negative voltage required at the gate to establish reverse-biasing of the junction. Oppositely the p-channel type operates with a negative drain voltage. In this case a positive bias is applied to the gate to reverse-bias the junction.

RF AMPLIFIER

A typical FET class-B or class-C rf amplifier is shown in Fig. 1-3. External bias can be used. Biasing according to class of operation is shown in the transfer characteristic. For class-A operation the biasing is at the center of the linear portion of the transfer curve. To operate the amplifier class B it is necessary that the level of external bias match the cutoff bias of the transistor. A class-C stage is, of course, biased beyond cutoff.

The input impedance of a FET rf amplifier can be kept at its highest by making certain that the peak of the positive alternation of the input signal does not extend to the near-zero bias level that results in gate current. However, for more convenient and efficient operation and a somewhat lower input impedance, the stage may be operated in such a manner that the gate current is drawn at the peak of the positive alternation. In such an arrangement one can use gate current to establish the required class-B or class-C biasing

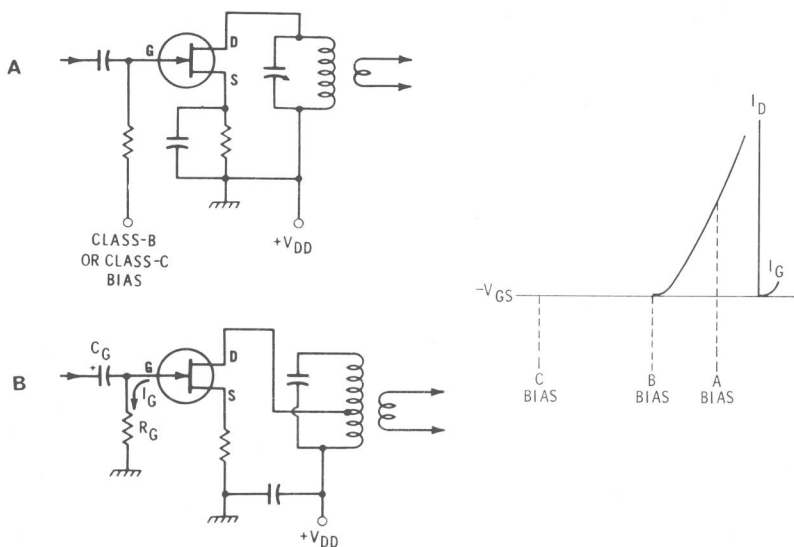


Fig. 1-3. FET class-B and class-C amplifiers.

using the circuit arrangement of Fig. 1-3B. The direction of the gate current is such that a negative bias is developed on the gate capacitor. With a proper time constant this capacitor charge remains constant and serves as the dc gate bias for the stage. As mentioned, the input impedance is now lower, and somewhat more input power is required.

The field-effect class-C amplifier is similar to a vacuum-tube stage in still another way. When the rf excitation is removed from its input, the drain current rises just as the plate current of a similarly designed vacuum-tube stage. It is advisable to use a protective source resistor which limits the drain current to a safe value in case rf excitation is lost. In vacuum-tube practice one often uses a cathode resistor as a safety device.

Approximate class-C waveforms are shown in Fig. 1-4. During the portion of the input wave that causes drain current there is a strong but short-duration burst of drain current. This burst of current contributes power to the output resonant circuit. In fact, at this time the tank capacitor is charged to a negative peak and the drain voltage is at minimum value.

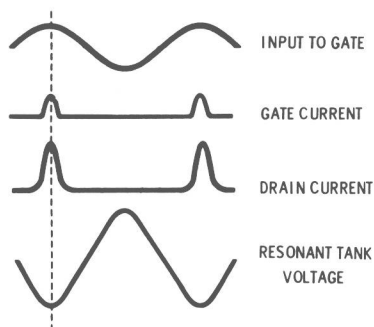


Fig. 1-4. FET class-C waveforms.

It is important to recognize that with a strong input signal the peak drain current rises from zero to a high peak value. Consequently there can be a substantial change in drain voltage and the power delivered to the drain resonant circuit is much greater than the signal power level delivered to the gate of the transistor. The energy delivered to the tank circuit is stretched out because of the energy-storage capability. As a result a sinusoidal rf voltage is developed across the tuned circuit.

The gate current is present only for a very short interval of time that coincides with the positive peak of the input voltage. Just enough gate current is drawn to charge the bias capacitor.

PROJECT 1: OUTPUT INDICATOR

Before starting construction of your first transmitter circuits, you should build a small piece of test equipment that is helpful in working with solid-state rf amplifiers. This output indicator is shown schematically in Fig. 1-5. It is nothing more than a simple diode detector circuit which develops a dc output voltage that corresponds to the amplitude of an rf signal. Useful readings are obtained for rf power levels considerably lower than 100 mW. A potentiometer is included, and permits the measurement of higher power levels. When measuring across a low-impedance source, connect the signal to be evaluated between inputs 1 and 3. In fact, the indicator can be left connected across the transmitter output to a low-impedance antenna when the transmitter is in operation and feeding power to the antenna.

If the transmitter is to be terminated in a specific impedance, that value can be connected between terminals 1 and 3. For example,

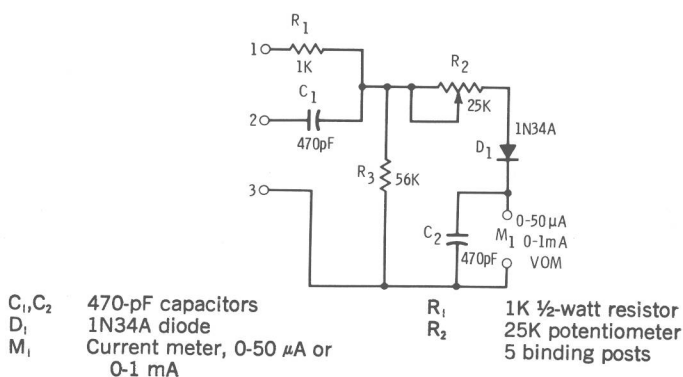


Fig. 1-5. Rf indicator.

if the transmitter is to supply power to a 50-ohm load, one can connect such a 50-ohm resistive termination (of proper power-handling capability) across terminals 1 and 3 and the transmitter will see a proper matched load.

If the signal is to be evaluated at a high-impedance point, use terminals 2 and 3. The presence of the capacitor also permits ob-

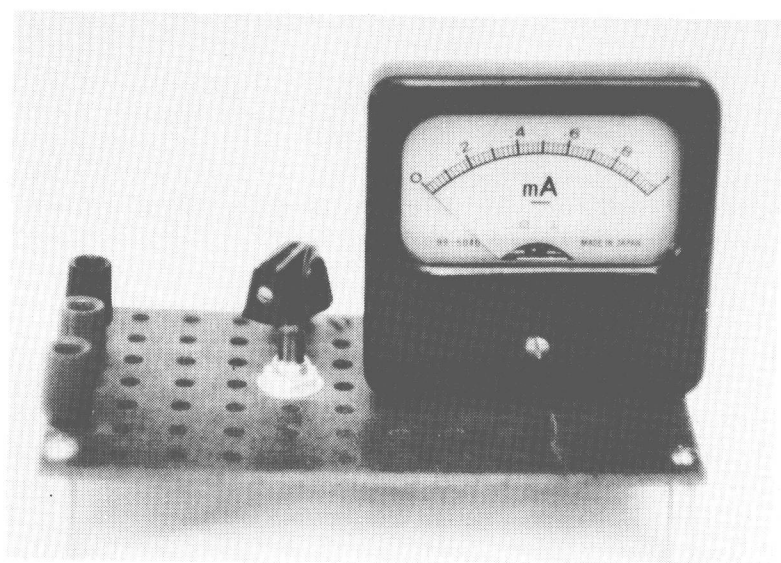


Fig. 1-6. Rf indicator with 0-1 mA meter.

servation where there is a dc as well as an rf component. The capacitor blocks the dc voltage from the detector circuit.

The indicator can be 0 to 1 milliammeter or one with an even higher sensitivity. A volt-ohm-milliammeter (vom) can also be used and provides some additional versatility because of a choice of current scales. The unit can be mounted on a small 3" \times 6" masonite pegboard. The five binding posts provide convenience in use. Such an arrangement with a mounted milliammeter is shown in Fig. 1-6.

PROJECT 2: FET CRYSTAL OSCILLATORS

Most projects of this chapter will be built on the single pegboard arrangement shown in Fig. 1-7. First mount four transistor sockets


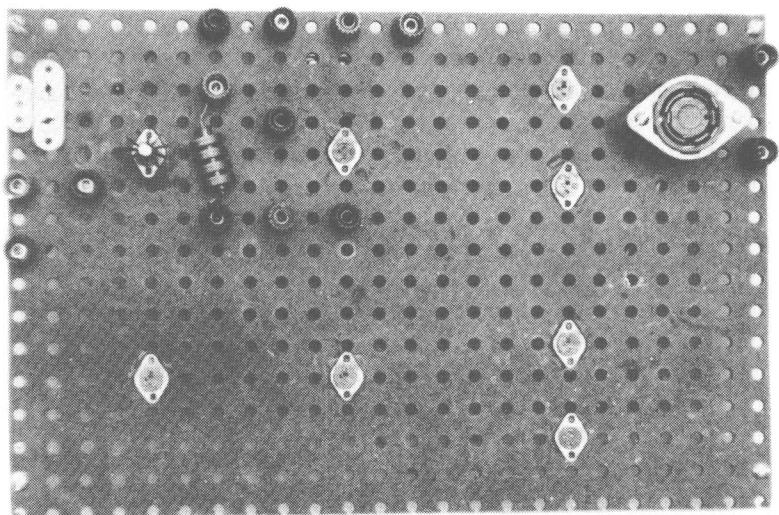


Fig. 1-7. Basic arrangement of pegboard for oscillator circuits.

as per the top half of arrangement. Experiments on crystal oscillator circuits will be made in the area at the top left. A FET and its heat sink are shown along with two crystal sockets to accommodate the two common size crystal plugs. Various binding posts have been mounted in positions that permit ease in making circuit changes. A five-prong tube socket has been mounted at the top right. In later projects, plug-in coils will be used in the tube socket.

20-40-80-160 Pierce Oscillator

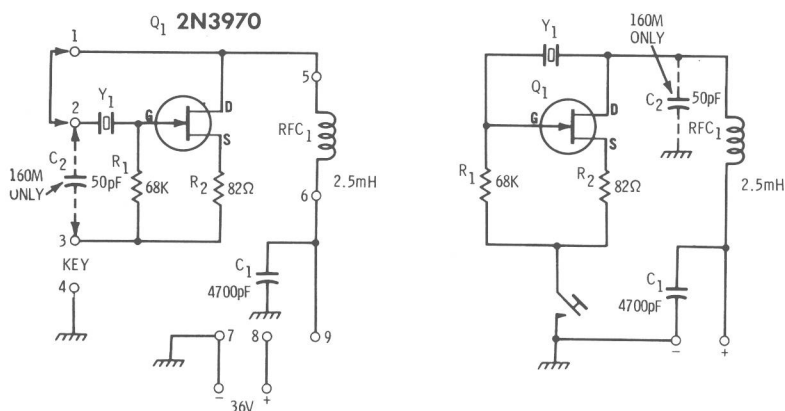Assemble the circuit of Fig. 1-8. Note that nine binding posts are used. A Pierce crystal oscillator circuit is formed by connecting a



C_1 4700-pF disc capacitor
 C_2 220-pF disc capacitor
 Q_1, Q_2 2N3970 transistors
 R_1 68K $\frac{1}{2}$ -watt resistor
 R_2 82-ohm $\frac{1}{2}$ -watt resistor

RFC 2.5-mH rf choke
 Miscellaneous Parts
 Pegboard
 Transistor sockets
 Binding posts

Fig. 1-8. Pierce crystal oscillators.

jumper between binding posts 1 and 2 and a 2.5-mH radio-frequency choke between posts 5 and 6.

Drain current can be measured by inserting a 0-100 milliammeter between terminals 8 and 9. When measurements are not being made a jumper can be inserted between binding posts 8 and 9.

The output of the crystal oscillator can be evaluated with the output indicator. Connect binding post 5 to binding post 2 of the indicator and binding post 3 of the indicator to one of the common (ground) binding posts of the oscillator (Fig. 1-9).

Operation—Wire the oscillator carefully to set up the circuit of Fig. 1-8B. Plug in a 40- or 80-meter crystal. Close the key or connect a jumper between posts 3 and 4 to turn on the oscillator. Note the drain current and the output indicator reading on 40 and 80 meters. Tune in the signal on your receiver.

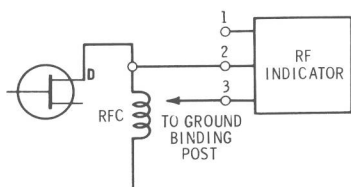


Fig. 1-9. Connection of the output indicator.

Insert a 160-meter crystal. The oscillator may be sluggish in starting on this frequency. A greater capacitive load on the drain output circuit will overcome the problem. Connect approximately a 50-pF capacitor from drain to common whenever operating on 160. One way of doing this is to connect the capacitor to binding post 3 or 4 from either binding post 1 or 2. It can be removed when operating on other bands.

Try a 20-meter crystal in the oscillator. Output reading will be about the same on all bands. Typical output readings fall between 0.35 and 0.5 (maximum sensitivity) milliamperes. Drain current falls to between 25 and 30 milliamperes and somewhat higher on 160 meters.

Drive Reading—Connect the gate circuit of what will be the second stage of the transmitter. This circuit consists of capacitor C_2 and resistors R_3 , R_4 , and R_5 (Fig. 1-10). The rf drive into this

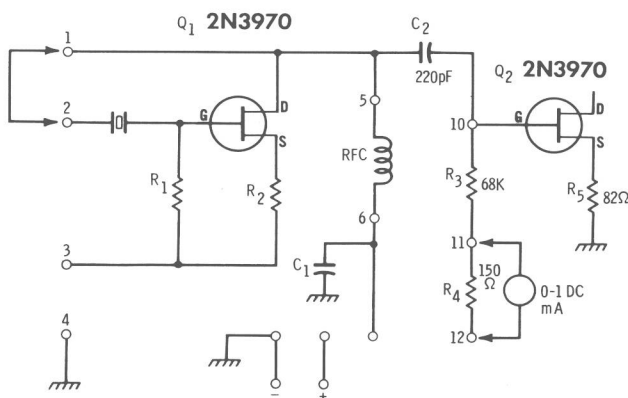


Fig. 1-10. Measurement of drive to next stage using gate current.

stage will cause a flow of gate-circuit charges (gate current). This is a rectified component and a dc meter connected across resistor R_4 will give a relative indication of the rf drive. The dc is of course a