

LINEAR INTEGRATED CIRCUITS PRACTICE AND APPLICATIONS

Sol D. PRENSKY ARTHUR H. SEIDMAN

TN431.1
PI

8264472

Linear Integrated Circuits

Practice and Applications



Sol D. Prensky

Associate Professor Emeritus
Fairleigh Dickinson University

Arthur H. Seidman

Professor of Electrical Engineering
Pratt Institute



E8264472



Reston Publishing Company, Inc., Reston, Virginia
A Prentice-Hall Company

842

Library of Congress Cataloging in Publication Data

Prensky, Sol D.

Linear integrated circuits.

Edition of the 1974 by S. D. Prensky published
under title: Manual of linear integrated circuits.

Includes index.

1. Linear integrated circuits. I. Seidman,
Arthur H., joint author. II. Title.
TK7874.P73 1981 621.381'73 80-26652
ISBN 0-8359-4084-5

© 1981 by

Reston Publishing Company, Inc.

A Prentice-Hall Company

Reston, Virginia

All rights reserved. No part of this book
may be reproduced in any way, or by any means,
without permission in writing from the publisher.

10 9 8 7 6 5 4 3 2 1

Printed in the United States of America

Linear Integrated Circuits

Practice and Applications

8264472

*In memory of Sol D. Prensky
teacher, writer—a warm and generous human being*

Preface

In considering the sustained progress of the field of integrated circuits, we find important major advances that have been made over a relatively short period. Most outstanding has been the dramatic development of the microprocessor (μP) in the digital IC field, accompanied by supplemental progress in the linear IC group. This significant progress has been sparked by important advances in large-scale-integration (LSI) technology in achieving considerably greater density of active devices on the IC chip, including both the bipolar and the MOS field-effect types of transistors, and also the new combination of both devices (called a BiMOS or BiFET chip). Combined with these improved fabrication techniques, we find clever circuit designs within the denser IC chip that offers a choice of various monolithic microprocessor units, which merit the proud description of "computer-on-a-chip."

This active development of microprocessors and their attendant memory circuits in the digital division has fostered a corresponding upsurge of advanced devices in the linear IC field. Exploiting the broad flexibility of the microprocessor, we find innovative designs that include linear ICs diverse areas, ranging from the automotive field for engine controls to the electronic-instruments field for various automatic testing functions. In these new functions, many advanced forms of linear ICs are employed to handle the analog signals that feed the digital processing.

Other linear IC developments, such as in the consumer-communication areas, all emphasize the continuing trend for replacing discrete circuits (with

their multiplicity of individual transistors and their numerous interconnections) with the more compact and reliable ICs. In the broad view, it is fair to say that the process of supplanting discrete transistor circuits by the emergent ICs is now as much a revolutionary development as was the previous upheaval that supplanted vacuum tubes with transistors.

For the linear IC field, advanced developments include newer versions of OP AMPS (including the previously mentioned BiFET types), increased utilization of the phase-locked-loops (PLL) units in the communications area, and a proliferation of devices interfacing with the newer digital developments. To cite some additional examples, we find more versatile A/D and D/A converters, more multipliers for signal conditioning and a greater variety of peripheral drivers for various interface and display purposes.

This work is an updating and expansion of Prensky's well-received *Manual of Linear Integrated Circuits: Operational Amplifiers and Analog ICs* published by Reston Publishing Company in 1974. Its aim is to provide the technician and engineer with practical information on the selection of linear ICs for use in a large variety of applications which include dc and audio amplifiers, waveform generation, D/A and A/D conversion, active filters, voltage regulators, and communication systems.

In keeping with the original theme of representing well-accepted linear IC models from all the major manufacturers, considerable care has been taken in presenting the extensive cross-reference list in Appendix III. This listing of around 400 frequently used model numbers is an important practical feature; it allows the user, often confronted with a clutter of type numbers, to rapidly identify a particular manufacturer's designation, and also to characterize it in relation to its general class (often as a second source of a better-known type).

This same feature of including types from all the major manufacturers has been carried out in the presentation of the selection guide for OP AMPS (Appendix II). Further, as a source for obtaining greater details on particular models that are available from the comprehensive data sheets supplied by the manufacturers, a current list of their addresses is given in Appendix IV.

The maturing growth of the semiconductor industry strengthens the trend toward "standardized" types, both for OP AMPS and for the other forms of linear ICs; to this desirable end, the manual serves as a practical tool to highlight such specific types, by illustrating selected applications of these versatile devices.

The authors are grateful to the many manufacturers who supplied us with material. Any errors, however, that may appear in the text are our responsibility.

SOL D. PRENSKY
ARTHUR H. SEIDMAN

Contents

Preface *xiii*

Chapter	1	Introduction to Linear Integrated Circuits	1
	1-1	General Significance of Linear Integrated Circuits	1
	1-2	Development of Linear Integrated Circuits	2
	1-3	Using a Simple Linear Integrated Circuit	3
	1-4	Types of Linear-Integrated-Circuit Functions	5
	1-5	Types of Linear Integrated Circuits	7
	1-6	Medium-Scale and Large-Scale Integration	7
	1-7	Standardization Tendencies for Linear Integrated Circuits	8
	1-8	Making a Practical Choice of an Industry-Standard OP-AMP Type	9
	1-9	Sequence of Presentation	9
	1-10	Linear Subsystems	9
Chapter	2	General Conditions Governing Linear Integrated Circuit Design	11
	2-1	Monolithic versus Discrete Components	11
	2-2	Monolithic <i>NPN</i> Transistors	12
	2-3	Monolithic Diodes	14
	2-4	Monolithic <i>PNP</i> Transistors	15

2-5	Monolithic Resistors	16
2-6	Monolithic Capacitors	17
2-7	Monolithic Components with No Discrete Counterparts	18
2-8	Basic Techniques in the Design of Linear Integrated Circuits	19
2-9	Monolithic versus Hybrid Integrated-Circuit Designs	20
2-10	Linear-Integrated-Circuit Arrays	20
2-11	Transistor Arrays	21
2-12	Monolithic Techniques with Transistor Arrays	25
2-13	Precautions in Applying Transistor Arrays	28
2-14	Multiple-Function Linear Integrated Circuits	29
2-15	Combining Transistor Families on a Single Chip	30
2-16	Amplifier Arrays	30
2-17	Advanced Forms of the Monolithic Chip	34
	<i>Questions</i>	34

Chapter 3 **Differential Amplifier Stage in Integrated-Circuit Design** 37

3-1	General Elements in Integrated-Circuit Design	37
3-2	Choice of Differential Amplifier for Integrated-Circuit Input Stage	39
3-3	Circuit Action of Differential-Amplifier Stage	40
3-4	Constant-Current Circuit	46
3-5	Practical Circuit for Single-Ended Stage	47
3-6	Common-Mode Rejection Ratio	49
3-7	Input-Stage Variations in Practical Integrated Circuits	50
	<i>Questions</i>	51
	<i>Problems</i>	52

Chapter 4 **Operational Amplifier Characteristics** 55

4-1	Basic Requirements for the Operational Amplifier	55
4-2	Analysis and Practical Example of Operational-Amplifier Action	56
4-3	Flexible Use of Operational-Amplifier Circuits	60
4-4	Data Sheet: Type 741 OP-AMP Characteristics	61
4-5	Major Operational-Amplifier Characteristics	66
4-6	Comparison Chart of Typical Values of OP-AMP Characteristics	67
4-7	Interpreting Operational-Amplifier Data Sheets	70
4-8	Approximate Values of Typical OP-AMP Specifications	71
	<i>Questions</i>	74
	<i>Problems</i>	75

Chapter 5 **General Operational Amplifier Applications** 77

5-1	Kinds of Operational Amplifier Applications	77
5-2	Choice of Operational Amplifier in Typical Applications	78

5-3	Basic Circuit Configurations	78
5-4	Inverting Voltage Amplifier	78
5-5	Noninverting Voltage Amplifier	80
5-6	Voltage Follower (Unity-Gain Amplifier)	82
5-7	Summing Amplifier	83
5-8	Integrating Amplifier	84
5-9	Differentiating Amplifier	86
5-10	Square-Wave Generator (Multivibrator)	88
5-11	Sine-Wave Oscillators	90
5-12	Linear Rectifiers	93
5-13	Peak Detector	95
5-14	Current-to-Voltage Converter	96
5-15	Differential (Instrumentation-Type) Amplifier	97
5-16	Current-Difference (Norton) OP AMP: Single-Supply Operation	101
5-17	Additional OP-AMP and LIC Circuits (BiFET and BiMOS)	104
	<i>Questions</i>	107
	<i>Problems</i>	108

Chapter 6 Testing and Breadboarding Operational Amplifiers 111

6-1	Levels of Testing Linear Integrated Circuits	111
6-2	Basic Laboratory Tests	111
6-3	Voltage Gain (Tests for Open-Loop, Closed-Loop, and Loop Gain)	112
6-4	Input-Resistance Tests	116
6-5	Bandwidth (Estimating and Testing)	119
6-6	Output-Resistance (R_o) Test	121
6-7	Common-Mode Rejection Tests	122
6-8	Input-Offset Error (I_B , I_{io} , and V_{io}) Tests	124
6-9	Improved-Specification Types of OP AMPS	125
6-10	Curve-Tracer Method of Testing Amplifiers	126
6-11	Breadboarding the Integrated-Circuit Package	129
6-12	Automated Linear-Integrated-Circuit Testing	132
6-13	Engineering Evaluation (Semiautomatic) Testing	133
6-14	Quick-Check Test Method for OP AMPS	135
	<i>Questions</i>	137
	<i>Problems</i>	138

Chapter 7 Power Amplifiers: Direct Current and Audio 141

7-1	Power Limitations in Integrated-Circuit Operational Amplifiers	141
7-2	High Output-Current Operational Amplifiers	142
7-3	Power Boosters	142
7-4	Power Operational Amplifier	143

7-5	Audio Power Amplifiers (to 1 or 2 Watts)	146
7-6	Higher-Power Integrated-Circuit Audio Amplifiers	148
	<i>Questions</i>	155
	<i>Problems</i>	156
Chapter 8	Consumer Communication Circuits	157
8-1	Impact of Linear Integrated Circuits on Communication Equipment	157
8-2	Broadcast FM Receiver Circuits	161
8-3	FM-IF Strips	163
8-4	FM Stereo Multiplex Decoders	168
8-5	Broadcast AM Receiver Circuits	171
8-6	Television Applications	176
8-7	Mixers, Modulators, and Multipliers	182
8-8	Phase-Locked Loop	186
	<i>Questions</i>	192
	<i>Problems</i>	192
Chapter 9	Regulators and Control Circuits	193
9-1	Power Control with Monolithic Circuits	193
9-2	Voltage Regulators	194
9-3	Series versus Shunt Regulators	196
9-4	Current Limiting	197
9-5	Representative Example of a Voltage Regulator	197
9-6	Applications of the 723-Type Regulator	200
9-7	Other Regulator Types	207
9-8	Zero-Voltage Switches	214
	<i>Questions</i>	217
	<i>Problems</i>	219
Chapter 10	Digital-Interface Circuits	221
10-1	Differential Voltage Comparators	221
10-2	Operation of Comparator	222
10-3	Comparator Characteristics	223
10-4	Advanced-Performance Comparators	225
10-5	Sense Amplifiers	227
10-6	Analog-to-Digital and Digital-to-Analog Converters	229
10-7	Borderline Linear-Digital Integrated Circuits	236
10-8	Complementary MOS (CMOS) Types	237
	<i>Questions</i>	237
	<i>Problems</i>	238
Chapter 11	Precision and Instrumentation Operational Amplifiers	239
11-1	Major High-Performance Characteristics	239
11-2	Development of Precision Operational Amplifiers	240

- 11-3 Selecting Operational Amplifiers for High-Performance Characteristics 241
- 11-4 Low-Bias-Current (I_B)-High-Input Impedance (Z_{in}) Types 245
- 11-5 Low Voltage-Drift Types 245
- 11-6 Additional High-Performance Features 247
- 11-7 Wide-Band (High-Slew-Rate) Types 247
- 11-8 Micropower Types 251
- 11-9 Instrumentation Amplifier 252
- 11-10 Representative Instrumentation Amplifier (Monolithic) 261
- 11-11 Modular Form of Instrumentation Amplifier 264
 - Questions* 268
 - Problems* 269

Chapter 12 Specialized Linear-Integrated-Circuit Applications 271

- 12-1 Expansion of Linear-Integrated-Circuit Functions 271
- 12-2 Programmable Amplifiers 272
- 12-3 Operational Amplifier as a Regulated Voltage Source 272
- 12-4 Current-Source Application 274
- 12-5 Active Filter Applications 275
- 12-6 Gyrators and Q -Factor in Active Filters 285
- 12-7 Logarithmic Amplifier 289
- 12-8 Low-Noise and High-Impedance (Electrometer) Applications 294
- 12-9 Sample-and-Hold Applications 297
- 12-10 Multiple (Triple and Quad) Operational Amplifiers 299
- 12-11 Voltage-Controlled Oscillator (VCO) and Waveform Generators 305
- 12-12 The 555 Timer 312
- 12-13 Multipliers, Dividers, Squarers, Square Rooters 315
- 12-14 Digital-Voltmeter System 321
- 12-15 Sources for Specific Technical Information 324
 - Questions* 325
 - Problems* 325
 - Bibliography* 327

Appendix I Decibel Conversion Chart 329

Appendix II Classification of LIC Groups and Selection Guide for OP AMPS 331

Appendix III Cross-Reference List of LICs and Key to Identification of Manufacturers' Types 333

Appendix IV Manufacturers' Addresses 343

Appendix V Answers to Selected Questions and Problems 345

Index 349

Chapter 1

Introduction to Linear Integrated Circuits

1-1 GENERAL SIGNIFICANCE OF LINEAR INTEGRATED CIRCUITS

The category of *linear integrated circuits* (LICs) can be distinguished, in a broad sense, from the category of digital integrated circuits (DICs); thus the numerous and diverse types of integrated circuits can be classified into these two large groups. Both forms of ICs (also known as *microcircuits*) have proved immensely popular, and they are rapidly supplanting circuits using discrete transistors. This stems from the greater convenience and increased reliability offered by these small devices.

The linear IC group encompasses circuits of the *analog type*, where the input, in general, is in the form of a smoothly varying signal and the output usually is an amplified version of the input signal. This is in contrast to the zero-one switching action of the digital IC. The *operational* amplifier (OP AMP) is an outstanding and popular example of the analog group, which, in addition, includes other nondigital types (even though the operation may be nonlinear). Thus the LIC group includes regulators and other forms of signal conditioners that are designated “linear” or analog, as opposed to the digital types. The DIC, on the other hand, depends essentially on its switching function, and this group encompasses a large number of devices, such as gates, flip-flops, memories, and microprocessors.

As might be expected, with the wide diversity of ICs there are some

devices that possess characteristics of both groups, as in the case of *interface circuits*. Examples of interface circuits include the analog-to-digital (A/D) converter and its counterpart, the digital-to-analog (D/A) converter. In addition, important use is made of these “in-between” types in providing a great variety of control circuits using the highly versatile microprocessor, where analog sensing elements are conditioned to work with the digital processing of microcomputers. These special types are generally classified as belonging to the linear group. Nevertheless, there need be no confusion about these classifications, as long as we do not interpret the designation of linear in too literal a fashion.

Thus the linear group may include devices that exhibit nonlinear transfer characteristics but that still are of an analog nature (such as the logarithmic amplifier). Keeping in mind the broad interpretation of these classifications, this text concentrates on the entire linear group as opposed to the other major (and very large) group of digital ICs.

1-2 DEVELOPMENT OF LINEAR INTEGRATED CIRCUITS

The linear group of ICs attained its importance and prominence when it eventually became possible to provide, at a reasonably low cost, amplifiers of the *operational-amplifier type*. The development can be traced from the time (approximately 1964) when pairs of transistors, forming *integrated differential amplifiers*, were first fabricated on a single silicon chip. This step represented a significant advance over the use of discrete transistors in the basic circuit; it demonstrated the ability of the IC to greatly reduce the troublesome temperature dependence of discrete transistors, even when the separate transistors were laboriously matched (as discussed later). Since both transistors of the differential pair could be fabricated simultaneously on the same IC chip, it was possible, by this step alone, to make an improvement by whole orders of magnitude in alleviating the temperature-drift problem—from millivolts for the discrete transistor to just microvolts per degree Celsius for the integrated pair.

About a year later, another enormous step forward was taken with the introduction of the *integrated general-purpose operational amplifier*. This IC was able to take good advantage of the integrated differential-amplifier stage for the first stage of a multistage amplifier and was capable of open-loop gains well beyond 10,000—all in a very compact package. By the use of an external feedback resistor, the IC operational amplifier (of the 709¹ type, for example) became a low-cost and highly versatile amplifier that incorporated 9 transistors and 12 associated resistors in a conveniently small package. This relatively simple operational amplifier could easily perform many of the functions of discrete amplifiers and could do so at a lower cost and in a much more reliable

¹ A popular IC type.

and versatile form. The IC operational amplifier offered designers a highly flexible tool that approached a *basic building block* around which a great number of desired circuits could be devised quite simply.

1-3 USING A SIMPLE LINEAR INTEGRATED CIRCUIT

The ease of use and the great utility of LICs can be illustrated by selecting a simple example in the form of a general-purpose operational amplifier (commonly called an OP AMP). Contrasted with the use of discrete components (such as transistors, resistors, and small capacitors) in a multistage amplifier, the use of an OP AMP can often make the design of a desired amplification function (either direct or alternating current) a straightforward operation; in many cases it would simply mean choosing values for two external resistors (R_f and R_i) to use with a general-purpose OP AMP, such as the very popular 741 type² illustrated in Fig. 1.1.

To gain a clear appreciation of the superior convenience and flexibility offered by the IC OP AMP compared to a traditional amplifier made up of discrete components, it is instructive to trace the steps needed in the case of both amplifiers to accomplish a typical amplification function.

Let us assume a project requiring a direct-coupled amplifier with a stable gain of, say, 500, where the input comes from a light sensor that provides a slowly varying dc signal ranging from 1 to 10 mV. (This would call for an output from the amplifier of $\frac{1}{2}$ to 5 V, as displayed on a dc voltmeter.) In the next two paragraphs we can follow the necessary procedures to accomplish the same purpose in each case.


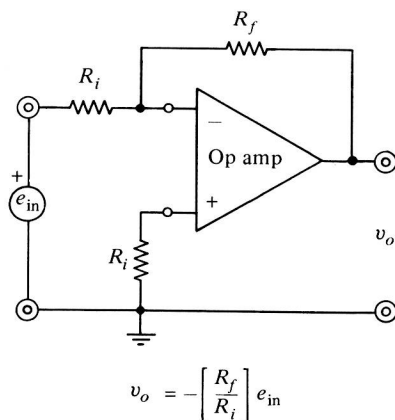


Figure 1.1 Functional symbol diagram of an operational amplifier (OP AMP); the simple gain formula applies to a typical operational amplifier used as an inverting amplifier.

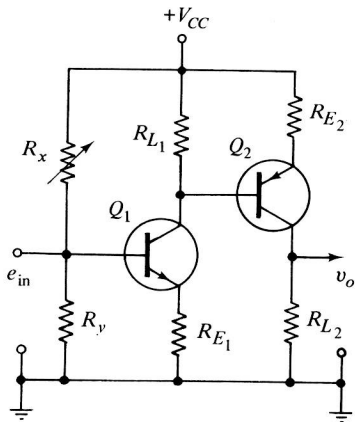² Another very popular IC type with internal compensation.



$$v_o \approx 0.7 \left[\left(\frac{R_{L2}}{R_{E2}} \right) \left(\frac{R_{L1}}{R_{E1}} \right) \right] e_{in}$$

Figure 1.2 Discrete form of direct-coupled amplifier: it requires calculation of proper values of at least six resistors to accomplish desired gain; compare this to a simple ratio of two resistors for the OP AMP in Fig. 1.1.

In the case of the *discrete amplifier*, we might choose the circuit of Fig. 1.2, calling for an *NPN* transistor (Q_1) followed by a *PNP* type (Q_2), arranged in the “compound” type of circuit, where the bias voltages can be handled more conveniently in this type of complementary transistor connection. Making use of simplified design relations, we would first establish the Q -point for the output stage to ensure that we stay within the linear operating range. With a supply voltage of around 20 V, this would call for a collector voltage of about half the supply, or approximately 10 V, for V_{CE2} at the Q -point, ensuring no distortion. Then, as suggested by Lenk,³ we would choose proper values for the resistors; for example, we might choose R_{L2} as 1 k Ω , requiring collector current of Q_2 to be about 10 mA. Proceeding from this, values of R_{E2} and then of R_{L1} and R_{E1} are selected for the proper gain relationship of R_L/R_E for each stage; then the selection of approximate values of R_x and R_y is made for obtaining proper bias currents. As an additional simplification, R_x is shown to be variable, so that it may be easily set to obtain the correct meter reading for collector current of Q_2 ; finally, a final adjustment of R_x is again made, if required, so that the full output range is obtained without distortion. It will be noted that even when a bit of cut-and-try process is used here to reduce unnecessarily precise calculations, the simplified procedure still involves working with six resistor values to accomplish the proper operation of the amplifier in producing a direct-coupled gain of about 500, together with a satisfactory output swing between $\frac{1}{2}$ and 5 V, as desired.

³ J. D. Lenk, *Handbook of Simplified Solid-State Circuit Design*, Prentice-Hall, Inc., Englewood Cliffs, N.J., 1971.