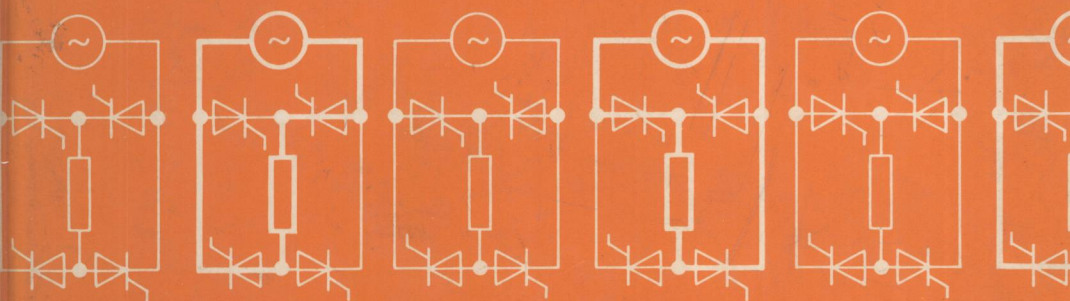


A Basic Guide to Power Electronics



Albert Kloss


TN 624
K1

8563915

A BASIC GUIDE TO POWER ELECTRONICS

Albert Kloss
*BBC, Brown, Boveri & Company Ltd.,
Baden, Switzerland*

Translated by
K. G. King

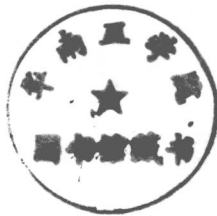

A Wiley-Interscience Publication



E8563915

JOHN WILEY & SONS
Chichester · New York · Toronto · Brisbane · Singapore

First published in German as
Leistungselektronik ohne Ballast
by Franzis-Verlag GmbH, München, 1980

Copyright ©1984 by John Wiley & Sons Ltd.

All right reserved.

No part of this book may be reproduced by any means, nor transmitted, nor translated into a machine language without the written permission of the publisher.

Library of Congress Cataloging in Publication Data:
Kloss, Albert.

A basic guide to power electronics.

Translation of: *Leistungselektronik ohne Ballast.*
'A Wiley-Interscience publication.'

Includes index.

1. Power electronics. I. Title.
TK7881.15.K55 1984 621.3815 84-7398

ISBN 0 471 90432 5

British Library Cataloguing in Publication Data:
Kloss, Albert

A basic guide to power electronics.

1. Electric current converters 2. Power electronics

I. Title II. *Leistungselektronik ohne Ballast. English*

621.3815'322 TK7872.C8

ISBN 0 471 90432 5

Phototypeset by Mathematical Composition Setters Ltd, 7 Ivy St, Salisbury, Wilts.
Printed by St. Edmundsbury Press Ltd., Suffolk.

**A BASIC GUIDE TO
POWER ELECTRONICS**

List of Symbols

CURRENTS

Instantaneous values

i	Alternating current, transformer current, valve current
i_{\sim}	Alternating current, supply (source) current
$i_{R,S,T}$	Phase currents
i_k	Short-circuit current, commutating current
i_{Th}	Thyristor current
$i_{1,2,\dots}$	Valve currents
i_1	Fundamental current
i_g	Triggering (gate) pulse
i_E	D.C. voltage-source current
i_d	Direct current
i_R	Current in resistor
i_C	Current in capacitor
i_m	Maximum value
I_m	Amplitude
I_F	Forward current, maximum value
i_{rr}	Reverse current peak

Relative values

i_d	Direct current
-------	----------------

Mean values

I_d	Direct current
I_{do}	Direct current with $\alpha = 0^\circ$
I_{dN}	Rated (nominal) direct current
I_{dk}	Short-circuit direct current
I_{VAV}	Valve current
I_{ThAV}	Thyristor current

R.M.S. values

I	Alternating current, transformer current
I_N	Rated (nominal) transformer current
I_k	Short-circuit current

$I_{V_{rms}}$	Valve current
$I_{Th_{rms}}$	Thyristor current
I_1	Fundamental component
I_n	Harmonic current
I_s	Supply current

VOLTAGES

Instantaneous values

v	Alternating voltage, line voltage, valve voltage
$v_{R,S,T}$	Phase voltages
v_{ph}	Phase voltage
v_n	Harmonic voltage
v_s	Supply voltage
v_{sec}	Secondary voltage
v_V	Valve voltage
$v_{1,2,\dots}$	Valve voltage
v_{Th}	Thyristor voltage
$v_{L,Lk}$	Voltage across inductance
v_C	Capacitor voltage
v_d	Direct voltage
v_D	Diode voltage
v_{rr}	Reverse recovery voltage peak
V_{Vm}	Valve voltage, maximum value

Relative values

v_d	Direct voltage
dx	Inductive d.c. voltage drop
dr	Ohmic d.c. voltage drop
e_k	Total short-circuit voltage
e_{kt}	Transformer short-circuit voltage

Mean values

V_d	Direct voltage
V_{dio}	Ideal no-load direct voltage, $\alpha = 0^\circ$
V_{do}	Direct voltage with $\alpha = 0^\circ$
E	D.C. voltage source
A	Voltage-time integral (area)

R.M.S. values

V	Line voltage
V_i	Fundamental component
$V_{V_{rms}}$	Valve voltage
V_{ph}	Phase voltage

V_{sec}	Secondary voltage
V_{p}	Primary voltage
V_0	Source voltage, no-load voltage

POWERS

P	Active power (mean)
S	Total apparent power
S_1	Fundamental frequency apparent power
S_t	Transformer rated power (VA)
Q	Total non-active power (reactive power)
Q_1	Fundamental frequency reactive power
Q_H	Harmonic non-active power, distortion power
Q_T	Transformer short-circuit volt-amperes
Q_s	Supply short-circuit capacity
p	Relative active power, instantaneous power
q_1	Relative fundamental frequency reactive power
q_C	Relative capacitive reactive power
s_1	Relative fundamental frequency apparent power
W	Energy

PARAMETERS, ABBREVIATIONS

L	Inductance in d.c. circuit
L_k	Commutating inductance
C	Capacitance
R	Resistance
R_i	Equivalent resistance
x_k	Commutating reactance
V	Valve
D	Diode
L_F	Filter inductance
L_μ	Transformer no-load (magnetising) inductance
K	Cathode
A	Anode
p, n	Semiconductor conductivity types
REC	Rectifier
INV	Inverter
G	Generator
M	Motor
ASM	Asynchronous (induction) motor
SM	Synchronous machine
HVDC	High-voltage d.c. (transmission)
Hg	Mercury
Si	Silicon
Se	Selenium
n	Harmonic order, rotational speed

ANGLES, ANGULAR INTERVALS, FACTORS

α	Delay angle
α'	Natural delay angle
ϕ	Phase angle
ϕ_1	Phase angle of fundamental component
ω	Angular interval at supply frequency
ω	Angular frequency of alternating (supply) voltage
ω_0	Natural angular frequency of oscillatory circuit
λ	Conduction angle, power factor
μ	Overlap (commutation) angle
f	Frequency
T	Period
τ	Time constant

HEAT

R_{th}	Thermal resistance (steady state)
r_{th}	Transient thermal resistance
P	Loss in valve
v_0	Threshold voltage
r	Equivalent (incremental) resistance
θ	Temperature
k_f	Current form factor

Preface

This book is directed both to students and to practising engineers and technicians.

The pillars of the book are the diagrams. They carry the most important information and it is possible as a first step to use the work as a picture book.

The main emphasis is placed upon a physical understanding of the problems considered. Practically oriented mathematical relationships are associated with, but separated from, individual sections of text. The reader can study the book in its essentials without having to become involved with mathematics.

The book is intended to serve as a textbook, with systematically structured material, and also as a practical work of reference.

The discussion concerns the most important aspect of power electronics—converter circuits for three-phase systems—and is centred on the three-phase bridge circuits with natural commutation which are the most widely used. Systematic treatment of the fundamentals is supported by the latest findings from industry and research. Many of the diagrams are based upon computer calculations.

The author has drawn upon long experience as an engineer with Brown Boveri and Co. at Baden, Switzerland, since 1969, and as delegate laecture at the Winterthur Technical and Engineering College (1971–1983).

The author would like to thank Mrs. M. Lochner for the painstakingly drawn diagrams and Mr. G. Lochner (Dipl. Ing.) for his critical checking of the manuscript.


IMPORTANT NOTICE

The circuits and methods reproduced in this book are given without any consideration to the patent situation. They are chosen purely for the purposes of interest and instruction, and may not be used commercially.

All the circuits and technical data in this book have been collected and assembled by the author with the utmost care and reproduced under the closest control. Nevertheless, errors may not have been entirely avoided. The publishers feel obliged, therefore, to make it clear that they can offer no guarantee, nor accept any legal responsibility or liability, in regard to any consequences attributable to erroneous statements. The author and the publishers will be grateful if any errors are brought to their notice.

Contents

List of Symbols	xiii
Preface	xv
1 The Structure of Power Electronics	1
Fundamentals	1
Converters	1
A.C.-a.c. and D.C.-d.c. converters	1
Internal operation of converters	3
The structure of converters	4
Application areas of converters	4
The principal features of power electronics	4
Problem areas of power electronics	5
2 The History of Power Electronics Development	6
Mercury arc rectifiers	6
Semiconductor valves	7
Converter circuits and application areas	8
3 Converter Valves	10
Fundamentals	10
Physical principles	10
Semiconductor valves	10
Construction of semiconductor valves	11
Operation of diodes and thyristors	12
The diode	12
The thyristor	12
Characteristics of diodes and thyristors	13
The thyristor compared with the transistor	14
Operational valves	15
Valve groups	16
Valve parameters	17
Dynamic characteristics of converter valves	18
Turn-on requirements of thyristors	18
Temperature dependence of valve characteristics	18
Losses in valves	19
Limits of survival, overload capacity, and reliability of valves ..	19
Statistical distribution of valve parameters	19
Special valves	20

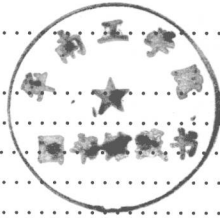

4	Simple Valve Circuits	21
	Principal elements of converter circuits	21
	The transient state—continuous occurrence in valve circuits	21
	Inductive valve circuit with a.c. supply	22
	Mathematical appendix I	24
	Inductive valve circuit with a.c. and d.c. voltage sources	26
	Mathematical appendix II	28
	Current interruption in an inductive valve circuit—commutation and freewheeling	29
	Capacitive valve circuits	31
	Oscillatory circuit including a valve	32
	Mathematical appendix III	32
	Power balance in valve circuits	33
	Mathematical appendix IV	37
	Energy balance	39
	Mathematical appendix V	40
5	The Structure of Multiple-Pulse Converter Circuits	41
	Single-pulse converter	41
	Two-pulse converter	41
	Six-pulse (three-phase) converter	41
	Mathematical appendix VI	43
6	Operation of the Three-Phase Bridge Circuit	47
	Uncontrolled three-phase bridge with ideal supply	47
	Mathematical appendix VII	50
	Uncontrolled three-phase bridge with inductive supply	51
	Equivalent circuit	51
	Discontinuous current operation with high load back-voltage	53
	Formation of continuous direct current—commutation	54
7	Theory of the Three-Phase Bridge	57
	Assumptions	57
	Uncontrolled three-phase bridge	57
	Simple commutation—typical operating mode of the three-phase bridge	57
	Complete load characteristic of the uncontrolled three-phase bridge	61
	Characteristics of the uncontrolled three-phase bridge	66
	Validity limits of the conventional theory for uncontrolled three-phase bridges	68
	Mathematical appendix VIII	68
	The controlled three-phase bridge	70
	Converter control—general	70
	Triggering pattern for the three-phase bridge	71
	Control of direct voltage—ideal conditions	73
	Mathematical appendix IX	74

Output characteristic of the controlled three-phase bridge in rectifier mode	76
Maximum-output condition, $\alpha = 0^\circ$	76
Control range $0^\circ \leq \alpha \leq 90^\circ$	77
Mathematical appendix X	82
Load characteristic of the controlled three-phase bridge in the inverter mode	84
General	84
Inverter characteristics	86
Mathematical appendix XI	89
Comparison of rectifiers and inverters	90
Converter operation with discontinuous direct current	91
Load current ripple	94
Mathematical appendix XII	95
The principal converter theories	97
8 Power Balance in Three-Phase Bridge Converters	100
General	100
Control reactive power of a converter	100
Commutation non-active power	103
Distortion power	105
Geometrical representation of the converter power balance	106
Power relationships in the transient state	109
Mathematical appendix XIII	112
9 Harmonics in the Three-Phase Bridge Converter	116
General	116
Principles of harmonics	117
Transient conditions	125
Mathematical appendix XIV	126
10 Fault Conditions in the Three-Phase Bridge	130
General	130
Valve breakdown	130
Inoperative valve	131
Phase failure	132
D.C.-side short circuit	133
Supply failure	135
Estimation of fault conditions	137
Mathematical appendix XV	137
11 The Three-Phase Bridge under Special Operating and Switching Conditions	144
The effect of ohmic resistances on load characteristics	145
Capacitive converter loading	146
The effect of transformer connections on load characteristics ...	147
The effect of supply short-circuit capacity on load characteristics	148
Mathematical appendix XVI	149

12	Double-Bridge Converters	152
	General	152
	Reversible converter drives	154
	Operating principle	154
	Fault conditions in the reversible converter	156
	Direct frequency changer	158
	Single-phase direct frequency changer	158
	Three-phase direct frequency changer	161
	Fault conditions in direct frequency changers	167
	Mathematical appendix XVII	167
	Intermediate-link frequency changer	169
	Operation of the intermediate-link frequency changer	169
	Power balance in the d.c.-link converter	172
	D.C.-link converter for three-phase drives	172
	Fault conditions in the d.c.-link converter	175
	Comparison of the d.c.-link converter with the direct frequency changer	176
	Mathematical appendix XVIII	178
	Series converter circuits	179
	General	179
	Twelve-pulse converter circuit	179
	Converter with sequential control	182
13	Converter-Supply Interactions	185
	General	185
	Loading on the three-phase system by the converter	185
	Mathematical appendix XIX	190
	Compensation for converter supply loading	192
	Mathematical appendix XX	194
	The effect of the supply on the converter	195
14	Converter Protection	197
	Protection philosophy	197
	Overvoltage protection of converter valves	199
	Overvoltages, general	199
	Switching-on of the converter	200
	Sustaining load for discontinuous current operation	201
	Commutation overvoltages in normal operation	202
	Turn-off overvoltages	206
	Thyristor stress due to high rate of rise of forward voltage ..	209
	Overvoltage protection devices	210
	Mathematical appendix XXI	211
	Overcurrent protection of converter valves	212
	Mathematical appendix XXII	215
15	Thermal Characteristics and Cooling of Converter Valves	216
	Losses and thermal resistance	216
	Cooling	218

Mathematical appendix XXIII	218
16 Specification of Converters	220
Calculation sequence	220
Choice of converter circuit	222
The main characteristics of converters in brief	223
Bibliography	225
Index	226

The Structure of Power Electronics

FUNDAMENTALS

The principles of power electronics cover electrical circuits and apparatus which achieve the control or conversion of electrical energy by means of electronic valves.*

Power electronic equipments are generally referred to as 'converters', and the valves are accordingly termed 'converter valves'.

Valve action takes place in solid-state semiconductors. Because power electronic apparatus contains no moving parts, it is often referred to as 'static' equipment. The term 'power electronics' stems from the development of high-power semiconductor valves during the nineteen-sixties. The expressions converter or rectifier technology were previously used.

CONVERTERS

Converters constitute the hardware of power electronics. According to their basic functions, converters can be divided into the following groups:

- Rectifiers (a.c.—d.c. converters)
- Inverters (d.c.—a.c. converters)
- A.C.—a.c. converters
- D.C.—d.c. converters

Rectifiers convert alternating current (a.c.) into direct current (d.c.). Conversely, inverters convert direct to alternating current.

With converters that convert from a.c. to a.c. or from d.c. to d.c. it is possible to change voltage, frequency, phase number, or polarity.

Circuits that can function as rectifiers or inverters, according to the way in which they are controlled, are often referred to simply as 'converters'.

With the exception of rectifiers, which can operate in an uncontrolled mode, all converters embody controllable valves.

A.C.—a.c. and D.C.—d.c. CONVERTERS

This group includes the following subgroups:

- Direct a.c. converters (direct frequency changers, cycloconverters)

* As often in continental usage, and in accordance with the *IEC International Electrotechnical Vocabulary*, Chapter 551, the term 'valve' is applied generally in this book to the class of rectifying and switching devices which includes solid-state diodes and thyristors as well as vacuum, gas, or vapour-filled tubes.

- Indirect a.c. converters (d.c.–link frequency changers)
- D.C. regulators (d.c. choppers)
- A.C. regulators

The direct frequency changer converts alternating current of one voltage, frequency, and phase number into a different voltage, frequency, and phase number directly, without a means of energy storage. The output frequency is usually lower than the input frequency.

The d.c.–link frequency changer serves basically the same purpose as the direct frequency changer, but includes in addition a means of energy storage in a direct current or direct voltage intermediate circuit. The output frequency is consequently independent of the input frequency.

In both d.c.–link and direct frequency changers energy can be translated in either direction. The d.c.–link frequency changer feeding a synchronous machine constitutes the so-called converter motor; connected in the rotor circuit of an asynchronous machine it forms a subsynchronous converter

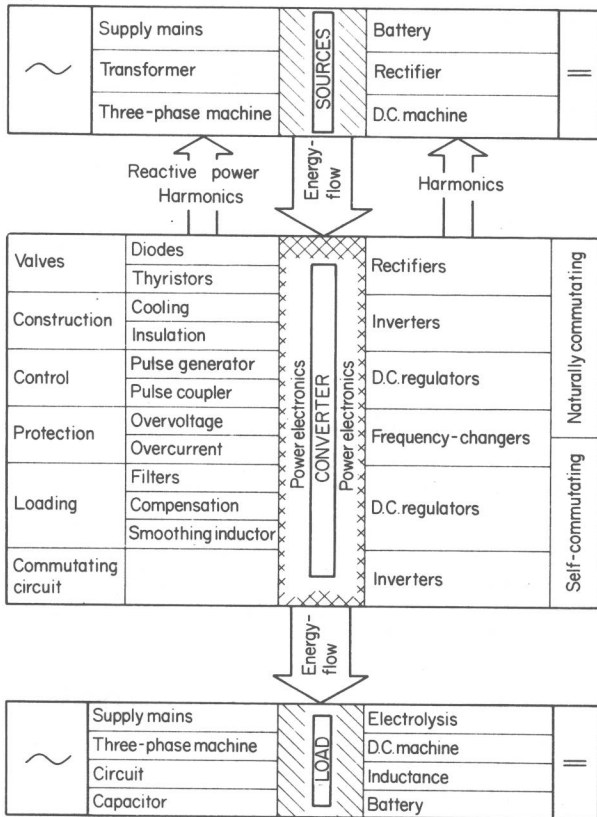


Figure 1. Diagrammatic presentation of the role of converters in energy conversion and control. The converters lie in the path of energy flowing between the source and the load. On the left are listed the components and the problem areas, on the right the classification of converter systems

cascade (the static Kraemer system), and in electricity supply systems it is used for high-voltage d.c. transmission.

The d.c. regulator facilitates the variation of d.c. voltage, without any intermediate circuit, but normally by dint of a forced commutation circuit (or valves with a turn-off facility).

The a.c. regulator affords a variation of a.c. voltage, at an unchanged frequency, again without an intermediate circuit.

The two regulators are not always counted as 'converters' but may be regarded as a distinct group. Figures 1 and 2 illustrate the classification of converters in terms of power flow, components, and grouping.

INTERNAL OPERATION OF CONVERTERS

Converter circuits are assemblies of converter valves, which function as controlled switching devices. The required conversion and control of voltage

	Source	Intermediate circuit	Load	Designation
Naturally commutating				Rectifier
				A.C. regulator
				Direct frequency changer
				D.C.-link frequency changer
				Inverter
Self-commutating				Direct-voltage-link frequency changer
				D.C. regulator
				Inverter

Figure 2. Systematic classification and simplified symbols of converter types. Converter circuits fall into two main groups: converters with natural (external) commutation and converters with forced commutation (self-commutating)