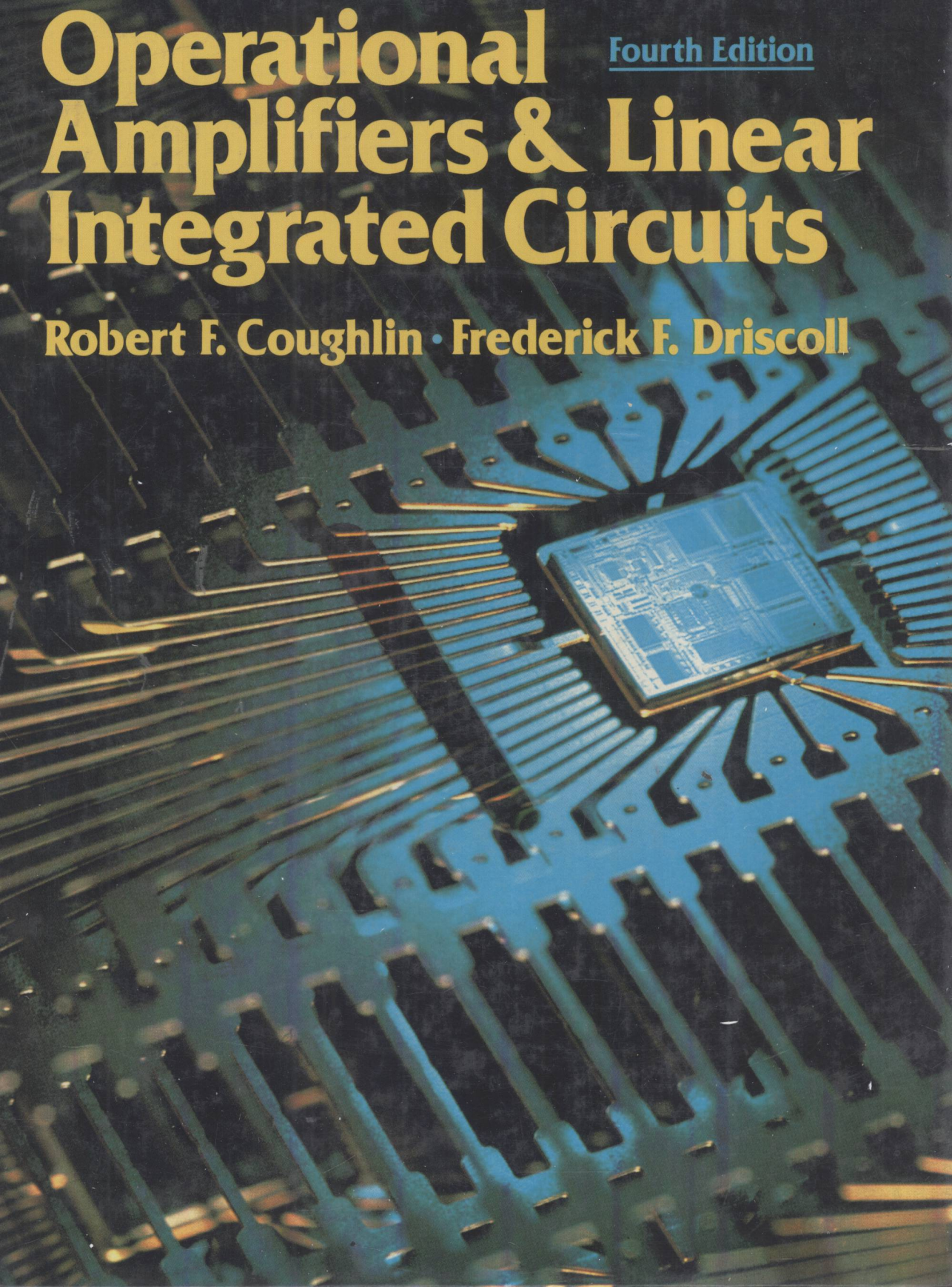


Operational Amplifiers & Linear Integrated Circuits

Fourth Edition

Robert F. Coughlin • Frederick F. Driscoll



TN 722-7
C 854
E. 4

9360069

9360069

FOURTH EDITION

OPERATIONAL AMPLIFIERS AND LINEAR INTEGRATED CIRCUITS

Robert F. Coughlin
Frederick F. Driscoll



E9360069



PRENTICE HALL, Englewood Cliffs, New Jersey 07632

Library of Congress Cataloging-in-Publication Data

Coughlin, Robert F.

Operational amplifiers and linear integrated circuits / Robert F. Coughlin, Frederick F. Driscoll. -- 4th ed.

p. cm.

Includes bibliographical references and index.

ISBN 0-13-639923-1

1. Operational amplifiers. 2. Linear integrated circuits.

I. Driscoll, Frederick F., 1943- . II. Title.

TK7871.58.O6C68 1991

621.39'5--dc20

90-43585

CIP

Editorial/production supervision: *Ellen Denning*

Interior design: *Jayne Conte*

Cover design: *Bruce Kenselaar*

Manufacturing buyer: *Ed O'Dougherty*

Cover photograph: Gary Gladstone/The Image Bank



© 1991, 1987, 1982, 1977 by Prentice-Hall Inc.

A Division of Simon & Schuster

Englewood Cliffs, New Jersey 07632

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

ISBN 0-13-639923-1

PRENTICE-HALL INTERNATIONAL (UK) LIMITED, *London*

PRENTICE-HALL OF AUSTRALIA PTY. LIMITED, *Sydney*

PRENTICE-HALL CANADA INC., *Toronto*

PRENTICE-HALL HISPANOAMERICANA, S.A., *Mexico*

PRENTICE-HALL OF INDIA PRIVATE LIMITED, *New Delhi*

PRENTICE-HALL OF JAPAN, INC., *Tokyo*

SIMON & SCHUSTER ASIA PTE. LTD., *Singapore*

EDITORIA PRENTICE-HALL DO BRASIL, LTDA., *Rio de Janeiro*

To Our Partners in Ballroom Dancing
and
Our Lifetime Partners,
Barbara and Jean

As
We Grow Older
We Grow Closer

Preface

It has been our purpose in the first three editions, and again now in the fourth edition of this text, to show that operational amplifiers and other linear integrated circuits are both fun and easy to use, especially if the application does not require the devices to operate near their design limits. It is the purpose of this book to show just how easy they are to use in a variety of applications involving instrumentation, signal generation, filter, and control circuits.

When first learning how to use an op amp, one should *not* be presented with a myriad of op amps and asked to make an informed selection. For this reason, our introduction begins with an inexpensive, reliable op amp that forgives most mistakes in wiring, ignores long lead capacitance, and does not burn out easily. Such an op amp is the 741, whose characteristics are documented in Appendix 1 and whose applications are sprinkled throughout the text.

If a slightly faster op amp is needed for a wider bandwidth, another inexpensive and widely used op amp is the 301. See Appendix 2 for its electrical characteristics and Chapter 10 to learn when one might prefer the 301 over the 741. We also use the stable CA3140 and TL081, which are pin-for-pin higher-frequency replacements for the 741.

Where appropriate, we have added specialized op amps: the LM339 single supply comparator in Chapter 2 and the LM311 high-performance comparator in Chapter 4. Where better dc performance is required, we have added BiFET op amps in Chapter 7. The excellent low-bias-current and low-offset-voltage OP-07 is also employed for instrumentation applications.

The fourth edition is organized into a set of core chapters that should be read first. They are Chapters 1 through 6 and proceed in a logical teaching sequence to show how the op amp can be used to solve a variety of application problems.

The limitations of op amps are not discussed in Chapters 1 to 6 because it is very important to gain confidence in using op amps before pushing performance to its limits. When studying transistors or other devices, we do not begin with their limitations. Regrettably, much of the early literature on integrated circuits begins with their limitations and thus obscures the inherent simplicity and overwhelming advantages of basic integrated circuits over basic transistor circuits. For these reasons, op amp limitations are not presented until Chapters 9 and 10 for those readers who need to understand some of their limitations with respect to dc and ac performance. Furthermore, not all op amp limitations apply to every op amp circuit. For example, dc op amp limitations such as offset voltages are usually not important if the op amp is used in an ac amplifier circuit. Thus dc limitations (Chapter 9) are treated separately from ac limitations (Chapter 10). The remaining chapters have been written to stand alone. They can be studied in any order after completion of Chapters 1 through 6.

The servoamplifier and subtractor circuits have been added to Chapter 5. Chapter 6 has been extensively rewritten to show the latest techniques using a modulator/demodulator IC and trigonometric function generator IC to make a *precision* triangle/square/sine-wave generator whose frequency can be adjusted over a wide range by a *single* resistor and whose amplitude can be adjusted without affecting frequency, or vice versa.

Chapter 7 deals with the specialized applications that can best be accomplished by op amps combined with diodes.

Chapter 8 is concerned with problems of measuring physical variables such as force, pressure weight, and temperature. Bridge and instrumentation amplifiers are ideal for these measurements.

Chapter 11 simplifies the design of active filters. The four basic types of active filters are shown: low-pass, high-pass, band-pass, and band-reject filters. Butterworth filters were selected because they are often used and easy to design. If you want to design a three-pole (60-dB/decade) Butterworth low- or high-pass filter,

Chapter 11 tells you how to do it in four steps with a pencil and paper. No calculator or computer program is required. Basic algebra is the only mathematics that is required throughout the text. The sections on bandpass and notch filters have been completely rewritten to simplify both their design procedures and fine tuning.

A fascinating integrated circuit, the multiplier, is presented in Chapter 12 because it makes analysis and design of communication circuits very easy. Modulators, demodulators, frequency shifters, a universal AM radio receiver, and a host of other applications are performed by the multiplier, an op amp, and a few resistors. This chapter has been retained because numerous instructors have written to say how useful it is as a hardware-oriented teaching tool that introduces the principles of single-sideband, suppressed-carrier, and standard amplitude-modulation principles used in radio communication.

Chapter 13 is included for those who need to use the ubiquitous 555 IC timer and/or the XR2240 counter timer.

A chapter (14) has been added (because of requests of many instructors) on digital-to-analog and analog-to-digital converters. More specifically, instructors have requested information on converters that (1) are microprocessor compatible, (2) simple to select via a data bus, (3) low in cost and easy to use, and (here comes the hard one) (4) stand-alone circuits for both a microprocessor-compatible DAC and an ADC that can be (a) breadboarded by students in a laboratory and (b) do *not* require a microprocessor. This has been done!

Since almost all linear integrated circuits require a regulated power supply, we have, because of requests from readers, retained material on power supply design and analysis and moved it to Chapter 15. The latest IC regulators are used to show how you can make excellent linear regulated supplies at low cost for (a) 5-V digital logic ICs, (b) ± 15 -V linear ICs, (c) combined (a) and (b) for microprocessor supplies, and (d) either positive or negative adjustable supplies.

In this fourth edition we have incorporated suggestions from students, instructors, and practicing engineers and technicians from all parts of the United States and from Indonesia, Poland, Japan, and the USSR.

This edition contains more than enough material for a single-semester course. All circuits have been personally lab tested by the authors and their recommendations for laboratory work have been added to the end of each chapter. The material is suitable for both nonelectronic specialists who just want to learn something about linear ICs and for electronic majors who wish to use linear ICs. In addition, we have added Learning Objectives to the beginning of each chapter, again in response to requests from readers.

We thank Mrs. Phyllis Wolff for the preparation of the original manuscript and continued support in this fourth edition. A special thanks to our colleague Robert S. Villanucci who has been particularly helpful with his suggestions and for testing of ideas and to Dean Alexander Avtgis for his continued support.

We also thank two highly respected analog engineers, Dan Sheingold of

Analog Devices and Bob Pease of National Semiconductors, for their constructive criticism, technical corrections, and guidance in areas we found difficult.

Finally, we thank our students for their insistence on relevant instruction that is immediately useful, and our readers for both their enthusiastic reception of this book and their perceptive comments.

ROBERT F. COUGHLIN
FREDERICK F. DRISCOLL

Boston, Mass.

Contents

PREFACE

xxiii

1 INTRODUCTION TO OP AMPS

1

Learning Objectives 1

1-0 Introduction 2

1-1 A Short History 2

1-1.1 *The Early Days*, 2

1-1.2 *Birth and Growth of the IC Op Amp*, 2

1-1.3 *Further Progress in Op Amp Development*, 3

1-1.4 *Op Amps Become Specialized*, 3

1-2 741 General-Purpose Op Amp 4

1-2.1 *Circuit Symbol and Terminals*, 4

1-2.2 *Circuit Schematic*, 4

1-3	Packaging and Pinouts	5
1-3.1	Packaging,	5
1-3.2	Combining Symbol and Pinout,	6
1-4	How to Identify or Order an Op Amp	8
1-4.1	The Identification Code,	8
1-4.2	Order Number Example,	9
1-5	Second Sources	9
1-6	Breadboarding Op Amp Circuits	10
1-6.1	The Power Supply,	10
1-6.2	Breadboarding Suggestions,	10
	Problems	11

2 FIRST EXPERIENCES WITH AN OP AMP

13

	Learning Objectives	13
2-0	Introduction	14
2-1	Op Amp Terminals	14
2-1.1	Power Supply Terminals,	15
2-1.2	Output Terminal,	15
2-1.3	Input Terminals,	17
2-1.4	Input Bias Currents and Offset Voltage,	18
2-2	Open-Loop Voltage Gain	18
2-2.1	Definition,	18
2-2.2	Differential Input Voltage, E_d ,	19
2-2.3	Conclusions,	19
2-3	Zero-Crossing Detectors	20
2-3.1	Noninverting Zero-Crossing Detector,	20
2-3.2	Inverting Zero-Crossing Detector,	21
2-4	Positive- and Negative-Voltage-Level Detectors	22
2-4.1	Positive-Level Detectors,	22
2-4.2	Negative-Level Detectors,	23
2-5	Typical Applications of Voltage-Level Detectors	24
2-5.1	Adjustable Reference Voltage,	24
2-5.2	Sound-Activated Switch,	24
2-5.3	Light Column Voltmeter,	26
2-5.4	Smoke Detector,	27
2-6	Signal Processing with Voltage-Level Detectors	28
2-6.1	Introduction,	28
2-6.2	Sine-to-Square Wave Converter,	28

2-7	Computer Interfacing with Voltage-Level Detectors	28
2-7.1	Introduction,	28
2-7.2	Quad Voltage Comparator, LM339,	29
2-7.3	Pulse-Width Modulator, Noninverting,	31
2-7.4	Inverting and Noninverting Pulse-Width Modulators,	34
2-8	Analog-to-Digital Conversion with a Microcomputer and a Pulse-Width Modulator	34
	Laboratory Exercises	34
	Problems	37

3 INVERTING AND NONINVERTING AMPLIFIERS

39

	Learning Objectives	39
3-0	Introduction	40
3-1	The Inverting Amplifier	40
3-1.1	Introduction,	40
3-1.2	Positive Voltage Applied to the Inverting Input,	41
3-1.3	Load and Output Currents,	42
3-1.4	Negative Voltage Applied to the Inverting Input,	43
3-1.5	AC Voltage Applied to the Inverting Input,	45
3-1.6	Design Procedure,	46
3-1.7	Analysis Procedure,	47
3-2	Inverting Adder and Audio Mixer	47
3-2.1	Inverting Adder,	47
3-2.2	Audio Mixer,	48
3-2.3	DC Offsetting an AC Signal,	49
3-3	Multichannel Amplifier	49
3-3.1	The Need for a Multichannel Amplifier,	49
3-3.2	Circuit Analysis,	51
3-3.3	Design Procedure,	52
3-4	Inverting Averaging Amplifier	52
3-5	Voltage Follower	53
3-5.1	Introduction,	53
3-5.2	Using the Voltage Follower,	54
3-6	Noninverting Amplifier	56
3-6.1	Circuit Analysis,	56
3-6.2	Design Procedure,	60
3-7	The "Ideal" Voltage Source	60
3-7.1	Definition and Awareness,	60
3-7.2	The Unrecognized Ideal Voltage Source,	60
3-7.3	The Practical Ideal Voltage Source,	61

- 3-8 Noninverting Adder 62
- 3-9 Single-Supply Operation 62
- 3-10 Difference Amplifiers 64
 - 3-10.1 *The Subtractor*, 64
 - 3-10.2 *Inverting–Noninverting Amplifier*, 66
- 3-11 Servoamplifier 66
 - 3-11.1 *Introduction*, 66
 - 3-11.2 *Servoamplifier Circuit Analysis*, 67
 - 3-11.3 *Delay Action*, 68
- Laboratory Exercises 69
- Problems 70

4 COMPARATORS AND CONTROLS

73

- Learning Objectives 73
- 4-0 Introduction 74
- 4-1 Effect of Noise on Comparator Circuits 74
- 4-2 Positive Feedback 76
 - 4-2.1 *Introduction*, 76
 - 4-2.2 *Upper-Threshold Voltage*, 77
 - 4-2.3 *Lower-Threshold Voltage*, 77
- 4-3 Zero-Crossing Detector with Hysteresis 78
 - 4-3.1 *Defining Hysteresis*, 78
 - 4-3.2 *Zero-Crossing Detector with Hysteresis as a Memory Element*, 79
- 4-4 Voltage-Level Detectors with Hysteresis 80
 - 4-4.1 *Introduction*, 80
 - 4-4.2 *Noninverting Voltage-Level Detector with Hysteresis*, 81
 - 4-4.3 *Inverting Voltage-Level Detector with Hysteresis*, 83
- 4-5 Voltage-Level Detector with Independent Adjustment of Hysteresis and Center Voltage 85
 - 4-5.1 *Introduction*, 85
 - 4-5.2 *Battery-Charger Control Circuit*, 87
- 4-6 On–Off Control Principles 89
 - 4-6.1 *Comparators in Process Control*, 89
 - 4-6.2 *The Room Thermostat as a Comparator*, 89
 - 4-6.3 *Selection/Design Guideline*, 89

4-7	An Independently Adjustable Setpoint Controller	89
4-7.1	Principle of Operation,	89
4-7.2	Output-Input Characteristics of an Independently Adjustable Setpoint Controller,	91
4-7.3	Choice of Setpoint Voltages,	91
4-7.4	Circuit for Independently Adjustable Setpoint Voltage,	93
4-7.5	Precautions,	93
4-8	IC Precision Comparator, 111/311	93
4-8.1	Introduction,	93
4-8.2	Output Terminal Operation,	94
4-8.3	Strobe Terminal Operation,	94
4-9	Window Detector	96
4-9.1	Introduction,	96
4-9.2	Circuit Operation,	98
4-10	Propagation Delay	98
4-10.1	Definition,	98
4-10.2	Measurement of Propagation Delay,	98
	Laboratory Exercises	100
	Problems	100

5

SELECTED APPLICATIONS OF OP AMPS

103

	Learning Objectives	103
5-0	Introduction	104
5-1	High-Resistance DC Voltmeter	104
5-1.1	Basic Voltage-Measuring Circuit,	104
5-1.2	Voltmeter Scale Changing,	105
5-2	Universal High-Resistance Voltmeter	106
5-2.1	Circuit Operation,	106
5-2.2	Design Procedure,	107
5-3	Voltage-to-Current Converters: Floating Loads	108
5-3.1	Voltage Control of Load Current,	108
5-3.2	Zener Diode Tester,	108
5-3.3	Diode Tester,	108
5-4	Light-Emitting-Diode Tester	110
5-5	Furnishing a Constant Current to a Grounded Load	111
5-5.1	Differential Voltage-to-Current Converter,	111
5-5.2	Constant-High-Current Source, Grounded Load,	112

5-5.3	<i>Interfacing a Microcomputer to a Teleprinter, 113</i>
5-5.4	<i>Digitally Controlled 4- to 20-mA Current Source, 114</i>
5-6	Short-Circuit Current Measurement and Current-to-Voltage Conversion 115
5-6.1	<i>Introduction, 115</i>
5-6.2	<i>Using the Op Amp to Measure Short-Circuit Current, 117</i>
5-7	Measuring Current from Photodetectors 117
5-7.1	<i>Photoconductive Cell, 117</i>
5-7.2	<i>Photodiode, 118</i>
5-8	Current Amplifier 118
5-9	Solar Cell Energy Measurements 120
5-9.1	<i>Introduction to the Problems, 120</i>
5-9.2	<i>Converting Solar Cell Short-Circuit Current to a Voltage, 120</i>
5-9.3	<i>Current-Divider Circuit (Current-to-Current Converter), 121</i>
5-10	Phase Shifter 122
5-10.1	<i>Introduction, 122</i>
5-10.2	<i>Phase-Shifter Circuit, 122</i>
5-11	The Constant-Velocity Recording Process 124
5-11.1	<i>Introduction to Record-Cutting Problems, 124</i>
5-11.2	<i>Groove Modulation with Constant-Velocity Recording, 124</i>
5-11.3	<i>Record Cutover and Noise, 126</i>
5-11.4	<i>Solution to Record Cutover and Noise Problems, 127</i>
5-12	Record Playback 127
5-12.1	<i>Need for Playback Equalization, 127</i>
5-12.2	<i>Preamplifier Gain and Signal Voltage Levels, 129</i>
5-12.3	<i>Playback Preamplifier Circuit Operation, 129</i>
5-13	Tone Control 131
5-13.1	<i>Introduction, 131</i>
5-13.2	<i>Tone-Control Circuit, 131</i>
5-14	Temperature-to-Voltage Converters 132
5-14.1	<i>AD590 Temperature Transducer, 132</i>
5-14.2	<i>Celsius Thermometer, 133</i>
5-14.3	<i>Fahrenheit Thermometer, 134</i>
	Laboratory Exercises 134
	Problems 134

6**SIGNAL GENERATORS****138**

- Learning Objectives 138
- 6-0 Introduction 139
- 6-1 Free-Running Multivibrator 139
 - 6-1.1 *Multivibrator Action, 139*
 - 6-1.2 *Frequency of Oscillation, 141*
- 6-2 One-Shot Multivibrator 143
 - 6-2.1 *Introduction, 143*
 - 6-2.2 *Stable State, 144*
 - 6-2.3 *Transition to the Timing State, 144*
 - 6-2.4 *Timing State, 144*
 - 6-2.5 *Duration of Output Pulse, 146*
 - 6-2.6 *Recovery Time, 146*
- 6-3 Triangle-Wave Generators 147
 - 6-3.1 *Theory of Operation, 147*
 - 6-3.2 *Frequency of Operation, 149*
 - 6-3.3 *Unipolar Triangle-Wave Generator, 150*
- 6-4 Sawtooth-Wave Generator 152
 - 6-4.1 *Circuit Operation, 152*
 - 6-4.2 *Sawtooth Waveshape Analysis, 152*
 - 6-4.3 *Design Procedure, 152*
 - 6-4.4 *Voltage-to-Frequency Converter, 154*
 - 6-4.5 *Frequency Modulation and Frequency Shift Keying, 155*
 - 6-4.6 *Disadvantages, 155*
- 6-5 Balanced Modulator/Demodulator, the AD630 156
 - 6-5.1 *Introduction, 156*
 - 6-5.2 *Input and Output Terminals, 156*
 - 6-5.3 *Input-Output Waveforms, 156*
- 6-6 Precision Triangle/Square-Wave Generator 158
 - 6-6.1 *Circuit Operation, 158*
 - 6-6.2 *Frequency of Oscillation, 158*
- 6-7 Sine-Wave Generation Survey 160
- 6-8 Universal Trigonometric Function Generator, the AD639 160
 - 6-8.1 *Introduction, 160*
 - 6-8.2 *Sine Function Operation, 161*
- 6-9 Precision Sine-Wave Generator 163
 - 6-9.1 *Circuit Operation, 163*
 - 6-9.2 *Frequency of Oscillation, 165*

Laboratory Exercises 166

Problems 167

7 OP AMPS WITH DIODES

169

Learning Objectives 169

7-0 Introduction to Precision Rectifiers 170

7-1 Linear Half-Wave Rectifiers 171

7-1.1 *Introduction, 171*

7-1.2 *Inverting Linear Half-Wave Rectifier, Positive Output, 172*

7-1.3 *Inverting Linear Half-Wave Rectifier, Negative Output, 174*

7-1.4 *Signal Polarity Separator, 175*

7-2 Precision Rectifiers: The Absolute-Value Circuit 176

7-2.1 *Introduction, 176*

7-2.2 *Types of Precision Full-Wave Rectifiers, 176*

7-3 Peak Detectors 180

7-3.1 *Positive Peak Follower and Hold, 180*

7-3.2 *Negative Peak Follower and Hold, 181*

7-4 AC-to-DC Converter 182

7-4.1 *AC-to-DC Conversion or MAV Circuit, 182*

7-4.2 *Precision Rectifier with Grounded Summing Inputs, 183*

7-4.3 *AC-to-DC Converter, 184*

7-5 Dead-Zone Circuits 185

7-5.1 *Introduction, 185*

7-5.2 *Dead-Zone Circuit with Negative Output, 185*

7-5.3 *Dead-Zone Circuit with Positive Output, 187*

7-5.4 *Bipolar-Output Dead-Zone Circuit, 188*

7-6 Precision Clipper 190

7-7 Triangular-to-Sine Wave Converter 190

Laboratory Exercises 191

Problems 192

8 DIFFERENTIAL, INSTRUMENTATION, AND BRIDGE AMPLIFIERS

193

Learning Objectives 193

8-0 Introduction 194

8-1	Basic Differential Amplifier	194
8-1.1	<i>Introduction, 194</i>	
8-1.2	<i>Common-Mode Voltage, 196</i>	
8-2	Differential versus Single-Input Amplifiers	197
8-2.1	<i>Measurement with a Single-Input Amplifier, 197</i>	
8-2.2	<i>Measurement with a Differential Amplifier, 198</i>	
8-3	Improving the Basic Differential Amplifier	199
8-3.1	<i>Increasing Input Resistance, 199</i>	
8-4.2	<i>Adjustable Gain, 199</i>	
8-4	Instrumentation Amplifier	201
8-4.1	<i>Circuit Operation, 201</i>	
8-4.2	<i>Referencing Output Voltage, 203</i>	
8-5	Sensing and Measuring with the Instrumentation Amplifier	204
8-5.1	<i>Sense Terminal, 204</i>	
8-5.2	<i>Differential Voltage Measurements, 205</i>	
8-5.3	<i>Differential Voltage-to-Current Converter, 207</i>	
8-6	Basic Bridge Amplifier	208
8-6.1	<i>Introduction, 208</i>	
8-6.2	<i>Basic Bridge Circuit Operation, 210</i>	
8-6.3	<i>Temperature Measurement with a Bridge Circuit, 211</i>	
8-6.4	<i>Bridge Amplifiers and Computers, 214</i>	
8-7	Adding Versatility to the Bridge Amplifier	214
8-7.1	<i>Grounded Transducers, 214</i>	
8-7.2	<i>High-Current Transducers, 214</i>	
8-8	The Strain Gage and Measurement of Small Resistance Changes	215
8-8.1	<i>Introduction to the Strain Gage, 215</i>	
8-8.2	<i>Strain-Gage Material, 216</i>	
8-8.3	<i>Using Strain-Gage Data, 217</i>	
8-8.4	<i>Strain-Gage Mounting, 217</i>	
8-8.5	<i>Strain-Gage Resistance Changes, 218</i>	
8-9	Measurement of Small Resistance Changes	218
8-9.1	<i>Need for a Resistance Bridge, 218</i>	
8-9.2	<i>Basic Resistance Bridge, 218</i>	
8-9.3	<i>Thermal Effects on Bridge Balance, 219</i>	
8-10	Balancing a Strain-Gage Bridge	220
8-10.1	<i>The Obvious Technique, 220</i>	
8-10.2	<i>The Better Technique, 221</i>	
8-11	Increasing Strain-Gage Bridge Output	222