

Solutions Manual

DIGITAL INTEGRATED CIRCUITS

Thomas A. DeMassa
Zack Ciccone

30802789



30802789

SOLUTIONS MANUAL TO ACCOMPANY
Digital Integrated Circuits

THOMAS A. DEMASSA

Arizona State University

ZACK CICCONE

Signal Processing Group, Inc.



JOHN WILEY & SONS, INC.

NEW YORK • CHICHESTER • BRISBANE • TORONTO • SINGAPORE

Section entitled "90 Minutes to SPICE" can be found at the end of this book.

Copyright © 1996 by John Wiley & Sons, Inc.

This material may be reproduced for testing or instructional purposes by people using the text.

ISBN 0-471-13720-0

Printed in the United States of America

Printed and bound by Malloy Lithographing, Inc.

10 9 8 7 6 5 4 3 2 1

EEE425/591 ASU COURSE OUTLINE

EEE 425 is a 4 credit hour undergraduate course with a lab
EEE 591 is a 3 credit hour graduate course without a lab

DIGITAL INTEGRATED CIRCUITS AND SYSTEMS

NUMBER OF LECTURE HOURS: 30 LECTURES

CLASS MEETINGS: twice a week for 15 weeks

SESSION LENGTH: 1hr and 15 minutes

PREREQUISITES: COURSE(S) IN ELECTRONIC CIRCUITS AND DIGITAL LOGIC

TEXTBOOK: "DIGITAL INTEGRATED CIRCUITS" T.A.DEMASSA, Z.CICCONE
John Wiley & Sons, November 1995

COURSE OBJECTIVES: TO PROVIDE EXTENSIVE KNOWLEDGE OF THE OPERATION AND DESIGN OF DIGITAL ICs INCLUDING TTL, ECL, NMOS, AND CMOS TECHNOLOGIES WITH EMPHASIS ON CMOS; TO INTRODUCE BiCMOS AND TO PROVIDE AN EXTENSIVE DESCRIPTION OF THE OPERATION AND DESIGN OF GaAs DIGITAL LOGIC FAMILIES; TO PROVIDE COMPUTATIONAL AND SPICE COMPARISONS REGARDING THE VOLTAGE TRANSFER CHARACTERISTIC, FAN-OUT, POWER DISSIPATION AND SPEED OF EACH; TO PROVIDE A DESCRIPTION OF RANDOM ACCESS MEMORY (RAM) AND READ-ONLY MEMORY (ROM).

COURSE DESCRIPTION: DIGITAL INTEGRATED CIRCUITS WITH EMPHASIS ON CMOS. OPERATION AND DESIGN OF TTL, ECL, NMOS, CMOS AND GaAs DIGITAL LOGIC CIRCUITS. ADDITIONAL TOPICS INCLUDE BiCMOS AND SEMICONDUCTOR MEMORY CIRCUITS.

500 LEVEL MEZZANINE COURSE AVAILABLE FOR GRADUATE CREDIT AT ASU

COURSE REQUIREMENTS:

HOMEWORK: 3 HOMEWORK SETS

EXAMINATIONS: 2 EXAMS AND A FINAL EXAM

GRADING:	3 EXAMS (1hr and 15 min)	60%	OR	3 EXAMS	50%
	FINAL EXAM	30%		FINAL EXAM	25%
	HOMEWORK	10%		HOMEWORK	10%
				LAB	15%

COURSE OUTLINE BY TOPICAL AREAS AND CHAPTERS

LECTURE 1: HWWORK PROBLs ASSIGNED(HPA):1.1,4,7,10,22,25
PROPERTIES OF DIGITAL CIRCUITS: inverting and noninverting gates, ideal logic elements, voltage transfer characteristic(VTC), logic swing, transition width, noise, fan-in, fan-out, transient characteristics, power dissipation, power-delay product

LECTURE 2: HPA:2.1,5,9,10,16,19; 3.1,2,6,9,11,14
DIODES: PN junction and MN Schottky, modeling, capacitance, SPICE model, diode-resistor logic, level-shifting and clamping diodes
BIPOLAR JUNCTION TRANSISTORS (BJTs): junction isolated and oxide isolated NPNs, multi-emitter, Schottky-clamped, lateral PNP, Ebers-Moll model, Gummel-Poon model, modes of operation, SPICE model, IC resistors and diodes

LECTURE 3: HPA: 4.1,4,8,12,17,23; 5.1,6,11,23,27
INTRODUCTION TO BJT DIGITAL CIRCUITS: analysis, BJT inverter, power dissipation
RESISTOR-TRANSISTOR LOGIC (RTL): inverter and noninverter, NOR gate, NAND gate, fan-out, power dissipation, active pull-up
SPICE simulation, DCTL and current hogging

LECTURE 4: HPA: 6.1,3,7,22,24,27
DIODE TRANSISTOR LOGIC (DTL): inverter, modified DTL, BJT modified, NAND gate, fan-out, power dissipation, SPICE simulation

LECTURE 5: HPA: 7.1,3,6,10,14,18,21
TRANSISTOR-TRANSISTOR LOGIC (TTL): inverter, charge removal, NAND gate, totem pole output, VTC, fanout, power dissipation, open collector, low power, high speed, SPICE simulation

LECTURE 6,7: HPA: 8.1,3,6,9,15,20,25; 9.1,5,13,15
SCHOTTKY TRANSISTOR-TRANSISTOR LOGIC (STTL): Schottky diodes, Schottky BJTs, STTL inverter, NAND gate, VTC, fan-out, power dissipation, low power LSTTL, SPICE simulation

LECTURE 8: HPA: 10.2,3,16,24
OTHER TTL GATES: AND gates, NOR gates, OR gates, AOI gates, XOR gates, Schmitt inverters and NAND gates, tri-state buffers

LECTURE 9: HPA: 11.1,6,8,14,19; 12.1,4,7,10
EMITTER-COUPLED LOGIC (ECL): BJT current switch, VTC, NOR/OR gate, output buffers, MECL I, fan-out, power dissipation, SPICE simulation. TEMPERATURE COMPENSATING ECL: MECL II, bias network, fan-out, power dissipation, SPICE simulation

LECTURE 10: HPA: 13.1,3,10,14; 14.1,5,8,10
MORE ECL: MECL III, ECL 10K, ECL100K, power dissipation, SPICE simulation

LECTURE 11: HPA: 15.2,3,5,6
OTHER ECL GATES: NOR/OR gates, collector dotting, series gating, NAND/AND gates, OR-AND gates, XNOR/XOR gates Schmitt triggers

SESSION 12: REVIEW AND PROBLEM SESSION

SESSION 13: EXAM 1

SESSION 14: EXAM 1 REVIEW AND INTRODUCTION TO MOSFETs

LECTURE 15: HPA:16.2,6,11,12;17.2,9,13,20;18.1,2,3,10
MOSFETs: metal gate, silicon gate, N- & P-channel, modes of operation, transconductance parameter, threshold voltage, capacitance, SPICE model, CMOS devices, IC caps, stacked MOSFETs
RESISTOR LOADED NMOS INVERTER: operation, graphical determination of VTC, calculation of critical voltages, power dissipation, SPICE simulation

LECTURE 16,17: 19.1,2,3,17; 20.1; 21.1,2,3,11
SATURATED ENHANCEMENT-ONLY LOADED NMOS INVERTER: same as R-loaded
LINEAR E-O LOADED NMOS INVERTER: same as R-loaded
ENHANCEMENT-DEPLETION LOADED NMOS INVERTER: same as R-loaded

LECTURE 18: HPA: 22.2,3,5,9,15,31,38,40,43,50
NMOS GATES: NOR, NAND, OR, AND, AOIs, OIAs, XOR/XNOR, transmission gates, Schmitt inverter

LECTURE 19,20: HPA: 23.1,2,3,4
CMOS INVERTER: operation, power dissipation, graphical determination of VTC, calculation of critical voltages, design of symmetric inverter or minimum size, inverter capacitance, dynamic response, SPICE simulation, latch-up, input clamping

LECTURE 21: HPA: 24.1,2,3,4,7,12,13,21,31,34,35
CMOS LOGIC GATES: NAND, NOR, AND, OR, AOI, OAI, XNOR/XOR

LECTURE 22 REVIEW FOR EXAM 2

LECTURE 23 EXAM 2

LECTURE 24: HPA: 25.1,2,4,7,11
CMOS TRI-STATE LOGIC GATES: high impedance Z-states, contention X-states, tri-state inverters, applications, transmission gates

LECT 25: HPA: 26.1,3,8,10,13,15; 27.1,3,5,7;28.2,4,8,16,19
CMOS SCHMITT TRIGGER GATES: inverter, operation and VTC, design, buffered, output, feedback, NAND gate. CMOS DRIVERS: cascaded inverters driving a load cap, multi-stage inverter driver, tri-state pad drivers, break-before-make circuit; DYNAMIC CMOS

LECTURE 26: HPA: 34.3,6,7,10; 35.2,5,7,10; 36.2,3,4,6
GaAs METAL SEMICONDUCTOR FETs (MESFETs): N-channel, E-D, E-O,
modes of operation, transconductance parameter, threshold
voltage, capacitance, SPICE simulation
DIRECT COUPLED NMESFET INVERTER (DCFL): E-O inverter, operation,
graphical determination of VTC, calculation of critical voltages,
power dissipation, fan-out, SPICE simulation SCHOTTKY DIODE
NMESFET LOGIC (SDFL) INVERTER: E-D inverters, operation, calcu-
lation of critical voltages, power dissipation, fan-out, SPICE
simulation. BUFFERED NMESFET LOGIC (BFL) INVERTER: same as SDFL
inverter.

LECTURE 27: HPA: 37.1,2,3,4; 38.1,2,3,9
GaAs LOGIC FAMILY GATES: DCFL NOR, NAND and OR GATES, SDFL NOR
and NAND gates, BFL NOR and NAND gates, complex AOI & OIA gates,
DCFL XOR, other OR/NOR gates

LECTURE 28/29: HPA: 32&33 All odd problems
SEMICONDUCTOR READ ONLY AND STATIC RANDOM ACCESS MEMORIES

LECTURE 30 EXAM 3

FINAL EXAM TO BE ANNOUNCED

CHAPTER 1 SOLUTIONS

1.1 (a) $V_{OH} = 3V$, $V_{OL} = 0.2V$, $V_{IL} = 0.7V$, $V_{IH} = 0.8V$, $V_M = 0.78V$

(b) $V_{LS} = V_{OH} - V_{OL} = 3 - 0.2 = 2.8V$

(c) $V_{TW} = V_{IH} - V_{IL} = 0.8 - 0.7 = 0.1V$

(d) $V_{NMH} = V_{OH} - V_{IH} = 3 - 0.8 = 2.2V$

$V_{NML} = V_{IL} - V_{OL} = 0.7 - 0.2 = 0.5V$

$V_{NSH} = V_{OH} - V_M = 3 - 0.75 = 2.25V$

$V_{NSL} = V_M - V_{OL} = 0.75 - 0.2 = 0.55V$

$V_{NIH} = V_{NSH} / V_{LS} = 2.25 / 2.8 = 0.8V$

$V_{NIL} = V_{NSL} / V_{LS} = 0.55 / 2.8 = 0.2V$

1.2 (a) $V_{OH} = 5V$, $V_{OL} = 0.4V$, $V_{IL} = 1.2V$, $V_{IH} = 1.4V$, $V_M = 1.36V$

(b) $V_{LS} = V_{OH} - V_{OL} = 5 - 0.4 = 4.6V$

(c) $V_{TW} = V_{IH} - V_{IL} = 1.4 - 1.2 = 0.2V$

(d) $V_{NMH} = V_{OH} - V_{IH} = 5 - 1.4 = 3.6V$

$V_{NML} = V_{IL} - V_{OL} = 1.2 - 0.4 = 0.8V$

$V_{NSH} = V_{OH} - V_M = 5 - 1.36 = 3.64V$

$V_{NSL} = V_M - V_{OL} = 1.36 - 0.4 = 0.96V$

$V_{NIH} = V_{NSH} / V_{LS} = 3.64 / 4.6 = 0.79V$

$V_{NIL} = V_{NSL} / V_{LS} = 0.96 / 4.6 = 0.21V$

1.3 (a) $V_{OH} = -0.8V$, $V_{OL} = -1.6V$, $V_{IL} = -1.2V$, $V_{IH} = -1V$, $V_M = -1.12V$

(b) $V_{LS} = V_{OH} - V_{OL} = -0.8 - (-1.6) = 0.8V$

(c) $V_{TW} = V_{IH} - V_{IL} = -1 - (-1.2) = 0.2V$

(d) $V_{NMH} = V_{OH} - V_{IH} = -0.8 - (-1) = 0.2V$

$V_{NML} = V_{IL} - V_{OL} = -1.2 - (-1.6) = 0.4V$

$V_{NSH} = V_{OH} - V_M = -0.8 - (-1.12) = 0.32V$

$V_{NSL} = V_M - V_{OL} = -1.12 - (-1.6) = 0.48V$

1.3 (CONT'D)

CHAPTER 1 SOLUTIONS (CONT)

$$V_{NIH} = V_{NSH} / V_{LS} = 0.32 / 0.8 = 0.4V$$

$$V_{NIL} = V_{NSL} / V_{LS} = 0.48 / 0.8 = 0.6V$$

1.4

$$(a) V_{OH} = 4.3V \quad V_{OL} = 0.2V \quad V_{IL} = 1.9V \quad V_{IH} = 2.1V \quad V_m = 1.99V$$

$$(b) V_{LS} = V_{OH} - V_{OL} = 4.3 - 0.2 = 4.1V$$

$$(c) V_{TW} = V_{IH} - V_{IL} = 2.1 - 1.9 = 0.2V$$

$$(d) V_{NMH} = V_{OH} - V_{IH} = 4.3 - 2.1 = 2.2V$$

$$V_{NML} = V_{IL} - V_{OL} = 1.9 - 0.2 = 1.7V$$


$$V_{NSH} = V_{OH} - V_m = 4.3 - 1.99 = 2.31V$$

$$V_{NSL} = V_m - V_{OL} = 1.99 - 0.2 = 1.79V$$

$$V_{NIH} = V_{NSH} / V_{LS} = 2.31 / 4.1 = 0.56V$$

$$V_{NIL} = V_{NSL} / V_{LS} = 1.79 / 4.1 = 0.44V$$

1.5

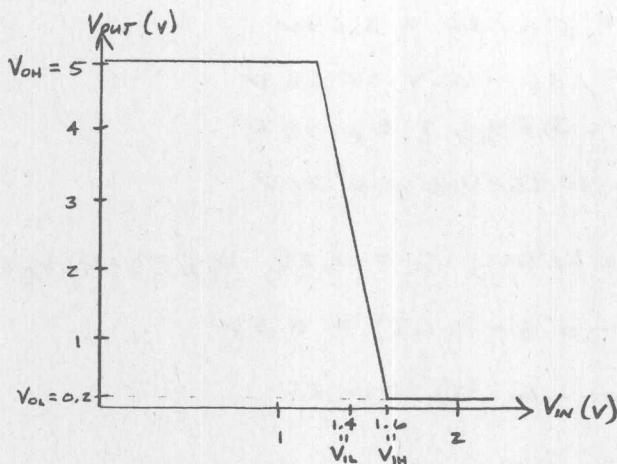


$$V_{LS} = V_{OH} - V_{OL} = 5 - 0.2 = 4.8V$$

$$V_{TW} = V_{IH} - V_{IL} = 1.6 - 1.4 = 0.2V$$

$$V_{NMH} = V_{OH} - V_{IH} = 5 - 1.6 = 3.4V$$

$$V_{NML} = V_{IL} - V_{OL} = 1.4 - 0.2 = 1.2V$$

1.6

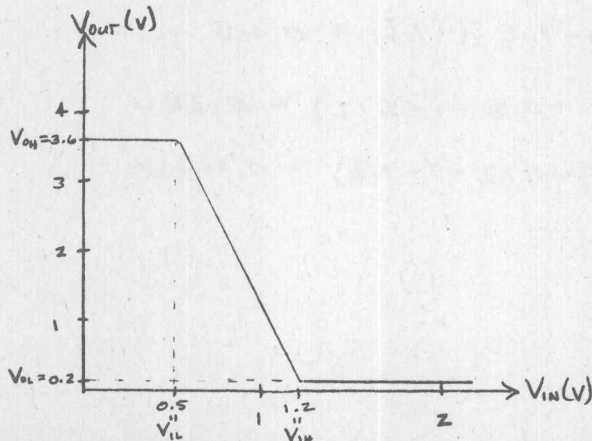

$$V_{LS} = V_{OH} - V_{OL} = 3.6 - 0.2 = 3.4V$$


$$V_{TW} = V_{IH} - V_{IL} = 1.2 - 0.5 = 0.7V$$

$$V_{NMH} = V_{OH} - V_{IH} = 3.6 - 1.2 = 2.4V$$

$$V_{NML} = V_{IL} - V_{OL} = 0.5 - 0.2 = 0.3V$$

CHAPTER 1 SOLUTIONS (CONT)

1.7

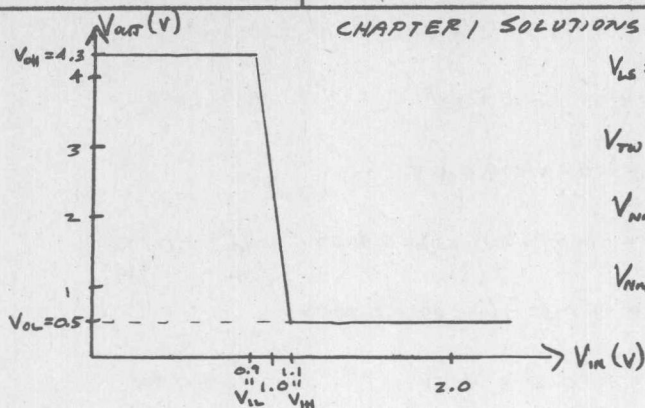


$$V_{LS} = V_{OH} - V_{OL} = 4.3 - 0.5 = 3.8V$$

$$V_{TW} = V_{IH} - V_{IL} = 1.1 - 0.9 = 0.2V$$

$$V_{NMH} = V_{OH} - V_{IH} = 4.3 - 1.1 = 3.2V$$

$$V_{NML} = V_{IL} - V_{OL} = 0.9 - 0.5 = 0.4V$$

1.8

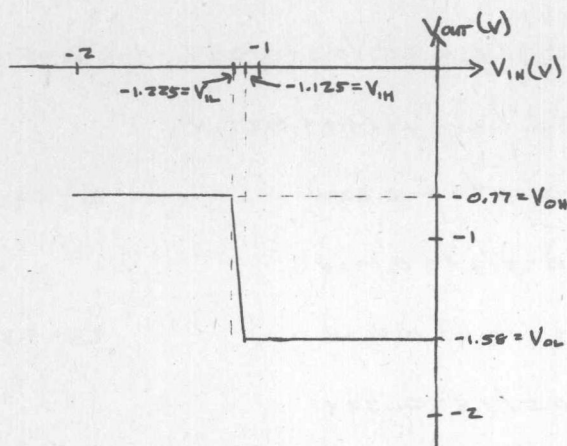


$$V_{LS} = V_{OH} - V_{OL} = -0.77 - (-1.58) = 0.81V$$

$$V_{TW} = V_{IH} - V_{IL} = -1.125 - (-1.225) = 0.1V$$

$$V_{NMH} = V_{OH} - V_{IH} = -0.77 - (-1.125) = 0.355V$$

$$V_{NML} = V_{IL} - V_{OL} = -1.225 - (-1.58) = 0.355V$$

1.9

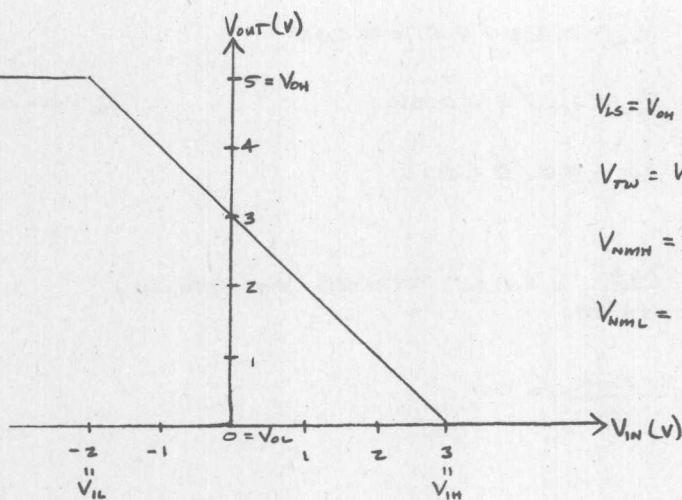

$$V_{LS} = V_{OH} - V_{OL} = 5 - 0 = 5V$$

$$V_{TW} = V_{IH} - V_{IL} = 3 - (-2) = 5V$$

$$V_{NMH} = V_{OH} - V_{IH} = 5 - 3 = 2V$$

$$V_{NML} = V_{IL} - V_{OL} = -2 - 0 = -2V$$

1.10

a) PROBLEM 1.5

$$V_{NSH} = V_{OH} - V_m = 5 - 1.5 = 3.5V$$

$$V_m = 1.5V$$

$$V_{NSL} = V_m - V_{OL} = 1.5 - 0.2 = 1.3V$$

PROBLEM 1.6

$$V_{NSH} = 3.6 - 0.85 = 2.75V$$

$$V_m = 0.85$$

$$V_{NSL} = 0.85 - 0.2 = 0.65V$$

1.10 (CONT)

CHAPTER 1 SOLUTIONS (CONT)

PROBLEM 1.7

$$V_{NSH} = 4.3 - 1.0 = 3.3V$$

$$V_m = 1.0V$$

$$V_{NSL} = 1.0 - 0.5 = 0.5V$$

PROBLEM 1.8

$$V_{NSH} = -0.77 - (-1.175) = 0.405V \quad V_m = -1.175$$

$$V_{NSL} = -1.175 - (-1.58) = 0.405V$$

PROBLEM 1.9

$$V_{NSH} = 5 - 0.5 = 4.5V$$

$$V_m = 0.5V$$

$$V_{NSL} = 0.5 - 0 = 0.5V$$

(b) PROBLEM 1.5

$$V_{NIH} = V_{NSH} / V_{LS} = 3.5 / 4.8 = 0.729V$$

$$V_{LS} = 5 - 0.2 = 4.8V$$

$$V_{NIL} = V_{NSL} / V_{LS} = 1.3 / 4.8 = 0.271V$$

PROBLEM 1.6

$$V_{NIH} = 2.75 / 3.4 = 0.809V$$

$$V_{LS} = 3.6 - 0.2 = 3.4V$$

$$V_{NIL} = 0.65 / 3.4 = 0.191V$$

PROBLEM 1.7

$$V_{NIH} = 3.3 / 3.8 = 0.868V$$

$$V_{LS} = 4.3 - 0.5 = 3.8V$$

$$V_{NIL} = 0.5 / 3.8 = 0.132V$$

PROBLEM 1.8

$$V_{NIH} = 0.405 / 0.81 = 0.50V$$

$$V_{LS} = -0.77 - (-1.58) = 0.81V$$

$$V_{NIL} = 0.405 / 0.81 = 0.50V$$

PROBLEM 1.9

$$V_{NIH} = 4.5 / 5 = 0.9V$$

$$V_{LS} = 5 - 0 = 5V$$

$$V_{NIL} = 0.5 / 5 = 0.1V$$

1.11

$$N_{LOW} = \frac{I_{OUT}(LOW)}{I_{IN}(LOW)} = \frac{7mA}{124\mu A} = 56.45 \Rightarrow 56 \text{ (MAX. FAN OUT)}$$

$$N_{HIGH} = \frac{I_{OUT}(HIGH)}{I_{IN}(HIGH)} = \frac{12mA}{0} = \infty$$

1.12

$$N_{LOW} = \frac{4.2mA}{0} = \infty$$

$$N_{HIGH} = \frac{4mA}{240\mu A} = 16.67 \Rightarrow 16 \text{ (MAX. FAN OUT)}$$

CHAPTER 1 SOLUTIONS (CONT)

$$1.13 N_{\text{LOW}} = \frac{57.5 \text{ mA}}{1.09 \text{ mA}} = 52.75 \Rightarrow 52 \text{ (MAX. FAN OUT)}$$

$$N_{\text{HIGH}} = \infty$$

$$1.14 N_{\text{LOW}} = \frac{79.3 \text{ mA}}{1 \text{ mA}} = 79.3 \Rightarrow 79 \text{ (MAX. FAN OUT)}$$

$$N_{\text{HIGH}} = \infty$$


$$1.15 N_{\text{LOW}} = \frac{199 \text{ mA}}{1.32 \text{ mA}} = 150.76 \Rightarrow 150 \text{ (MAX FAN OUT)}$$

$$N_{\text{HIGH}} = \infty$$

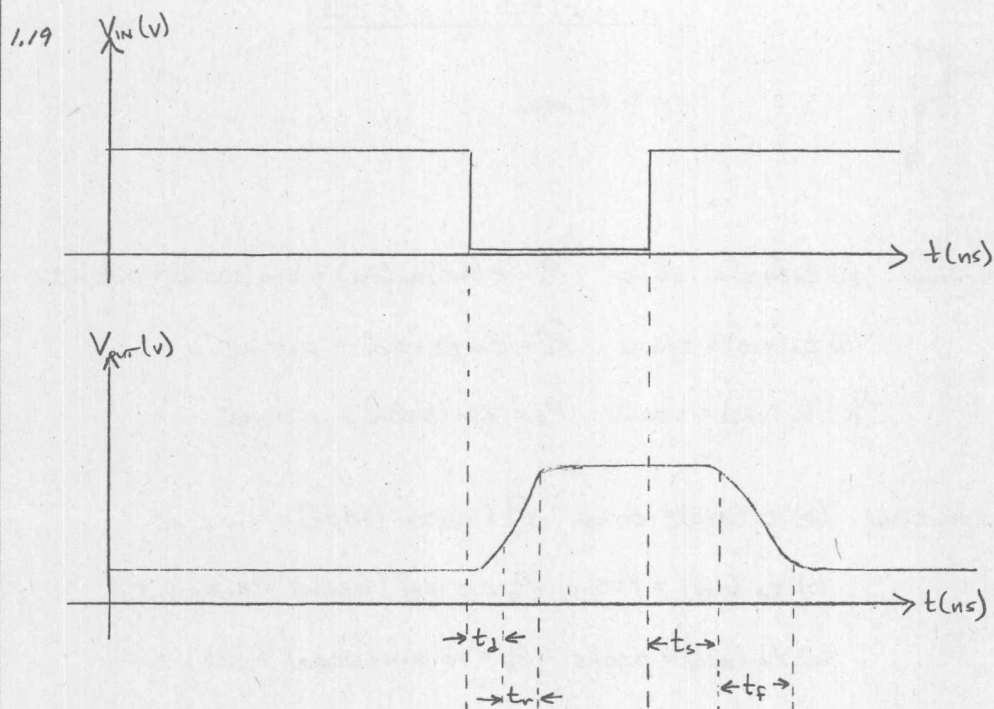1.16 YES! I_{OL} AND I_{IL} ARE BOTH IN. THIS IS PHYSICALLY IMPOSSIBLE.

$$1.17 t_d \approx 20\text{s} \quad t_s \approx 20\text{s} \quad t_r \approx t_f \approx 15\text{s} \quad t_{PHL} \approx t_{PLH} \approx 27.5\mu\text{s} \quad t_p(\text{AVG}) = 27.5\mu\text{s}$$

$$1.18 t_d \approx 20\text{s} \quad t_s \approx 20\text{s} \quad t_r \approx 40\text{s} \quad t_f \approx 20\text{s} \quad t_{PHL} \approx t_{PLH} \approx 27.5\mu\text{s} \quad t_p(\text{AVG}) = 27.5\mu\text{s}$$



WHERE, $t_r = 10\text{ns}$ AND $t_f = 30\text{ns}$


CHAPTER 1 SOLUTIONS (CONT)

1.20 SAME SKETCH AS #19, BUT WITH $t_r = 5\text{ns}$ AND $t_f = 7\text{ns}$.

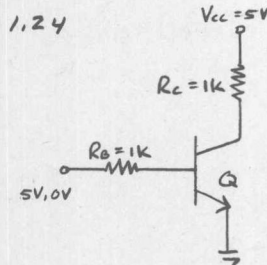1.21 SAME SKETCH AS #19, BUT WITH $t_r = 2\text{ns}$ AND $t_f = 3\text{ns}$.

$$1.22 P_{cc}(\text{AVG}) = \frac{I_{cc}(\text{OH}) + I_{cc}(\text{OL})}{2} V_{cc} = \frac{(4.2\text{mA} + 1.7\text{mA})}{2} (5) = 14.75\text{mW}$$

$$1.23 P_{cc}(\text{AVG}) = \frac{(0.52\text{mA} + 4.2\text{mA})}{2} (5) = 1.41\text{mW}$$



$$P_{\text{SUPPLIED}} = \frac{P_{\text{BISS FOR Q LUTOFF}} + P_{\text{BISS FOR Q SAT}}}{2}$$

$$= \frac{0 + 5 \left(\frac{5-0.7}{2} \right) - 5 \left(\frac{5-0.2}{2} \right)}{2}$$

$$= 22.75\text{mW}$$

1.25 $P(\text{AVG}) = 2\text{mW}$ (a) $t_p(\text{AVG}) = 100\text{ns}$ $P_0 = P(\text{AVG}) t_p(\text{AVG}) = 2\text{m}(100\text{n}) = 0.2\text{nJ}$

(b) $t_p(\text{AVG}) = 250\text{ns}$ $P_0 = 2\text{m}(250\text{n}) = 0.5\text{nJ}$

(c) $t_p(\text{AVG}) = 500\text{ns}$ $P_0 = 2\text{m}(500\text{n}) = 1.0\text{nJ}$

1.26 $P(\text{AVG}) = 10.2\text{mW}$ (a) $t_p(\text{AVG}) = 100\text{ns}$ $P_0 = 10.2\text{m}(100\text{n}) = 1.02\text{nJ}$

(b) $t_p(\text{AVG}) = 250\text{ns}$ $P_0 = 10.2\text{m}(250\text{n}) = 2.55\text{nJ}$

(c) $t_p(\text{AVG}) = 500\text{ns}$ $P_0 = 10.2\text{m}(500\text{n}) = 5.1\text{nJ}$

CHAPTER 2 SOLUTIONS

2.1 SEE FIGURE 2.2 (a)

2.2 SEE FIGURE 2.2 (b)

2.3 THE TYPE OF METAL MOST OFTEN USED IN SCHOTTKY MN SILICON DIODES IS PLATINUM SILICIDE (Pt_2Si_2) WHICH PROVIDES A BARRIER TO ELECTRON FLOW IN ONE DIRECTION.

THIS IS ACCOMPLISHED THROUGH THE DEPOSITION OF PT ON Si AND HEATING (ANNEALING) AT 600°C TO FORM Pt_2Si_2 .

2.4 $I_0 = 1\text{mA}$ $V_0 = 0.7\text{V}$ $\phi_T = 25.9\text{mV}$ (AT ROOM TEMP.)

$$I_b = I_s (e^{V_0/\phi_T} - 1)$$

$$I_s = \frac{I_0}{e^{V_0/\phi_T} - 1} = \frac{1\text{m}}{e^{0.7/25.9\text{m}} - 1} = 1.83 \times 10^{-15}\text{A}$$

2.5 AT ROOM TEMP.:

$$V_1 \rightarrow I_1$$

$$V_2 \rightarrow 10 I_2$$

$$I_1 = 10 I_2$$

$$\frac{I_1}{I_2} = 10 = \frac{e^{40V_1}}{e^{40V_2}} = e^{40(V_1 - V_2)}$$

$$\ln 10 = \ln e^{40(V_1 - V_2)}$$

$$\ln 10 = 40(V_1 - V_2)$$

$$(V_1 - V_2) = 0.06\text{V}$$

2.6


(a) $I_{01} = I_{s1} (e^{V_{01}/\phi_T} - 1)$

$$I_{02} = I_{s2} (e^{V_{02}/\phi_T} - 1)$$

$$V_{01} + V_{02} = 1$$

$$V_{01} = 1 - V_{02}$$
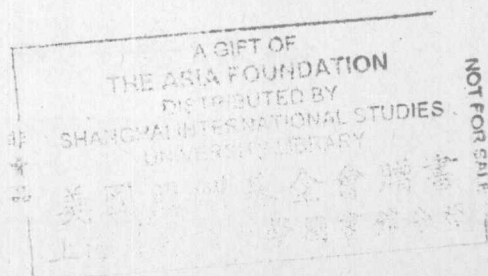
$$I_{01} = I_{02} \text{ (SERIES CIRCUIT)}$$



2.6 (CONT'D)

CHAPTER 2. SOLUTIONS (CONT)

$$I_{s1} (e^{V_{D1}/\phi_T} - 1) = I_{s2} (e^{V_{D2}/\phi_T} - 1)$$

$$I_{s1} (e^{(1-V_{D2})/\phi_T} - 1) = I_{s2} (e^{V_{D2}/\phi_T} - 1)$$

1 IS NEGLIGIBLE:

$$\frac{I_{s1}}{I_{s2}} = \frac{e^{V_{D2}/\phi_T}}{e^{(1-V_{D2})/\phi_T} - 1} = e^{\frac{1}{\phi_T}(2V_{D2} - 1)}$$

$$\ln\left(\frac{I_{s1}}{I_{s2}}\right) = \frac{1}{\phi_T}(2V_{D2} - 1)$$

$$1 + \phi_T \ln\left(\frac{I_{s1}}{I_{s2}}\right) = 2V_{D2}$$

$$\frac{1}{2} (1 + \phi_T \ln\left(\frac{I_{s1}}{I_{s2}}\right)) = V_{D2} = 0.44V$$

$$V_{D1} = 1 - V_{D2} = 1 - 0.44 = 0.56V$$

SUBSTITUTE VALUES INTO I_{D1} OR I_{D2} :

$$I_{D1} = I_{s1} (e^{V_{D1}/\phi_T} - 1) = 10^{-14} (e^{0.56/0.0259} - 1) = 0.02 \text{ mA}$$

$$(b) I_{D1} = I_{s1} (e^{V_{D1}/\phi_T} - 1)$$

$$I_{D2} = I_{s2} (e^{V_{D2}/\phi_T} - 1)$$

$$I_{D1} + I_{D2} = 1 \text{ mA}$$

$$V_{D1} = V_{D2} \text{ (PARALLEL CIRCUIT)}$$

$$I_{D2} = (1 \times 10^{-3}) - I_{D1}$$

$$\frac{I_{D1}}{I_{s1}} = \frac{I_{D2}}{I_{s2}}$$

$$\frac{I_{D1}}{I_{s1}} = \frac{(1 \times 10^{-3}) - I_{D1}}{I_{s2}}$$

$$I_{D1} + \frac{I_{s2}}{I_{s1}} I_{D1} = 1 \times 10^{-3}$$

$$I_{D1} = \frac{1 \times 10^{-3}}{(1 + I_{s2}/I_{s1})} = \frac{1 \times 10^{-3}}{(1 + 10^{-12}/10^{-14})} = 0.01 \text{ mA}$$

$$I_{D2} = (1 \times 10^{-3}) - (0.01 \times 10^{-3}) = 0.99 \text{ mA}$$

SUBSTITUTE CURRENT VALUES INTO EITHER EQUATION:

$$V_D = \ln\left(\frac{I_{D1}}{I_{s1}} + 1\right) \phi_T = \ln\left(\frac{0.01 \times 10^{-3}}{1 \times 10^{-14}} + 1\right) 0.0259 = 0.54V$$

CHAPTER 2 SOLUTIONS (CONT)

$$2.7(a) I_0 = I_s (e^{v_d/\phi_T} - 1)$$

$$I_s = \frac{I_0}{e^{v_d/\phi_T} - 1} = \frac{1\text{m}}{e^{0.3/25.9\text{m}} - 1} = 9.32\text{ nA (AT ROOM TEMP.)}$$

$$(b) I_0 = I_s (e^{v_d/\phi_T} - 1) = 10^{-14} (e^{0.3/25.9\text{m}} - 1) = 1.07\text{ nA (AT ROOM TEMP.)}$$

$$2.8 I_0 = I_s (e^{v_d/\phi_T} - 1), \text{ USE } I_s = 10\text{ nA}, \phi_T = 25.9\text{ mV AT ROOM TEMP.}$$

$$I_0 (V_0 = 0.1) = 10\text{ n} (e^{0.1/25.9\text{m}} - 1) = 0.465\text{ }\mu\text{A}$$

$$I_0 (V_0 = 0.2) = 10\text{ n} (e^{0.2/25.9\text{m}} - 1) = 0.02\text{ mA}$$

$$I_0 (V_0 = 0.5) = 10\text{ n} (e^{0.5/25.9\text{m}} - 1) = 2.42\text{ }\mu\text{A}$$

$$I_0 (V_0 = 0.7) = 10\text{ n} (e^{0.7/25.9\text{m}} - 1) = 5.466\text{ }\mu\text{A}$$

$$I_0 (V_0 = 0.8) = 10\text{ n} (e^{0.8/25.9\text{m}} - 1) = 259.7\text{ }\mu\text{A}$$

$$I_0 (V_0 = 1) = 10\text{ n} (e^{1/25.9\text{m}} - 1) = 586.3\text{ }\mu\text{A}$$

$$I_0 (V_0 = 2) = 10\text{ n} (e^{2/25.9\text{m}} - 1) = 3.44 \times 10^{-25}\text{ A}$$

$$2.9 I_0 = I_s (e^{v_d/\phi_T} - 1), \text{ USE } \phi_T = 0.0259\text{ V AND } I_s = 10^{-14}\text{ A}$$

$$I_0 (V_0 = 0.1) = 10^{-14} (e^{0.1/0.0259} - 1) = 465\text{ fA}$$

$$I_0 (V_0 = 0.2) = 10^{-14} (e^{0.2/0.0259} - 1) = 22.6\text{ pA}$$

$$I_0 (V_0 = 0.5) = 10^{-14} (e^{0.5/0.0259} - 1) = 2.42\text{ }\mu\text{A}$$

$$I_0 (V_0 = 0.7) = 10^{-14} (e^{0.7/0.0259} - 1) = 5.47\text{ mA}$$

$$I_0 (V_0 = 0.8) = 10^{-14} (e^{0.8/0.0259} - 1) = 259.7\text{ mA}$$

$$I_0 (V_0 = 1.0) = 10^{-14} (e^{1/0.0259} - 1) = 586.3\text{ A}$$

$$2.10 I_0 = I_s (e^{v_d/\phi_T} - 1), \text{ USE } \phi_T = 0.0259\text{ V AND } I_s = 10^{-14}\text{ A}$$

$$I_0 (V_0 = -1\text{m}) = 10^{-14} (e^{-1\text{m}/0.0259} - 1) = -0.379\text{ fA}$$

$$I_0 (V_0 = -2\text{m}) = 10^{-14} (e^{-2\text{m}/0.0259} - 1) = -0.743\text{ fA}$$

$$I_0 (V_0 = -10\text{m}) = 10^{-14} (e^{-10\text{m}/0.0259} - 1) = -3.20\text{ fA}$$

$$I_0 (V_0 = -200\text{m}) = 10^{-14} (e^{-200\text{m}/0.0259} - 1) = -9.99\text{ fA}$$


$$I_0 (V_0 = -500\text{m}) = 10^{-14} (e^{-500\text{m}/0.0259} - 1) = -10.0\text{ fA}$$

2.11 $I_s = 10^{-14} \text{ A}$ $\phi_T = 0.0259 \text{ V}$

$$I_0 (V_{DS} = 1) = 10^{-14} (e^{1/0.0259} - 1) = 586.3 \text{ A} \quad \ln I_0 = 6.37 \text{ A}$$

$$I_0 (V_{DS} = 2) = 10^{-14} (e^{2/0.0259} - 1) = 3.44 \text{ A} \quad \ln I_0 = 44.98 \text{ A}$$
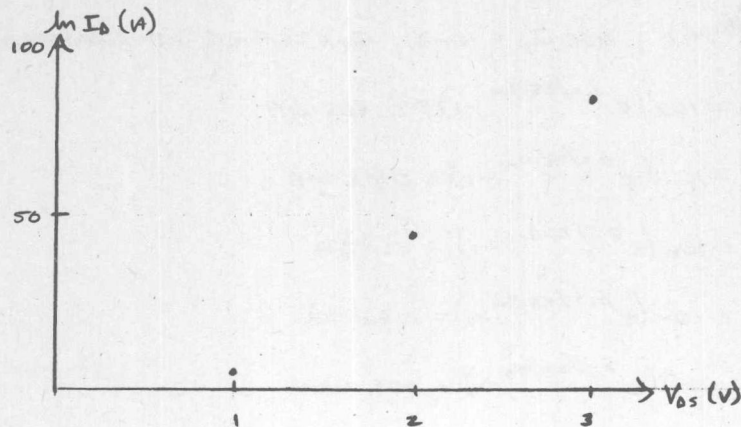
$$I_0 (V_{DS} = 3) = 10^{-14} (e^{3/0.0259} - 1) = 2.02 \times 10^{36} \text{ A} \quad \ln I_0 = 83.6$$



$$\ln I_0 = \ln I_s + \frac{q V_{DS}}{kT}$$

2.12 $I_0 = I_s (e^{V_D/\phi_T} - 1)$, USE $\phi_T = 0.0259 \text{ V}$ AND $I_s = 10^{-15} \text{ A}$

PROBLEM 2.9

$$I_0 (V_0 = 0.1) = 10^{-15} (e^{0.1/0.0259} - 1) = 46.5 \text{ fA}$$

$$I_0 (V_0 = 0.2) = 10^{-15} (e^{0.2/0.0259} - 1) = 2.26 \text{ pA}$$

$$I_0 (V_0 = 0.5) = 10^{-15} (e^{0.5/0.0259} - 1) = 0.242 \text{ nA}$$

$$I_0 (V_0 = 0.7) = 10^{-15} (e^{0.7/0.0259} - 1) = 0.547 \text{ nA}$$

$$I_0 (V_0 = 0.8) = 10^{-15} (e^{0.8/0.0259} - 1) = 25.97 \text{ nA}$$

$$I_0 (V_0 = 1) = 10^{-15} (e^{1/0.0259} - 1) = 58.63 \text{ A}$$

PROBLEM 2.10

$$I_0 (V_0 = -1\text{m}) = 10^{-15} (e^{-1\text{m}/0.0259} - 1) = -0.0379 \text{ fA}$$

$$I_0 (V_0 = -2\text{m}) = 10^{-15} (e^{-2\text{m}/0.0259} - 1) = -0.0743 \text{ fA}$$

$$I_0 (V_0 = -10\text{m}) = 10^{-15} (e^{-10\text{m}/0.0259} - 1) = 0.82 \text{ fA}$$

$$I_0 (V_0 = -200\text{m}) = 10^{-15} (e^{-200\text{m}/0.0259} - 1) = -0.999 \text{ fA}$$

$$I_0 (V_0 = -500\text{m}) = 10^{-15} (e^{-500\text{m}/0.0259} - 1) = -1.0 \text{ fA}$$