

**Second Edition**

**JOHN M. DOYLE**

# **pulse fundamentals**

Updated to stress practical applications  
of modern solid-state devices and circuits to a wide variety  
of electronic instruments and systems.

73.767  
275

# ***PULSE***

# ***FUNDAMENTALS***

***2nd EDITION***

**John M. Doyle**

Prentice-Hall, Inc., Englewood Cliffs, New Jersey

**5504603**

*Library of Congress Cataloging in Publication Data*

DOYLE, JOHN M.

Pulse fundamentals.

(Prentice-Hall series in electronic technology)

1. Pulse techniques (Electronics) I. Title.

TK7835.D69 1973 621.3815'34 72-10886

ISBN 0-13-741116-2

© 1973 by  
Prentice-Hall, Inc.  
Englewood Cliffs, N.J.

All rights reserved. No part  
of this book may be reproduced  
in any form or by any means  
without permission in writing  
from the publisher.

DR 52 / 11

10 9 8 7 6 5 4 3 2 1

Printed in the United States of America

PRENTICE-HALL INTERNATIONAL, INC., *London*  
PRENTICE-HALL OF AUSTRALIA, PTY., LTD., *Sydney*  
PRENTICE-HALL OF CANADA, LTD., *Toronto*  
PRENTICE-HALL OF INDIA PRIVATE LIMITED, *New Delhi*  
PRENTICE-HALL OF JAPAN, INC., *Tokyo*

# ***PREFACE***

The second edition of this book bears little resemblance to its predecessor. The extensive changes were dictated, for the most part, by the continuing evolution of active devices. To reflect current practices, only solid-state devices are covered. The content has also been altered to comply with numerous requests for more quantitative information.

The reader is assumed to have completed courses in electric-circuit theory and bipolar transistor physics and circuits. The mathematical prerequisites are a working knowledge of algebra and trigonometry. Elementary forms of the differential and integral calculus are used occasionally where such use serves to enhance understanding. Thus the book should be readily understood by anyone engaged in a meaningful electronics program at the college level. It should also meet the requirements of graduate engineers, particularly those concerned with applications, who have not yet acquired suitable skills in this area.

Admittedly, some of the quantitative discussions are rather lengthy. In every such case, however, a careful step-by-step approach is used to provide sound insight into the operation of the device or circuit under investigation. A great deal of thought was given to the possibility of showing end equations only with detailed analyses contained in appendices. But appendices are often overlooked, and the resulting loss could far outweigh any advantages that may result from this approach.

The book is divided into two parts: (a) the steady-state and transient switching characteristics of selected devices and (b) switching and pulse circuits.

Devices included in Part 1 are the junction, avalanche, tunnel, backward, and semiconductor-metal junction diodes, the junction and insulated gate field-effect transistors, various thyristors, and the unijunction transistor. A separate chapter is devoted to integrated circuits. Attention is concentrated on the physical behavior of the devices. With this background, the reader should experience little difficulty in adapting any of the devices to any desired application. Without such knowledge, the capabilities of the industrial worker are definitely limited.

Part 2 is concerned with linear and nonlinear waveshaping, various amplifiers employed in pulse-type circuits, multivibrators, blocking oscillators, voltage comparators, voltage and current time-base generators, transmission gates, and basic counting circuits.

Throughout, the transistor is considered to be the prime active device. In Part 2 the discussion of transistor circuits is followed immediately by an investigation of counterpart circuits that use other devices covered in Part 1. This integrated approach should prove beneficial to the reader, for the similarities and differences between the various configurations is made apparent without delay.

Exercises are included at the end of each chapter and an answer book for all problems involving computation is available to qualified instructors upon written request to the publisher.

I am pleased to acknowledge my indebtedness to the many manufacturers who supplied information in the form of device characteristics and technical papers, the publishers who permitted excerpts from previously copyrighted publications, and to the reviewers whose comments led to numerous improvements in the book. An effort has been made to acknowledge all such assistance by appropriate notation in the references appearing at the end of each chapter.

As always, my wife Rita was ever ready to spend countless hours in helping with preparation of the manuscript, and it is to her that this book is dedicated.

*John M. Doyle*

*Amesbury, Mass.  
December, 1971*

# CONTENTS

## *Preface*

xv

## *1. Introduction*

1

- 1.1 Historical Developments 1
- 1.2 Typical Pulse Applications 2
- 1.3 Definitions 6
- 1.4 General Considerations 9
- 1.5 Digital Circuits 9
- 1.6 Decimal to Binary Conversions and Vice Versa 11
- 1.7 An Introduction to Logic Circuits 12

## *Part 1*

### *The Steady-State and Transient Switching Characteristics of Selected Devices*

## *2. Diodes*

19

- 2.1 The Ideal Switch 19
- 2.2 Deviations from the Ideal Switch 20
- 2.3 The Junction Diode 24
- 2.4 Temperature Dependence of Junction Characteristics 27
- 2.5 Reverse-Bias Breakdown 27
- 2.6 Transition (Barrier) Capacitance 29
- 2.7 Diode Resistance 30
- 2.8 Diode Forward-Recovery Time 32
- 2.9 Diode Reverse-Recovery Time 33
- 2.10 The Avalanche (Zener) Diode 36
- 2.11 The Tunnel Diode 38
- 2.12 The Backward Diode 42
- 2.13 Semiconductor-Metal Junction Diodes 43

### 3. *Junction and Field-Effect Transistors* 47

- 3.1 Operating Regions of a Transistor 47
- 3.2 Operation in the Cutoff Region 48
- 3.3 Operation in the Saturation Region 52
- 3.4 Maximum Ratings of Importance 54
- 3.5 Punch Through 58
- 3.6 The Transient Response 58
- 3.7 Avalanche Transistors 64
- 3.8 Field-Effect Transistors 69
- 3.9 The JFET 70
- 3.10 The FET in Switching Circuits 73
- 3.11 The IGFET (MOSFET) 75
- 3.12 MOSFET Symbols 78

### 4. *Thyristors and the UJT* 83

- 4.1 Four-Layer Diode 83
- 4.2 Mechanism of the Transition 85
- 4.3 Rate Effect 86
- 4.4 The Silicon-Controlled Switch 87
- 4.5 Turning Off the SCS 92
- 4.6 Rate Effect in the SCS 94
- 4.7 Response of the SCS 96
- 4.8 The Silicon-Controlled Rectifier 97
- 4.9 Firing Requirements for the SCR 98
- 4.10 Firing a Single SCR 100
- 4.11 The Unijunction Transistor 108
- 4.12 The Complementary Unijunction Transistor 112

### 5. *Integrated Circuits* 119

- 5.1 Classification of Integrated Circuits 119
- 5.2 Thin-Film Technology 120
- 5.3 Cathode Sputtering and Vacuum Evaporation 121
- 5.4 Thin-Film Components 121
- 5.5 Semiconductor Technology 124
- 5.6 Monolithic Circuits—Structure and Junction Isolation 125
- 5.7 Monolithic Components 126
- 5.8 IC Packages 127
- 5.9 Digital ICs 132
- 5.10 Linear ICs 140

## Part 2

# Switching and Pulse Circuits

### 6. Linear Waveshaping 145

- 6.1 The High-Pass  $RC$  Filter 145
- 6.2 The  $RC$  Time Constant 147
- 6.3 The Universal Time-Constant Chart 148
- 6.4 The Capacitor Discharge Period 149
- 6.5 A Mathematical Solution for  $v_c$  and  $i$  in  $RC$  Circuits 151
- 6.6 Network Response 153
- 6.7 Response to a Square Wave Input 156
- 6.8 Effects of Rise Time on Amplitude of Output Waveform 157
- 6.9 Response of the High-Pass  $RC$  Filter to a Ramp Voltage 158
- 6.10 The  $RC$  Differentiator 159
- 6.11 The Low-Pass  $RC$  Filter 162
- 6.12 Response of the Low-Pass  $RC$  Filter to a Pulse Input 162
- 6.13 Response of a Low-Pass  $RC$  Filter to a Square Wave Input 163
- 6.14 Response of a Low-Pass  $RC$  Filter to a Ramp Input 164
- 6.15 The  $RC$  Integrator 164
- 6.16  $RL$  Circuits 166
- 6.17  $RLC$  Circuits 167
- 6.18 Ringing Oscillator 170
- 6.19  $RLC$  Peaker 170

### 7. Pulse Transformers and Electromagnetic Delay Lines 175

- 7.1 Pulse Transformers 175
- 7.2 Response of Pulse Transformers 178
- 7.3 Electromagnetic Delay Lines: Introduction 182
- 7.4 Transmission Lines: General 182
- 7.5 Coefficient of Reflection 189
- 7.6 Cutoff Frequency 190
- 7.7 Distributed-Parameter Delay Lines 191
- 7.8 Lumped-Parameter Delay Lines 194
- 7.9 Pulse-Forming Networks: General 195
- 7.10 Switching Operations in Transmission-Line Circuits 195
- 7.11 Reflections at Line Terminals 197
- 7.12 Charging an Open-End Line 203
- 7.13 Pulse Formation by Discharge of an Open-End Line 206
- 7.14 Pulse Formation by a Shorted-End Line 207
- 7.15 Pulse-Forming Networks 208



<b>8.</b>	<b><i>Transistor Equivalent Circuits and Parameters</i></b>	<b>215</b>
8.1	The Hybrid Parameters—CB Configuration	215
8.2	Hybrid Parameters—CE Configuration	221
8.3	Hybrid Parameters—CC Configuration	223
8.4	Relating the $h^b$ , $h^e$ , and $h^c$ Parameters	224
8.5	A Comparison of Performance Quantities	224
8.6	The Hybrid- $\pi$ Parameters	225
<b>9.</b>	<b><i>Wideband Amplifiers</i></b>	<b>229</b>
9.1	A Universal-Response Curve for RC Coupled Amplifiers	229
9.2	Distortion	230
9.3	The RC Coupled Amplifier	231
9.4	Effects of Interelectrode Capacitances on Input Impedance at High Frequencies	238
9.5	Frequency Response and the Unbypassed Emitter	240
9.6	Gain-Bandwidth Product of a Resistively Loaded Amplifier	246
9.7	Transistor Figure of Merit	247
9.8	Pulse Rise Time as a Function of Bandwidth	248
9.9	High-Frequency Shunt Compensation	249
9.10	Series Compensation	255
9.11	Transient Response of Multistage Compensated Amplifiers	256
9.12	Low-Frequency Compensation	256
9.13	Feedback in Pulse Amplifiers	258
9.14	FET Wideband Amplifiers	261
9.15	Wideband Amplifiers Using FET-Bipolar Transistor Combinations	264
<b>10.</b>	<b><i>Other Amplifiers of Interest</i></b>	<b>275</b>
10.1	Direct-Coupled Transistor Amplifiers: General	275
10.2	Typical Circuit Configurations	275
10.3	Drift of a Single Stage	278
10.4	Gain Stability of a Single Stage	280
10.5	Typical Differential-Amplifier Circuit Configurations	280
10.6	Drift in the Differential Amplifier	286
10.7	Gain Stability in the Differential Amplifier	287
10.8	Chopper Amplifiers	288
10.9	Transistor Choppers	290
10.10	Chopper Transistor Characteristics	296
10.11	MOSFETs as Low-Level Choppers	300
10.12	An Integrated Circuit dc Amplifier	304

## 11. *Nonlinear Wave Shaping* 319

- 11.1 Series-Diode Clipper 319
- 11.2 Parallel-Diode Clipper 321
- 11.3 Biased-Diode Clipper 321
- 11.4 Zener-Diode Clippers 324
- 11.5 The Transistor Clipper 325
- 11.6 The Emitter-Coupled Clipper 326
- 11.7 Temperature Compensation in Diode-Clipper Circuits 328
- 11.8 Diode Clamping 329
- 11.9 Steady-State Behavior of a Diode Clamp 332
- 11.10 Practical Diode Clamps 335
- 11.11 Base Clamping 337
- 11.12 Keyed (Synchronized) Clamping 338
- 11.13 The CE Inductively Loaded Transistor Switch 340
- 11.14 The QC Inductively Loaded Transistor Switch 346
- 11.15 The CE Capacitively Loaded Transistor Switch 347
- 11.16 The Capacitively Loaded Emitter Follower 349
- 11.17 Collector-Catching Diodes 351
- 11.18 Nonsaturating Transistor Switches 352

## 12. *Astable Multivibrators* 355

- 12.1 Definitions 355
- 12.2 A Bipolar Transistor MV 356
- 12.3 Equivalent Circuits 358
- 12.4 Disadvantages of the Conventional Astable MV 359
- 12.5 A JFET Astable MV 360
- 12.6 A MOSFET Astable MV 361
- 12.7 Tunnel-Diode Astable MV 362
- 12.8 The SCS Astable MV 365
- 12.9 The UJT Astable MV 366
- 12.10 The Astable Emitter-Coupled MV 372
- 12.11 Synchronization of the MV 376
- 12.12 Applications 380

## 13. *Bistable Multivibrators* 385

- 13.1 Detailed Operation 385
- 13.2 Speed-Up Capacitors 388
- 13.3 Symmetrical Triggering of a Binary 391
- 13.4 Unsymmetrical Triggering of a Binary 393
- 13.5 Direct-Coupled Bistable MV 395

- 13.6 A JFET Binary 396
- 13.7 A MOSFET Binary 397
- 13.8 A Four-Layer Diode Binary 398
- 13.9 The UJT Binary 398
- 13.10 The Schmitt-Trigger Circuit: Basic Operation 402
- 13.11 Determination of the Upper- and Lower-Trip Points 403
- 13.12 Effects of Various Parameters on Operation of the Schmitt-Trigger Circuit 407
- 13.14 An Improved Form of the Bipolar Transistor Schmitt-Trigger Circuit 408
- 13.15 Pairing Bipolar Transistor Schmitt-Trigger Circuits 409
- 13.16 Binary Applications 411

## 14. Monostable Multivibrators 415

- 14.1 Detailed Operation—Bipolar Transistors 415
- 14.2 A MOSFET Monostable MV 420
- 14.3 The UJT Monostable MV 422
- 14.4 Tunnel-Diode Monostable MV 422
- 14.5 Bipolar Transistor Emitter-Coupled Monostable MV: General 424
- 14.6 Operation of the Emitter-Coupled Circuit 425
- 14.7 Modifications in the Basic Emitter-Coupled Monostable MV 428
- 14.8 Some Interesting Variations of the Monostable Circuit 431
- 14.9 Multiplying the Pulse Width of the Monostable MV 434
- 14.10 Applications of the Monostable MV 438

## 15. Blocking Oscillators 443

- 15.1 General 443
- 15.2 The Astable Blocking Oscillator 444
- 15.3 An Astable Circuit for Eliminating Overshoot 447
- 15.4 Monostable Blocking Oscillator 449
- 15.5 Triggering the Blocking Oscillator 450
- 15.6 Additional Methods for Controlling the Pulse Duration of a Blocking Oscillator 451
- 15.7 A Push-Pull Blocking Oscillator 454
- 15.8 Synchronized Operation of the Push-Pull Blocking Oscillator 458
- 15.9 A Crystal-Controlled Blocking Oscillator 458

<b>16.</b>	<b><i>Voltage Comparators</i></b>	<b>463</b>
16.1	A Current-Switch Comparator	463
16.2	A High-Speed Differential Comparator	468
16.3	The Schmitt-Trigger Regenerative Comparator	469
16.4	A Tunnel-Diode Comparator	471
16.5	Using Tunnel Diodes to Speed Up a Comparator	472
16.6	A Sense Detector	474
16.7	An Analog-to-Digital Converter	474
<b>17.</b>	<b><i>Voltage Time-Base Generators</i></b>	<b>477</b>
17.1	A Simple Astable Voltage-Sweep Circuit	477
17.2	The Gated-Clamp Transistor Sweep Circuit	479
17.3	The Bootstrap Sweep Generator: Basic Concepts	482
17.4	Detailed Operation of the Bootstrap Sweep Circuit	483
17.5	Double-Bootstrap Sweep	486
17.6	The Miller Sweep Circuit: Introduction	487
17.7	Miller Effect	488
17.8	The Operational Amplifier	489
17.9	Operation of Typical Miller Sweep Circuits	495
17.10	Hold-Off	498
<b>18.</b>	<b><i>Current Time-Base Generators</i></b>	<b>501</b>
18.1	The Basic Current-Sweep Circuit	501
18.2	The Requirement for a Trapezoidal Waveshape	503
18.3	A Trapezoidal Waveform Generator	505
18.4	Another Look at the Required Yoke Waveform	506
18.5	Generating the Impulse Approximation	507
18.6	A Practical Sawtooth Current Generator	508
18.7	A Practical Miller-Sweep Current Generator	510
<b>19.</b>	<b><i>Transmission Gates</i></b>	<b>515</b>
19.1	Unidirectional Diode Gate	515
19.2	The Coincidence Gate	517
19.3	Bidirectional Gates	519
19.4	Four-Diode Gate	521
19.5	Six-Diode Gate	522
19.6	A Simple Transistor Gate	523
19.7	A Two-Transistor Gate	524
19.8	Removing the Pedestal in the Output Waveform	524

**20. *Basic Counting Circuits* 529**

- 20.1 Terminology 529
- 20.2 A Serial-Up Counter 531
- 20.3 A Serial-Down Counter 533
- 20.4 Frequency Limitation of a Serial Counter 533
- 20.5 A FF Ring Counter 535
- 20.6 A UJT Ring Counter 536
- 20.7 A Tunnel-Diode Ring Counter 538
- 20.8 Parallel-Up Counter 539
- 20.9 Parallel-Down Counter 540
- 20.10 Modulus Counters 540
- 20.11 A Mod-10 (Decade) Counter 541

***APPENDIX A* 545**

An Abbreviated Table of Exponential Functions 545

***Index* 551**

# 1

## *Introduction*

Pulse circuits are defined as those circuits required for the generation and control of precisely timed waveforms. They differ widely from those used in radio communications equipment, in which the waveform of the operating voltage is usually sinusoidal or a simple combination of sinusoidal waves. Some pulse circuits are used to develop square, sawtooth, trapezoidal, or peaked waves of voltage, which are required in indicating, timing, and modulating circuits of television, radar equipment, and so forth. The circuit-operating conditions in most cases range from *full on* to *full off* and do not fall into the simple classifications of class *A*, *B*, and *C* operation. The circuits, therefore, are named for the function they perform rather than for their type of operation.

### *1.1 Historical Developments*

Pulses, in the form of dots and dashes, were used to convey intelligence by wire in the earliest days of electrical communication. Marconi used short and long pulses in his "wireless" to form the modulation envelope for radio-frequency energy.

The advent of the triode vacuum tube made possible modern radio communication and the transmission of intelligence by means of an amplitude-modulated carrier. In this scheme the prime-signal source is a sinusoidal-

signal generator. In modern technology many electronic systems have been developed that require the use of pulses as the prime-signal source.

## 1.2 Typical Pulse Applications

Pulses are used in radar, which is an electronic system that detects the presence, range, and direction of objects. The block diagram of a typical radar system is shown in Fig. 1-1. It consists of a timer, modulator, transmitter, transmit-receive (TR) switch, antenna, receiver, indicator, and power supply.

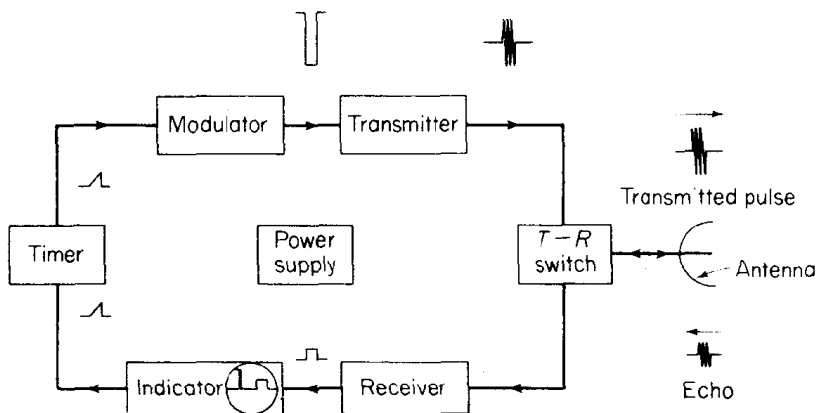


Figure 1-1. Block diagram of a radar set.

The timer synchronizes the indicator and transmitter circuits. At regular intervals it produces a pulse that causes the sweep (horizontal movement of the scanning spot) to start in the indicator. At the same instant, or after a precisely predetermined time, the timer produces a signal that is also applied to the modulator.

When the modulator receives the synchronizing timing pulse, it develops a high-voltage, high-power pulse that turns the transmitter on for a short time interval.

The transmitter is a very high frequency (vhf), high-power generator of radio-frequency (rf) energy. It produces a radio wave of constant frequency and amplitude during the short time during which it is turned on by the modulator.

The TR switch is operated electrically, and it effectively disconnects the antenna from the receiver during the production of the transmitter pulse and connects it to the transmitter. During the remainder of the operating period, the TR switch connects the antenna to the receiver.

The antenna acts as a radiator of the transmitter-produced energy when the transmitter is pulsed. A small portion of the radio wave transmitted

from the radar set travels to the object (*target*) and is reflected as shown in Fig. 1-1. The reflected waves, called *echoes*, are picked up by the antenna and conveyed to the receiver. The antenna is designed to be directive for both transmission and reception so that the *bearing* (direction) as well as the *range* (distance) of the target may be determined.

The receiver amplifies the echoes and provides *video* pulses, called *pips*, of sufficient amplitude to produce visual indications on the indicator.

The indicator can be regarded as an electrical stop watch that measures precisely the small time interval required for the transmitter pulses to travel to the target and for the echoes to return. Because the speed of propagation of radio waves is known with great accuracy, the range can be determined as accurately as the time interval can be measured.

Pulses are also used in radio *telemetry*. Here certain variables, such as changes in temperature of the outer casing of a rocket, are sensed and measured in flight. This information is then transmitted to a ground station where permanent records are made for analysis by engineers.

A simplified explanation of telemetry can be given with the help of Fig. 1-2. The output signal of a pickup device, termed a *transducer*, is shown as a sinusoidal waveform. This signal is applied to several contacts on the

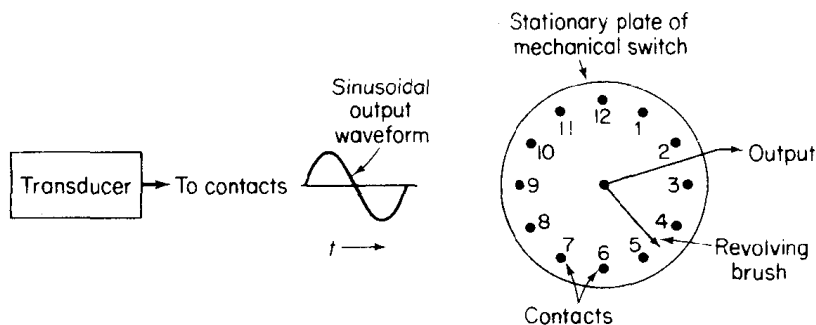


Figure 1-2. Sampling the output of a transducer.

stationary plate of a mechanical switch. A revolving brush then passes over each contact and samples the transducer output. Assuming that each contact is of uniform area and that the brush is revolving at a constant speed, the switch output is a series of pulses having uniform width, and the amplitude of each successive pulse is proportional to the corresponding amplitude of the signal wave, as shown in Fig. 1-3. The output of the switch is now *pulse-amplitude modulated*, abbreviated PAM. It is apparent that the successive pulses reproduce the signal wave rather faithfully. If the number of samples per second exceeds twice the highest frequency contained in the signal wave, the original signal can be reconstructed from the succession of pulses.

The PAM signal is next used to modulate an FM transmitter whose output is radiated by means of a suitable antenna.



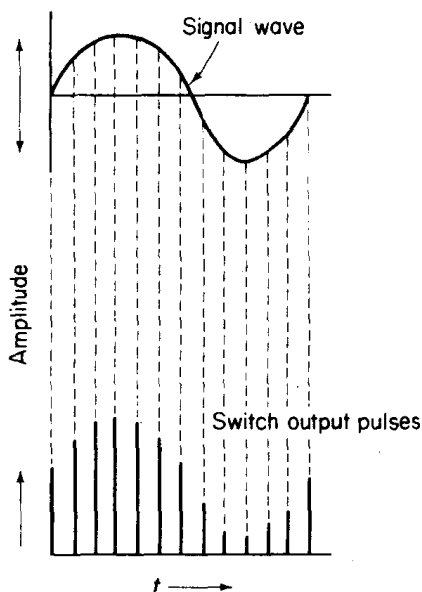


Figure 1-3. A pulse-amplitude modulated signal.

At the ground station the signal is picked up by a special type of antenna and applied to the input terminals of a highly sensitive receiver. The receiver amplifies the weak signal and separates the FM carrier signal from the PAM signal. The PAM output signal of the receiver is then applied to a detector, whose instantaneous output voltage is proportional to the instantaneous amplitude of the input voltage. This voltage is used to operate a mechanical reproducer that reconstructs an essentially faithful reproduction of the signal produced originally by the pickup transducer.

A reexamination of Fig. 1-3 shows considerable unallocated time between successive pulses. For example, the time required for each pulse may be  $10\ \mu\text{sec}$  and the elapsed time between pulses may be  $100\ \mu\text{sec}$ .

Use of this unallocated time introduces the possibility of *time-division multiplexing*, in which successive intervals of time are assigned to different signal (information) channels. In practice, this is exactly what is done in radio telemetering. One transducer may be used to record, say, temperature variations; separate transducers may measure other variables, such as atmospheric pressure and cosmic radiation. The output signal of each transducer is applied to successive contacts on the mechanical switch. This operation is shown in Fig. 1-4. The amplitudes of the successive output pulses from the switch are now proportional to the corresponding amplitudes of each signal wave.

At the output of the ground-station receiver, suitable filters are required to separate the various transducer signals from the composite PAM signal, but this filtering represents no great technical difficulty. Once separated, the individual signals are handled in the manner described previously.