

Applications of Analog Integrated Circuits

SIDNEY SOCLOF



Applications of Analog Integrated Circuits

SIDNEY SOCLOF

*California State University
Los Angeles*



232

PRENTICE-HALL, INC., Englewood Cliffs, NJ 07632

8750232

Library of Congress Cataloging in Publication Data

Soclof, Sidney.

Applications of analog integrated circuits.

(Prentice-Hall series in solid state physical electronics)

Includes bibliographies and index.

1. Analog electronic systems. 2. Integrated circuits. I. Title. II. Series.

TK7870.S529 1985

621.381'73

84-15026

ISBN 0-13-039173-5

ISSN 001

Editorial/production supervision and

interior design: *Ellen Denning*

Cover design: *Lundgren Graphics, Ltd.*

Manufacturing buyer: *Anthony Caruso*

© 1985 by Prentice-Hall, Inc., Englewood Cliffs, New Jersey 07632

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

ISBN 0-13-039173-5 01

PRENTICE-HALL INTERNATIONAL, INC., *London*

PRENTICE-HALL OF AUSTRALIA PTY. LIMITED, *Sydney*

EDITORIA PRENTICE-HALL DO BRASIL, LTDA., *Rio de Janeiro*

PRENTICE-HALL CANADA INC., *Toronto*

PRENTICE-HALL OF INDIA PRIVATE LIMITED, *New Delhi*

PRENTICE-HALL OF JAPAN, INC., *Tokyo*

PRENTICE-HALL OF SOUTHEAST ASIA PTE. LTD., *Singapore*

WHITEHALL BOOKS LIMITED, *Wellington, New Zealand*

Preface

This is a book on the characteristics and applications of analog integrated circuits. The integrated circuits discussed in this book are used in a wide variety of applications in the areas of communications, control systems, signal processing, optoelectronics, digital systems interfacing, and as transducers for temperature, pressure, magnetic fields, and light sensing. There is enough material in this book for a two-semester senior or graduate-level course. By suitable selection of material, this book can also serve quite well for just a one-semester course. The background and preparation needed for this book is two semesters of basic electronics. This should preferably include some introductory material on the basic operation and characteristics of operational amplifiers.

Chapter 1 is a compendium of representative examples of the applications of operational amplifiers. Also presented in this chapter are some examples of applications of voltage comparators, which are devices that are very closely related to operational amplifiers. Only applications material is presented here since the basic characteristics of operational amplifiers are covered in many other books.

Integrated-circuit voltage regulators are discussed in Chapter 2. In addition to a presentation of the basic theory, characteristics, and the protective circuitry of voltage regulators, there are examples of various types of voltage regulators given including adjustable-positive and negative regulators, three-terminal fixed regulators, and switching-mode regulators.

In Chapter 3, integrated-circuit power amplifiers are investigated. The power conversion efficiency and distortion of power amplifiers is considered and examples are given of integrated-circuit audio power amplifiers. Examples of power-operational amplifiers are also presented.

In Chapter 4, attention is turned to the high-frequency performance of integrated circuits with a discussion of wide bandwidth or video amplifiers. First there is a discussion of the performance of common-emitter, cascode, emitter-follower, and FET circuits at high frequencies. This is followed by a presentation of examples of video-amplifier integrated circuits. Then some examples of operational amplifiers that have very wide bandwidths and high slewing rates are given. At the end of the chapter, unity gain buffers are discussed.

Modulators, demodulators, and phase-detector integrated circuits are discussed in Chapter 5. These are very closely related topics since the same basic circuit can be used for all three functions. The chapter opens with an analysis of the basic circuit configuration that is used for these three functions. Then some applications examples are given including amplitude modulation and demodulation, frequency modulation and FM detection, frequency doubling, and phase detection.

Integrated circuits that are used to generate various types of waveforms are presented in Chapter 6. Examples of voltage-controlled oscillators in which the frequency can be varied by an input voltage are considered first, followed by a discussion of waveform generators for the production of square, triangular, pulse, and sinusoidal waveforms.

The phase-locked loops of Chapter 7 are an important element of many communications and signal processing systems. The basic operation of these devices are discussed first, followed by examples of various applications such as AM and FM detection, frequency synthesis, and stereo demodulation.

The nonlinear characteristics of transistors and diodes can be used to good advantage to make circuits capable of multiplication, division, squaring, square rooting, rms-to-dc conversion, logarithmic conversion, exponential conversion, and other functions. This is the subject of Chapter 8, where the basic principles and examples of circuits to perform these various operations are presented.

Most integrated circuits have electrical inputs and outputs. In Chapter 9 integrated-circuit transducers are presented in which there is a non-electrical input such as temperature, pressure, or magnetic field. The related topic of light-sensitive devices is presented in Chapter 15.

Analog-to-digital and digital-to-analog converters are essential elements for the communication between analog and digital systems. These integrated circuits are discussed in Chapter 10 and various examples are given.

In Chapter 11, analog switches and sample-and-hold circuits are analyzed. These circuits are used in various signal processing applications such as signal multiplexing and demultiplexing and are also used in conjunction with analog-to-digital converters.

A very different type of integrated circuit considered in this book is the charge transfer device of Chapter 12. The two basic types of charge transfer devices considered are the charge-coupled device and the bucket-brigade device. After a study of the basic principles of operation of these devices, a number of applications examples are presented.

There are many monolithic and hybrid integrated circuits that are rather specialized in application and these are presented in Chapter 13. These include instrumentation amplifiers, isolation amplifiers, micropower and low-voltage integrated circuits, high-voltage integrated circuits, frequency-to-voltage converters, companders, elec-

tronic attenuators, two-wire transmitters, tuned amplifiers, FM circuits, AM radio circuits, and integrated circuits for television.

The subject of Chapter 14 is not a specific integrated circuit, but rather the general topic of noise in integrated circuits and electronic systems. This is an important topic since electrical noise will set the lower limit on the detectability of signals. Various noise sources in electronic devices including bipolar transistors and field-effect transistors are first considered, followed by a noise analysis of differential amplifiers. Next, operational amplifiers are considered, and at the end of the chapter some examples of low-noise operational amplifiers are discussed.

An important area of applications for integrated circuits is in optoelectronics and this is the subject of Chapter 15. Topics included in this chapter are photodiodes and phototransistors, radiation detectors and radiation damage, optically-coupled isolators, optoelectronic analog signal transmission, slotted and reflective emitter-sensor modules, and linear and area image sensors. The last topic dealing with image sensors represents an increasingly important type of integrated circuit and is discussed at length.

At the end of every chapter, (except Chapter 13), there are problems representative of the material covered in the chapter. Also at the end of every chapter is a list of general references for further reading or study.

SIDNEY SOCLOF

**PRENTICE-HALL SERIES IN SOLID STATE
PHYSICAL ELECTRONICS**

Nick Holonyak, Jr., *Editor*

CHEO Fiber Optics
GREEN Solar Cells: Operating Principles, Technology, and System
Applications
HAUS Waves and Fields in Optoelectronics
NUSSBAUM Contemporary Optics for Scientists and Engineers
SOCLOF Analog Integrated Circuits
SOCLOF Applications of Analog Integrated Circuits
STREETMAN Solid State Electronic Devices, 2nd ed.
UMAN Introduction to the Physics of Electronics
VAN DER ZIEL Solid State Physical Electronics, 3rd ed.
VERDEYEN Laser Electronics

868037

Contents

| | |
|---|----|
| PREFACE | xi |
| 1 APPLICATIONS OF OPERATIONAL AMPLIFIERS AND VOLTAGE COMPARATORS | 1 |
| 1.1 Op-Amp Applications | 1 |
| 1.2 Voltage Comparator Circuit Applications | 24 |
| Problems | 27 |
| 2 VOLTAGE REGULATORS | 30 |
| 2.1 Output Resistance and Load Regulation | 31 |
| 2.2 Regulator within a Regulator Design | 34 |
| 2.3 Voltage Regulator Protection Circuitry | 35 |
| 2.4 Thermal Shutdown | 46 |
| 2.5 Adjustable Positive Voltage Regulator Example | 49 |
| 2.6 Three-Terminal Regulators (Fixed Regulators) | 60 |
| 2.7 Negative Voltage Regulators | 71 |
| 2.8 Switching Voltage Regulators | 73 |
| Problems | 93 |

3 POWER AMPLIFIERS

98

- 3.1 Basic Considerations 98
- 3.2 Class A Power Amplifier 99
- 3.3 Class B Power Amplifier 100
- 3.4 Class AB Push-Pull Output-Stage Examples 108
- 3.5 Single-Supply Audio Power Amplifier Example 109
- 3.6 IC Audio Power Amplifier Examples 112
- 3.7 Distortion in Push-Pull Class AB Power Amplifiers 123
- 3.8 Power Operational Amplifiers 126
- 3.9 Power MOSFETs 131
- Problems 133

4 VIDEO AMPLIFIERS

136

- 4.1 Transistor Frequency Response 137
- 4.2 Transistor Unity-Gain Frequency 140
- 4.3 Multistage Amplifier Bandwidth and Rise Time 142
- 4.4 Design Considerations for Video Amplifiers 143
- 4.5 Video-Amplifier Common-Emitter-Stage Example 144
- 4.6 Differential Video Amplifier Analysis: Type 733 145
- 4.7 Cascode-Amplifier Configuration 151
- 4.8 Use of Emitter-Follower Stages in Wide-Band Amplifiers 154
- 4.9 Differential Video Amplifier Example: CA3040 157
- 4.10 Wide-Bandwidth and Fast-Slewing Operational Amplifiers 161
- 4.11 Very Wide-Bandwidth Operational Amplifier: HA-2539 161
- 4.12 FET High-Frequency Amplifiers 163
- 4.13 Unity-Gain Buffers 165
- Problems 166

5 MODULATORS, DEMODULATORS, AND PHASE DETECTORS

171

- 5.1 Balanced Modulator-Demodulator Analysis 171
- 5.2 Conversion Transfer Conductance and Gain 176

| | | |
|----------|--|------------|
| 5.3 | Amplitude Modulation | 177 |
| 5.4 | Frequency Modulation | 182 |
| 5.5 | Frequency Doubler | 186 |
| 5.6 | Phase Detector Using the Balanced Modulator-Demodulator | 187 |
| | Problems | 189 |
| 6 | VOLTAGE-CONTROLLED OSCILLATORS AND WAVEFORM GENERATORS | 193 |
| 6.1 | Voltage-Controlled Oscillators | 193 |
| 6.2 | Waveform Generators | 202 |
| | Problems | 218 |
| 7 | PHASE-LOCKED LOOPS | 221 |
| 7.1 | Lock-In Range | 222 |
| 7.2 | Capture Range | 223 |
| 7.3 | The PLL as an FM Detector | 225 |
| 7.4 | PLL Frequency Synthesizer | 228 |
| 7.5 | PLL as an AM Detector | 228 |
| 7.6 | Stereo Demodulation | 230 |
| 7.7 | IC PLL Example: LM565 | 231 |
| 7.8 | PLL Design Example | 233 |
| | Problems | 234 |
| 8 | MULTIPLIERS, DIVIDERS, AND FUNCTION CONVERTERS | 237 |
| 8.1 | Characteristics of Multipliers | 237 |
| 8.2 | Multiplication Techniques | 239 |
| 8.3 | Logarithmic-Exponential Multiplier | 242 |
| 8.4 | Multifunction Converter | 248 |
| 8.5 | Analysis of the Four-Quadrant Variable Transconductance Multiplier | 256 |
| 8.6 | Logarithmic Conversion | 260 |
| | Problems | 268 |
| 9 | IC TRANSDUCERS: TEMPERATURE, MAGNETIC FIELD, AND PRESSURE | 273 |
| 9.1 | IC Temperature Sensors | 273 |
| 9.2 | IC Magnetic Field Sensors: The Hall Effect | 284 |

| | | | |
|-------|--|-----|-----|
| 9.3 | Pressure Transducers | 292 | |
| | Problems | 296 | |
| 10 | DIGITAL-TO-ANALOG AND ANALOG-TO-DIGITAL CONVERTERS | | 299 |
| 10.1 | Digital-to-Analog Converters | 299 | |
| 10.2 | Analog-to-Digital Converters | 323 | |
| | Problems | 344 | |
| 11 | ANALOG SWITCHES AND SAMPLE-AND-HOLD CIRCUITS | | 350 |
| 11.1 | Analog Switches | 350 | |
| 11.2 | Sample-and-Hold Circuits | 364 | |
| | Problems | 374 | |
| 12 | CHARGE-TRANSFER DEVICES: ANALOG DELAY LINES | | 377 |
| 12.1 | Charge-Coupled Devices | 377 | |
| 12.2 | Bucket-Brigade Devices | 387 | |
| 12.3 | Charge-Transfer Device Sampling Rate | 393 | |
| 12.4 | Applications of Charge-Transfer-Devices | 393 | |
| | Problems | 405 | |
| 13 | SPECIAL-FUNCTION INTEGRATED CIRCUITS | | 407 |
| 13.1 | Instrumentation Amplifiers | 407 | |
| 13.2 | Isolation Amplifiers | 409 | |
| 13.3 | Micropower Integrated Circuits: Transistor Operation at Low Current Levels | 411 | |
| 13.4 | High-Voltage Integrated Circuits | 418 | |
| 13.5 | Voltage-Sharing Circuits | 420 | |
| 13.6 | IC Power Transistors with Internal Protection Circuitry | 422 | |
| 13.7 | Transistor Geometry and Current Crowding | 425 | |
| 13.8 | Frequency-to-Voltage Converters | 427 | |
| 13.9 | Companders | 430 | |
| 13.10 | Electronic Attenuator | 432 | |
| 13.11 | Two-Wire Transmitter | 433 | |
| 13.12 | Tuned Amplifier Integrated Circuits | 436 | |
| 13.13 | FM Sound Circuit | 436 | |

| | | |
|-----------------|--|------------|
| 13.14 | FM Stereo Demodulator Integrated Circuit | 440 |
| 13.15 | AM Radio System Integrated Circuit | 442 |
| 13.16 | Integrated Circuits for Television: Chroma Demodulator | 446 |
| 13.17 | Active Filter ICs | 447 |
| 13.18 | Switched-Capacitor Filter ICs | 447 |
| 14 | NOISE IN INTEGRATED CIRCUITS AND ELECTRONIC SYSTEMS | 449 |
| 14.1 | Thermal Noise | 451 |
| 14.2 | Shot Noise | 455 |
| 14.3 | Comparison of Shot Noise and Thermal Noise | 456 |
| 14.4 | Transistor Noise | 457 |
| 14.5 | Noise of a Differential-Amplifier Circuit | 465 |
| 14.6 | Noise of a Darlington Compound Transistor | 467 |
| 14.7 | MOSFET Noise Characteristics | 468 |
| 14.8 | Op-Amp Noise Analysis | 469 |
| 14.9 | Low-Noise Op Amps | 472 |
| | Problems | 473 |
| 15 | OPTOELECTRONIC INTEGRATED CIRCUITS AND SYSTEMS | 477 |
| 15.1 | Applications of Optoelectronics | 477 |
| 15.2 | Photodiodes | 479 |
| 15.3 | Phototransistors | 482 |
| 15.4 | Radiation Detectors | 486 |
| 15.5 | Radiation Damage | 487 |
| 15.6 | Optically Coupled Isolators | 489 |
| 15.7 | Optoelectronic Analog Signal Transmission | 490 |
| 15.8 | Slotted and Reflective Emitter-Sensor Modules | 493 |
| 15.9 | Fiber Optics | 494 |
| 15.10 | Image Sensors | 500 |
| 15.11 | Charge-Coupled Devices for Image Sensing | 513 |
| | Problems | 526 |
| | APPENDIX PHYSICAL CONSTANTS, CONVERSION FACTORS, AND PARAMETERS | 533 |
| | INDEX | 535 |
| Contents | | ix |

Applications of Operational Amplifiers and Voltage Comparators

1

The operational amplifier (op amp) is a basic building block for many analog integrated-circuit (IC) systems and is useful in a very wide range of applications. In this chapter a number of op-amp applications are presented and briefly described. The equations presented for the op amp in this chapter are based on the assumption of an ideal op amp, with a very high open-loop gain. They do not take into account such effects as the input offset voltage, the input bias current, and the input offset current, nor is the effect of a finite open-loop gain and the frequency variation thereof considered.

A device closely related to the op amp is the voltage comparator. Some examples of circuits using voltage comparators are presented in this chapter.

A detailed description of the characteristics and internal circuitry of op amps and voltage comparators is beyond the scope of this book. Such descriptions may be found in many other books, as indicated by the references at the end of this chapter. Particular reference is made to *Analog Integrated Circuits*, by the present author, and *Analog Integrated Circuit Analysis and Design*, by Gray and Meyer.

For all the op-amp and voltage comparator circuits presented in this chapter, the usual convention with respect to inverting (−) and noninverting (+) input terminals will be used; that is, the inverting (−) input terminal is the upper input terminal and the noninverting (+) input is the lower input terminal.

1.1 OP-AMP APPLICATIONS

1. *Voltage follower* (Figure 1.1): This circuit produces a unity voltage gain with $V_o = V_s$. It is characterized by a very high input impedance Z_{IN} and a very low output impedance Z_o and is very useful as a buffer in coupling high-impedance sources to low-impedance loads.

8750232

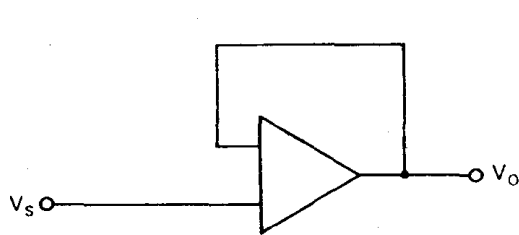


Figure 1.1 Voltage follower.

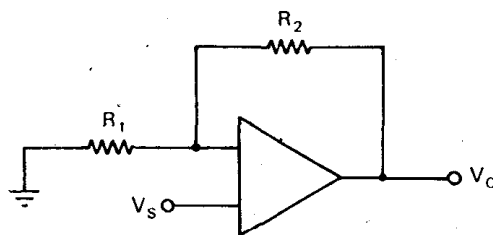


Figure 1.2 Noninverting amplifier.

2. *Noninverting amplifier* (Figure 1.2): For this circuit $V_O = (1 + R_2/R_1)V_S$. It has a very high Z_{IN} and a low Z_O .
3. *Inverting amplifier* (Figure 1.3): For this circuit $V_O = -(R_2/R_1)V_S$. It has an input impedance of $Z_{IN} = R_1$ and a very low output impedance.
4. *Summing amplifier* (Figure 1.4): For this circuit $V_O = -R_F(V_1/R_1 + V_2/R_2 + V_3/R_3 + V_4/R_4 + \dots)$. The input impedance with respect to the various input signals V_1, V_2, V_3, \dots will be R_1, R_2, R_3, \dots , respectively.
5. *Difference amplifier* (Figure 1.5): This circuit produces an output voltage that is directly proportional to the difference of the two input signals as given by $V_O = (R_2/R_1)(V_1 - V_2)$. The input impedance with respect to the V_1 input is $R_1 + R_2$, and for the V_2 signal input it is R_1 .
6. *Algebraic summation amplifier* (Figure 1.6): This circuit is an extension of the simple summing circuit, and the output voltage will represent an algebraic summation of the various input signals with coefficients determined by the resistance ratios.
7. *Current-to-voltage converter* (Figure 1.7): This circuit produces an output voltage that is directly proportional to the input current as given by $V_O = -I_S R_F$. The input impedance is equal to the feedback resistance divided by the amplifier open-loop gain A_{OL} as given by $Z_{IN} = R_F/A_{OL}$. In addition to this very low input resistance, it has a very low output impedance.
8. *Voltage-to-current converter* (Figure 1.8): The current I_L through the load resistance R_L is given by $I_L = V_S/R_1$ and is thus independent of R_L so that this circuit acts as a constant-current source. Since the current produced by

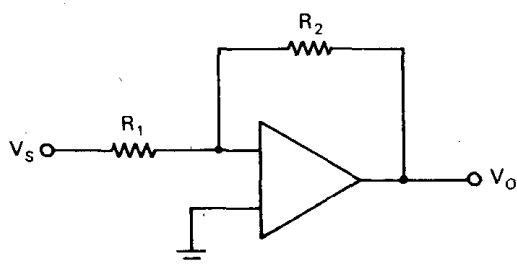


Figure 1.3 Inverting amplifier.

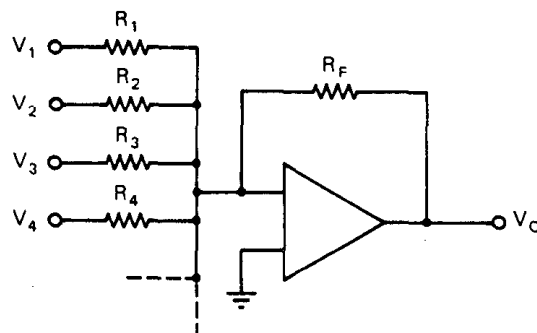


Figure 1.4 Summing amplifier.

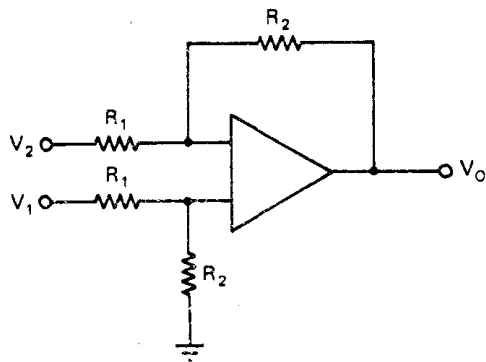


Figure 1.5 Difference amplifier.

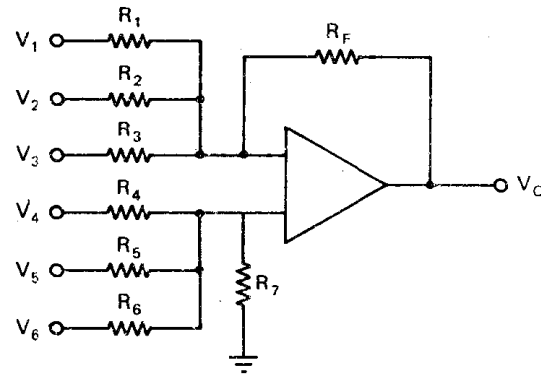


Figure 1.6 Algebraic summation amplifier.

this circuit is independent of the load resistance R_L but is directly proportional to the signal or control voltage V_S , this circuit is a voltage-controlled constant-current source. Note that neither end of the load resistance may be grounded.

9. *Constant-current source with grounded load (Howland current source)* (Figure 1.9): The current I_L through the load resistance R_L is given by $I_L = (V_1 - V_2)/R_1$ and is thus independent of R_L . Since the current is independent of R_L but is directly proportional to the input voltage differential, this circuit is a voltage-controlled constant-current source. Note that in this circuit a grounded load resistor may be used.
10. *Integrator* (Figure 1.10): The output voltage V_O will be proportional to the integral of the input voltage V_S over the integration period T as given by $V_O = -(1/R_1 C_1) \int_0^T V_S dt$. The integration period is controlled by switch S_1 , which opens at time $t = 0$ to start the integration process and closes at $t = T$ to terminate the integration and discharge the capacitor C_1 in preparation for the next integration cycle.

Resistor R_1 can be omitted and this circuit can be operated as a current integrator with $V_O = (1/C_1) \int_0^T I_S dt = Q/C_1$, where Q is the total electrical charge delivered to the circuit over the integration period.

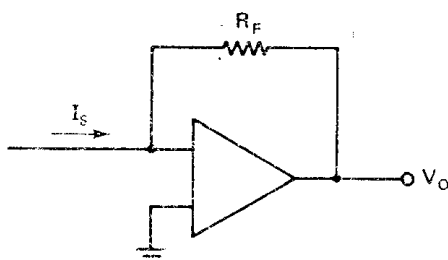


Figure 1.7 Current-to-voltage converter.

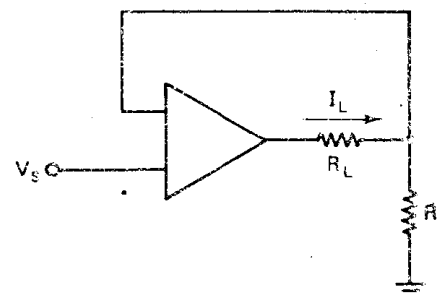


Figure 1.8 Voltage-to-current converter

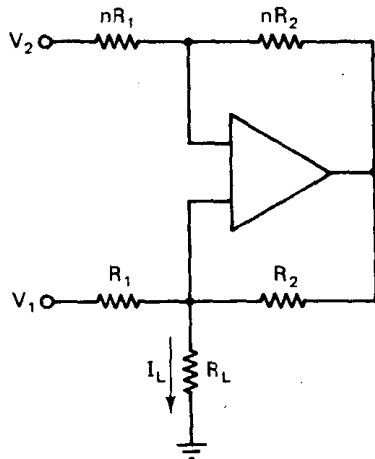


Figure 1.9 Constant-current source with grounded load (Howland current source).

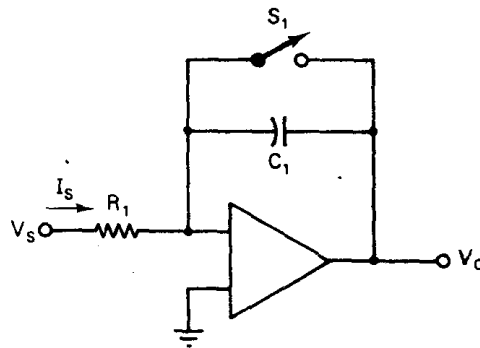


Figure 1.10 Integrator.

11. **Active low-pass filter** (Figure 1.11): In the frequency domain (sinusoidal excitation) the closed-loop gain of this circuit is given by $A_{CL} = -(R_F/R_1)/(1 + j\omega R_F C_F)$. It is a low-pass amplifier with a zero-frequency gain of $A_{CL}(0) = -R_F/R_1$ and a 3-dB bandwidth $BW = 1/(2\pi R_F C_F)$. In the time domain the response to a unit-step-function voltage input will be given by $V_O(t) = -(R_F/R_1)[1 - \exp(-t/R_F C_F)]$. For input signals whose period T is short compared to the $R_F C_F$ time constant ($T \lesssim R_F C_F/5$) the output voltage will be approximately the integral of the input voltage.

12. **Differentiator and active high-pass filter** (Figure 1.12): If $R_1 = 0$, this circuit will be an "ideal" differentiator with the output voltage being the time derivative of the input voltage as given by $V_O = -R_F C_1 (dV_S/dt)$. The use of a small-value resistor for R_1 may, however, be desirable to limit the high-frequency gain. An excessively high-frequency gain can be a problem due to the amplification of the noise voltage. The value of R_1 should be chosen such that the $R_1 C_1$ time constant will be small compared to the period of the input signal.

In the frequency domain (sinusoidal excitation) this circuit acts as a high-pass amplifier with a gain given by $A_{CL} = V_O/V_S = j\omega R_F C_1/(1 + j\omega R_1 C_1)$.

13. **Summing integrator** (Figure 1.13): This is a simple extension of the simple

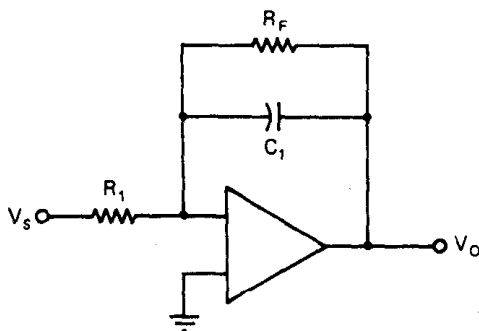


Figure 1.11 Active low-pass filter.

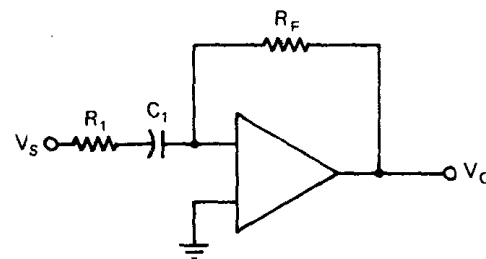


Figure 1.12 Differentiator and active high-pass filter.

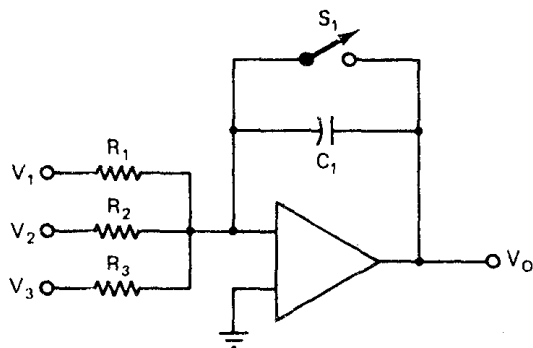


Figure 1.13 Summing integrator.

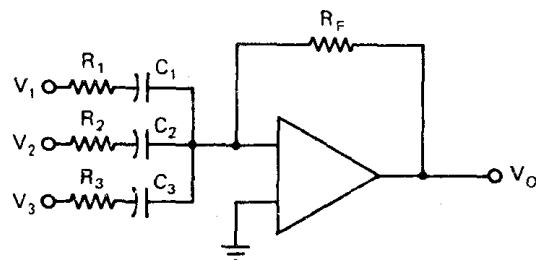


Figure 1.14 Summing differentiator.

integrator circuit. For this circuit

$$V_O = -\frac{1}{C_1} \int_0^T \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) dt$$

14. *Summing differentiator* (Figure 1.14): This is an extension of the simple differentiator circuit. For this circuit

$$V_O = -R_F \left(\frac{C_1 dV_1}{dt} + \frac{C_2 dV_2}{dt} + \frac{C_3 dV_3}{dt} \right)$$

if $R_1 C_1 \ll T$, $R_2 C_2 \ll T$, and $R_3 C_3 \ll T$, where T is the period of the input signal.

15. *Precision half-wave rectifier* (Figure 1.15): This circuit produces $V_O = V_S$ for $V_S > 0$ and $V_O = 0$ for $V_S \leq 0$. It acts as a precision half-wave rectifier, or detector for communications circuits, as a result of the forward voltage drop of the diode being divided by the amplifier open-loop gain.
16. *Precision full-wave rectifier (absolute-value circuit)* (Figure 1.16): For this circuit $V_O = |V_S|$. Again, in this case the effect of the forward voltage drop of the diode is essentially nullified as a result of the very high open-loop gain of the amplifier.
17. *Precision peak detector* (Figure 1.17): The output voltage will be equal to the highest positive peak value of the input voltage. Amplifier A_2 is used as a unity-gain buffer for load isolation so that the current drawn by the load will not discharge C_1 .
18. *Amplifier with electronic gain control* (Figure 1.18): This circuit is useful for

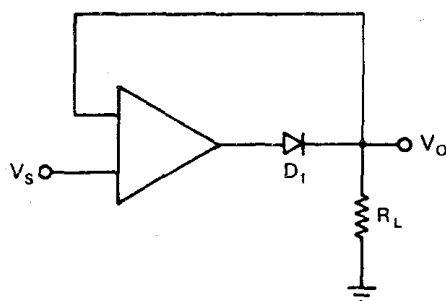


Figure 1.15 Precision half-wave rectifier.