

Digital Design for COMPUTER DATA ACQUISITION



**Charles D.
Spencer**

TP 334.7
S745-

Digital Design for Computer Data Acquisition

Charles D. Spencer

*Department of Physics
Ithaca College*



E2010001627

CAMBRIDGE UNIVERSITY PRESS

CAMBRIDGE

NEW YORK PORT CHESTER MELBOURNE SYDNEY

CAMBRIDGE UNIVERSITY PRESS

Cambridge, New York, Melbourne, Madrid, Cape Town, Singapore, São Paulo, Delhi

Cambridge University Press

The Edinburgh Building, Cambridge CB2 8RU, UK

Published in the United States of America by Cambridge University Press, New York

www.cambridge.org

Information on this title: www.cambridge.org/9780521102551

© Cambridge University Press 1990

This publication is in copyright. Subject to statutory exception and to the provisions of relevant collective licensing agreements, no reproduction of any part may take place without the written permission of Cambridge University Press.

First published 1990

This digitally printed version 2009

A catalogue record for this publication is available from the British Library

Library of Congress Cataloguing in Publication data

Spencer, Charles D.

Digital design for computer data acquisition / Charles D. Spencer

p. cm.

Includes bibliographical references.

ISBN 0-521-37199-6

1. Digital electronics. 2. Computer interfaces. 3. Automatic data collection systems. I. Title

TK7868.D5S65 1990

621.39'81-dc20

89-71224

ISBN 978-0-521-37199-5 hardback

ISBN 978-0-521-10255-1 paperback

Analog Devices® is a registered trademark of Analog Devices, Inc. Apple® and Applesoft BASIC® are registered trademarks of Apple Computer, Inc. Macintosh™ is a trademark licensed to Apple Computer, Inc. IBM PC®, XT™, AT®, and PS/2® are registered trademarks of International Business Machines, Inc. Intel™ is a trademark of Intel Corp. Microsoft® and QuickBASIC™ are registered trademarks of Microsoft Corp.

The circuits and software in this publication have been carefully tested and the author has double-checked all diagrams and program text. However, the author and publisher make no warranty for the circuits and software and shall not be liable for any computer damage that might result from their use.

Digital Design for Computer Data Acquisition

To Eulalah, Bob, and Susie

Preface

Advances in electronics during the past decade have led to a variety of computer based instruments. Manufacturers continually add flexibility to traditional research tools as they introduce devices not previously feasible. With measurements made by computers, keyboards replace switches, real-time graphics is common, powerful software is ready to analyze results, and data are easily saved and/or transferred to larger computers. Another important development is adaptability. Minor changes in software and/or hardware can significantly alter a system's capabilities. This book is for people interested in both digital design and adaptable computer based data acquisition.

The Parallel Data Collector (or PDC) has been developed at Ithaca College. It works on Apple II and on IBM PC/XT/AT and compatible computers. With commercially available I/O ports, it also works with Macintosh and IBM PS/2 machines. The PDC can be a frequency meter, voltage recorder, pulse height analyzer, multichannel scaler and many other instruments. The system supports voltage, time and counting measurements with programmable parameters such as voltage conversion rate, time accuracy and counting interval. This book first describes the design principles and integrated circuits which comprise the PDC and then explains the system itself. The central idea is that it's better to master and apply a few concepts than to acquire a broad background with no particular objective in mind.

This book is mostly a text on digital electronics and interfacing. But it also tells "how to" build a powerful, adaptable data acquisition system. Problems at the end of each chapter reinforce the material and many are suitable for laboratory exercises. The later chapters present the PDC's hardware and software as well as construction details and guidelines for testing and troubleshooting. Every circuit has been built and used and every program entered and evaluated. No previous knowledge of digital electronics is assumed.

Chapter 1 outlines how computers communicate with outside circuitry and reviews commercial data acquisition systems.

Chapter 2 introduces digital electronics starting with basic logic gates and ending with tri-state bus drivers.

Chapter 3 describes parallel I/O ports which link a host computer (and its software) with data acquisition circuitry. Designs are explained for the

expansion slots of Apple II's and IBM PC/XT/AT and compatibles. Construction and testing details are in Appendices D and E. Vendors are listed for commercial ports for these systems and for IBM PS/2's and Macintoshes. Also, the three software concepts needed for PDC operations are explained and illustrated.

Chapters 4-6 are tutorials on three specific devices: the AD573 Analog-to-Digital Converter (ADC), the 6264 static memory and the 8253 Programmable Interval Timer (PIT).

Chapter 4 presents the 10-bit, 20 μ sec AD573. After covering basic operations, circuitry which interfaces the device to the parallel ports is presented. Control software is illustrated.

Chapter 5 explains the operation of the 6264 8K by 8-bit static RAM. Interface circuitry is presented along with a program which loads values in and afterwards retrieves values from the memory. Hardware and software for a 1.0000 MHz digital recorder are given.

Chapter 6 presents the Intel 8253 PIT. The focus is on control signal generation and counting measurement. After describing how to interface the chip to the parallel ports, software for all operations is given. To illustrate the use of PIT's in instruments, a programmable scaler is explained. Later, PIT's become the most important PDC building block.

Chapters 7 and 8 cover the PDC's control and ADC modules. Guidelines for construction, testing and troubleshooting are given.

Chapter 9 shows how to make the PDC into a comprehensive measurement system with the capability to repeatedly determine two voltages, count events and measure time, all in a variety of formats with multiple programmable parameters. Numerous examples are given along with details on construction, testing and troubleshooting.

Chapter 10 explains the hardware and software for a programmable rate "fast" voltage recorder. Construction and testing details are included.

All circuit diagrams and program listings in this book have been double-checked for errors. However, neither I nor the publisher warrants the information. I have made every effort to document all trademarks.

I wish to thank Professor Jack Peck of the Ithaca College Psychology Department for reading the manuscript and making many worthwhile suggestions. Erik Herrmann checked the manuscript for technical errors. I'm indebted to my physics colleagues, Professors Peter Seligmann and Dan Britotta, for many of the ideas incorporated in the PDC. Also, the following Ithaca College physics and physics-computing majors built and tested PDC hardware and software: Doug Wilson, Mike Dailey, Matt Dubois, Jerry Bush, Brendan Madden, Jerry Walker, J. B. Chupick and Erik Herrmann.

*Charles D. Spencer
Ithaca, New York*

Contents

Preface	xi
1 Computer Measurement	1
1 Ports and Expansion Slots	1
2 GPIB Standard	2
3 Parallel I/O Ports	3
2 Introduction to Digital Electronics	4
1 Basic Logic Gates	5
2 Integrated Circuits, Breadboarding and Troubleshooting	9
3 Sequential Logic and Digital Clocks	13
4 Flip-flops	16
5 Electrical Properties of TTL Integrated Circuits	22
6 Hexadecimal, Binary and Decimal Numbers	27
7 74192 and 74193 Counters	30
8 74138 Decoder/demultiplexer	37
9 74152 Data Selector/multiplexer	41
10 74373 Latch/buffer and 74244 Buffer	44
11 Conclusions	47
Exercises	47
3 Parallel I/O Ports	52
1 Specifications	52
2 Port Design for the IBM PC Expansion Slot	53
3 Port Design for the Apple II Expansion Slot	63
4 Commercial Parallel I/O Ports	71
5 Software	73
Exercises	83
4 Tutorial on the AD573 ADC	85
1 Operation and Interface	86
2 Software	90
3 Example Application - A Voltmeter	94
4 Troubleshooting Voltmeter Hardware and Software	95
5 Conclusions	98
Exercises	98
5 Tutorial on the 6264 RAM	100
1 Operation	100
2 Address Generator	103
3 Parallel Ports Interface	104

4	Software	109
5	Troubleshooting the Interface and Software	112
6	Example Application - A Digital Recorder	115
7	Troubleshooting the Recorder	125
8	Summary	127
	Exercises	127
6	Tutorial on the Intel 8253 PIT	129
1	Basic Operations	129
2	Output Pattern Generation	130
3	Using Counters for Measurement	135
4	Programming, Loading and Reading	137
5	Parallel Ports Interface	142
6	Program, Load and Read Software	143
7	Troubleshooting Hardware and Software	150
8	Example Application - A Scaler	152
9	Troubleshooting the Scaler	158
10	A Potential Fatal Fault	158
	Exercises	160
7	Control/Data Interface	162
1	Overview	162
2	PIT Controls	165
3	Memory Controls	174
4	Read ADC Controls	177
5	START/STOP*	179
6	Monitor Inputs	181
7	CDI Circuit and Software	181
8	Construction	189
9	Testing and Troubleshooting	196
	Exercises	200
8	ADC Module	203
1	Circuit	203
2	Layout and Components	205
3	Construction	206
4	Testing and Troubleshooting	208
5	Conclusions	209
	Exercises	209
9	Comprehensive Measurement System	211
1	Overview	211
2	Counter	213
3	Timer	228
4	Voltage Measurer	235
5	Complete CMS Circuit	250
6	Example of Integrated Measurement	250

7 Construction	257
8 Testing and Troubleshooting	262
9 Conclusions	267
Exercises	268
10 Fast Voltage Measurer	276
1 Introduction	276
2 Memory and Address Generator Circuitry	277
3 Measurement and Storage Circuitry	280
4 Initiation and Termination Circuitry	283
5 Read Memory Circuitry	287
6 Software	290
7 Example Measurement	295
8 Construction	297
9 Testing and Troubleshooting	304
10 Conclusions	308
Exercises	308
Appendix A References	311
Appendix B Vendors	313
Appendix C IC Pin Assignments	314
Appendix D IBM Parallel Ports	319
1 Components and Layout	319
2 Connectors and Cable	320
3 Wiring	323
4 Testing and Troubleshooting	326
Appendix E Apple II Parallel Ports	333
1 Components and Layout	333
2 Connectors and Cable	334
3 Wiring	335
4 Testing and Troubleshooting	337
Appendix F Computer Architecture	344
1 Components	344
2 Memory Write and Read Machine Cycles	346
3 I/O on Computers with Motorola Microprocessors	347
4 I/O on Computers with Intel Microprocessors	348
5 Computer Expansion Slots	349
Index	350

1 Computer Measurement

What does someone do who wants to use computers for data acquisition? No matter which way the goal is pursued, it's necessary to know how computers communicate with the external circuits which make measurements. This chapter summarizes choices and introduces the approach used in this book.

1.1 Ports and Expansion Slots

Measurement Circuits (MC's) can be connected to computers through game ports, serial ports and expansion slots. In each case, software must send values to and get values from the MC's. The following sections review and compare the approaches.

1.1.1 Game Port Communication

On an Apple II, communication between its game port and an MC occurs as follows. Up to three digital signals generated by an MC are connected to the three game port push buttons. The computer ascertains a signal's high or low state by peeking a specified address and then seeing if the value is greater than 127 which means the signal is high. Similarly, one or more of the game port's four enunciator outputs are connected to an MC. The computer makes an output high by peeking a specified address and low by peeking a different address.

Game port data acquisition is practical when the number of input and output bits can be limited which is the case with the few commercially available systems. They are typically self-contained units starting with, for instance, a temperature probe and ending with a data plot. Their low cost, reliability and operational simplicity make them attractive for instructional laboratories.

1.1.2 Serial Communication

The most widely adopted standard in computers is RS-232 serial communication. For virtually any machine, serial ports either are or can be installed (at low cost).

To communicate serially, an MC must have a Universal Asynchronous Receiver/Transmitter (UART). This large scale integrated circuit receives a

byte one bit at a time from the computer's serial port and makes the value available as eight separate signals. Similarly, the chip takes eight signals (generated by the MC) and sends them one bit at a time to the computer's serial port which assembles the value. To realistically set up and control the UART, the MC needs its own microprocessor, memory and software. This means serial data acquisition systems are also computers.

Even at maximum bits-per-second, serial communication is relatively slow. Therefore, measuring one voltage thousands of times a second or several voltages hundreds of times a second requires the MC to temporarily store data values in its own memory. Then, after acquisition, the host computer inputs the values. Data acquisition and storage are most efficiently carried out by the same microprocessor which manages the UART.

Serial systems are necessarily complex and require two levels of software: programs for the MC's processor and programs for the host computer (which include calls to the system software which operates the serial port).

A number of excellent serial data acquisition systems are available for popular computers. They are typically self-contained and come with all hardware and software.

1.1.3 Parallel Communication

Apple II, Macintosh II, IBM PC/XT/AT, IBM PS/2 and all compatibles have expansion slots. Communication between an MC occupying a slot and the computer is fast and easy. For systems with Intel microprocessors, an 8- or 16-bit value is sent to an MC by execution of an out to I/O port. Similarly, an 8- or 16-bit value is obtained from an MC by execution of an input from I/O port. With 8 or 16 bits sent or received in parallel, communication is hundreds of times faster than is possible with serial or game ports.

Data acquisition systems with every imaginable capability are available for the expansion slots of popular computers, especially IBM PC's.

Since these systems work only in the expansion slot for which they were designed, they cannot be moved from say an IBM PC to an IBM PS/2.

1.2 GPIB Standard

Because serial MC's are overly complex and expansion slot systems are not portable, a need exists for a fast parallel interface which makes different computers "look" the same to data acquisition circuitry. Of the several standards proposed over the years, by far the most successful is the IEEE-488 General Purpose Interface Bus (GPIB). It presents to an MC eight connections for sending and receiving data and eight management lines. The protocol is sufficiently elaborate that multiple MC's can be simultaneously interfaced. In addition, a variety of printers, plotters and other devices work through GPIB.

GPIB systems may be purchased for any computer with expansion slots. Versions are also available which interface serially (although their operation is slower). GPIB's usually come with software which initializes and sets up the system and then communicates with whatever MC's and other devices are connected.

Because GPIB makes different computers "look" the same, manufacturers can produce a variety of MC's knowing the market is independent of whatever computer is currently popular. And users can purchase MC's knowing they can upgrade computers without replacing their data acquisition systems.

1.3 Parallel I/O Ports

Another communications approach has many of GPIB's advantages and some of its own. Parallel I/O ports can be acquired for any computer with expansion slots. An OUT (or POKE) operation sends an 8- or 16-bit value to a port where it remains until the next OUT (or POKE). An IN (or PEEK) operation gets the 8- or 16-bit value currently at an input port. MC's connected to the ports supply the inputs and use the outputs.

The ports make different computers "look" the same to MC's and have the advantage of fast parallel communication, the same as GPIB. However, the ports require simpler and less expensive hardware. And software is just sequences of OUT's and IN's (or POKE's and PEEK's) as opposed to calls to system routines supplied by the manufacturer.

Parallel ports are a reasonable interface for data acquisition systems. Also, they are especially helpful for the teaching goals of this book. Their design in Chapter 3 illustrates and reinforces the digital electronics in Chapter 2. After visualizing IN's and OUT's, Chapters 4, 5 and 6 explain and demonstrate how software uses the ports to operate an analog-to-digital converter, an 8K static RAM and a programmable interval timer. The later chapters show how to combine these devices into a variety of useful MC's.

2 Introduction to Digital Electronics

Modern Integrated Circuits (IC's) have changed the effort and skills required to design and construct systems which carry out sophisticated digital operations. While it's desirable to understand how IC's work in terms of semiconductor physics and while good engineering practices are necessary in commercial products, it's now possible to successfully put together data acquisition hardware without first mastering these subjects.

Only fifteen different IC's are required for the parallel ports circuits of Chapter 3, for the analog-to-digital converter, memory and programmable interval counter circuits of Chapters 4-6, and for the measurement systems of Chapters 7-10. The purpose of this chapter is to introduce these and a few other IC's as well as associated design principles. Section 2.1 covers basic logic gates. Section 2.2 introduces integrated circuits, breadboarding and troubleshooting. Section 2.3 presents digital clocks. Section 2.4 introduces the 7474 flip-flop and a variety of timing and control operations. Section 2.5 outlines electrical properties of logic gates. Section 2.6 presents binary, hexadecimal and decimal number systems. Section 2.7 covers the 74192 and 74193 counters and several applications. Section 2.8 presents the 74138 decoder/demultiplexer and additional control applications. Section 2.9 introduces the 74152 multiplexer. And Section 2.10 presents tri-state gates, buses and the 74373 and 74244 buffers. While these topics provide a complete background for this book, readers are referred to Appendix A for more comprehensive introductions to digital electronics.

In general, a logic gate may be thought of as shown in Figure 2.1. It has one or more inputs and one or more outputs, and requires +5 volts and ground. The inputs must be in one of two states (+5 volts or zero volts). The outputs, with an exception discussed later, must be in one of the same two states. Depending on the circumstances, +5 volt inputs and outputs are thought of as **true**, **on**, **high** or the digit 1. Zero volt inputs and outputs are referred to as **false**, **off**, **low** or the digit 0.

Actually, low is indicated by a range of voltages around 0 and high by a larger range around +5. Sometimes it's necessary to worry about where low ends and high begins, but not here.

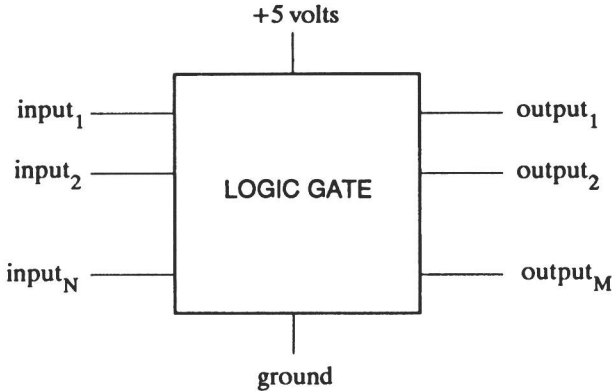


Figure 2.1. Logic gates have one or more inputs and one or more outputs. Inputs and outputs are either high (+5 volts) or low (zero volts).

Logic gates are combined to carry out desired operations. This is accomplished on two levels: symbolic and actual. Circuits are thought about in efficient symbolic terms. Afterward, they are implemented by wiring together actual integrated circuits. The approach in this chapter is to first present logic operations and then discuss building, testing and troubleshooting procedures.

2.1 Basic Logic Gates

Basic logic gates are characterized by one or more inputs and a single output. A common way to specify a gate's operation is with a truth table which gives the output for every possible combination of inputs.

Only three basic gates are required for all circuits in this book: AND, OR, and INVERTER. Their circuit symbols, logic operations and truth tables are given in Figure 2.2. For completeness, NAND, NOR and EXCLUSIVE-OR are described. For all gates except the INVERTER, it's straightforward to extend the logic operation, circuit symbol and truth table from two to three or more inputs.

As can be seen from the truth table, the output of an AND gate is high only if all inputs are high. On the other hand, the output of an OR gate is high if only one input is high. An INVERTER gate's output is always opposite the input. NAND and NOR gates are the same as AND and OR, respectively, with the outputs inverted. Finally, the output of an EXCL-OR is high if two inputs are not equal and low only when all inputs are equal. The following sections show how to use the truth tables in Figure 2.2 to think about and apply basic gates.

AND


If A AND B are true, then Q is true.

A	B	Q
0	0	0
1	0	0
0	1	0
1	1	1

OR

If A OR B is true, then Q is true.

A	B	Q
0	0	0
1	0	1
0	1	1
1	1	1

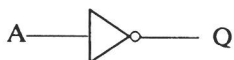INVERTER

Q is the inverse of A.

A	Q
0	1
1	0

NAND

If A AND B are true, then Q is not true.

A	B	Q
0	0	1
1	0	1
0	1	1
1	1	0

NOR

If A OR B is true, then Q is not true.

A	B	Q
0	0	1
1	0	0
0	1	0
1	1	0


EXCL-OR

If A = B, then Q is low; if A ≠ B, then Q is high.

A	B	Q
0	0	0
1	0	1
0	1	1
1	1	0

Figure 2.2. Circuit symbols and truth tables for six basic logic gates.

Figure 2.3. An AND application where one input is a control which determines whether or not the signal at the other input passes to Q.

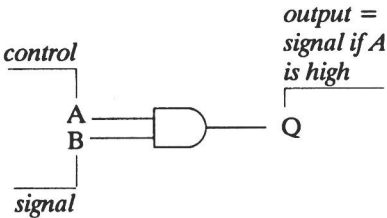

2.1.1 AND

An application of AND logic is to think of one of the inputs as a control and the other as a “signal,” such as a digital clock. If the control input A is high, the output Q equals the signal input B, be it high or low or alternating between high and low. This can be seen by looking at input B and output Q on the rows of the truth table where A is high. On the other hand, when control is low, the output is low no matter what the signal is. This can be seen by looking at the rows of the truth table where A is low. So the signal passes the AND gate only when control is high. The idea is shown in Figure 2.3.

Consider the four-input AND gate in Figure 2.4. The output is high only if all four inputs are high.

2.1.2 OR

A way to think about OR logic is that the output is low only if all inputs are low. This helps visualize the operation of the circuit in Figure 2.5. With the two inverters, the four inputs to the OR gate are all low only when the 4 bits A, B, C and D are, in order, 0110. If any bit is different, at least one OR input is high and therefore the output is high.

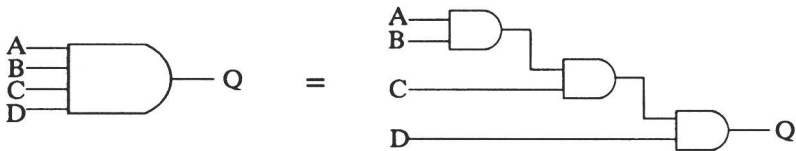


Figure 2.4. A 4-input AND gate implemented with three 2-input gates.

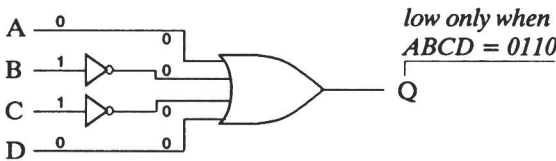


Figure 2.5. An OR based circuit.