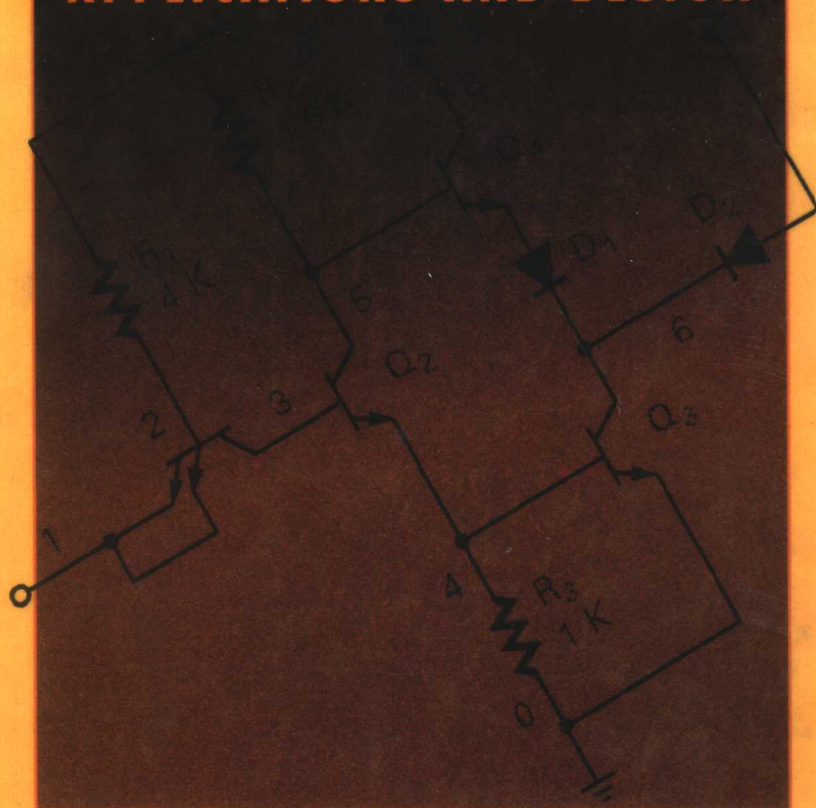


经 典 原 版 书 库

# 数字逻辑 应用与设计

(英文版)

## DIGITAL LOGIC APPLICATIONS AND DESIGN



JOHN M. YARBROUGH

(美) John M. Yarbrough 著



机械工业出版社  
China Machine Press



中信出版社  
CITIC PUBLISHING HOUSE

THOMSON

经典原版书库

# 数字逻辑 应用与设计

(英文版)

Digital Logic  
Applications and Design

(美) John M. Yarbrough 著



机械工业出版社  
China Machine Press



中信出版社  
CITIC PUBLISHING HOUSE

John M. Yarbrough: Digital Logic Applications and Design

Original copyright © 1997 by PWS Publishing Company. All rights reserved.

First published by PWS Publishing Company, a division of Thomson Learning, United States of America.

Reprinted for People's Republic of China by Thomson Asia Pte Ltd and China Machine Press and CITIC Publishing House under the authorization of Thomson Learning. No part of this book may be reproduced in any form without the prior written permission of Thomson Learning and China Machine Press.

本书影印版由美国汤姆森学习出版集团授权机械工业出版社和中信出版社出版。未经出版者书面许可，不得以任何方式复制或抄袭本书内容。

版权所有，侵权必究。

**本书版权登记号：图字：01-2001-5322**

### **图书在版编目（CIP）数据**

数字逻辑应用与设计/（美）亚伯勒（Yarbrough, J. M.）著。—北京：机械工业出版社，2002.8

（经典原版书库）

书名原文：Digital Logic Applications and Design

ISBN 7-111-10837-X

I. 数… II. 亚… III. 数学逻辑—英文 IV. TP302.2

中国版本图书馆CIP数据核字（2002）第063167号

机械工业出版社（北京市西城区百万庄大街22号 邮政编码 100037）

责任编辑：华章

北京忠信诚印刷厂印刷·新华书店北京发行所发行

2002年8月第1版第1次印刷

787mm×1092mm 1/16·44.75印张

印数：0 001-3 000册

定价：69.00元

凡购本书，如有倒页、脱页、缺页，由本社发行部调换

The purpose of *Digital Logic: Applications and Design* is to provide electrical, electronic, and computer engineering students, and engineering technology students with material fundamental to the design and analysis of digital circuits. It can also be used by practicing engineers, technologists, and technicians or anyone else, for that matter, with a basic science background, for self-study or as a review.

The typical audience might consist of college sophomores taking the first or second of a series of quarter or semester course(s) in digital logic and circuits. The material is comprehensive; that is, it covers classical combinational and sequential logic. It also covers material on PAL, PLA, GAL, and EPLD realization of logic circuits and has a chapter on circuit analysis of TTL, ECL, and CMOS logic families.

There are 10 chapters in the book, starting with basic principles and number systems, continuing on through combinational logic topics, sequential circuit analysis and design, asynchronous sequential circuit material, and ending with coverage of digital switching circuits. The organization of the book is as follows:

- Chapter 1 introduces digital concepts, number systems, binary codes, and arithmetic.
- Chapter 2 develops logic symbols and Boolean algebra.
- Chapter 3 defines combinational logic and the generation of switching equations from truth tables. It continues in the simplification of switching equations using Karnaugh maps, Quine-McClusky, and map-entered variable algorithms.
- Chapter 4 continues the treatment of combinational logic with design problems, multiplexers, decoders, adders, subtractors, and arithmetic logic units.
- Chapter 5 treats flip-flops, including timing specifications. The chapter continues with simple counters, MSI integrated circuit counters, and registers.
- Chapter 6 introduces synchronous sequential circuit design. Included are Mealy and Moore sequential circuit models, state diagram notation, development of transition and excitation tables, and derivation of excitation and output equations. Analysis of synchronous circuits and the design of counters is included.
- Chapter 7 continues with such sequential circuit design topics as state equivalence and reduction, state assignment, algorithm state machines, and linked sequential machines.

- Chapter 8 develops asynchronous sequential circuit analysis and design. Fundamental and pulse mode circuits are discussed, analysis of asynchronous circuits, derivation of flow tables, state assignment problems, and design examples are included. Some discussion of data synchronizers and mixed-operating mode logic is given.
- Chapter 9 introduces memory chips as a means of realizing combinational and sequential circuits. PLD design is discussed and examples given. The chapter also introduces two field programmable gate array (FPGA) architectures; the Xilinx and Actel FPGA devices.
- Chapter 10 concludes the text by presenting a fairly comprehensive treatment of digital integrated circuit logic families. Included are discussions of TTL, ECL, and CMOS circuits. In addition, tristate, open collector, and mixed logic subfamily interfacing is presented.

The electronics aspect of digital design and analysis is absent from many texts on digital logic. Combinational and sequential logic design from a strictly logic perspective is, in my view, incomplete. Digital integrated circuits are electronic devices. Factors such as fan-out considerations, power supply current, propagation delay, and timing analysis, all affect the design of working systems. To address the electronics as well as the logic aspects of digital design, the entire book uses actual IC devices. Becoming familiar with the wide array of ICs available to the logic designer is as important as knowing Boolean algebra and state diagram notation. I have attempted to show the internal logic as well as the logic symbols for many of the SSI and MSI devices commonly used.

Even though PLDs, FPGAs, and ASIC devices are the choices of industry logic designers, an understanding of fundamental principles imparted by using standard ICs prepares the student for dealing with ASIC libraries. Once the logic design principles are learned, any FPGA or ASIC design system can be mastered and used. It would be difficult to move directly from Boolean algebra, combinational, and sequential logic design principles into designing circuits using FPGAs and ASIC devices. FPGA and ASIC design platforms and software are still too expensive to find their way into undergraduate curricula. Writing a text using a given hardware platform and design software would necessarily exclude those not using that particular hardware and software combination.

I know that *almost* anyone can connect a series of digital integrated circuits to provide some useful result under ideal conditions. But what about nonideal conditions? The answer is found in Chapter 10 on "Digital Integrated Circuits," whose purpose is to develop the connection between the "logic" and the electronics that implement that logic. For those who have a good transistor circuits background, much of the early part of Chapter 10 can be eliminated by going straight to the specifications and characteristics of the IC themselves. For students more concerned with digital logic as a prelude to computer architecture courses and software, Chapter 10 can be skipped altogether.

---

## COURSE PARTITIONING

Several partitions are possible with the material presented in the book, depending on relative emphasis, length of lecture and laboratory course (quarter or semester), and the amount of credit given. Some examples are shown here.

1. Quarter calendar, three-course sequence with emphasis on circuits as logic. Three lectures and three laboratory courses.
  - a. First quarter: 3 credit lecture, 2 credit laboratory.
    - Chapter 1. "Digital Concepts and Number Systems"
    - Chapter 2. "Boolean Switching Algebra"
    - Chapter 3. "Principles of Combinational Logic"
    - Chapter 10. "Digital Integrated Circuits" (portions of Chapter 10 may be treated lightly or omitted depending on the emphasis of IC families and transistor circuits)
  - b. Second quarter: 3–4 credit lecture, 1–2 credit laboratory.
    - Chapter 4. "Analysis and Design of Combinational Logic"
    - Chapter 5. "Flip-Flops, Simple Counters, and Registers"
    - Chapter 6. "Introduction to Sequential Circuits"
  - c. Third quarter: 3–4 credit lecture, 1–2 credit laboratory.
    - Chapter 7. "Sequential Circuit Design"
    - Chapter 8. "Asynchronous Sequential Circuits"
    - Chapter 9. "Programmable Logic and Memory"
2. Semester calendar with the same coverage as given in the three-term course sequence.
  - a. First semester.
    - Chapter 1. "Digital Concepts and Number Systems"
    - Chapter 2. "Boolean Switching Algebra"
    - Chapter 10. "Digital Integrated Circuits"
    - Chapter 3. "Principles of Combinational Logic"
    - Chapter 4. "Analysis and Design of Combinational Logic"
  - b. Second semester.
    - Chapter 5. "Flip-Flops, Simple Counters, and Registers"
    - Chapter 6. "Introduction to Sequential Circuits"
    - Chapter 7. "Sequential Circuit Design"
    - Chapter 8. "Asynchronous Sequential Circuits"
    - Chapter 9. "Programmable Logic and Memory"

Laboratory assignments can be made from selected problems given at the end of each chapter. For example, Chapter 5, "Flip-Flops, Simple Counters, and Registers," might yield the following laboratory assignments:

1. Latches and flip-flops (problems 3, 4, 5, 6, 7, 8, 9)
  - a. Construct an S'R' latch from NAND gates. Verify the characteristic table and derive the characteristic equation.
  - b. Add additional NAND gates to convert the S'R' latch to a level triggered J-K flip-flop. Verify the operation by constructing a characteristic table. Identify the operation when  $J = K = 1$ . Suggest a solution for the problem encountered (convert the level trigger to a pulse trigger).
  - c. Convert the pulse triggered J-K flip-flop to a D flip-flop and a T flip-flop. Verify the operation of each by creating characteristic tables. Derive the characteristic equations.
  - d. Predict and measure power consumption and propagation delay.
2. Counters (problem 25)
  - a. Design a modulo-8 counter using standard IC flip-flops.
    1. Construct the state diagram.

2. Determine the number of flip-flops needed.
3. Make a binary state assignment (000, 001, 010, 111).
4. Create a state table and a transition table.
5. Using *D* flip-flops create an excitation table (compare the transition and excitation tables).
6. Generate the simplified excitation equations.
7. Construct the circuit using TTL integrated circuit packages (*D* flip-flops, AND, NAND, etc. gates).
- b. Predict the timing diagram for the modulo-8 counter.
- c. Test the circuit operation.
  1. Single step through each state and verify state transitions.
  2. Connect a function generator to the clock inputs. Set the function generator to produce a square wave between 0 and 5 V at a frequency of 10 KHz. Measure the *Q* outputs of the flip-flops using an oscilloscope and produce a timing diagram.
3. Johnson counter (problem 26)
4. Special purpose pulse generator (problem 33)
5. Register system (problem 43)

---

## SUPPLEMENTAL PACKAGE

- A solutions manual to all text problems (only odd answers are given in the text)
- For selected text illustrations, a set of transparency masters to use as overheads
- A lab manual is being developed, which is unique because other texts at this level do not have one (ask your West sales representative when it will be available)

---

## ACKNOWLEDGMENTS

No author can complete a text without the assistance of many people. I would like to thank Jack Stewart, a student at Oregon Institute of Technology; the publishing professionals at West, and the following reviewers and accuracy checkers who deserve particular mention:

Gail Allwine	Thomas Casavant
Gonzaga University (WA)	University of Iowa (IA)
Kenneth J. Ayala	Aaron Collins
Western Carolina University (NC)	Clemson University (SC)
Dee Bailey	Darrow Dawson
Mt. Hood Community College (OR)	University of Missouri-Rolla (MO)
William E. Barnes	Richard Eason
New Jersey Institute of Technology (NJ)	University of Maine (ME)
Robert Belge	Joe Enekes
Syracuse University (NY)	Humber College (Ontario, Canada)
John Brannon	Milos Ercegovac
Embry-Riddle Aeronautical University (FL)	University of California-Los Angeles (CA)

Barry S. Fagin  
Dartmouth College (NH)

Verne Hansen  
Weber State University (UT)

Ralph Horvath  
Michigan Technological University (MI)

Michael Horn  
University of Hartford (CT)

Ernest Joerg  
Westchester Community College (NY)

Harold Klock  
Ohio University (OH)

Willard Korfhage  
Polytechnic University (NY)

Sura Lekhukul  
St. Cloud State University (MN)

Albert L. McHenry  
Arizona State University (AZ)

James Migel  
Red River Community College  
(Manitoba, Canada)

John Nagi  
Hudson Valley Community College  
(NY)

John R. Pavlat  
Iowa State University (IA)

James Rankin  
St. Cloud State University (MN)

Dennis Suchecki  
San Diego Mesa College (CA)



Preface xi

<b>CHAPTER 1</b>	<b>Digital Concepts and Number Systems</b>	<b>1</b>
	Introduction	1
1.1	Digital and Analog: Basic Concepts	1
1.2	Some History of Digital Systems	4
1.3	Impact of Digital Technology on Society	6
1.4	Defining the Problem, an Introduction to Algorithms	7
1.5	Digital Systems Overview	9
1.6	Introduction to Number Systems	9
1.7	Positional Number Systems	10
1.7.1	Decimal Numbers	10
1.7.2	Binary Numbers	11
1.7.3	Octal Numbers	12
1.7.4	Hexadecimal Numbers	12
1.7.5	Counting in Base $r$	13
1.8	Number System Conversion	14
1.8.1	Binary to Hexadecimal Conversion	15
1.8.2	Hexadecimal and Octal to Binary Conversion	16
1.8.3	Binary to Decimal Conversion	16
1.8.4	Successive Division Radix Conversion	17
1.8.5	Fractional Radix Conversion, Successive Multiplication	18
1.8.6	Radix Conversion Algorithm	20
1.8.7	Decimal to Any Radix	21
1.8.8	Any Radix to Decimal	23
1.9	Binary Codes	23
1.9.1	Natural Binary Coded Decimal	23
1.9.2	Binary Codes (Weighted)	24
1.9.3	BCD Self-Complementing Codes	25

1.9.4	Unit Distance Code	26
1.9.5	Alphanumeric Codes	28
1.9.6	Signed Number Binary Codes	28
1.9.7	Signed Magnitude Codes	28
1.9.8	Complement Codes	29
1.10	Arithmetic	32
1.10.1	Binary Arithmetic	32
1.10.2	Binary Arithmetic Using Complement Codes	35
1.10.3	Hexadecimal Arithmetic	38
	Summary	42
	References	43
	Glossary	44
	Questions and Problems	45

## CHAPTER 2 Boolean Switching Algebra

48

	Introduction	48
2.1	Binary Logic Functions	48
2.1.1	IEEE Logic Symbols	54
2.1.2	Functions, Symbols, and Truth Tables	55
2.2	Switching Algebra	57
2.2.1	Equivalence	58
2.2.2	Closure	58
2.2.3	Identity	59
2.2.4	Associative Properties	59
2.2.5	Distributive Properties	61
2.2.6	Commutative Properties	62
2.2.7	Complement Property	62
2.2.8	Duality Property	62
2.2.9	Absorption Property	62
2.2.10	Idempotency Property	63
2.2.11	Binary Variables and Constants	63
2.2.12	DeMorgan's Theorems	64
2.3	Functionally Complete Operation Sets	68
2.4	Reduction of Switching Equations Using Boolean Algebra	70
2.5	Realization of Switching Functions	73
2.5.1	Conversion of Switching Functions to Logic Diagrams	73
2.5.2	Converting Logic Diagrams to Switching Equations	77
	Summary	80
	References	80
	Glossary	81
	Questions and Problems	82

## CHAPTER 3 Principles of Combinational Logic 84

- Introduction 84
- 3.1 Definition of Combinational Logic 84
  - 3.1.1 Problem Statements to Truth Tables 85
  - 3.1.2 Deriving Switching Equations 89
- 3.2 Canonical Forms 91
- 3.3 Generation of Switching Equations from Truth Tables 93
- 3.4 Karnaugh Maps 96
  - 3.4.1 Three- and Four-Variable Karnaugh Maps 97
  - 3.4.2 Five- and Six-Variable Karnaugh Maps 107
  - 3.4.3 Simplification Using Five-Variable Karnaugh Maps 109
  - 3.4.4 Simplification Using Six-Variable Karnaugh Maps 112
  - 3.4.5 Incompletely Specified Functions (Don't Care Terms) 113
  - 3.4.6 Simplifying Maxterm Equations 117
- 3.5 Quine-McClusky Minimization Technique 120
  - 3.5.1 Quine-McClusky Using Don't Care Terms 123
  - 3.5.2 Reduced Prime Implicant Tables 125
- 3.6 Map-Entered Variables 129
- 3.7 Mixed Logic Combinational Circuits 135
  - 3.7.1 Logic Symbols 136
  - 3.7.2 Conversion to Bubble Logic 140
  - 3.7.3 Synthesizing Switching Functions Using Bubble Notation 142
- 3.8 Multiple Output Functions 146
- Summary 149
- References 150
- Glossary 150
- Questions and Problems 151

## CHAPTER 4 Analysis and Design of Combinational Logic 156

- Introduction 156
- 4.1 General Approach to Combinational Logic Design 156
- 4.2 Introduction to Digital Integrated Circuits 164
- 4.3 Decoders 171
  - 4.3.1 BCD Decoders 181
- 4.4 Encoders 185
- 4.5 Digital Multiplexers 190
  - 4.5.1 Using Multiplexers as Boolean Function Generators 194
- 4.6 Adders and Subtractors 201
  - 4.6.1 Cascading Full-Adders 205
  - 4.6.2 Look-Ahead Carry 206

4.6.3	MSI Adders	207
4.6.4	Using MSI Adders as Subtractors	208
4.6.5	Using an MSI Adder as a BCD to Excess-3 Code Converter	211
4.6.6	BCD Adder	212
4.7	Binary Comparators	215
4.8	Arithmetic Logic Units	222
4.9	Array Multipliers	225
4.10	Tristate Buffers	228
4.11	Combinational Logic Hazards	231
4.11.1	Static Hazards	232
4.11.2	Dynamic Hazards	236
	Summary	237
	References	237
	Glossary	238
	Questions and Problems	239

## **CHAPTER 5 Flip-Flops, Simple Counters, and Registers 243**

	Introduction	243
5.1	Sequential Circuit Models	243
5.2	Flip-Flops	248
5.2.1	Flip-Flop Logic Symbols, Function, and Triggering	248
5.3	Flip-Flop Timing Specifications	265
5.3.1	Clock Parameters, Pulse Width, and Skew	265
5.3.2	Flip-Flop Timing, Setup, Hold, and Delay	267
5.3.3	Flip-Flop Metastability	268
5.4	Simple Counters	271
5.4.1	Divide by 2, 4, and 8 Counters (Asynchronous)	272
5.4.2	Johnson Counter (Synchronous)	274
5.4.3	Ring Counter (Synchronous)	275
5.5	MSI Integrated Circuit Counters	276
5.5.1	MSI Asynchronous Counters	277
5.5.2	MSI Synchronous Counters	279
5.5.3	Control Signal Generation by Decoding Counter Outputs	283
5.5.4	A Counter Application: Digital Clock	287
5.5.5	IEEE Standard Symbols for MSI Counters	291
5.6	Registers	295
5.6.1	Registers Data Input and Output	295
5.6.2	Tristate Registers	300
5.6.3	Registers Connected to a Common Data Bus	305
5.6.4	Register Transfer Timing Considerations	310
	Summary	312
	References	313

Glossary	314
Questions and Problems	316

## CHAPTER 6 Introduction to Sequential Circuits 322

Introduction	322
6.1 Mealy and Moore Models	322
6.2 State Machine Notation	323
6.2.1 Present State, Next State	324
6.2.2 State Diagram	324
6.2.3 State Table	328
6.2.4 Transition Table	329
6.2.5 Excitation Table and Equations	330
6.2.6 Excitation Realization Cost	336
6.3 Synchronous Sequential Circuit Analysis	339
6.3.1 Analysis Principles	340
6.3.2 Analysis Examples	340
6.4 Construction of State Diagrams	348
6.4.1 Up-Down Decade Counter	349
6.4.2 Sequence Detectors	349
6.4.3 Serial EX-3 to BCD Code Converter	354
6.5 Counter Design	356
6.5.1 Modulo-8 Synchronous Counter	357
6.5.2 Up-Down Decade Counter Design	360
Summary	369
References	370
Glossary	370
Questions and Problems	371

## CHAPTER 7 Sequential Circuit Design 375

Introduction	375
7.1 State Equivalence	375
7.2 State Reduction	376
7.2.1 Equivalence Classes	376
7.2.2 Implication Charts	378
7.3 State Reduction of Incompletely Specified State Tables	384
7.3.1 Merger Graphs	386
7.4 State Assignment Techniques	389
7.4.1 State Assignment Permutations	390
7.4.2 State Assignment Algorithm	392
7.4.3 Implication Graph	396

7.5	Algorithm State Machines	399
7.5.1	ASM Symbols	399
7.5.2	Elapsed Time Measurement, an ASM Design Example	404
7.6	Linked Sequential Machines	413
7.6.1	Computer Simulator and Graphic Plotter Interface, a Linked Sequential Machine Design Example	415
	Summary	432
	References	433
	Glossary	433
	Questions and Problems	434

## CHAPTER 8 Asynchronous Sequential Circuits 441

	Introduction to Asynchronous Sequential Machines	441
8.1	Fundamental and Pulse Mode Asynchronous Sequential Machines	442
8.2	Analysis of Asynchronous Sequential Machines	444
8.3	Deriving Flow Tables	452
8.4	State Assignment	456
8.4.1	Races and Cycles	456
8.4.2	Shared Row State Assignment	458
8.4.3	Multiple Row State Assignment	460
8.4.4	One Hot State Assignment	461
8.5	Asynchronous Design Problems	462
8.5.1	Asynchronous Design Problem 1	463
8.5.2	Asynchronous Design Problem 2	465
8.6	Data Synchronizers	470
8.6.1	Interface Protocol Asynchronous Cell	472
8.7	Mixed Operating Mode Asynchronous Circuits	474
	Summary	477
	References	478
	Glossary	479
	Questions and Problems	480

## CHAPTER 9 Programmable Logic and Memory 485

	Introduction	485
9.1	Memory	486
9.1.1	ROM, PROM, and EPROM	486
9.2	Using an EPROM to Realize a Sequential Circuit	491
9.3	Programmable Logic Devices	495
9.3.1	Programmable Logic Array (PLA)	496
9.3.2	Programmable Array Logic	498

9.3.3	Designing an Up-Down Decade Counter Using a PAL	502
9.3.4	Generic Array Logic	507
9.3.5	Designing a Synchronous Sequential Circuit Using a GAL	509
9.4	Erasable Programmable Logic Devices	514
9.4.1	Altera EP600 EPLD	517
9.4.2	Sequential Circuit Realization Using an EP600	519
9.5	PLD Computer-Aided Design	523
9.5.1	PLD Realization of Combinational Logic	525
9.5.2	Realizing Truth Tables Using a PLD Language	529
9.5.3	Realizing Flip-Flops Using a PLD Language	530
9.5.4	Realizing State Machines Using a PLD Language	530
9.6	Field Programmable Gate Arrays	534
9.6.1	Xilinx FPGA	535
9.6.2	System Development Tools for the Xilinx FPGA	542
9.6.3	Xilinx Macro Library	543
9.6.4	Actel FPGA	543
	Summary	549
	References	550
	Glossary	551
	Questions and Problems	552

## CHAPTER 10 Digital Integrated Circuits

556

	Introduction	556
10.1	Diodes as Switches	556
10.1.1	Diode Gates	558
10.2	Bipolar Transistor Switch	561
10.3	Diode Transistor Logic	562
10.4	Evolution from DTL to TTL	563
10.5	Transistor-Transistor Logic	565
10.5.1	TTL Circuit Operation	567
10.5.2	TTL Specifications	569
10.5.3	TTL Subfamilies	573
10.5.4	Schottky Junctions	578
10.5.5	Comparison of TTL Subfamily Specifications	579
10.5.6	Open Collector TTL Circuits	580
10.5.7	Tristate TTL Devices	584
10.5.8	Mixed TTL Subfamily Fan-Out	585
10.5.9	Other TTL Circuits	587
10.6	Emitter-Coupled Logic	590
10.6.1	Emitter-Coupled Logic Circuit	590
10.6.2	ECL Specifications	594
10.6.3	ECL to TTL and TTL to ECL Interfacing	595

10.7	Complementary Metal Oxide Semiconductor	597
10.7.1	Field Effect Transistors	597
10.7.2	MOSFETs	603
10.7.3	MOSFET Logic Gates	606
10.7.4	CMOS Logic Gates	609
10.7.5	Power Dissipation for High-Speed CMOS	612
10.7.6	Propagation Delay for High-Speed CMOS	613
10.7.7	CMOS Noise Margins	613
10.7.8	CMOS Subfamilies	613
	Summary	615
	References	615
	Glossary	616
	Questions and Problems	617
Appendix 1	TTL Analysis Spice Exercise	623
Appendix 2	Answers to Odd-Numbered Questions and Problems	627
	Index	689



# DIGITAL CONCEPTS AND NUMBER SYSTEMS

---

## INTRODUCTION

Digital circuits, processing discrete information, are found in an astonishingly wide range of electronic systems. Consumer microwave ovens and television, advanced industrial controls, space communications, traffic control radar and hospital critical care units are all designed using digital techniques. Advances in digital circuit manufacturing have provided systems designers with more functions contained in less space, thereby improving system reliability and increasing speed. Digital systems operate on numbers that represent some real logical or arithmetic function. It is the designer's task to establish the relationship between the numbers and the task being performed. This chapter develops the use of numbers and how they represent real world conditions in digital systems.

The use of the words *digit* and *digital* was probably in association with counting; it can apply to decimal numbers (0, 1, 2, 3, . . . , 9) or numbers in another base such as binary (0, 1). Counting in decimal numbers and the number of fingers or toes are probably directly related in human history. More appropriate for students of electronics and computers, digital systems are systems that process discrete information. A digital system is simply one that receives input, processes or controls activity, and outputs information in a discrete or noncontinuous manner. The information may be encoded or represented in a variety of ways; it can be in the familiar base 10 number system or in some other number system, such as base 2 (binary).

Digital design is the *application of a set of rules and techniques for developing digital circuits and subsystems to create a solution for some problem.*

---

## 1.1 DIGITAL AND ANALOG: BASIC CONCEPTS

The difference between analog and digital lies in the method of encoding information. Digital electronics uses discrete quantities to represent information while analog electronics deals with continuous signals. **Discrete** means distinct or separated as opposed to **continuous** or connected. Analog systems process information that varies continuously. Examples of analog represented variables include temperature as measured with a mercury thermometer, clocks with hands, sine wave voltages indicated on a galva-