

国外电子与通信教材系列

英文改编版

PEARSON
Prentice
Hall


数字电子技术

(第九版)

Digital Fundamentals, Ninth Edition

[美] Thomas L. Floyd 著

余 璆 改编

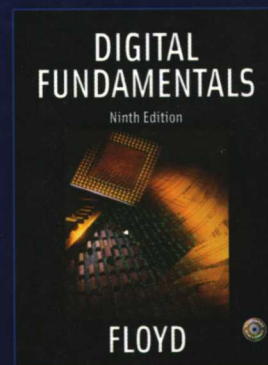

电子工业出版社

Publishing House of Electronics Industry
<http://www.phei.com.cn>

国外电子与通信教材系列

数字电子技术

(第九版)

(英文改编版)

Digital Fundamentals

Ninth Edition

[美] Thomas L. Floyd 著

余 璆 改编

電子工業出版社

Publishing House of Electronics Industry

北京 · BEIJING

内 容 简 介

本书是关于数字电子技术的经典教材,内容涉及数字电子技术的基本概念、数制、逻辑门、布尔代数和逻辑化简、组合逻辑分析、组合逻辑的作用、计数器、移位寄存器、存储器、可编程逻辑与软件、集成电路技术等。全书的特色在于示例与习题丰富、图解清晰、语言流畅、写作风格简约。

本书可作为高等院校电子信息类专业本科生的教材,也可供相关技术、科研管理人员使用,或作为继续教育的参考书。

Original edition, entitled *Digital Fundamentals*, Ninth Edition by Thomas L. Floyd, published by Pearson Education, Inc, publishing as Prentice Hall, Copyright 2006.

All rights reserved. No part of this book may be reproduced or transmitted in any form or by any means, electronics or mechanical, including photocopying, recording or by any information storage retrieval system, without permission from Pearson Education, Inc. China Adapted edition published by Pearson Education Asia Ltd. and Publishing House of Electronics Industry, Copyright © 2006. This Adapted edition is manufactured in the People's Republic of China, and is authorized for sale only in Peoples's Republic of China excluding Hong Kong and Macau.

本书影印改编版由电子工业出版社和Pearson Education 培生教育出版亚洲有限公司合作出版。未经出版者预先书面许可,不得以任何方式复制或抄袭本书的任何部分。本书影印改编版在中国大陆地区生产,仅限于在中国大陆地区销售。本书影印改编版贴有 Pearson Education 培生教育出版集团激光防伪标签,无标签者不得销售。

版权贸易合同登记号 图字:01-2006-3105

图书在版编目(CIP)数据

数字电子技术 = Digital Fundamentals: 第9版: 改编版 / (美) 弗洛伊德 (Floyd, T. L.) 著, 余璆改编.

北京: 电子工业出版社, 2006.6

(国外电子与通信教材系列)

ISBN 7-121-02632-5

I. 数... II. ①弗... ②余... III. 数字电路 - 电子技术 - 教材 - 英文 IV. TN79

中国版本图书馆CIP数据核字(2006)第048928号

责任编辑: 谭海平

印 刷: 北京市天竺颖华印刷厂

出版发行: 电子工业出版社

北京市海淀区万寿路173信箱 邮编: 100036

经 销: 各地新华书店

开 本: 787 × 980 1/16 印张: 32.25 字数: 825千字

印 次: 2006年6月第1次印刷

定 价: 45.00元

凡购买电子工业出版社的图书,如有缺损问题,请向购买书店调换;若书店售缺,请与本社发行部联系。联系电话:(010) 68279077。质量投诉请发邮件至 zltts@phei.com.cn, 盗版侵权举报请发邮件至 dbqq@phei.com.cn。

序

2001年7月间,电子工业出版社的领导同志邀请各高校十几位通信领域方面的老师,商量引进国外教材问题。与会同志对出版社提出的计划十分赞同,大家认为,这对我国通信事业、特别是对高等院校通信学科的教学工作会很有好处。

教材建设是高校教学建设的主要内容之一。编写、出版一本好的教材,意味着开设了一门好的课程,甚至可能预示着一个崭新学科的诞生。20世纪40年代MIT林肯实验室出版的一套28本雷达丛书,对近代电子学科、特别是对雷达技术的推动作用,就是一个很好的例子。

我国领导部门对教材建设一直非常重视。20世纪80年代,在原教委教材编审委员会的领导下,汇集了高等院校几百位富有教学经验的专家,编写、出版了一大批教材;很多院校还根据学校的特点和需要,陆续编写了大量的讲义和参考书。这些教材对高校的教学工作发挥了极好的作用。近年来,随着教学改革不断深入和科学技术的飞速进步,有的教材内容已比较陈旧、落后,难以适应教学的要求,特别是在电子学和通信技术发展神速、可以讲是日新月异的今天,如何适应这种情况,更是一个必须认真考虑的问题。解决这个问题,除了依靠高校的老师和专家撰写新的符合要求的教科书外,引进和出版一些国外优秀电子与通信教材,尤其是有选择地引进一批英文原版教材,是会有好处的。

一年多来,电子工业出版社为此做了很多工作。他们成立了一个“国外电子与通信教材系列”项目组,选派了富有经验的业务骨干负责有关工作,收集了230余种通信教材和参考书的详细资料,调来了100余种原版教材样书,依靠由20余位专家组成的出版委员会,从中精选了40多种,内容丰富,覆盖了电路理论与应用、信号与系统、数字信号处理、微电子、通信系统、电磁场与微波等方面,既可作为通信专业本科生和研究生的教学用书,也可作为有关专业人员的参考材料。此外,这批教材,有的翻译为中文,还有部分教材直接影印出版,以供教师用英语直接授课。希望这些教材的引进和出版对高校通信教学和教材改革能起一定作用。

在这里,我还要感谢参加工作的各位教授、专家、老师与参加翻译、编辑和出版的同志们。各位专家认真负责、严谨细致、不辞辛劳、不怕琐碎和精益求精的态度,充分体现了中国教育工作者和出版工作者的良好美德。

随着我国经济建设的发展和科学技术的不断进步,对高校教学工作会不断提出新的要求和希望。我想,无论如何,要做好引进国外教材的工作,一定要联系我国的实际。教材和学术专著不同,既要注意科学性、学术性,也要重视可读性,要深入浅出,便于读者自学;引进的教材要适应高校教学改革的需要,针对目前一些教材内容较为陈旧的问题,有目的地引进一些先进的和正在发展中的交叉学科的参考书;要与国内出版的教材相配套,安排好出版英文原版教材和翻译教材的比例。我们努力使这套教材能尽量满足上述要求,希望它们能放在学生们的课桌上,发挥一定的作用。

最后,预祝“国外电子与通信教材系列”项目取得成功,为我国电子与通信教学和通信产业的发展培土施肥。也恳切希望读者能对这些书籍的不足之处、特别是翻译中存在的问题,提出意见和建议,以便再版时更正。



中国工程院院士、清华大学教授
“国外电子与通信教材系列”出版委员会主任

出版说明

进入21世纪以来,我国信息产业在生产和科研方面都大大加快了发展速度,并已成为国民经济发展的支柱产业之一。但是,与世界上其他信息产业发达的国家相比,我国在技术开发、教育培训等方面都还存在着较大的差距。特别是在加入WTO后的今天,我国信息产业面临着国外竞争对手的严峻挑战。

作为我国信息产业的专业科技出版社,我们始终关注着全球电子信息技术的发展方向,始终把引进国外优秀电子与通信信息技术教材和专业书籍放在我们工作的重要位置上。在2000年至2001年间,我社先后从世界著名出版公司引进出版了40余种教材,形成了一套“国外计算机科学教材系列”,在全国高校以及科研部门中受到了欢迎和好评,得到了计算机领域的广大教师与科研工作者的充分肯定。

引进和出版一些国外优秀电子与通信教材,尤其是有选择地引进一批英文原版教材,将有助于我国信息产业培养具有国际竞争能力的技术人才,也将有助于我国国内在电子与通信教学工作中掌握和跟踪国际发展水平。根据国内信息产业的现状、教育部《关于“十五”期间普通高等教育教材建设与改革的意见》的指示精神以及高等院校老师们反映的各种意见,我们决定引进“国外电子与通信教材系列”,并随后开展了大量准备工作。此次引进的国外电子与通信教材均来自国际著名出版商,其中影印教材约占一半。教材内容涉及的学科方向包括电路理论与应用、信号与系统、数字信号处理、微电子、通信系统、电磁场与微波等,其中既有本科专业课程教材,也有研究生课程教材,以适应不同院系、不同专业、不同层次的师生对教材的需求,广大师生可自由选择 and 自由组合使用。我们还将与国外出版商一起,陆续推出一些教材的教学支持资料,为授课教师提供帮助。

此外,“国外电子与通信教材系列”的引进和出版工作得到了教育部高等教育司的大力支持和帮助,其中的部分引进教材已通过“教育部高等学校电子信息科学与工程类专业教学指导委员会”的审核,并得到教育部高等教育司的批准,纳入了“教育部高等教育司推荐——国外优秀信息科学与技术系列教学用书”。

为做好该系列教材的翻译工作,我们聘请了清华大学、北京大学、北京邮电大学、南京邮电大学、东南大学、西安交通大学、天津大学、西安电子科技大学、电子科技大学、中山大学、哈尔滨工业大学、西南交通大学等著名高校的教授和骨干教师参与教材的翻译和审校工作。许多教授在国内电子与通信专业领域享有较高的声望,具有丰富的教学经验,他们的渊博学识从根本上保证了教材的翻译质量和专业学术方面的严格与准确。我们在此对他们的辛勤工作与贡献表示衷心的感谢。此外,对于编辑的选择,我们达到了专业对口;对于从英文原书中发现的错误,我们通过与作者联络、从网上下载勘误表等方式,逐一进行了修订;同时,我们对审校、排版、印制质量进行了严格把关。

今后,我们将进一步加强同各高校教师的密切关系,努力引进更多的国外优秀教材和教学参考书,为我国电子与通信教材达到世界先进水平而努力。由于我们对国内外电子与通信教育的发展仍存在一些认识上的不足,在选题、翻译、出版等方面的工作中还有许多需要改进的地方,恳请广大师生和读者提出批评及建议。

电子工业出版社

教材出版委员会

主 任	吴佑寿	中国工程院院士、清华大学教授
副主任	林金桐	北京邮电大学校长、教授、博士生导师
	杨千里	总参通信部副部长, 中国电子学会会士、副理事长 中国通信学会常务理事, 博士生导师
委 员	林孝康	清华大学教授、博士生导师、电子工程系副主任、通信与微波研究所所长 教育部电子信息科学与工程类专业教学指导分委员会委员
	徐安士	北京大学教授、博士生导师、电子学系主任
	樊昌信	西安电子科技大学教授、博士生导师 中国通信学会理事、IEEE 会士
	程时昕	东南大学教授、博士生导师、移动通信国家重点实验室主任
	郁道银	天津大学副校长、教授、博士生导师 教育部电子信息科学与工程类专业教学指导分委员会委员
	阮秋琦	北京交通大学教授、博士生导师 计算机与信息技术学院院长、信息科学研究所所长 国务院学位委员会学科评议组成员
	张晓林	北京航空航天大学教授、博士生导师、电子信息工程学院院长 教育部电子信息科学与电气信息类基础课程教学指导分委员会副主任委员 中国电子学会常务理事
	郑宝玉	南京邮电大学副校长、教授、博士生导师 教育部电子信息与电气学科教学指导委员会委员
	朱世华	西安交通大学副校长、教授、博士生导师 教育部电子信息科学与工程类专业教学指导分委员会副主任委员
	彭启琮	电子科技大学教授、博士生导师、通信与信息工程学院院长 教育部电子信息科学与电气信息类基础课程教学指导分委员会委员
	毛军发	上海交通大学教授、博士生导师、电子信息与电气工程学院副院长 教育部电子信息与电气学科教学指导委员会委员
	赵尔沅	北京邮电大学教授、《中国邮电高校学报(英文版)》编委会主任
	钟允若	原邮电科学研究院副院长、总工程师
	刘 彩	中国通信学会副理事长兼秘书长, 教授级高工 信息产业部通信科技委副主任
	杜振民	电子工业出版社原副社长
	王志功	东南大学教授、博士生导师、射频与光电集成电路研究所所长 教育部高等学校电子电气基础课程教学指导分委员会主任委员
	张中兆	哈尔滨工业大学教授、博士生导师、电子与信息技术研究院院长
	范平志	西南交通大学教授、博士生导师、计算机与通信工程学院院长

读者意见调查表

感谢您对电子工业出版社的支持！

为帮助我们进步，请将您的宝贵意见填于下表并寄回我们。

您购买的出版物名称	
先进性和实用性	<input type="checkbox"/> 很好 <input type="checkbox"/> 好 <input type="checkbox"/> 一般 <input type="checkbox"/> 不太好 <input type="checkbox"/> 差
图书文字可读性 (光盘使用方便性)	<input type="checkbox"/> 很好 <input type="checkbox"/> 好 <input type="checkbox"/> 一般 <input type="checkbox"/> 不太好 <input type="checkbox"/> 差 (<input type="checkbox"/> 很好 <input type="checkbox"/> 好 <input type="checkbox"/> 一般 <input type="checkbox"/> 不太好 <input type="checkbox"/> 差)
图书篇幅适宜度 (光盘界面设计)	<input type="checkbox"/> 很合适 <input type="checkbox"/> 合适 <input type="checkbox"/> 一般 <input type="checkbox"/> 不合适 <input type="checkbox"/> 差 (<input type="checkbox"/> 很好 <input type="checkbox"/> 好 <input type="checkbox"/> 一般 <input type="checkbox"/> 不太好 <input type="checkbox"/> 差)
出版物中差错	<input type="checkbox"/> 极少 <input type="checkbox"/> 较少 <input type="checkbox"/> 一般 <input type="checkbox"/> 较多 <input type="checkbox"/> 太多
图书封面(光盘盘面及包装) 设计水平	<input type="checkbox"/> 很好 <input type="checkbox"/> 好 <input type="checkbox"/> 一般 <input type="checkbox"/> 不太好 <input type="checkbox"/> 差
图书(光盘盘面及包装) 印刷装订质量	<input type="checkbox"/> 很好 <input type="checkbox"/> 好 <input type="checkbox"/> 一般 <input type="checkbox"/> 不太好 <input type="checkbox"/> 差
纸张质量(光盘材质)	<input type="checkbox"/> 很好 <input type="checkbox"/> 好 <input type="checkbox"/> 一般 <input type="checkbox"/> 不太好 <input type="checkbox"/> 差
定价	<input type="checkbox"/> 很便宜 <input type="checkbox"/> 便宜 <input type="checkbox"/> 合理 <input type="checkbox"/> 贵 <input type="checkbox"/> 太贵
对宣传工作的感觉	<input type="checkbox"/> 很好 <input type="checkbox"/> 好 <input type="checkbox"/> 一般 <input type="checkbox"/> 不好 <input type="checkbox"/> 差
对服务质量的感覺	<input type="checkbox"/> 很好 <input type="checkbox"/> 好 <input type="checkbox"/> 一般 <input type="checkbox"/> 不好 <input type="checkbox"/> 差
从何处获取出版物信息	<input type="checkbox"/> 书目报 <input type="checkbox"/> 电子社宣传材料 <input type="checkbox"/> 书店 <input type="checkbox"/> 他人转告 <input type="checkbox"/> 网站 <input type="checkbox"/> 报刊
您认为电子工业出版社 应改进的方面	<input type="checkbox"/> 先进性和实用性 <input type="checkbox"/> 文字可读性(光盘使用方便性) <input type="checkbox"/> 篇幅适宜度(光盘界面设计) <input type="checkbox"/> 出版物中差错 <input type="checkbox"/> 设计水平 <input type="checkbox"/> 印刷装订质量 <input type="checkbox"/> 纸张质量(光盘材质) <input type="checkbox"/> 定价 <input type="checkbox"/> 宣传工作 <input type="checkbox"/> 服务质量
您的具体意见或建议	
读者姓名: _____ 联系方式: _____ 从事工作: <input type="checkbox"/> 技术研发 <input type="checkbox"/> 技术管理 <input type="checkbox"/> 经营管理 <input type="checkbox"/> 行政管理 <input type="checkbox"/> 教育培训 <input type="checkbox"/> 在校学习	

表格寄回 邮寄地址: 北京市万寿路 173 信箱电子工业出版社外版室 邮政编码: 100036 收信人: 冯小贝
 传真: (010) 88254560 收件人: 冯小贝
 电子信箱: fengxiaobei@phei.com.cn

教学支持说明

本书系我社获全球最大的教育出版集团——Pearson Education Group 独家授权之英文版。

Pearson Education 旗下的国际知名教育图书出版公司 Prentice Hall 的高品质的电子与通信类出版物是全美及全球高校采用率最高的教材, 享誉全球教育界、工商界和技术界。为秉承 Prentice Hall 出版公司对于其教材类产品的一贯教学支持, Pearson Education 将向采纳本书作为教材的教师免费提供网上教学支持课件。任何一位注册的教师都可直接下载所有在线的教学辅助资料。

为确保此资源仅为教师教学所使用, 烦请填写如下情况调查表, 并回寄或传真给电子工业出版社。

证 明

兹证明 _____ 大学 _____ 系 / 院 _____ 专业 _____ 学年 (学期)
开设的 _____ 课程, 共 _____ 学时, 现采用电子工业出版社出版的英文原版/
简体中文版 _____ (书名 / 作者) 作为主要教材。
任课教师为 _____, 学生 _____ 个班共 _____ 人。

任课教师需要与本书配套的教学辅助资料。

电 话: _____

传 真: _____

E-mail: _____

联系地址: _____

邮 编: _____

建议和要求:

系 / 院主任: _____ (签字)

(系 / 院办公室章)

_____ 年 _____ 月 _____ 日

本书还配有其他教学辅导资料, 相关事宜敬请访问 Prentice Hall 的相关网站: <http://www.prenhall.com>。

请与我们联系

Publishing House of Electronics Industry

电子工业出版社: www.phei.com.cn

www.hxedu.com.cn

北京市万寿路 173 信箱外版教材事业部

邮编: 100036

电话: 010-88254555

传真: 010-88254560

E-mail: Te_service@phei.com.cn

Pearson Education Beijing Office

培生教育出版集团北京办事处

北京市西三环北路 19 号外研大厦 2202 室

邮编: 100089

电话: 010-88819178

传真: 010-88819170

E-mail: service@pearsoned.com.cn

Contents

1	Digital Concepts	1
1-1	Digital and Analog Quantities	2
1-2	Binary Digits, Logic Levels, and Digital Waveforms	4
2	Number Systems, Operations, and Codes	11
2-1	Decimal Numbers	12
2-2	Binary Numbers	13
2-3	Decimal-to-Binary Conversion	16
2-4	Binary Arithmetic	19
2-5	1's and 2's Complements of Binary Numbers	23
2-6	Signed Numbers	25
2-7	Arithmetic Operations with Signed Numbers	31
2-8	Hexadecimal Numbers	37
2-9	Octal Numbers	43
2-10	Binary Coded Decimal (BCD)	45
2-11	Digital Codes	48
2-12	Error Detection and Correction Codes	51
3	Logic Gates	64
3-1	The Inverter	65
3-2	The AND Gate	68
3-3	The OR Gate	75
3-4	The NAND Gate	80
3-5	The NOR Gate	85
3-6	The Exclusive-OR and Exclusive-NOR Gates	90
4	Boolean Algebra and Logic Simplification	99
4-1	Boolean Operations and Expressions	100
4-2	Laws and Rules of Boolean Algebra	101

4-3	DeMorgan's Theorem	107
4-4	Boolean Analysis of Logic Circuits	110
4-5	Simplification Using Boolean Algebra	112
4-6	Standard Forms of Boolean Expressions	116
4-7	Boolean Expressions and Truth Tables	122
4-8	The Karnaugh Map	126
4-9	Karnaugh Map SOP Minimization	128
4-10	Karnaugh Map POS Minimization	137
5	Combinational Logic Analysis	151
5-1	Basic Combinational Logic Circuits	152
5-2	Implementing Combinational Logic	156
5-3	The Universal Property of NAND and NOR Gates	162
5-4	Combinational Logic Using NAND and NOR Gates	164
5-5	Logic Circuit Operation with Pulse Waveform Inputs	169
6	Functions of Combinational Logic	178
6-1	Basic Adders	179
6-2	Parallel Binary Adders	182
6-3	Ripple Carry versus Look-Ahead Carry Adders	189
6-4	Comparators	192
6-5	Decoders	197
6-6	Encoders	205
6-7	Code Converters	209
6-8	Multiplexers (Data Selectors)	212
6-9	Demultiplexers	221
6-10	Parity Generators/Checkers	222
7	Latches, Flip-Flops, and Timers	238
7-1	Latches	239
7-2	Edge-Triggered Flip-Flops	245
7-3	Flip-Flop Operating Characteristics	257
7-4	Flip-Flop Applications	260
7-5	One-Shots	265
7-6	The 555 Timer	270

8	Counters	283
8-1	Asynchronous Counter Operation	284
8-2	Synchronous Counter Operation	292
8-3	Up/Down Synchronous Counters	300
8-4	Design of Synchronous Counters	303
8-5	Cascaded Counters	313
8-6	Counter Decoding	317
8-7	Counter Applications	320
8-8	Logic Symbols with Dependency Notation	325
9	Shift Registers	338
9-1	Basic Shift Register Functions	339
9-2	Serial In/Serial Out Shift Registers	340
9-3	Serial In/Parallel Out Shift Registers	344
9-4	Parallel In/Serial Out Shift Registers	346
9-5	Parallel In/Parallel Out Shift Registers	350
9-6	Bidirectional Shift Registers	352
9-7	Shift Register Counters	355
9-8	Shift Register Applications	359
9-9	Logic Symbols with Dependency Notation	365
10	Memory and Storage	374
10-1	Basics of Semiconductor Memory	375
10-2	Random-Access Memories (RAMs)	379
10-3	Read-Only Memories (ROMs)	392
10-4	Programmable ROMs (PROMs and EPROMs)	397
10-5	Flash Memories	400
10-6	Memory Expansion	405
10-7	Special Types of Memories	411
11	Introduction to Digital Signal Processing	420
11-1	Digital Signal Processing Basics	421
11-2	Converting Analog Signals to Digital	422
11-3	Analog-to-Digital Conversion Methods	428
11-4	Digital-to-Analog Conversion Methods	438

12 Integrated Circuit Technologies	450
12-1 Basic Operational Characteristics and Parameters	451
12-2 CMOS Circuits	459
12-3 TTL Circuits	464
12-4 Practical Considerations in the Use of TTL	469
12-5 Comparison of CMOS and TTL Performance	477
12-6 Emitter-Coupled Logic (ECL) Circuits	478
12-7 PMOS, NMOS, and E ² CMOS	479
Answers to Odd-Numbered Problems	488

1

DIGITAL CONCEPTS

CHAPTER OUTLINE

- 1-1 Digital and Analog Quantities
- 1-2 Binary Digits, Logic Levels, and Digital Waveforms

WWW VISIT THE COMPANION WEBSITE

Study aids for this chapter are available at
<http://www.prenhall.com/floyd>

NEW AND KEY TERMS

Key terms are in order of appearance in the chapter.

- Analog [模拟] Being continuous or having continuous values.
- Digital [数字的] Related to digits or discrete quantities; having a set of discrete values.
- Binary [二进制] Having two values or states; describes a number system that has a base of two and utilize 1 and 0 as its digits.
- Bit [(二进制数)位] A binary digit, which can be either a 1 or a 0.
- Pulse [脉冲] A sudden change from one level to another, followed after a time, called the pulse width, by a sudden change back to the original level.
- Clock [时钟] The basic timing signal in a digital system; a periodic waveform in which each interval between pulses equals the time for one bit.
- Timing diagram [时序图] A graph of digital waveforms showing the time relationship of two or more waveforms.
- Data [数据] A logic circuit that performs a specified logic operation such as AND or OR.
- Serial [串行] Having one element following another, as in a serial transfer of bits; occurring in sequence rather than simultaneously.
- Parallel [并行] In digital systems, data occurring simultaneously on several lines; the transfer or processing of several bits simultaneously.
- Logic [逻辑] In digital electronics, the decision-making capability of gate circuits, in which a HIGH represents a true statement and a LOW represents a false one.

WORDS FOR LOW LEVEL

- Discrete [离散的] ● Clarity [清楚] ● Amplifier [扩音器] ● Reproduction [复制品] ● Compact disk [光盘]
- Laser [激光] ● Diode [二极管] ● Optical [光学的] ● Code [编码] ● TTL (Transistor-Transistor Logic) [晶体管-晶体管逻辑(电路)] ● Edge [边沿] ● Amplitude [幅值] ● Overlap [重叠] ● Transition [转换] ● Reciprocal [倒数] ● Instantaneously [同时] ● Stray capacitive [杂散(寄生)电容的] ● Duty cycle [占空比]

1-1 DIGITAL AND ANALOG QUANTITIES

Electronic circuits can be divided into two broad categories, digital and analog. Digital electronics involves quantities with discrete values, and analog electronics involves quantities with continuous values. Although you will be studying digital fundamentals in this book, you should also know something about analog because many applications require both; and interfacing between analog and digital is important.


After completing this section, you should be able to

- Define *analog*
- Define *digital*
- Explain the difference between digital and analog quantities
- State the advantages of digital over analog
- Give examples of how digital and analog quantities are used in electronics

An analog quantity is one having continuous values. A digital quantity is one having a discrete set of values. Most things that can be measured quantitatively occur in nature in analog form. For example, the air temperature changes over a continuous range of values. During a given day, the temperature does not go from, say, 70° to 71° instantaneously; it takes on all the infinite values in between. If you graphed the temperature on a typical summer day, you would have a smooth, continuous curve similar to the curve in Figure 1-1. Other examples of analog quantities are time, pressure, distance, and sound.

FIGURE 1-1

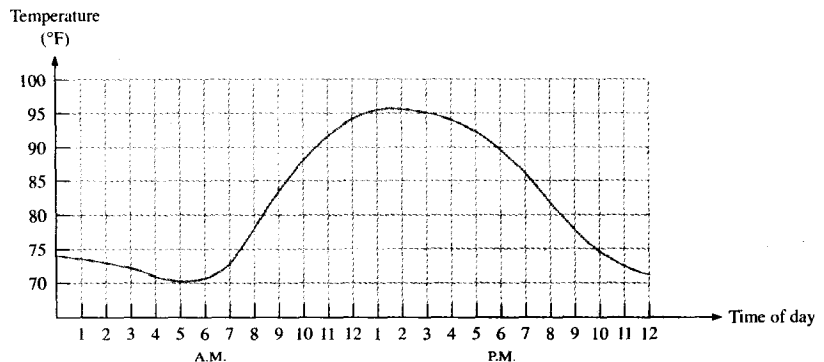Graph of an analog quantity (temperature versus time).



Rather than graphing the temperature on a continuous basis, suppose you just take a temperature reading every hour. Now you have sampled values representing the temperature at discrete points in time (every hour) over a 24-hour period, as indicated in Figure 1-2. You have effectively converted an analog quantity to a form that can now be digitized by representing each sampled value by a digital code. It is important to realize that Figure 1-2 itself is not the digital representation of the analog quantity.

The Digital Advantage Digital representation has certain advantages over analog representation in electronics applications. For one thing, digital data can be processed and transmitted more efficiently and reliably than analog data. Also, digital data has a great advantage when storage is necessary. For example, music when converted to digital form can be stored more compactly and reproduced with greater accuracy and clarity than is possible when it is in analog form. Noise (unwanted voltage fluctuations) does not affect digital data nearly as much as it does analog signals.

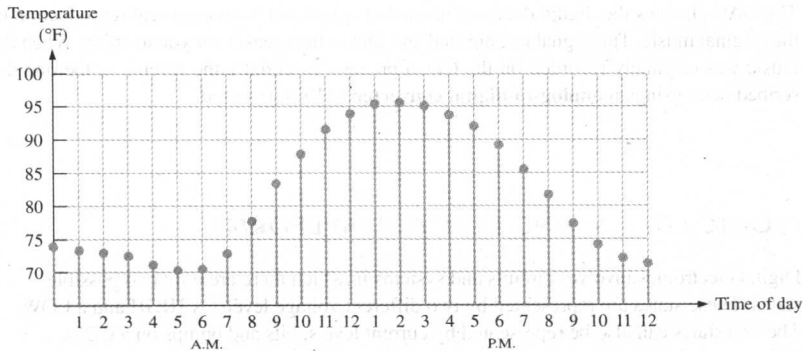


FIGURE 1-2

Sampled-value representation (quantization) of the analog quantity in Figure 1-1. Each value represented by a dot can be digitized by representing it as a digital code that consists of a series of 1s and 0s.

An Analog Electronic System

A public address system, used to amplify sound so that it can be heard by a large audience, is one simple example of an application of analog electronics. The basic diagram in Figure 1-3 illustrates that sound waves, which are analog in nature, are picked up by a microphone and converted to a small analog voltage called the audio signal. This voltage varies continuously as the volume and frequency of the sound changes and is applied to the input of a linear amplifier. The output of the amplifier, which is an increased reproduction of input voltage, goes to the speaker(s). The speaker changes the amplified audio signal back to sound waves that have a much greater volume than the original sound waves picked up by the microphone.

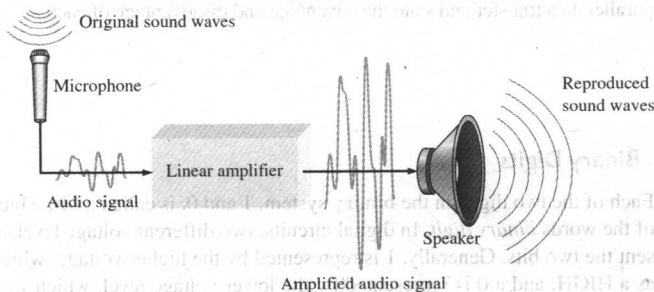


FIGURE 1-3

A basic audio public address system.

A System Using Digital and Analog Methods

The compact disk (CD) player is an example of a system in which both digital and analog circuits are used. The simplified block diagram in Figure 1-4 illustrates the basic principle. Music in digital form is stored on the compact disk. A laser diode optical system picks up the digital data from the rotating disk and transfers it to the **digital-to-analog converter (DAC)**.

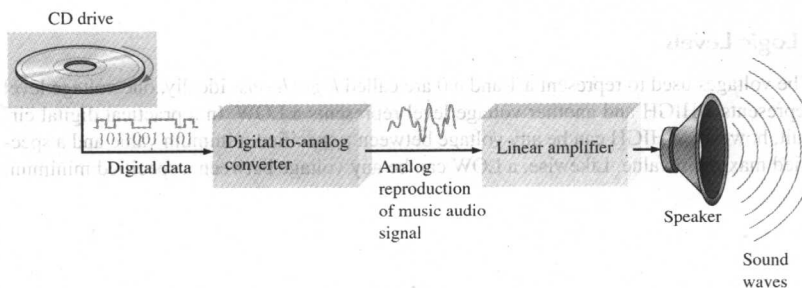


FIGURE 1-4

Basic block diagram of a CD player.

Only one channel is shown.

The DAC changes the digital data into an analog signal that is an electrical reproduction of the original music. This signal is amplified and sent to the speaker for you to enjoy. When the music was originally recorded on the CD, a process, essentially the reverse of the one described here, using an **analog-to-digital converter (ADC)** was used.

1-2 BINARY DIGITS, LOGIC LEVELS, AND DIGITAL WAVEFORMS

Digital electronics involves circuits and systems in which there are only two possible states. These states are represented by two different voltage levels: A HIGH and a LOW. The two states can also be represented by current levels, bits and bumps on a CD or DVD, etc. In digital systems such as computers, combinations of the two states, called *codes*, are used to represent numbers, symbols, alphabetic characters, and other types of information. The two-state number system is called *binary*, and its two digits are 0 and 1. A binary digit is called a *bit*.

After completing this section, you should be able to

- Define *binary* ■ Define *bit* ■ Name the bits in a binary system ■ Explain how voltage levels are used to represent bits ■ Explain how voltage levels are interpreted by a digital circuit ■ Describe the general characteristics of a pulse ■ Determine the amplitude, rise time, fall time, and width of a pulse ■ Identify and describe the characteristics of a digital waveform ■ Determine the amplitude, period, frequency, and duty cycle of a digital waveform ■ Explain what a timing diagram is and state its purpose ■ Explain serial and parallel data transfer and state the advantage and disadvantage of each

Binary Digits

Each of the two digits in the **binary** system, 1 and 0, is called a **bit**, which is a contraction of the words *binary digit*. In digital circuits, two different voltage levels are used to represent the two bits. Generally, 1 is represented by the higher voltage, which we will refer to as a HIGH, and a 0 is represented by the lower voltage level, which we will refer to as a LOW. This is called **positive logic** and will be used throughout the book.

HIGH = 1 and LOW = 0

Another system in which a 1 is represented by a LOW and a 0 is represented by a HIGH is called *negative logic*.

Groups of bits (combinations of 1s and 0s), called *codes*, are used to represent numbers, letters, symbols, instructions, and anything else required in a given application.

Logic Levels

The voltages used to represent a 1 and a 0 are called *logic levels*. Ideally, one voltage level represents a HIGH and another voltage level represents a LOW. In a practical digital circuit, however, a HIGH can be any voltage between a specified minimum value and a specified maximum value. Likewise, a LOW can be any voltage between a specified minimum

COMPUTER NOTE



The concept of a digital computer can be traced back to Charles Babbage, who developed a crude mechanical computation device in the 1830s. John Atanasoff was the first to apply electronic processing to digital computing in 1939. In 1946, an electronic digital computer called ENIAC was implemented with vacuum-tube circuits. Even though it took up an entire room, ENIAC didn't have the computing power of your handheld calculator.

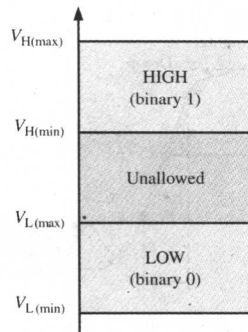


FIGURE 1-5

Logic level ranges of voltage for a digital circuit.

and a specified maximum. There can be no overlap between the accepted range of HIGH levels and the accepted range of LOW levels.

Figure 1-5 illustrates the general range of LOWs and HIGHs for a digital circuit. The variable $V_{H(max)}$ represents the maximum HIGH voltage value, and $V_{H(min)}$ represents the minimum HIGH voltage value. The maximum LOW voltage value is represented by $V_{L(max)}$, and the minimum LOW voltage value is represented by $V_{L(min)}$. The voltage values between $V_{L(max)}$ and $V_{H(min)}$ are unacceptable for proper operation. A voltage in the unallowed range can appear as either a HIGH or a LOW to a given circuit and is therefore not an acceptable value. For example, the HIGH values for a certain type of digital circuit called CMOS may range from 2 V to 3.3 V and the LOW values may range from 0 V to 0.8 V. So, for example, if a voltage of 2.5 V is applied, the circuit will accept it as a HIGH or binary 1. If a voltage of 0.5 V is applied, the circuit will accept it as a LOW or binary 0. For this type of circuit, voltages between 0.8 V and 2 V are unacceptable.

Digital Waveforms

Digital waveforms consist of voltage levels that are changing back and forth between the HIGH and LOW levels or states. Figure 1-6(a) shows that a single positive-going pulse is generated when the voltage (or current) goes from its normally LOW level to its HIGH level and then back to its LOW level. The negative-going pulse in Figure 1-6(b) is generated when the voltage goes from its normally HIGH level to its LOW level and back to its HIGH level. A digital waveform is made up of a series of pulses.

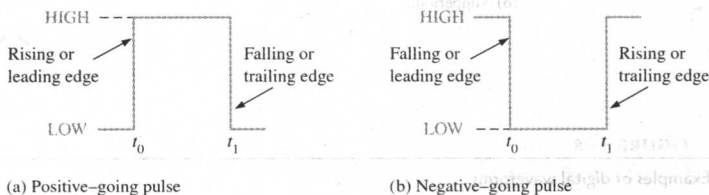


FIGURE 1-6

Ideal pulses.

The Pulse As indicated in Figure 1-6, a pulse has two edges: a **leading edge** that occurs first at time t_0 and a **trailing edge** that occurs last at time t_1 . For a positive-going pulse, the leading edge is a rising edge, and the trailing edge is a falling edge. The pulses in Figure 1-6 are ideal because the rising and falling edges are assumed to change in zero time (instantaneously). In practice, these transitions never occur instantaneously, although for most digital work you can assume ideal pulses.

Figure 1-7 shows a nonideal pulse. In reality, all pulses exhibit some or all of these characteristics. The overshoot and ringing are sometimes produced by stray inductive and