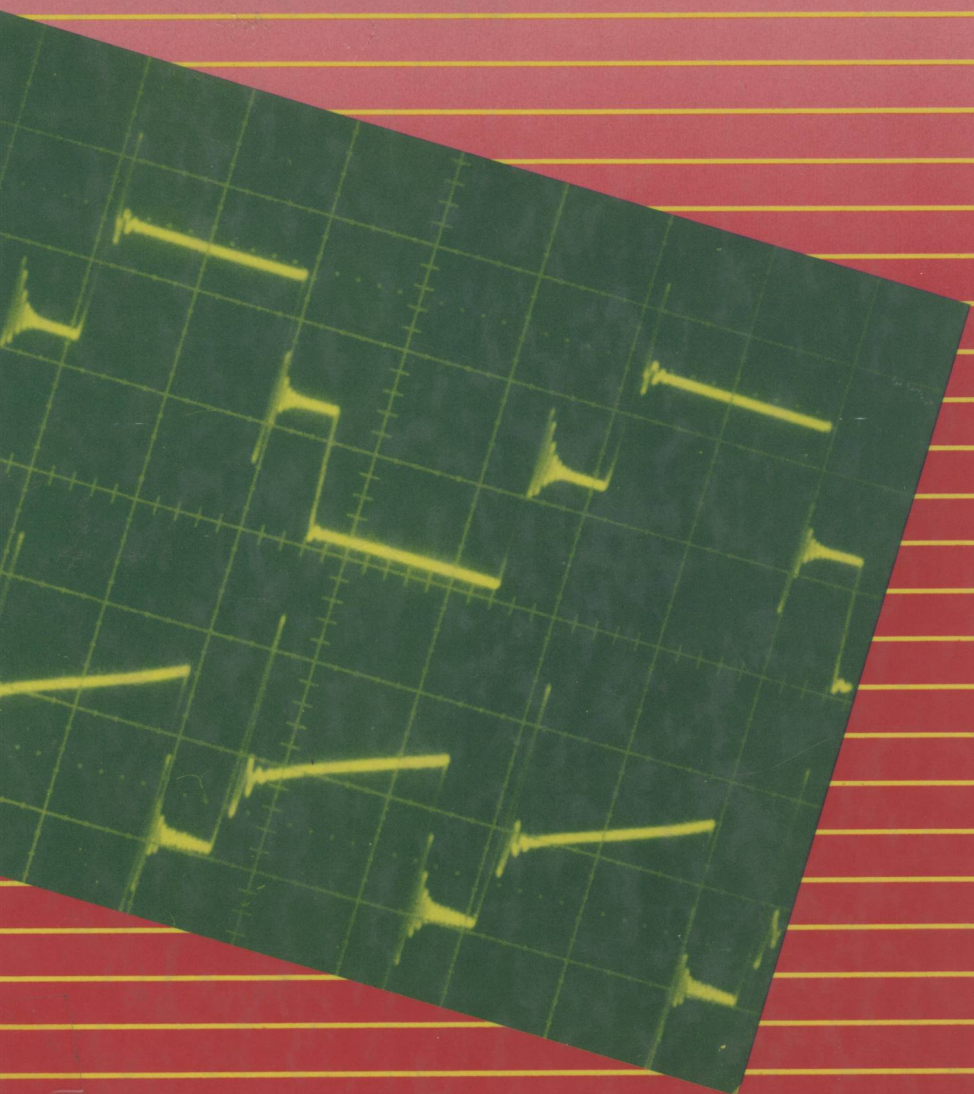


# **SWITCHING POWER SUPPLY DESIGN**



**ABRAHAM I. PRESSMAN**

# Switching Power Supply Design

**Abraham I. Pressman**

*President, Swiichtronix Power, Inc.*

*Waban, Massachusetts*



E9262535

**McGraw-Hill, Inc.**

New York St. Louis San Francisco Auckland Bogotá  
Caracas Hamburg Lisbon London Madrid  
Mexico Milan Montreal New Delhi Paris  
San Juan São Paulo Singapore  
Sydney Tokyo Toronto

## Library of Congress Cataloging-in-Publication Data

Pressman, Abraham I.

Switching power supply design / Abraham I. Pressman.

p. cm.

Includes bibliographical references and index.

ISBN 0-07-050806-2

1. Electronic apparatus and appliances—Power supply.
  2. Microelectronics—Power supply.
  3. Electric current converters.
- I. Title.

TK7868.P6P75 1991

621.381'044—dc20

91-3261

CIP

Copyright © 1991 by McGraw-Hill, Inc. All rights reserved. Printed in the United States of America. Except as permitted under the United States Copyright Act of 1976, no part of this publication may be reproduced or distributed in any form or by any means, or stored in a data base or retrieval system, without the prior written permission of the publisher.

1 2 3 4 5 6 7 8 9 0 DOC/DOC 9 7 6 5 4 3 2 1

ISBN 0-07-050806-2

*The sponsoring editor for this book was Daniel A. Gonneau, the editing supervisor was Joseph Bertuna, and the production supervisor was Pamela A. Pelton. It was set in Century Schoolbook by McGraw-Hill's Professional Book Group composition unit.*

*Printed and bound by R. R. Donnelley & Sons Company.*

Information contained in this work has been obtained by McGraw-Hill, Inc., from sources believed to be reliable. However, neither McGraw-Hill nor its authors guarantees the accuracy or completeness of any information published herein and neither McGraw-Hill nor its authors shall be responsible for any errors, omissions, or damages arising out of use of this information. This work is published with the understanding that McGraw-Hill and its authors are supplying information but are not attempting to render engineering or other professional services. If such services are required, the assistance of an appropriate professional should be sought.

---

# Switching Power Supply Design

## Other McGraw-Hill Books of Interest

---

### Handbooks

- AVALLONE AND BAUMEISTER • *Standard Handbook for Mechanical Engineers*  
BENSON • *Audio Engineering Handbook*  
BENSON • *Television Engineering Handbook*  
BILLINGS • *Switchmode Power Supply Handbook*  
COOMBS • *Printed Circuits Handbook*  
DI GIACOMO • *VLSI Handbook*  
FINK AND BEATY • *Standard Handbook for Electrical Engineers*  
FINK AND CHRISTIANSEN • *Electronics Engineers' Handbook*  
FLANAGAN • *Handbook of Transformer Applications*  
HARPER • *Handbook of Electronic Packaging and Interconnection*  
INGLIS • *Electronic Communications Handbook*  
JOHNSON AND JASIK • *Antenna Engineering Handbook*  
JURAN • *Quality Control Handbook*  
KAUFMAN AND SEIDMAN • *Handbook of Electronics Calculations*  
KAUFMAN AND SEIDMAN • *Handbook for Electronics Engineering Technicians*  
STOUT AND KAUFMAN • *Handbook of Operational Amplifier Circuit Design*  
WILLIAMS AND TAYLOR • *Electronic Filter Design Handbook*

### Encyclopedias

- CONCISE ENCYCLOPEDIA OF SCIENCE AND TECHNOLOGY  
ENCYCLOPEDIA OF ELECTRONICS AND COMPUTERS  
ENCYCLOPEDIA OF ENGINEERING

### Dictionaries

- DICTIONARY OF SCIENTIFIC AND TECHNICAL TERMS  
DICTIONARY OF ELECTRICAL AND ELECTRONIC ENGINEERING  
DICTIONARY OF ENGINEERING

### Other

- ANTOGNETTI • *Power Integrated Circuits*  
CHRYSSIS • *High-Frequency Switching Power Supplies*  
GROSSNER • *Transformers in Electronic Circuits*  
MITCHELL • *DC/DC Switching Regulator Analysis*  
ROMBAUT • *Power Electronic Converters: AC/AC Conversion*  
SEGUIER • *Power Electronic Converters: AC/DC Conversion*

*To my wife Annie*

# Preface

Much has changed in the power conversion field since the author's previous book on switching power supply design (*Switching and Linear Power Supply, Power Converter Design*, 1978).

The main goal of these changes has been to make the power supply smaller. As integrated circuits packed more features in a smaller volume, it became essential also to decrease the size of a system's power supply. Switching power supply packing density currently ranges from 2 to 6 load watts per cubic inch ( $\text{W/in}^3$ ) as compared to about 1  $\text{W/in}^3$  a decade ago. Newer resonant converter techniques offer a possibility of 20 to 40  $\text{W/in}^3$ .

Higher switching frequencies, made possible by power MOSFET transistors, newer topologies, and integrated-circuit pulse-width-modulating chips, which pack more control and supervisory features in a smaller volume, have contributed to making present-day power supplies smaller. All these new technologies are covered in this book.

It has been the author's experience, in teaching a course on modern switching power supply design to all levels of engineers from most of the major American electronics companies, that those who have a good understanding of the fundamental principles can easily solve their day-to-day design problems as well as assess and adapt to new technologies.

Thus, this book covers the new technologies in a tutorial way so that the reader can understand the fundamental reasons for various effects. Explanations for various significant waveshapes and explanations for alternative design decisions are given. Care has been taken to avoid offering "handy-dandy" design equations without showing how they were derived. All equations that effect a design decision are derived from fundamental relations.

Magnetics design is emphasized; for, the majority of power supply designers are primarily circuits-oriented. They appreciate and can analyze problems when they can see DC voltage levels, voltage spikes, and waveshapes on an oscilloscope. But the locus of operation on a  $BH$  loop cannot be seen on an oscilloscope. Thus, circuits designers too often shy away from or do not fully understand magnetics design. They leave that to a magnetics specialist who may not appreciate how cir-

cuits characteristics effect magnetics design decisions. It is hoped the emphasis on magnetics herein may help correct that problem.

Throughout this text and throughout the literature, idealized voltage-current waveforms are often shown. But I feel it is very valuable from a tutorial viewpoint to view actual Polaroid waveforms taken at critical points on working circuits. Seeing an actual photographed waveform with its spikes, rings, and oddities conveys a great deal more information and confidence about a circuit than does an idealized, hand-drawn waveform. Such photographed waveforms are presented at critical points at various frequencies on some of the most commonly used topologies.

This book is directed primarily to design engineers and engineering students at the undergraduate and graduate level. It may also be of significant value to people who are not directly involved in start-from-scratch designs, and whose main interest is power supply design analysis, design review, test, and debugging.

The material contained herein is a consolidation and, hopefully, a simpler, clearer explanation and logical reorganization of the highpoints of all the proven and practical aspects of modern switching power supply technology. As such, credit for the material belongs to the innumerable engineers, designers in industry, and universities that have brought switching power supply technology to its present advanced state.

*Abraham I. Pressman*



## ABOUT THE AUTHOR

ABRAHAM I. PRESSMAN is founder and president of Switchtronix Power, Inc., a company specializing in power supply design, design review, and consultation. He is well known as the author of the best-selling book, *Switching and Linear Power Supply Design, Power Converter Design* (1978). Mr. Pressman teaches a course on switching power supply design that has been attended by groups from major international electronics, communications, and computer corporations.

# Contents

Preface xvii

## Part 1 Topologies

<b>Chapter 1. Fundamental Switching Regulators—Buck, Boost, and Inverter Topologies</b>	<b>3</b>
1.1 Introduction	3
1.2 Linear Regulators—Switching Regulator Ancestors	4
1.2.1 Basic operation—merits and drawbacks / 4	
1.2.2 Linear regulator drawbacks / 5	
1.2.3 Power dissipation in the series-pass transistor / 5	
1.2.4 Linear regulator efficiency versus output voltage / 6	
1.2.5 Linear regulators with PNP series-pass transistors for lesser required headroom / 8	
1.3 “Buck” Switching Regulator Topology	9
1.3.1 Basic operation / 9	
1.3.2 Significant current waveforms in buck regulator / 12	
1.3.3 Buck regulator efficiency neglecting AC switching losses / 13	
1.3.4 Buck regulator efficiency including AC switching losses / 13	
1.3.5 Optimum switching frequency in buck regulator / 16	
1.3.6 Design relations—output filter inductor selection / 17	
1.3.7 Design relations—output filter capacitor selection / 21	
1.3.8 DC-isolated, regulated voltage from a buck regulator / 23	
1.4 Boost Switching Regulator Topology	24
1.4.1 Basic operation / 24	
1.4.2 Quantitative relations—boost regulator / 26	
1.4.3 Discontinuous and continuous modes in boost regulator / 27	
1.4.4 Discontinuous-mode boost regulator design relations / 28	
1.4.5 Boost regulator applications and flyback comparison / 31	
1.5 Polarity Inverting Switching Regulator Topology	32
1.5.1 Basic operation / 32	
1.5.2 Design relations in polarity inverter / 34	
Reference	35

<b>Chapter 2. Push-Pull and Forward Converter Topologies</b>	<b>37</b>
2.1 Introduction	37
2.2 Push-Pull Topology	37
2.2.1 Basic operation—master/slave outputs /	37
2.2.2 Slave line-load regulation /	40
2.2.3 Slave absolute output voltage levels /	41
2.2.4 Master output inductor minimum current limitations /	41
2.2.5 Flux imbalance in push-pull topology /	42
2.2.6 Indications of flux imbalance /	45
2.2.7 Testing for flux imbalance /	48
2.2.8 Coping with flux imbalance /	49
2.2.9 Power transformer design relations /	51
2.2.10 Primary, secondary peak and rms currents /	55
2.2.11 Transistor voltage stress and leakage inductance spikes /	58
2.2.12 Power transistor losses /	60
2.2.13 Output power and input voltage limitations in push-pull topology /	63
2.2.14 Output filter design relations /	64
2.3 Forward Converter Topology	66
2.3.1 Basic operation /	66
2.3.2 Design relations: output/input voltage, on time, turns ratios /	70
2.3.3 Slave output voltages /	71
2.3.4 Secondary load, free-wheeling diode, and inductor currents /	72
2.3.5 Relations between primary current, output power, and input voltage /	73
2.3.6 Maximum off-voltage stress in power transistor /	74
2.3.7 Practical input voltage/output power limits /	74
2.3.8 Forward converter with unequal power and reset winding turns /	75
2.3.9 Forward converter magnetics /	78
2.3.10 Power transformer design relations /	81
2.3.11 Output filter design relations /	84
2.4 Double-Ended Forward Converter Topology	86
2.4.1 Basic operation /	86
2.4.2 Design relations and transformer design /	88
2.5 Interleaved Forward Converter Topology	89
2.5.1 Basic operation—merits, drawbacks, and output power limits /	89
2.5.2 Transformer design relations /	92
2.5.3 Output filter design /	92
<b>Chapter 3. Half- and Full-Bridge Converter Topologies</b>	<b>93</b>
3.1 Introduction	93
3.2 Half-Bridge Converter Topology	93
3.2.1 Basic operation /	93
3.2.2 Half-bridge magnetics /	95
3.2.3 Output filter calculations /	97
3.2.4 Blocking capacitor to avoid flux imbalance /	97
3.2.5 Half-bridge leakage inductance problems /	98

3.2.6	Double-ended forward converter versus half bridge /	99
3.2.7	Practical output power limits in half bridge /	100
3.3	Full-Bridge Converter Topology	101
3.3.1	Basic operation /	101
3.3.2	Full-bridge magnetics /	103
3.3.3	Output filter calculations /	104
3.3.4	Transformer primary blocking capacitor /	104
Chapter 4.	Flyback Converter Topologies	105
4.1	Introduction	105
4.2	Flyback Converter—Areas of Application	105
4.3	Discontinuous-Mode Flybacks—Basic Operation	107
4.3.1	Relation between output voltage versus input voltage, on time, output load /	108
4.3.2	Design relations and sequential decision requirements /	109
4.3.3	Flyback magnetics /	114
4.3.4	Flyback disadvantages /	121
4.3.5	Flybacks for 120- or 220-V-AC operation with no doubler and full-wave rectifier switching /	125
4.4	Continuous-Mode Flybacks—Basic Operation	127
4.4.1	Discontinuous-mode to continuous-mode transition /	130
4.4.2	Design relations—continuous-mode flybacks /	132
4.5	Interleaved Flybacks	137
4.5.1	Summation of secondary currents in interleaved flybacks /	138
4.6	Double-Ended Discontinuous-Mode Flyback	138
4.6.1	Area of application /	138
4.6.2	Basic operation /	139
4.6.3	Leakage inductance effect in double-ended flyback /	140
References		141
Chapter 5.	Current-Mode and Current-Fed Topologies	143
5.1	Introduction	143
5.2	Current-Mode Advantages	144
5.2.1	Avoidance of flux imbalance in push-pull converters /	144
5.2.2	Instantaneous correction against line voltage changes without the delay in an error amplifier (voltage feedforward characteristics) /	145
5.2.3	Ease and simplicity of feedback-loop stabilization /	145
5.2.4	Paralleling outputs /	146
5.2.5	Improved load current regulation /	146
5.3	Current-Mode versus Voltage-Mode Control Circuits	146
5.3.1	Voltage-mode control circuitry /	146
5.3.2	Current-mode control circuitry /	149
5.4	Detailed Explanation of Current-Mode Advantages	154
5.4.1	Line voltage regulation /	154
5.4.2	Elimination of flux imbalance /	154
5.4.3	Simplified loop stabilization resulting from elimination of output inductor in small-signal analysis /	155
5.4.4	Mechanism of load current regulation /	156

5.5	Current-Mode Deficiencies and Problems	158
5.5.1	Constant peak versus constant average output inductor problems / 158	
5.5.2	Response to an output inductor current disturbance / 161	
5.5.3	Slope compensation to correct problems in current mode / 161	
5.5.4	Slope compensation with a positive-going ramp voltage / 163	
5.5.5	Implementing slope compensation / 164	
5.6	Voltage-Fed and Current-Fed Topologies	165
5.6.1	Introduction and definitions / 165	
5.6.2	Deficiencies of voltage-fed, width-modulated full-wave bridge / 166	
5.6.3	Buck-voltage-fed full-wave bridge topology—basic operation / 170	
5.6.4	Buck-voltage-fed full-wave bridge advantages / 172	
5.6.5	Drawbacks in buck-voltage-fed full-wave bridge / 174	
5.6.6	Buck-current-fed full-wave bridge topology—basic operation / 175	
5.6.7	Flyback-current-fed push-pull topology / 189	
	References	208
Chapter 6.	Miscellaneous Topologies	211
6.1	SCR Resonant Topologies—Introduction	211
6.2	SCR Basics	213
6.3	SCR Turnoff by Resonant Sinusoidal Anode Currents—Single-Ended Resonant Inverter Topology	216
6.4	SCR Resonant Bridge Topologies—Introduction	222
6.4.1	SCR half-bridge resonant converter, series-loaded—basic operation / 224	
6.4.2	Design calculations—SCR half-bridge resonant converter, series-loaded / 226	
6.4.3	Design example—SCR half-bridge resonant converter, series-loaded / 229	
6.4.4	SCR half-bridge resonant converter, shunt-loaded / 230	
6.4.5	Single-ended SCR resonant converter topology design / 230	
6.5	Cuk Converter Topology—Introduction	237
6.5.1	Cuk converter—basic operation / 237	
6.5.2	Relation between output/input voltage and $Q$ on time / 239	
6.5.3	Rates of change of currents in $L_1$ , $L_2$ / 240	
6.5.4	Reducing input ripple currents to zero / 241	
6.5.5	Isolated outputs in the Cuk converter / 242	
6.6	Low Output Power “Housekeeping” or “Auxiliary” Topologies—Introduction	242
6.6.1	Housekeeping power supply—on output or input ground / 243	
6.6.2	Housekeeping supply alternatives / 244	
6.6.3	Specific housekeeping supply block diagrams / 245	
6.6.4	Royer oscillator housekeeping supply—basic operation / 248	
6.6.5	Minimum-parts-count flyback as a housekeeping supply / 260	
6.6.6	Buck regulator with DC-isolated output as a housekeeping supply / 262	
	References	263

## Part 2 Magnetics and Circuits Designs

<b>Chapter 7. Transformer and Magnetics Design</b>	<b>267</b>
7.1 Introduction	267
7.2 Transformer Core Materials and Geometries and Peak Flux Density Selection	268
7.2.1 Ferrite core losses versus frequency and flux density for widely used core materials / 268	
7.2.2 Ferrite core geometries / 271	
7.2.3 Peak flux density selection / 275	
7.3 Maximum Transformer Core Output Power, Peak Flux Density, Core and Bobbin Areas, and Coil Current Density	277
7.3.1 Derivation of output power relations for forward converter topology / 277	
7.3.2 Derivation of output power relations for push-pull topology / 280	
7.3.3 Derivation of output power relations for half-bridge topology / 286	
7.3.4 Output power relations in full-bridge topology / 287	
7.3.5 Conversion of output power equations into charts permitting core and operating frequency selection at a glance / 288	
7.4 Transformer Temperature Rise Calculations	294
7.5 Transformer Copper Losses	298
7.5.1 Introduction / 298	
7.5.2 Skin effect / 300	
7.5.3 Skin effect—quantitative relations / 301	
7.5.4 AC/DC resistance ratio for various wire sizes at various frequencies / 303	
7.5.5 Skin effect with rectangular current waveshapes / 306	
7.5.6 Proximity effect / 308	
References	317
<b>Chapter 8. Bipolar Power Transistor Base Drives</b>	<b>319</b>
8.1 Introduction	319
8.2 Objectives of Bipolar Base Drive Circuits	320
8.2.1 Sufficiently high current throughout the on time / 320	
8.2.2 A spike of high base input current $I_{b1}$ at instant of turnon / 321	
8.2.3 A spike of high reverse base current $I_{b2}$ at the instant of turnoff / 322	
8.2.4 A base-to-emitter reverse voltage spike $-1$ to $-5$ V in amplitude at the instant of turnoff / 324	
8.2.5 A scheme to permit the circuit to work equally well with high- or low-beta transistors / 324	
8.2.6 High efficiency / 325	
8.3 Baker Clamps	325
8.3.1 Baker clamp operation / 328	
8.3.2 Transformer coupling into a Baker clamp / 330	
8.3.3 Transformerized Baker clamp / 336	
8.3.4 Inherent Baker clamping in Darlington transistors / 338	
8.3.5 Proportional base drive / 339	
8.3.6 Miscellaneous base drive schemes / 345	
References	351

<b>Chapter 9. MOSFET Power Transistors and Input Drive Circuits</b>	<b>353</b>
9.1 Introduction	353
9.2 MOSFET Basics	354
9.2.1 MOSFET drain current versus drain-to-source voltage characteristics ( $I_d - V_{ds}$ )	356
9.2.2 MOSFET input impedance and required gate currents	359
9.2.3 MOSFET gate rise and fall times for desired drain current rise and fall times	361
9.2.4 MOSFET gate drive circuits	362
9.2.5 MOSFET $R_{ds}$ temperature characteristics and safe operating area limits	365
9.2.6 MOSFET gate threshold voltage and temperature characteristic	369
9.2.7 MOSFET switching speed and temperature characteristics	370
9.2.8 MOSFET current ratings	371
9.2.9 Paralleling MOSFETs	374
9.2.10 MOSFETs in push-pull topology	377
9.2.11 MOSFET maximum gate voltage specifications	378
9.2.12 MOSFET drain-to-source ("body") diode	379
References	380
 <b>Chapter 10. Magnetic-Amplifier Postregulators</b>	 <b>381</b>
10.1 Introduction	381
10.2 Linear and Buck Regulator Postregulators	382
10.3 Magnetic Amplifiers—Introduction	383
10.3.1 Square hysteresis loop magnetic core as a fast acting on/off switch with electrically adjustable on/off time	385
10.3.2 Blocking and firing times in magnetic-amplifier postregulators	388
10.3.3 Magnetic-amplifier core resetting and voltage regulation	389
10.3.4 Slave output voltage shutdown with magnetic amplifiers	390
10.3.5 Square hysteresis loop core characteristics and sources	391
10.3.6 Core loss and temperature rise calculations	396
10.3.7 Design example—magnetic-amplifier postregulator	402
10.3.8 Magnetic-amplifier gain	407
10.3.9 Magnetic amplifiers for a push-pull output	408
10.4 Magnetic Amplifier Pulse-Width Modulator and Error Amplifier	408
10.4.1 Circuit details, magnetic amplifier pulse-width modulator-error amplifier	409
References	412
 <b>Chapter 11. Turnon, Turnoff Switching Losses and Snubbers</b>	 <b>413</b>
11.1 Introduction	413
11.2 Transistor Turnoff Losses without a Snubber	414
11.3 RCD Turnoff Snubber Operation	416
11.4 Selection of Capacitor Size in RCD Snubber	418
11.5 Design Example—RCD Snubber	419
11.5.1 RCD snubber returned to positive supply rail	420
11.6 Nondissipative Snubbers	421

11.7	Snubber Reduction of Leakage Inductance Spike to Avoid Second Breakdown	422
11.8	Transformer-Aided Snubber	425
	References	426
<b>Chapter 12.</b>	<b>Feedback-Loop Stabilization</b>	<b>427</b>
12.1	Introduction	427
12.2	Mechanism of Loop Oscillation	429
12.2.1	Gain criterion for a stable circuit /	429
12.2.2	Gain slope criteria for a stable circuit /	430
12.2.3	Gain characteristic of LC output filter with and without equivalent series resistance (ESR) in output capacitor /	433
12.2.4	Pulse-width-modulator gain /	436
12.2.5	Total output LC filter plus modulator and sampling network gain /	437
12.3	Shaping Error-Amplifier Gain-versus-Frequency Characteristic	437
12.4	Error-Amplifier Transfer Function, Poles, and Zeros	440
12.5	Rules for Gain Slope Changes Due to Zero and Pole Frequencies	442
12.6	Derivation of Transfer Function of an Error Amplifier with Single Zero and Single Pole from Its Schematic	444
12.7	Calculation of Type 2 Error-Amplifier Phase Shift from Its Zero and Pole Locations	445
12.8	Phase Shift through LC Filter Having ESR in Its Output Capacitor	446
12.9	Design Example—Stabilizing a Forward Converter Feedback Loop with a Type 2 Error Amplifier	448
12.10	Type 3 Error Amplifier—When Used and Transfer Function	451
12.11	Phase Lag through a Type 3 Error Amplifier as Function of Zero and Pole Locations	453
12.12	Type 3 Error Amplifier Schematic, Transfer Function, and Zero and Pole Locations	454
12.13	Design Example—Stabilizing a Forward Converter Feedback Loop with a Type 3 Error Amplifier	456
12.14	Component Selection to Yield Desired Type 3 Error-Amplifier Gain Curve	458
12.15	Conditional Stability in Feedback Loops	459
12.16	Stabilizing a Discontinuous-Mode Flyback Converter	461
12.16.1	DC gain from error-amplifier output to output voltage node /	461
12.16.2	Discontinuous-mode flyback transfer function or AC voltage gain from error-amplifier output to output voltage node /	462
12.17	Error-Amplifier Transfer Function for Discontinuous-Mode Flyback	464
12.18	Design Example—Stabilizing a Discontinuous-Mode Flyback Converter	465
12.19	Transconductance Error Amplifiers	468
	References	470
<b>Chapter 13.</b>	<b>Resonant Converters</b>	<b>471</b>
13.1	Introduction	471



13.2	Resonant Forward Converter	473
13.2.1	Measured waveforms in a resonant forward converter	476
13.3	Resonant Converter Operating Modes	479
13.3.1	Discontinuous and continuous; above resonance and below resonance operating modes	479
13.4	Resonant Half Bridge in Continuous-Conduction Mode	481
13.4.1	Parallel resonant converter (PRC) and series resonant converter (SRC)	481
13.4.2	AC equivalent circuits and gain curves for series- and parallel-loaded half bridges in continuous-conduction mode	482
13.4.3	Regulation with series-loaded half bridge in continuous-conduction mode (CCM)	484
13.4.4	Regulation with parallel-loaded half bridge in continuous-conduction mode	485
13.4.5	Series-parallel resonant converter in continuous-conduction mode	486
13.4.6	Zero-voltage-switching quasi-resonant (CCM) converters	488
13.5	Resonant Power Supplies—Conclusion	490
	References	492

## Part 3 Typical Switching Power Supply Waveforms

Chapter 14.	Waveforms	495
14.1	Introduction	495
14.2	Forward Converter Waveshapes	496
14.2.1	$V_{dc}$ , $I_d$ photos at 80 percent of full load	497
14.2.2	$V_{dc}$ , $I_{dc}$ photos at 40 percent of full load	499
14.2.3	Overlap of drain voltage and drain current at turnon/turnoff transitions	499
14.2.4	Relative timing of drain current, drain-to-source voltage, and gate-to-source voltage	502
14.2.5	Relative timing of input voltage to output inductor, output inductor current rise and fall times, and power transistor drain-to-source voltage	502
14.2.6	Relative timing of critical waveforms in PWM driver chip (UC3525A) for forward converter of Fig. 14.1	503
14.3	Push-Pull Topology Waveshapes—Introduction	504
14.3.1	Transformer center tap currents and drain-to-source voltages at maximum load currents for maximum, nominal, and minimum supply voltages	505
14.3.2	Opposing $V_{dc}$ waveshapes, relative timing, and flux locus during dead time	509
14.3.3	Relative timing of gate input voltage, drain-to-source voltage, and drain currents	511
14.3.4	Drain current as measured with a current probe in series in the drain as compared with measurement with a current probe in series in the transformer center tap	511
14.3.5	Output ripple voltage and rectifier cathode voltage	511
14.3.6	Oscillatory ringing at rectifier cathodes at transistor turnon	513
14.3.7	AC switching loss due to overlap of falling drain current and rising drain voltage at turnoff	515